
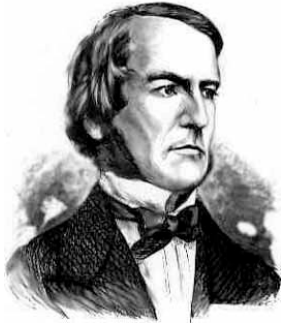


# 6.1 Combinational Circuits

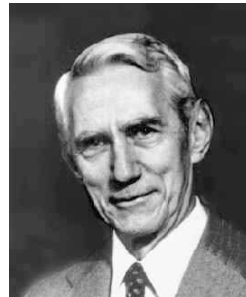

George Boole (1815 - 1864)



Claude Shannon (1916 - 2001)

- Earlier lectures.
- TOY machine.



- Next two lectures.
- Digital circuits.



- Culminating lecture.
- Putting it all together and building a TOY machine.
    - (on paper, we mean)

## Digital Circuits

### What is a digital system?

- Digital: signals are 0 or 1.
- Analog: signals vary continuously.

### Why digital systems?

- Accuracy and reliability.
- Staggeringly fast and cheap.

### Basic abstractions.

- On, off.
- Switch that can turn something on or off.


### Digital circuits and you.

- ➔ ▪ Computer microprocessors.
- Antilock brakes.
- Cell phones.
- Ipods
- ...

## Wires

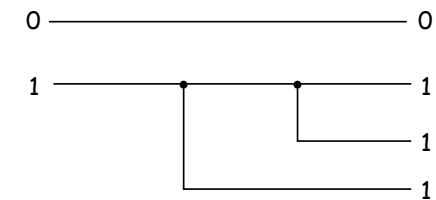
### Wires.

- Propagate logical values from place to place.
- Signals "flow" from left to right.
  - A drawing convention, sometimes violated
  - Actually: flow from producer to consumer(s) of signal



Input


Output

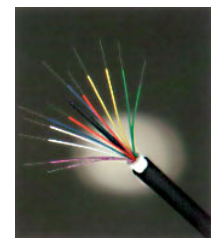

## Logic Gates

### Logical gates.

- Fundamental building blocks.

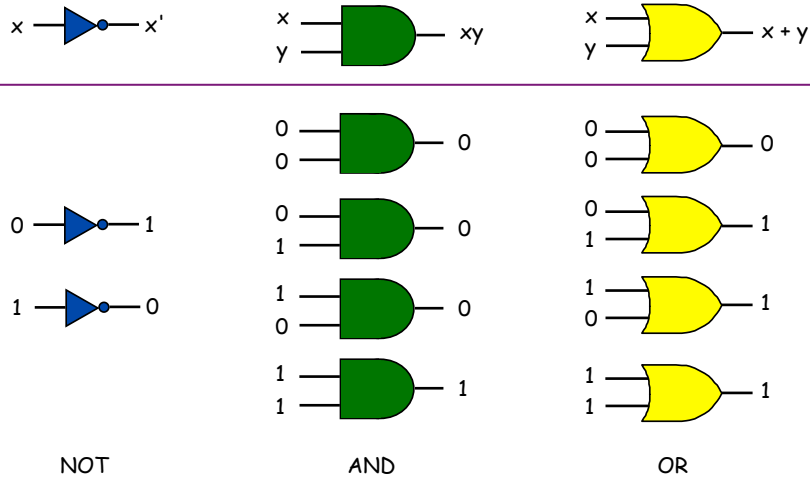


6

## Multiway AND Gates

### $AND(x_0, x_1, x_2, x_3, x_4, x_5, x_6, x_7)$ .

- 1 if all inputs are 1.
- 0 otherwise.

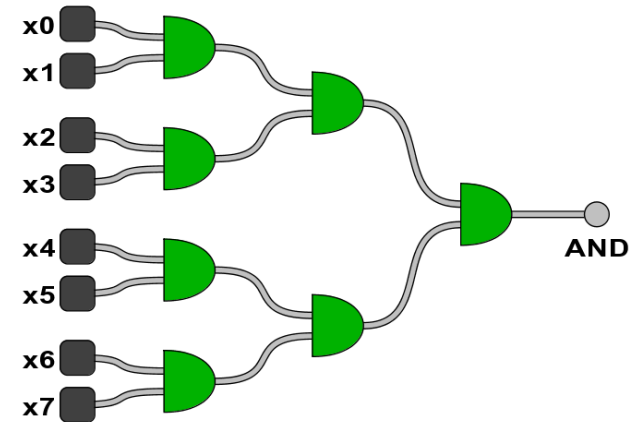


7

## Multiway OR Gates
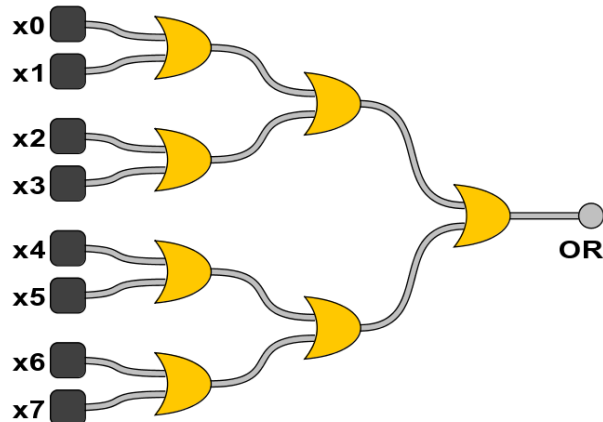
### $OR(x_0, x_1, x_2, x_3, x_4, x_5, x_6, x_7)$ .

- 1 if at least one input is 1.
- 0 otherwise.



8

## Boolean Algebra

### History.

- Developed by Boole to solve mathematical logic problems (1847).
- Shannon master's thesis applied it to digital circuits (1937).


"possibly the most important, and also the most famous, master's thesis of the [20th] century" --Howard Gardner

### Basics.

- Boolean variable: value is 0 or 1.
- Boolean function: function whose inputs and outputs are 0, 1.
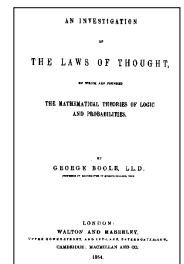
### Relationship to circuits.

- Boolean variables: signals.
- Boolean functions: circuits.




9

## Truth Table

### Truth table.

- Systematic method to describe Boolean function.
- One row for each possible input combination.
- N inputs  $\Rightarrow 2^N$  rows.

AND Truth Table		
x	y	AND(x, y)
0	0	0
0	1	0
1	0	0
1	1	1

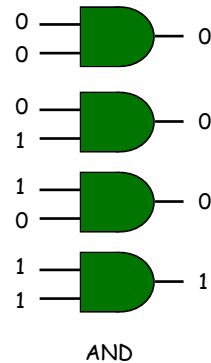

## Truth Table for Functions of 2 Variables

### Truth table.

- 16 Boolean functions of 2 variables.
  - every 4-bit value represents one

Truth Table for All Boolean Functions of 2 Variables									
x	y	ZERO	AND		x	y	XOR	OR	
0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1

Truth Table for All Boolean Functions of 2 Variables									
x	y	NOR	EQ	y'		x'		NAND	ONE
0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1

11

12

## Truth Table for Functions of 3 Variables

### Truth table.

- 16 Boolean functions of 2 variables.
  - every 4-bit value represents one
- 256 Boolean functions of 3 variables.
  - every 8-bit value represents one
- $2^{(2^N)}$  Boolean functions of N variables!

Some Functions of 3 Variables						
x	y	z	AND	OR	MAJ	ODD
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	0	1	0	1
0	1	1	0	1	1	0
1	0	0	0	1	0	1
1	0	1	0	1	1	0
1	1	0	0	1	1	0
1	1	1	1	1	1	1



## Universality of AND, OR, NOT

### Any Boolean function can be expressed using AND, OR, NOT.

- "Universal."
- $XOR(x,y) = xy' + x'y$

Notation	Meaning
x'	NOT x
x y	x AND y
x + y	x OR y

Expressing XOR Using AND, OR, NOT							
x	y	x'	y'	x'y	xy'	x'y + xy'	XOR
0	0	1	1	0	0	0	0
0	1	1	0	1	0	1	1
1	0	0	1	0	1	1	1
1	1	0	0	0	0	0	0

Exercise. Show {AND, NOT}, {OR, NOT}, {NAND}, {AND, XOR} are universal.

Hint. Use DeMorgan's Law:  $(xy)' = (x' + y')$  and  $(x + y)' = (x'y)'$

13

14

## Sum-of-Products

Any Boolean function can be expressed using AND, OR, NOT.


- Sum-of-products is systematic procedure.
  - form AND term for each 1 in truth table of Boolean function
  - OR terms together

Expressing MAJ Using Sum-of-Products								
x	y	z	MAJ	$x'yz$	$xy'z$	$xyz'$	$xyz$	$x'yz + xy'z + xyz' + xyz$
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0
0	1	1	1	1	0	0	0	1
1	0	0	0	0	0	0	0	0
1	0	1	1	0	1	0	0	1
1	1	0	1	0	0	1	0	1
1	1	1	1	0	0	0	1	1

## Translate Boolean Formula to Boolean Circuit

Use sum-of-products form.

- $XOR(x, y) = xy' + x'y$ .

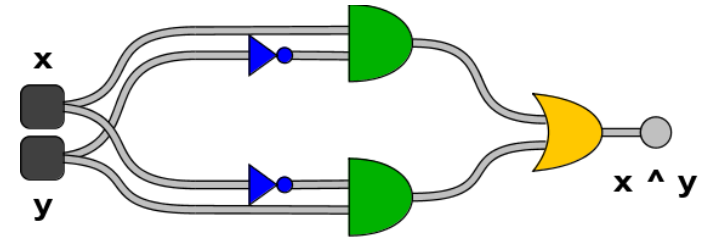


15

16
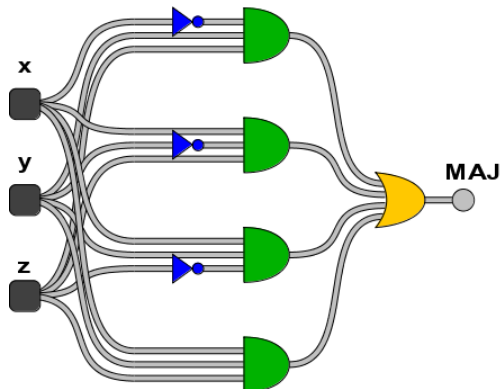
## Translate Boolean Formula to Boolean Circuit

Use sum-of-products form.


- $MAJ(x, y, z) = x'yz + xy'z + xyz' + xyz$ .



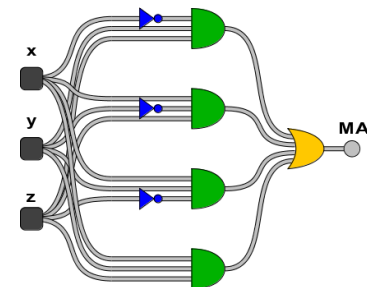
## Simplification Using Boolean Algebra

Many possible circuits for each Boolean function.

- Sum-of-products not necessarily optimal in:
  - number of gates (space)
  - depth of circuit (time)
- $MAJ(x, y, z) = x'yz + xy'z + xyz' + xyz = xy + yz + xz$ .



size = 8, depth = 3

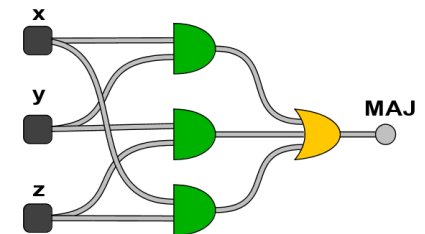

size = 4, depth = 2

17

18

## Expressing a Boolean Function Using AND, OR, NOT

### Ingredients.

- AND gates.
- OR gates.
- NOT gates.
- Wire.

### Instructions.

- Step 1: represent input and output signals with Boolean variables.
- Step 2: construct truth table to carry out computation.
- Step 3: derive (simplified) Boolean expression using sum-of products.
- Step 4: transform Boolean expression into circuit.

## ODD Parity Circuit

### ODD(x, y, z).

- 1 if odd number of inputs are 1.
- 0 otherwise.

Expressing ODD Using Sum-of-Products								
x	y	z	ODD	$x'y'z$	$x'yz'$	$xy'z'$	$xyz$	$x'y'z + x'yz' + xy'z' + xyz$
0	0	0	0	0	0	0	0	0
0	0	1	1	1	0	0	0	1
0	1	0	1	0	1	0	0	1
0	1	1	0	0	0	0	0	0
1	0	0	1	0	0	1	0	1
1	0	1	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0
1	1	1	1	0	0	0	1	1


19

21

## ODD Parity Circuit
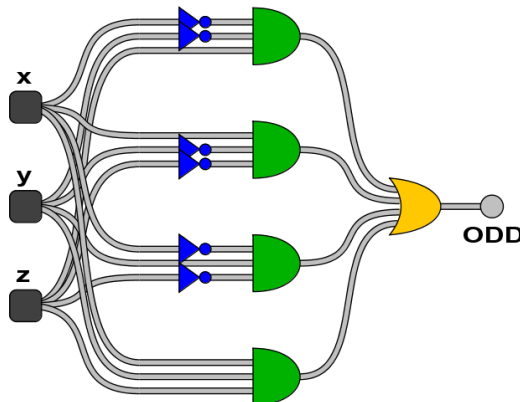
### ODD(x, y, z).

- 1 if odd number of inputs are 1.
- 0 otherwise.



22

## Let's Make an Adder Circuit


### Goal: $x + y = z$ for 4-bit integers.

- We build 4-bit adder: 9 inputs, 4 outputs.
- Same idea scales to 128-bit adder.
- Key computer component.

1	1	1	0
2	4	8	7
+	3	5	7
<hr/>			
6	0	6	6

### Step 1.

- Represent input and output in binary.

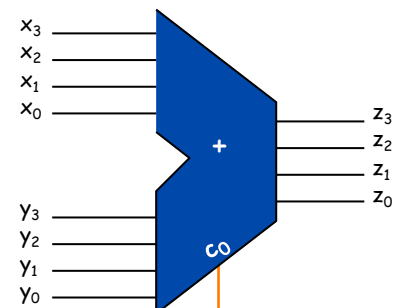

1	1	0	0
0	0	1	0
+	0	1	1
<hr/>			
1	0	0	1

$x_3$	$x_2$	$x_1$	$x_0$
+	$y_3$	$y_2$	$y_1$
<hr/>			
$z_3$	$z_2$	$z_1$	$z_0$

23

## Let's Make an Adder Circuit

Goal:  $x + y = z$  for 4-bit integers.

Step 2. (first attempt)

- Build truth table.
- Why is this a bad idea?
  - 128-bit adder:  $2^{256+1}$  rows > # electrons in universe!

				$c_0$
	$x_3$	$x_2$	$x_1$	$x_0$
+	$y_3$	$y_2$	$y_1$	$y_0$
	$z_3$	$z_2$	$z_1$	$z_0$

4-Bit Adder Truth Table												
$c_0$	$x_3$	$x_2$	$x_1$	$x_0$	$y_3$	$y_2$	$y_1$	$y_0$	$z_3$	$z_2$	$z_1$	$z_0$
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	0	0	0	1	1	0	0	1
0	0	0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	0	0	1	0	1	0	1	0	1
0	0	0	0	0	1	0	0	0	0	1	0	0
0	0	0	0	0	1	0	1	0	1	0	1	1
0	0	0	0	1	0	0	0	0	0	0	0	0
0	0	0	0	1	0	1	0	0	0	0	0	0
0	0	0	0	1	1	0	0	0	0	0	0	0
0	0	0	0	1	1	1	0	0	0	0	0	0
0	0	0	0	1	1	1	1	0	0	0	0	0
0	0	0	0	1	1	1	1	1	0	0	0	0
0	0	0	0	1	1	1	1	1	1	0	0	0
0	0	0	0	1	1	1	1	1	1	1	0	0
0	0	0	0	1	1	1	1	1	1	1	1	0
0	0	0	0	1	1	1	1	1	1	1	1	1

}  $2^{28+1} = 512$  rows!

## Let's Make an Adder Circuit

Goal:  $x + y = z$  for 4-bit integers.

Step 2. (do one bit at a time)

- Build truth table for carry bit.
- Build truth table for summand bit.

				$c_3$	$c_2$	$c_1$	$c_0 = 0$
	$x_3$	$x_2$	$x_1$	$x_0$			
+	$y_3$	$y_2$	$y_1$	$y_0$			
	$z_3$	$z_2$	$z_1$	$z_0$			

Carry Bit			
$x_i$	$y_i$	$c_i$	$c_{i+1}$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Summand Bit			
$x_i$	$y_i$	$c_i$	$z_i$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

## Let's Make an Adder Circuit

Goal:  $x + y = z$  for 4-bit integers.

Step 3.

- Derive (simplified) Boolean expression.

				$c_3$	$c_2$	$c_1$	$c_0 = 0$
	$x_3$	$x_2$	$x_1$	$x_0$			
+	$y_3$	$y_2$	$y_1$	$y_0$			
	$z_3$	$z_2$	$z_1$	$z_0$			

Carry Bit				
$x_i$	$y_i$	$c_i$	$c_{i+1}$	MAJ
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1


Summand Bit				
$x_i$	$y_i$	$c_i$	$z_i$	ODD
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

## Let's Make an Adder Circuit

Goal:  $x + y = z$  for 4-bit integers.

Step 4.

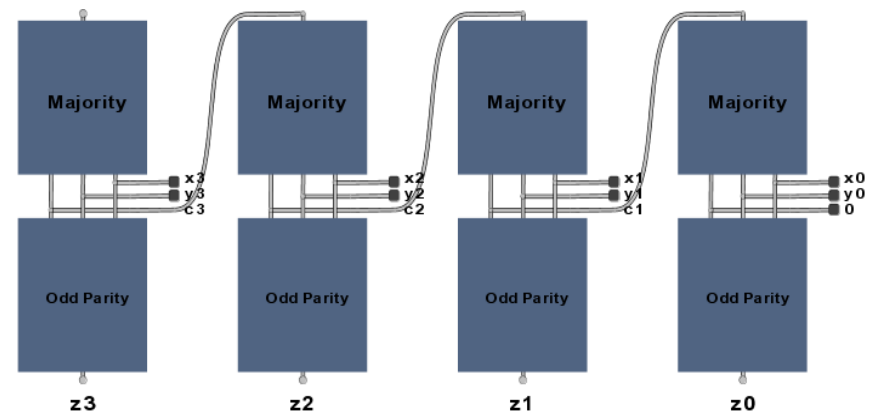- Transform Boolean expression into circuit.
- Chain together 1-bit adders.




## Let's Make an Adder Circuit

Goal:  $x + y = z$  for 4-bit integers.
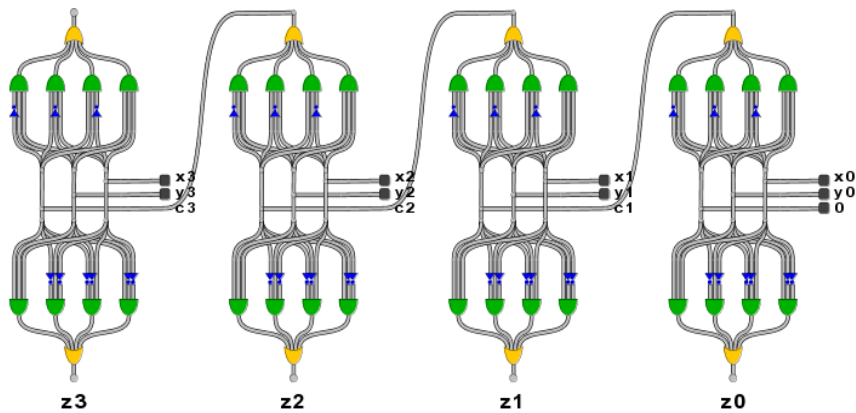
### Step 4.

- Transform Boolean expression into circuit.
- Chain together 1-bit adders.




28

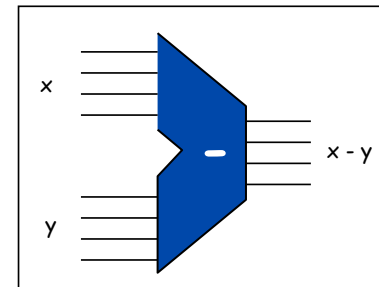
## Subtractor

Subtractor circuit:  $z = x - y$ .

- One approach: design like adder circuit.
- Better idea: reuse adder circuit.
  - 2's complement: to negate an integer, flip bits, then add 1



4-Bit Subtractor Interface

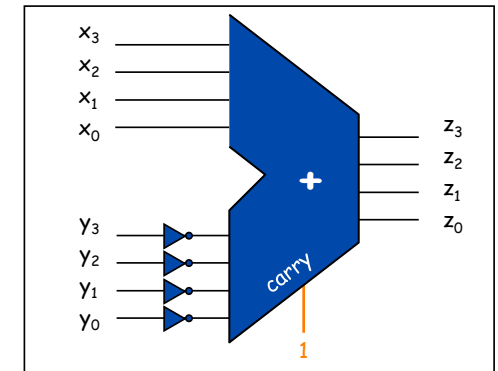

4-Bit Subtractor Implementation


29

## Arithmetic Logic Unit: Interface

### ALU Interface.


- Add, subtract, bitwise and, bitwise xor, shift left, shift right, copy.
- Associate 3-bit integer with 5 primary ALU operations.
  - ALU performs operations in parallel
  - control wires select which result ALU outputs

op	2	1	0
+, -	0	0	0
&	0	0	1
^	0	1	0
<<, >>	0	1	1
input 2	1	0	0

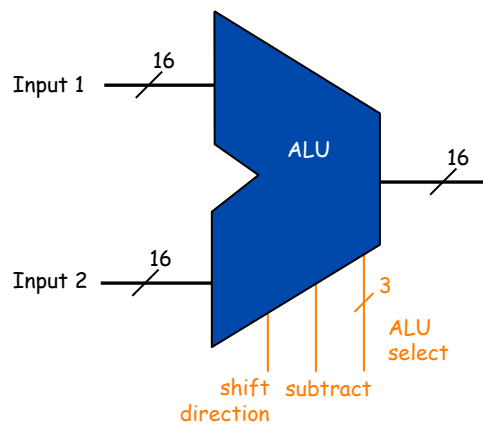

30

## Arithmetic Logic Unit: Implementation

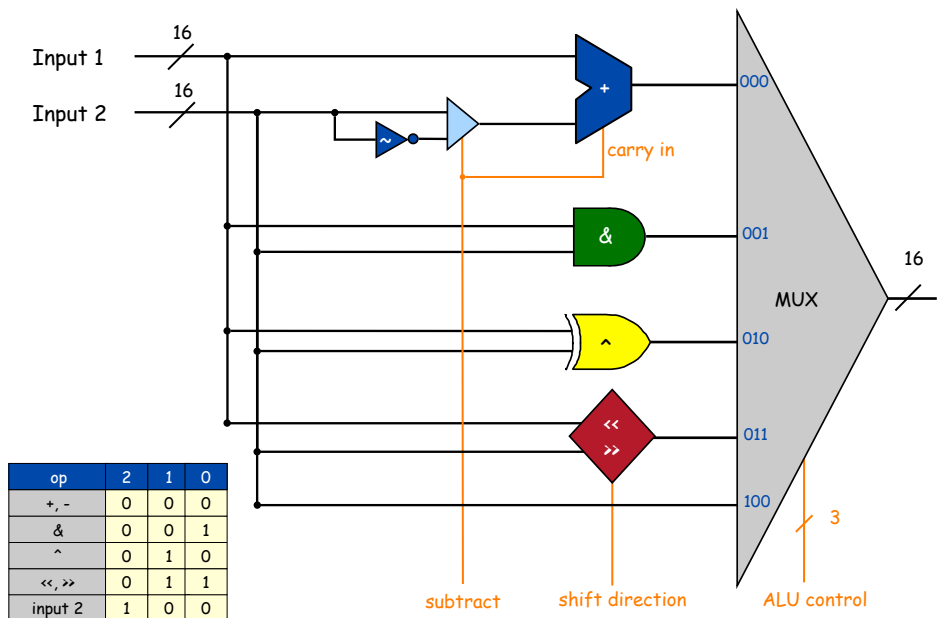

op	2	1	0
+, -	0	0	0
&	0	0	1
^	0	1	0
<<, >>	0	1	1
input 2	1	0	0

31

## Summary

Lessons for software design apply to hardware design!

- Interface describes behavior of circuit.
- Implementation gives details of how to build it.

Layers of abstraction apply with a vengeance!

- On/off.
- Controlled switch (transistor).
- Gates (AND, OR, NOT).
- Boolean circuit (MAJ, ODD).
- Adder.
- ...
- Arithmetic logic unit.
- ...
- TOY machine.