 


6.2: Sequential Circuits




COS126: General Computer Science · <http://www.cs.Princeton.EDU/~cos126>

Last lecture: Boolean logic and combinational circuits.

- Basic abstraction = controlled switch.
- In principle, can build TOY computer with a combinational circuit.
 - $255 \times 16 = 4,080$ inputs $\Rightarrow 2^{4080}$ rows in truth table!
 - no simple pattern
 - each circuit element used at most once

This lecture: reuse circuit elements by storing bits in "memory."

 
Next lecture: glue components together to make TOY computer.



Sequential vs. Combinational Circuits


Combinational circuits.

 - Output determined solely by inputs.
- Can draw solely with left-to-right signal paths.



Sequential circuits.

 - Output determined by inputs AND previous outputs.
- Feedback loop.



Flip-Flop

Flip-flop.


- A small and useful sequential circuit.
- Abstraction that "remembers" one bit.
- Basis of important computer components:
 - memory
 - counter

We will consider several flavors.

SR Flip-Flop

What is the value of Q if:

- S = 1 and R = 0? ⇒ Q is surely 1

 


5

SR Flip-Flop

What is the value of Q if:

 - S = 1 and R = 0? ⇒ Q is surely 1.
- S = 0 and R = 1? ⇒ Q is surely 0




6

SR Flip-Flop

What is the value of Q if:

 - S = 1 and R = 0? ⇒ Q is surely 1.
- S = 0 and R = 1? ⇒ Q is surely 0.
- S = 0 and R = 0? ⇒ Q is possibly 0




7

SR Flip-Flop

What is the value of Q if:

 - S = 1 and R = 0? ⇒ Q is surely 1.
- S = 0 and R = 1? ⇒ Q is surely 0.
- S = 0 and R = 0? ⇒ Q is possibly 0... or possibly 1!




8

SR Flip-Flop

What is the value of Q if:

 - $S = 1$ and $R = 0$? \Rightarrow Q is surely 1.
- $S = 0$ and $R = 1$? \Rightarrow Q is surely 0.
- $S = 0$ and $R = 0$? \Rightarrow Q is possibly 0 . . . or possibly 1.




While $S = R = 0$, Q remembers what it was the last time S or R was 1.


SR Flip-Flop

SR Flip-Flop.

 - $S = 1, R = 0$ (set) \Rightarrow "Flips" bit on.
- $S = 0, R = 1$ (reset) \Rightarrow "Flips" bit off.
- $S = R = 0$ \Rightarrow Status quo.
- $S = R = 1$ \Rightarrow Not allowed.



Implementation

 

Interface

9

10


Truth Table and Timing Diagram

Truth table.

- Values vary over time.
- $S(t), R(t), Q(t)$ denote value at time t.

SR Flip Flop Truth Table			
S(t)	R(t)	Q(t)	Q(t+ ϵ)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	
1	1	1	

Sample timing diagram for SR flip-flop.

 


11

Clock

Clock.

 - Fundamental abstraction.
 - regular on-off pulse
- External analog device.
- Synchronizes operations of different circuit elements.
- 1 GHz clock means 1 billion pulses per second.



12

How much does it Hert?

Frequency is inverse of cycle time.

- Expressed in *hertz*.
- Frequency of 1 Hz means that there is 1 cycle per second.
- Hence:
 - 1 kilohertz (kHz) means 1000 cycles/sec.
 - 1 megahertz (MHz) means 1 million cycles/sec.
 - 1 gigahertz (GHz) means 1 billion cycles/sec.
 - 1 terahertz (THz) means 1 trillion cycles/sec.

By the way, no such thing as 1 "hert" !





Heinrich Rudolf Hertz
(1857-1894)

13

Clocked SR Flip-Flop

Clocked SR Flip-Flop.

  - Same as SR flip-flop except S and R only active when clock is 1.





14

Clocked D Flip-Flop

Clocked D Flip-Flop.

  - Output follows D input while clock is 1.
- Output is remembered while clock is 0.





15

Fetch-Execute Cycle

Fetch-execute cycle for TOY.

- Need 1-bit counter.


 
 


16

1-Bit Counter

1-bit counter.

   - Circuit that oscillates between 1 and 0.






17

1-Bit Counter

1-bit counter.

  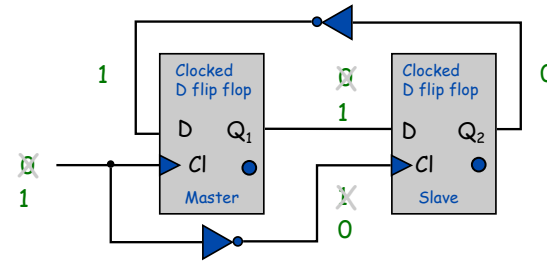- Circuit that oscillates between 1 and 0.






18

1-Bit Counter

1-bit counter.

   - Circuit that oscillates between 1 and 0.






19

1-Bit Counter

1-bit counter.

  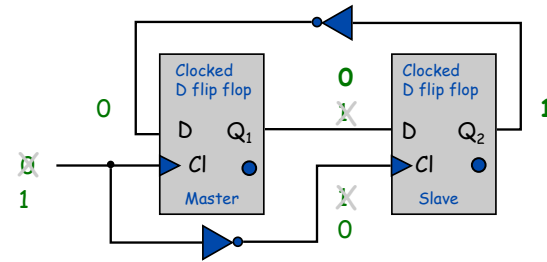- Circuit that oscillates between 1 and 0.




20

1-Bit Counter

1-bit counter.

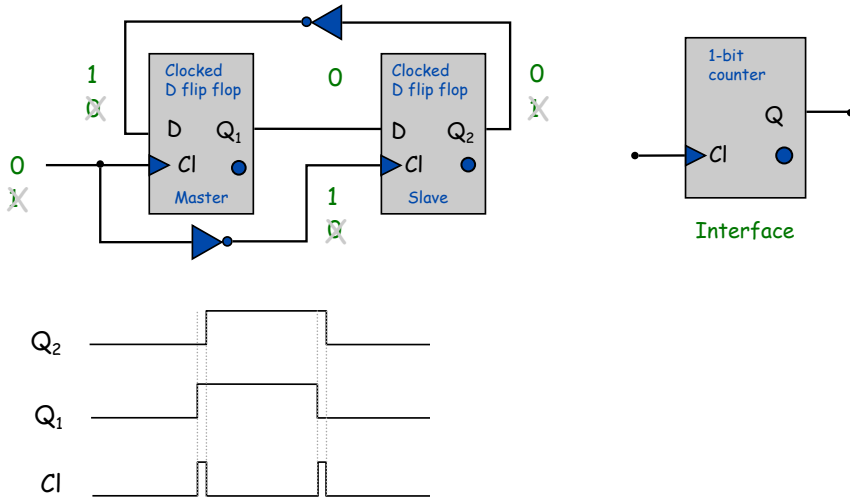- Circuit that oscillates between 1 and 0.




21

1-Bit Counter

1-bit counter.

 - Circuit that oscillates between 1 and 0.





22

Fetch-Execute Cycle

Fetch-execute cycle for TOY.

- Need 1-bit counter.

  

23

Memory Overview

Computers and TOY have many types of memory.

- Program counter.
- Registers.
- Main memory.

We implement each bit of memory with a clocked D flip-flop.

Need mechanism to organize and manipulate GROUPS of related bits.


- TOY has 16-bit words.
- Memory hierarchy makes architecture manageable.

24

Bus

16-bit bus.

 - Bundle of 16 wires.
- Memory transfer, register transfer.



8-bit bus.

- Bundle of 8 wires.
- TOY memory address.



4-bit bus.

- Bundle of 4 wires.
- TOY register address.




25

Stand-Alone Register


k-bit register.

- Stores k bits.
- Register contents always available on output.
- If write enable is asserted, k input bits get copied into register.

 Ex: Program Counter, 16 TOY registers, 256 TOY memory locations.



16-bit Register Interface

 

16-bit Register Implementation

26


Register File Interface

n-by-k register file.

- Bank of n registers; each stores k bits.
- Read and write information to *one* of n registers.
 - $\log_2 n$ address inputs specifies which one
- Addressed bits always appear on output.
- If write enable and clock are asserted, k input bits are copied into addressed register.

 Examples.

- TOY registers: $n = 16, k = 16$.
- TOY main memory: $n = 256, k = 16$.
- Real computer: $n = 256$ million, $k = 32$.
 - 1 GB memory
 - (1 Byte = 8 bits)




256 x 16 Register File Interface

27

Register File Implementation

Implementation example: TOY main memory.

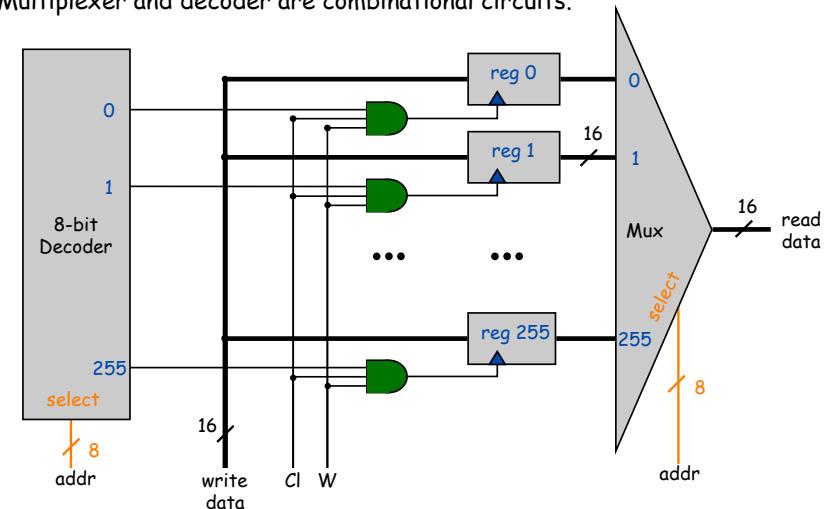- Use 256 16-bit registers.
- Multiplexer and decoder are combinational circuits.




28

Register File Implementation: Reading

Implementation example: TOY main memory.

 - Use 256 16-bit registers.
- Multiplexer is combinational circuit.




29

2ⁿ-to-1 Multiplexer


◀ n = 8 for main memory

2ⁿ-to-1 multiplexer.

 - n select inputs, 2ⁿ data inputs, 1 output.
- Copies "selected" data input bit to output.



8-to-1 Mux Interface

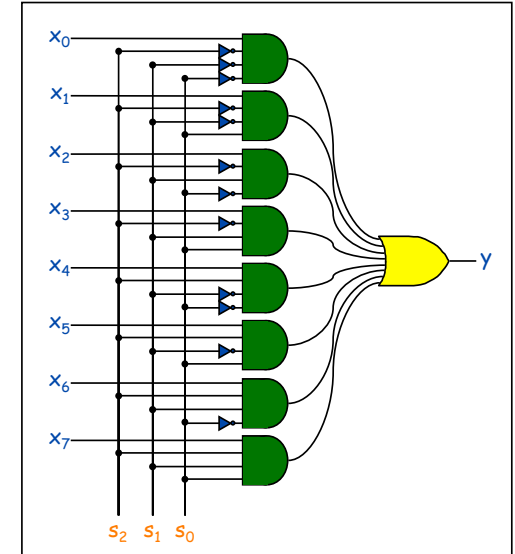

8-to-1 Mux Implementation


30

2ⁿ-to-1 Multiplexer


◀ n = 8 for main memory

2ⁿ-to-1 multiplexer.

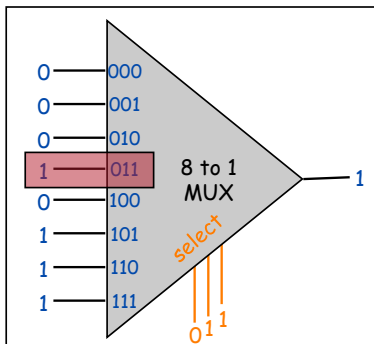- n select inputs, 2ⁿ data inputs, 1 output.
- Copies "selected" data input bit to output.



8-to-1 Mux Interface

 

8-to-1 Mux Implementation


31

2ⁿ-to-1 Multiplexer, Width = k


◀ n = 8, k = 16 for main memory

2ⁿ-to-1 multiplexer, width = k.

 - Select from one of 2ⁿ k-bit buses.
- Copies k "selected" data bits to output.
- Layering k 2ⁿ-to-1 multiplexers.



Interface for 2-to-1 MUX, width = 4

 


Implementation for 2-to-1 MUX, width = 4

32

Register File Implementation: Writing

Implementation example: TOY main memory.

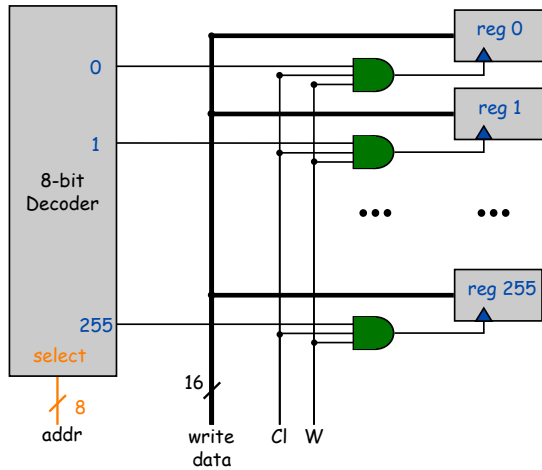- Use 256 16-bit registers.
- Decoder is combinational circuit.




33

n-Bit Decoder


n = 8 for main memory

n-bit decoder.

 - n address inputs, 2^n data outputs.
- Addressed output bit is 1; others are 0.



3-Bit Decoder Interface

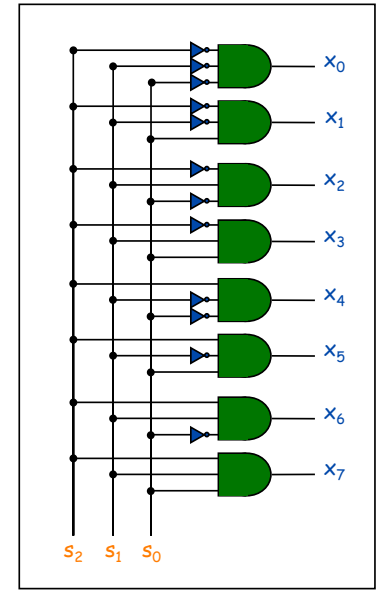

3-Bit Decoder Implementation


34

n-Bit Decoder


n = 8 for main memory

n-bit decoder.

 - n address inputs, 2^n data outputs.
- Addressed output bit is 1; others are 0.



3-Bit Decoder Interface

 


3-Bit Decoder Implementation

35

Register File Implementation: Reading and Writing

Implementation example: TOY main memory.

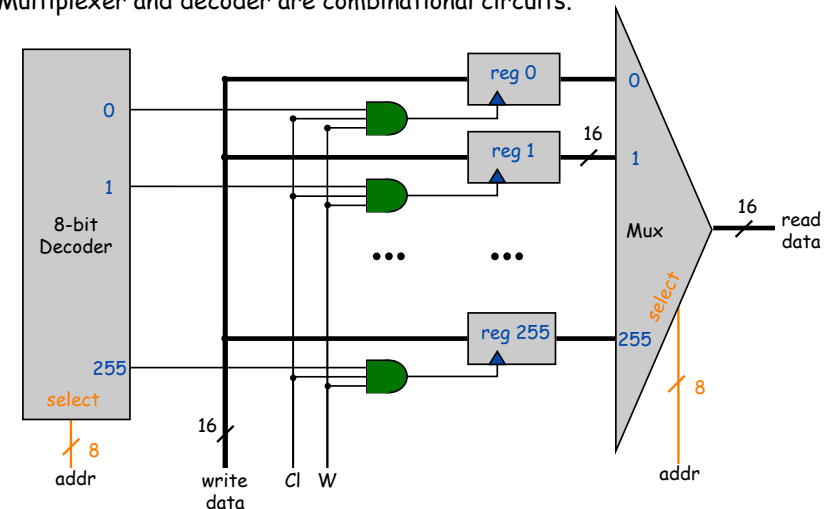- Use 256 16-bit registers.
- Multiplexer and decoder are combinational circuits.



36

Summary

Sequential circuits add "state" to digital hardware.

- Flip-flop. Represents 1 bit.
- TOY register. 16 D flip-flops.
- TOY main memory. 256 registers.

Actual technologies for register file and memory are different.

- Register files are relatively small and very fast.
 - expensive per bit
- Memories are relatively large and pretty fast.
 - amazingly cheap per bit
- Drastic evolution of technology over time

Next time: we build a complete TOY computer.