

Combinational Circuits

Q. What is a combinational circuit?

A. Digital: signals are 0 or 1. ← analog circuits: signals vary continuously

A. No feedback: no loops. ← sequential circuits: loops allowed (stay tuned)

Q. Why combinational circuits?

A. Accurate, reliable, general purpose, fast, cheap.

Basic abstractions.

- On, off.
- Wire: propagates on/off value.
- Switch: controls propagation of on/off values through wires.

Applications. Cell phone, iPod, antilock brakes, **microprocessors**, ...




Building Blocks

Wires

Wires.

 - ON (1): connected to power.
- OFF (0): not connected to power.
- If a wire is connected to a wire that is on, that wire is also on.
- Typical drawing convention: "flow" from top, left to bottom, right.



Controlled Switch



Controlled switch.

- 3 connections: input, output, control.

Controlled Switch

Controlled switch.

  
- 3 connections: input, output, control.
- control OFF: output is **connected** to input



Controlled Switch

Controlled switch.




 
- 3 connections: input, output, control.
- control ON: output is **disconnected** from input



Controlled Switch

Controlled switch.

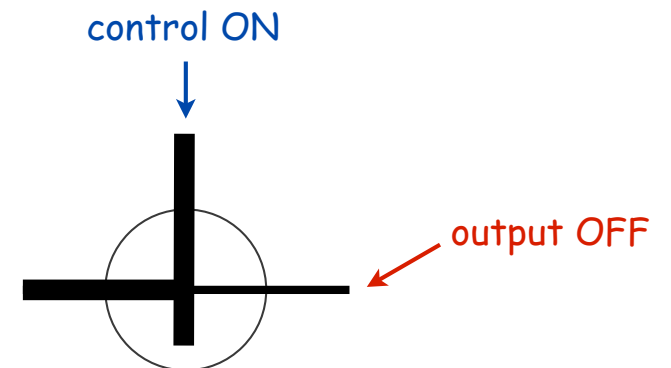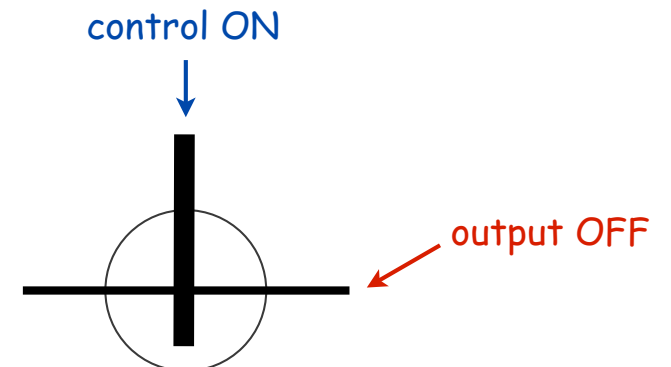 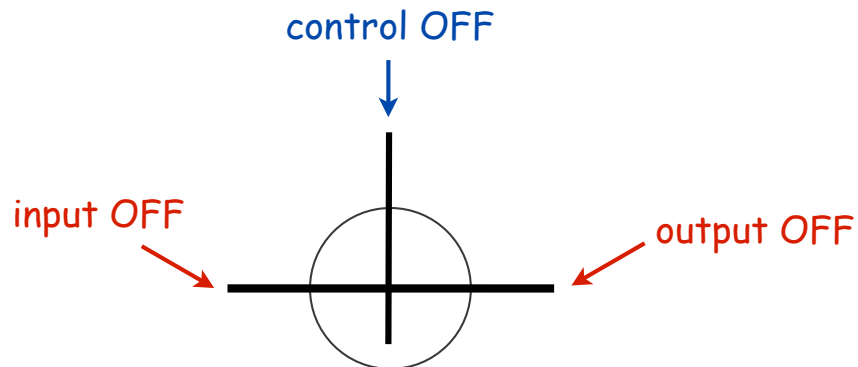- 3 connections: input, output, control.
- control OFF: output is **connected** to input
- control ON: output is **disconnected** from input




idealized model of "pass transistors" found in real integrated circuits

Implementing a Controlled Switch

Relay implementation.

 - 3 connections: input, output, control.
- Magnetic force pulls on a contact that cuts electrical flow.



First Level of Abstraction

Separates physical world from logical world.

- we assume that switches operate as specified
- that is the only assumption
- physical realization of switch is irrelevant to design

Physical realization dictates performance


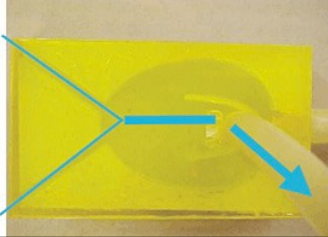

- size
- speed
- power

New technology **immediately** gives new computer.

Better switch? Better computer.






Controlled Switches: A First Level of Abstraction

Some amusing attempts to prove the point:

Technology	"Information"	Switch
pneumatic	air pressure	
fluid	water pressure	
relay	electric potential	

Controlled Switches: A First Level of Abstraction

Real-world examples that prove the point:

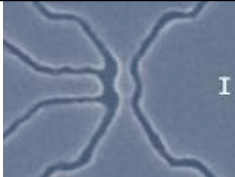technology	switch
relay	
vacuum tube	
transistor	
"pass transistor" in integrated circuit	
atom-thick transistor	

Controlled Switches: A First Level of Abstraction ?

VLSI = Very Large Scale Integration

Technology:

Deposit materials on substrate.

Key property:

Crossing lines are controlled switches.

Key challenge in physical world:


Fabricating physical circuits
with billions of controlled switches

Key challenge in "abstract" world:


Understanding behavior of circuits
with billions of controlled switches

Bottom line: Circuit = Drawing (!)


drawing

 


drawing

 

circuit

 

Circuit Anatomy


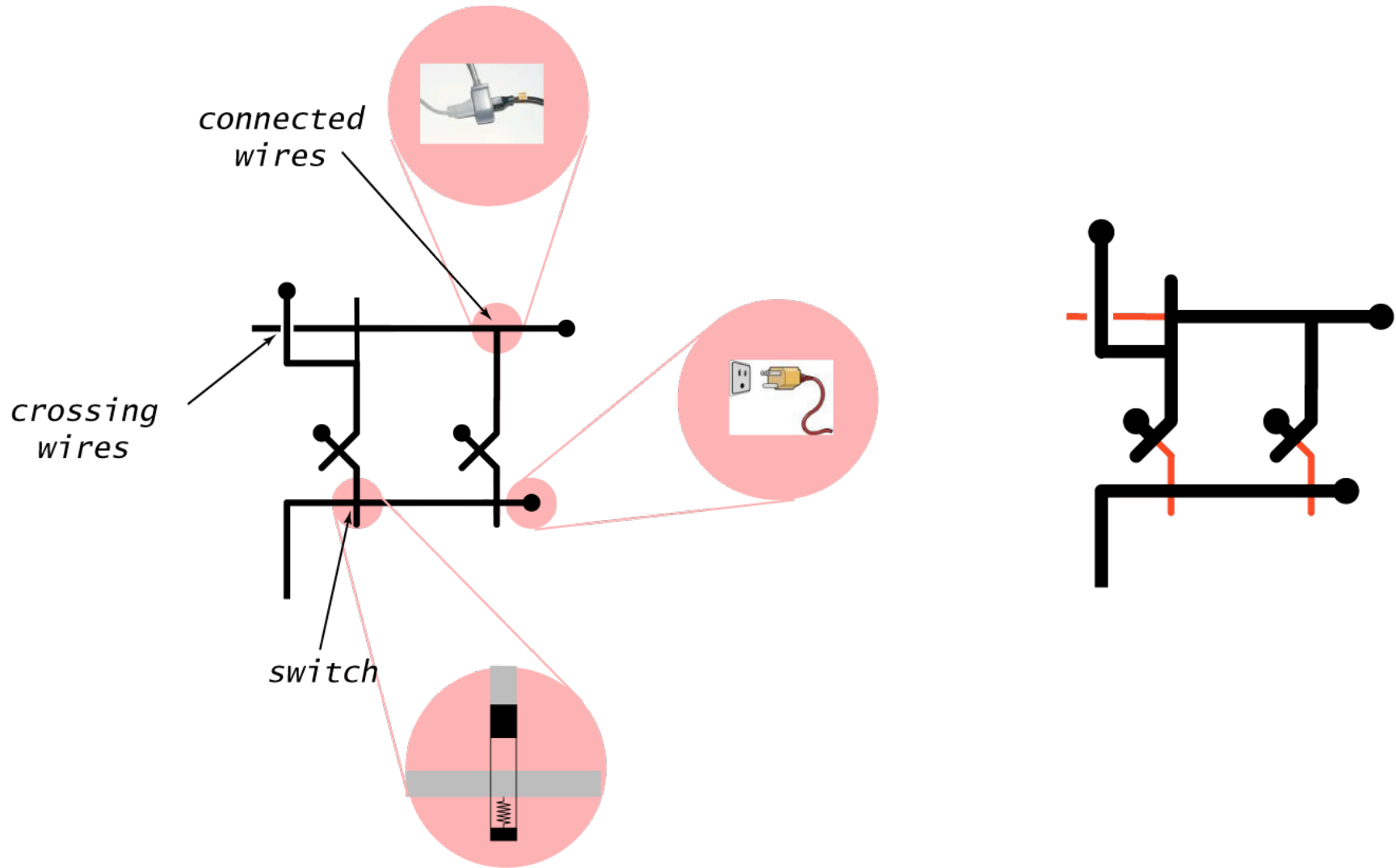


need more "levels of abstraction" to understand circuit behavior

Second Level of Abstraction: Logic Gates



NOT = x'

x	NOT
0	1
1	0

  



OR = $x+y$

x	y	OR
0	0	0
0	1	1
1	0	1
1	1	1

  

AND = xy




x	y	AND
0	0	0
0	1	0
1	0	0
1	1	1

  

Second Level of Abstraction: Logic Gates




NOT = x'

x	NOT
0	1
1	0

   




OR = $x+y$

x	y	OR
0	0	0
0	1	1
1	0	1
1	1	1

   

AND = xy

x	y	AND
0	0	0
0	1	0
1	0	0
1	1	1

 
 
 


implementations with switches




Multiway Gates

Multiway gates.

   - OR: 1 if any input is 1; 0 otherwise.
- AND: 1 if all inputs are 1; 0 otherwise.
- Generalized: negate some inputs.



symbol

 
 
 


gate




Multiway Gates

Multiway gates.

   - OR: 1 if any input is 1; 0 otherwise.
- AND: 1 if all inputs are 1; 0 otherwise.
- Generalized: negate some inputs.



symbol

   

gate


Building blocks (summary)

Wires

Controlled switches

Gates

Generalized multiway gates

 


Boolean Algebra

Boolean Algebra

History.

- Developed by Boole to solve mathematical logic problems (1847).
- Shannon master's thesis applied it to digital circuits (1937).

 ↖ “possibly the most important, and also the most famous, master's thesis of the [20th] century” — Howard Gardner



Boolean algebra.

- Boolean variable: value is 0 or 1.
- Boolean function: function whose inputs and outputs are 0, 1.

Relationship to circuits.

- Boolean variable: signal.
- Boolean function: circuit.



Copyright 2004, Sidney Harris
<http://www.sciencecartoonsplus.com>






Truth Table

Truth table.

- Systematic method to describe Boolean function.
- One row for each possible input combination.
- n inputs $\Rightarrow 2^n$ rows.

x	y	$x y$
0	0	0
0	1	0
1	0	0
1	1	1

AND truth table

     

Truth Table for Functions of 2 Variables

Truth table.

- 16 Boolean functions of 2 variables.


← every 4-bit value represents one

x	y	<i>ZERO</i>	<i>AND</i>		x		y	<i>XOR</i>	<i>OR</i>
0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1

truth table for all Boolean functions of 2 variables

x	y	<i>NOR</i>	<i>EQ</i>	y'		x'		<i>NAND</i>	<i>ONE</i>
0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1

 truth table for all Boolean functions of 2 variables



Truth Table for Functions of 3 Variables

Truth table.

- 16 Boolean functions of 2 variables.
- 256 Boolean functions of 3 variables.
- $2^{(2^n)}$ Boolean functions of n variables!

← every 4-bit value represents one

← every 8-bit value represents one

← every 2^n -bit value represents one

x	y	z	AND	OR	MAJ	ODD
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	0	1	0	1
0	1	1	0	1	1	0
1	0	0	0	1	0	1
1	0	1	0	1	1	0
1	1	0	0	1	1	0
1	1	1	1	1	1	1

some functions of 3 variables

Universality of AND, OR, NOT

Fact. Any Boolean function can be expressed using *AND*, *OR*, *NOT*.

- {*AND*, *OR*, *NOT*} are **universal**.
- **Ex:** $XOR(x, y) = xy' + x'y$.

notation	meaning
x'	<i>NOT</i> x
$x y$	x <i>AND</i> y
$x + y$	x <i>OR</i> y

Expressing *XOR* Using *AND*, *OR*, *NOT*

x	y	x'	y'	$x'y$	xy'	$x'y + xy'$	$x \text{ XOR } y$
0	0	1	1	0	0	0	0
0	1	1	0	1	0	1	1
1	0	0	1	0	1	1	1
1	1	0	0	0	0	0	0

Exercise. Show {*AND*, *NOT*} are universal. (Hint: DeMorgan's law: $(x' y) = x + y$.)

Exercise. Show {*NOR*} is universal. (Stay tuned for easy proof)

Sum-of-Products

Sum-of-products. Systematic procedure for representing a Boolean function using *AND*, *OR*, *NOT*.



proves that $\{ AND, OR, NOT \}$ are universal

- Form *AND* term for each 1 in Boolean function.
- *OR* terms together.

x	y	z	MAJ	$x'yz$	$xy'z$	xyz'	xyz	$x'yz + xy'z + xyz' + xyz$
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0
0	1	1	1	1	0	0	0	1
1	0	0	0	0	0	0	0	0
1	0	1	1	0	1	0	0	1
1	1	0	1	0	0	1	0	1
1	1	1	1	0	0	0	1	1

expressing *MAJ* using sum-of-products

Translate Boolean Formula to Boolean Circuit

Sum-of-products. *XOR*.

$$XOR = x'y + xy'$$

<i>x</i>	<i>y</i>	<i>XOR</i>
0	0	0
0	1	1
1	0	1
1	1	0

Truth table




Circuit

Translate Boolean Formula to Boolean Circuit

Sum-of-products. *XOR*.


Key transformation from abstract to real circuit

$$XOR = x'y + xy'$$

 


x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0

Truth table

 

Abstract circuit

 


Circuit

Translate Boolean Formula to Boolean Circuit

Example 1. XOR.


Key transformation from abstract to real circuit

$$XOR = x'y + xy'$$

 


x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0

Truth table

 

Abstract circuit

 

Circuit

Translate Boolean Formula to Boolean Circuit

Example 2. Majority.

$$MAJ = x'yz + xy'z + xyz' + xyz$$

x	y	z	MAJ
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Truth table




Circuit

Translate Boolean Formula to Boolean Circuit

Example 2. Majority.


$$MAJ = x'yz + xy'z + xyz' + xyz$$

x	y	z	MAJ
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

Truth table

Abstract circuit

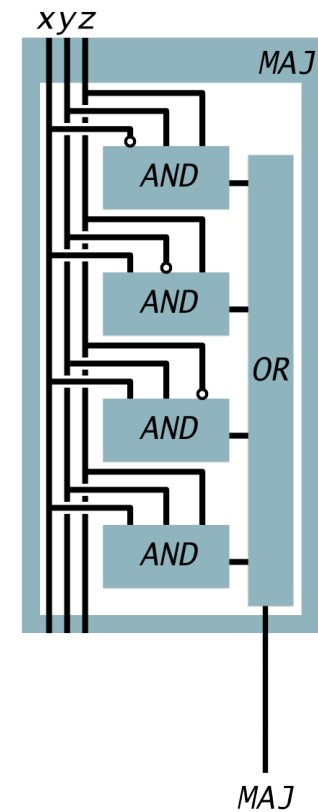


Circuit

Translate Boolean Formula to Boolean Circuit

Example 2. Majority.


$$MAJ = x'yz + xy'z + xyz' + xyz$$

x	y	z	MAJ
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

Truth table

Abstract circuit

 


Circuit

Translate Boolean Formula to Boolean Circuit

Example 2. Majority.

$$MAJ = x'yz + xy'z + xyz' + xyz$$

x	y	z	MA.
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

Truth table

Abstract circuit


Circuit

Simplification Using Boolean Algebra


Many possible circuits for each Boolean function.

- Sum-of-products not necessarily optimal in:
 - number of switches (space)
 - depth of circuit (time)

 Ex. $MAJ(x, y, z) = x'yz + xy'z + xyz' + xyz = xy + yz + xz$.



size = 10, depth = 2

 

size = 7, depth = 2

Combinational Circuit Design: Summary

Problem: Compute the value of a boolean function

Ingredients.

- *AND* gates.
- *OR* gates.
- *NOT* gates.
- Wire.

Instructions.

- Step 1: represent input and output signals with Boolean variables.
- Step 2: construct truth table to carry out computation.
- Step 3: derive (simplified) Boolean expression using sum-of products.
- Step 4: transform Boolean expression into circuit.

Bottom line (profound idea):


It is easy to design a circuit to compute *ANY* boolean function.

Caveat (stay tuned): Circuit might be huge.

Translate Boolean Formula to Boolean Circuit

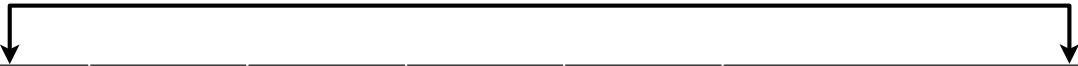Example 3. Odd parity

- 1 if odd number of inputs are 1.
- 0 otherwise.



x	y	z	ODD	$x'y'z$	$x'yz'$	$xy'z'$	xyz	$x'y'z + x'yz' + xy'z' + xyz$
0	0	0	0	0	0	0	0	0
0	0	1	1	1	0	0	0	1
0	1	0	1	0	1	0	0	1
0	1	1	0	0	0	0	0	0
1	0	0	1	0	0	1	0	1
1	0	1	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0
1	1	1	1	0	0	0	1	1

Expressing ODD using sum-of-products

Translate Boolean Formula to Boolean Circuit

Example 3. Odd parity

- 1 if odd number of inputs are 1.
- 0 otherwise.

$$MAJ = x'yz + xy'z + xyz' + xyz$$

x	y	z	MAJ
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



$$ODD = x'y'z + x'yz' + xy'z' + xyz$$

x	y	z	ODD
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1




Translate Boolean Formula to Boolean Circuit


Example 3. Odd parity

- 1 if odd number of inputs are 1.
- 0 otherwise.

$$MAJ = x'yz + xy'z + xyz' + xyz$$

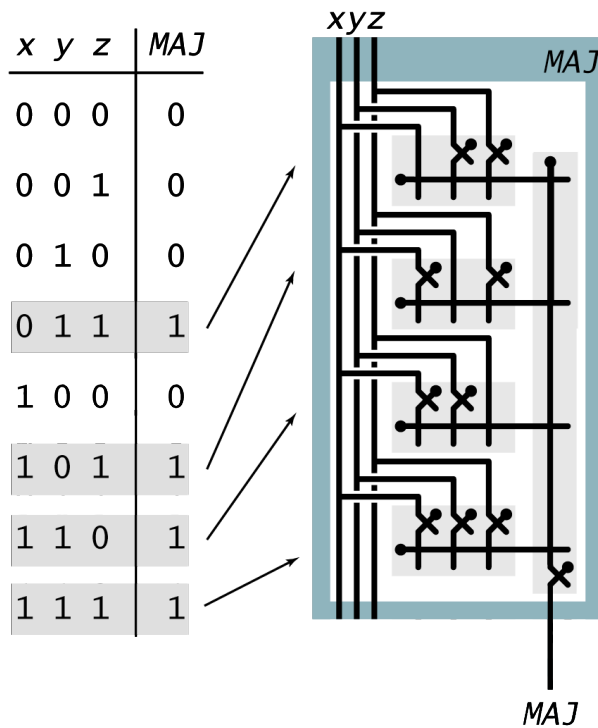

$$ODD = x'y'z + x'yz' + xy'z' + xyz$$

 

Adder Circuit

Let's Make an Adder Circuit

Goal. $x + y = z$ for 4-bit integers.

same idea scales to 64-bit adder in your computer


- We build 4-bit adder: 9 inputs, 4 outputs.
- Each output bit is a **boolean function** of the inputs.
- Standard method applies.

Step 1. Represent input and output in binary.

	1	1	1	0
	2	4	8	7
+	3	5	7	9
	6	0	6	6

	1	1	0	0
	0	0	1	0
+	0	1	1	1
	1	0	0	1

	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
	z_3	z_2	z_1	z_0

 

Let's Make an Adder Circuit

Goal. $x + y = z$ for 4-bit integers.

Step 2. [first attempt]

- Build truth table.

c_{out}	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
	z_3	z_2	z_1	z_0

4-bit adder truth table

c_0	x_3	x_2	x_1	x_0	y_3	y_2	y_1	y_0	z_3	z_2	z_1	z_0
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	0	0	0	1	1	0	0	1	1
0	0	0	0	0	0	1	0	0	0	1	0	0
.
1	1	1	1	1	1	1	1	1	1	1	1	1

} $2^{8+1} = 512$ rows!

Q. Why is this a bad idea?

A. 128-bit adder: 2^{256+1} rows \gg # electrons in universe!

Let's Make an Adder Circuit

Goal. $x + y = z$ for 4-bit integers.

Step 2. Do one bit at a time!

- Build truth table for carry bit.
- Build truth table for summand bit.

c_{out}	c_3	c_2	c_1	$c_0 = 0$
	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
	z_3	z_2	z_1	z_0

carry bit

x_i	y_i	c_i	c_{i+1}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

summand bit

x_i	y_i	c_i	z_i
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Let's Make an Adder Circuit

Goal. $x + y = z$ for 4-bit integers.

c_{out}	c_3	c_2	c_1	$c_0 = 0$
	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
	z_3	z_2	z_1	z_0

Step 3. A surprise!

- carry bit is **majority** function
- summand bit is **odd parity** function.

carry bit

x_i	y_i	c_i	c_{i+1}	<i>MAJ</i>
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

summand bit


x_i	y_i	c_i	z_i	<i>ODD</i>
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Let's Make an Adder Circuit


Goal. $x + y = z$ for 4-bit integers.

Step 4.

 - Transform Boolean expression into circuit (use known components!).
- Chain together 1-bit adders.
- That's it!




Adder: Interface

 


A **bus** is a group of wires that connect (carry data values) to other components.

Adder: Component Level View

 


Adder: Switch Level View

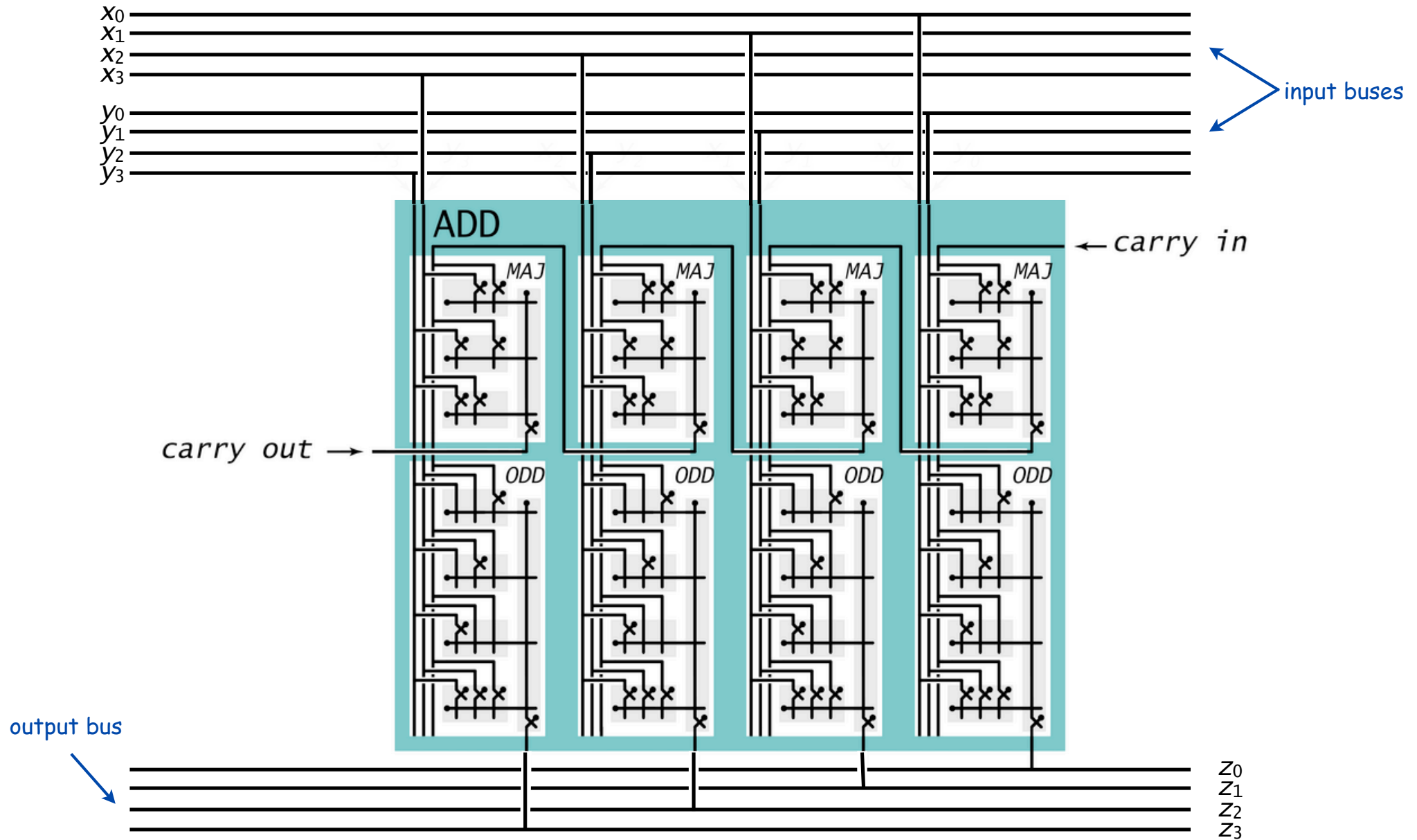


Useful Combinational Circuits


Adder

 

Incrementer (easy, add 0001)

 


Bitwise AND, XOR (easy)

 

Decoder [next slide]

Shifter (clever, but we'll skip details)

Multiplexer [next lecture]

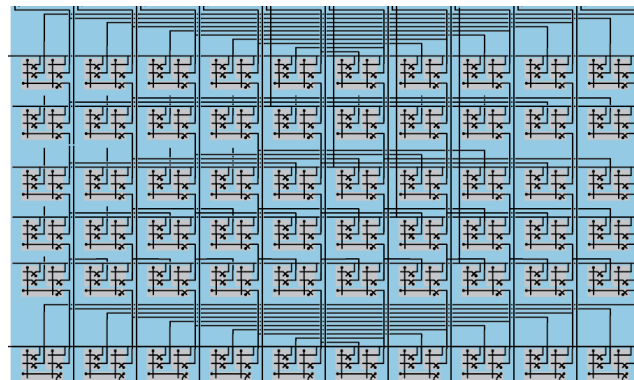


Decoder

Decoder. [n-bit]

- n address inputs, 2^n data outputs.
- Addressed output bit is 1; others are 0.
- Compact implementation of n Boolean functions

x_0	x_1	x_2	z_0	z_1	z_2	z_3	z_4	z_5	z_6	z_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 


3-bit Decoder

Decoder

Decoder. [n-bit]

- n address inputs, 2^n data outputs.
- Addressed output bit is 1; others are 0.
- Compact implementation of n Boolean functions

x_0	x_1	x_2	z_0	z_1	z_2	z_3	z_4	z_5	z_6	z_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 

3-bit Decoder

Decoder application: Your computer's ALU!

ALU: Arithmetic and Logic Unit


- implements instructions
- input, output connects to registers via buses

Ex: TOY-Lite (10 bit words)

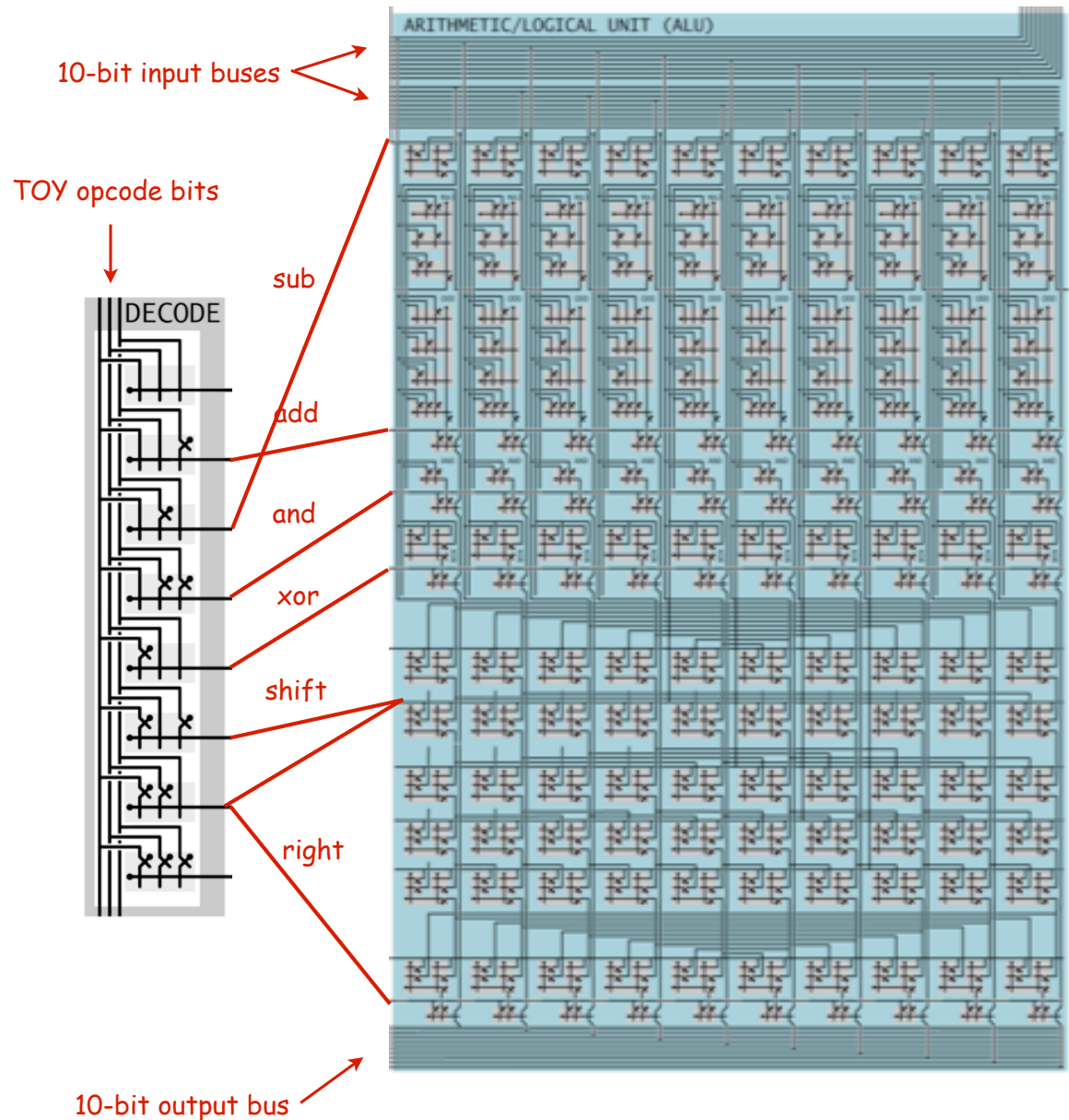- 1: add
- 2: subtract
- 3: and
- 4: xor
- 5: shift left
- 6: shift right

Details:


- All circuits compute their result.
- Decoder lines AND all results.
- "one-hot" OR collects answer.



Summary

Lessons for software design apply to hardware design!

 - Interface describes behavior of circuit.
- Implementation gives details of how to build it.



Layers of abstraction apply with a vengeance!

- On/off.
- Controlled switch. [relay, transistor]
- Gates. [AND, OR, NOT]
- Boolean circuit. [MAJ, ODD]
- Adder.
- Shifter.
- Arithmetic logic unit.
- ...
- TOY machine (stay tuned).
- Your computer.

