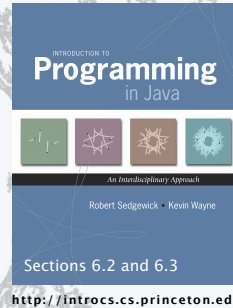


<http://xkcd.com/730/>

1



<http://introc.cs.princeton.edu>

21. Central Processing Unit

Let's build a computer!

CPU = Central Processing Unit

Computer

- Display
- Touchpad
- Battery
- Keyboard
- ...
- CPU (difference between a TV set and a computer)

Previous lecture

- Combinational circuits
- ALU (calculator)

This lecture

- Sequential circuits with *memory*
- CPU (computer)



CPU →



3

A smaller computing machine: TinyTOY

TOY instruction-set architecture.

- 256 16-bit words of memory.
- 16 16-bit registers.
- 1 8-bit program counter.
- 2 instruction types
- 16 instructions.




Type 1 instruction



4 bits to specify one of 16 registers

Type 2 instruction

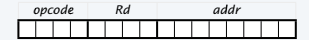


8 bits to specify one of 256 memory words

TinyTOY instruction-set architecture.

- 16 10-bit words of memory.
- 4 10-bit registers.
- 1 4-bit program counter.
- 2 instruction types
- 16 instructions.




Type 1 instruction

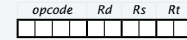

2 bits to specify one of 4 registers

Type 2 instruction

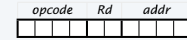

4 bits to specify one of 16 memory words

Purpose of TinyTOY. Illustrate CPU circuit design for a "typical" computer.

4

Review: the state of the machine

Contents of memory, registers, and PC at a particular time

- Provide a **record** of what a program has done.
- **Completely determines** what the machine will do.

ALU and IR hold
intermediate states
of computation




5

CPU circuit components for TinyTOY

TinyTOY CPU

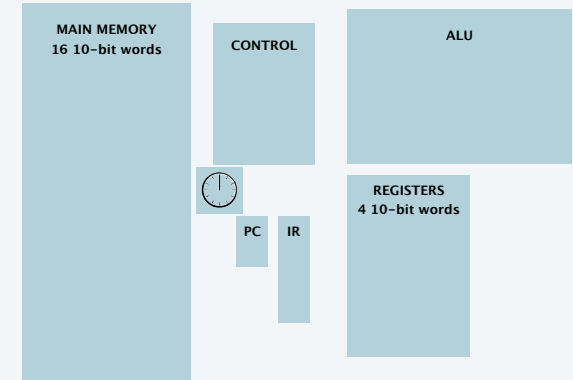- ALU
- Memory
- Registers
- PC
- Control
- Clock




Goal. Complete CPU circuit for TinyTOY (same design extends to TOY and to your computer).

6

Perspective

Q. Why TinyTOY?

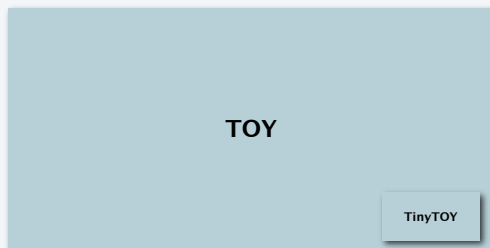A. Toy circuit width would be about 5 times TinyTOY circuit width.




Sobering fact. The circuit for your computer is *hundreds to thousands* of times wider.

Reassuring fact. Design of all three is based on the same fundamental ideas.

7

COMPUTER SCIENCE
SEDGWICK / WAYNE

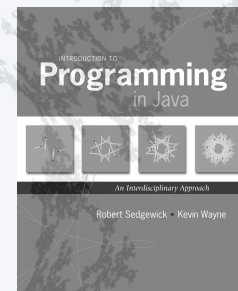

<http://introcs.cs.princeton.edu>

21. CPU

- Bits and registers
- Main memory and register banks
- Program counter
- Putting the pieces together

Sequential circuits

Q. What is a sequential circuit?

A. A digital circuit (all signals are 0 or 1) *with feedback* (loops).

Q. Why sequential circuits?

A. *Memory* (difference between a DFA and a Turing machine).

Basic abstractions


- On and off.
- Wire: Propagates an on/off value.
- Switch: Controls propagation of on/off values through wires.
- Flip-flop: *Remembers* a value.

9

A new ingredient: Circuits with memory



Feedback leads to circuits with one of two states

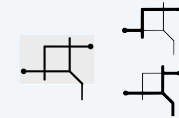- Ex. two switches, each blocked by the other.
- State determined by whichever switches first.
- Stable (once set, state never changes).



An SR flip-flop is two cross-coupled NOR gates.

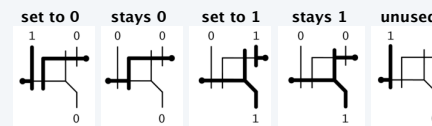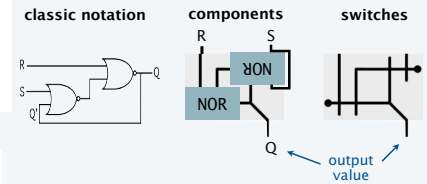- Adds an extra line to each switch.
- R (reset) sets state to 0.
- S (set) sets state to 1.



Note. Feedback with three switches is *not* stable.




Caveat. Timing of switch vs. propagation delay.

10

One bit in a processor register (PC and IR)

Add logic to an SR flip-flop for more precise control

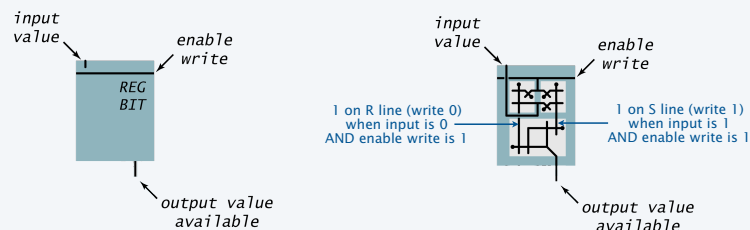- Provide data value on an input wire instead of using S and R controls.
- Use *enable write* signal to control timing of write.
- Flip-flop value is always available.



11


Processor registers

Processor registers (PC and IR)


- Store W bits.
- Input and output on W -wire busses.
- Register contents always available on output bus.
- When enable write is asserted, W input bits get copied into register.

Ex 1. PC holds 4-bit address.

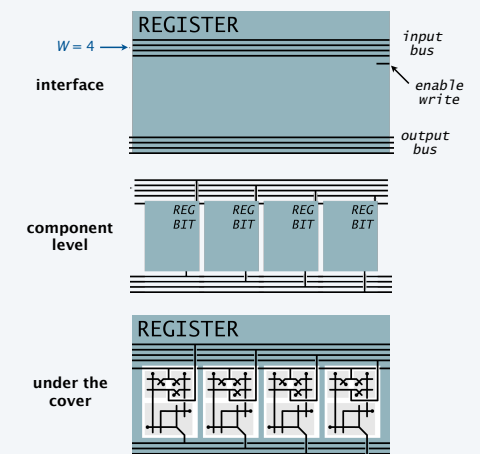Ex 2. IR holds 10-bit current instruction.




12

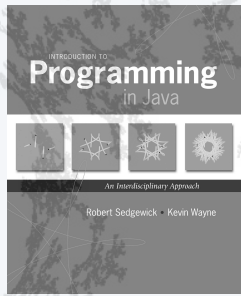

21. CPU

- Bits and registers
- Main memory and register banks
- Program counter
- Putting the pieces together

<http://introc.cs.princeton.edu>

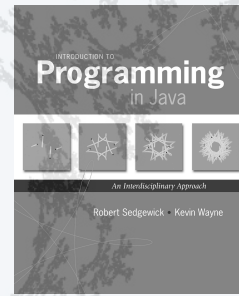

21. CPU


- Bits and registers
- Main memory and register banks
- Program counter
- Putting the pieces together

<http://introc.cs.princeton.edu>

One bit in a main memory bank

Add a selection mechanism

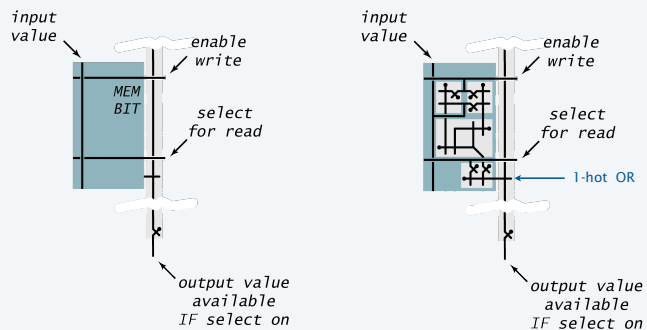- Flip-flop value is *not* always available.
- Use *select for read* signal to make it available.
- "1-hot" OR to collect the one bit value that is selected.




15

Main memory bank: interface

Main memory bank.

- Bank of N words; each stores W bits.
- Read and write data to one of N words.
- Address inputs select one word.
- Addressed word always on output bus.
- When write enabled, W input bits are copied into addressed word.

	number of words	bits per word	address bits
this slide	4	6	2
tinyTOY	16	10	4
TOY	256	16	8
your computer	1 billion	64	32

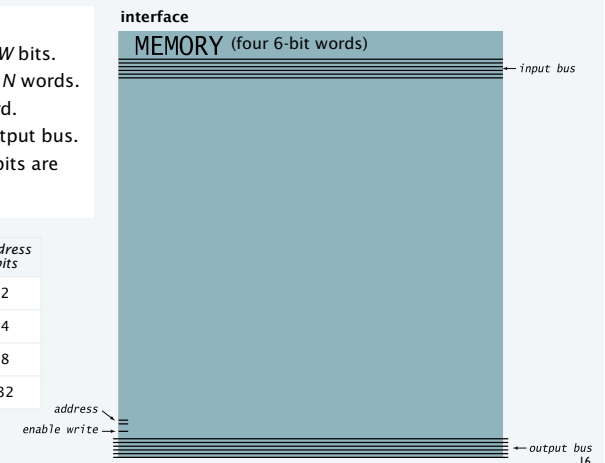

16

Main memory bank: component level


Main memory bank.

- Bank of N words; each stores W bits.
- Read and write data to one of N words.
- Address inputs select one word.
- Addressed word always on output bus.
- When write enabled, W input bits are copied into addressed word.

Basic mechanisms

- A decoder uses address to switch on one line (through the addressed word)
- "1-hot" OR gates at each bit position take word contents to the output bus.

Example: Read word 2 (10)

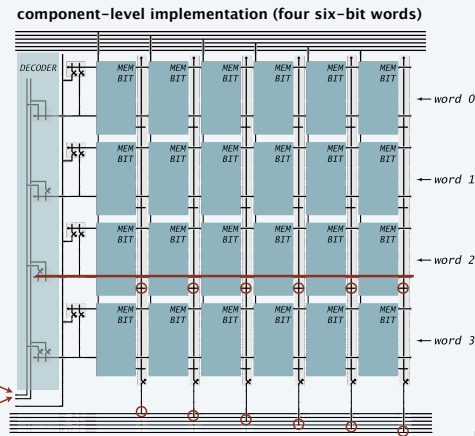


17

Main memory bank: switch level

Main memory bank.

- Bank of N words; each stores W bits.
- Read and write data to one of N words.
- Address inputs select one word.
- Addressed word always on output bus.
- When write enabled, W input bits are copied into addressed word.

switch-level implementation

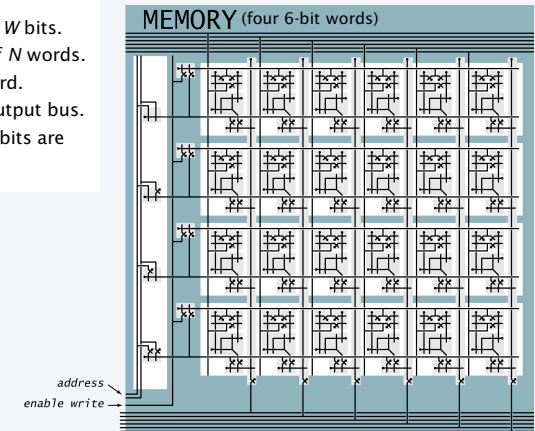

18


TinyTOY main memory bank

Interface

- Input bus for "store"
- Output bus for "load"
- Address bits to select a word
- *Enable write* control signal

Connections

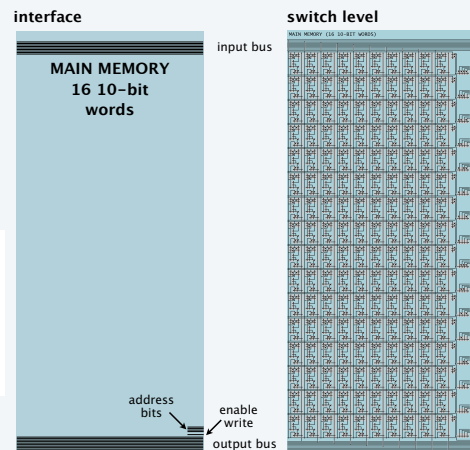- Input bus from registers
- Output bus to IR and registers
- Address bits from PC, IR, registers
- *Enable write* from "control"





19

One bit in a TinyTOY register bank

Need a second selection mechanism to read two registers at once

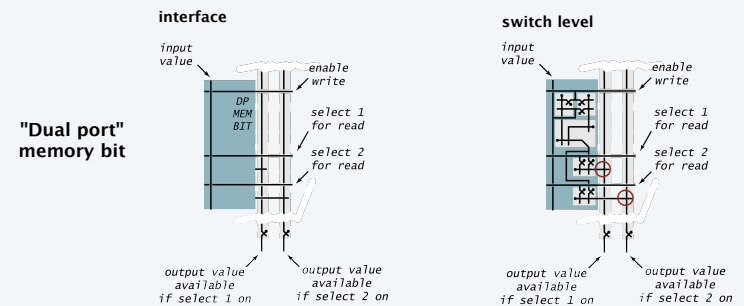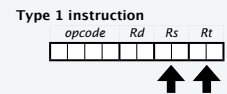- Flip-flop value is *not* always available.
- Use *select 1 for read* signal to make it available on output line 1.
- Use *select 2 for read* signal to make it available on output line 2.
- "1-hot" OR to collect the selected bit values on each line.



20


TinyTOY register bank

Interface

- Input bus
- Two output busses
- Address bits to select word
- Address bits to select 2nd word
- *Enable write* control signal


Connections

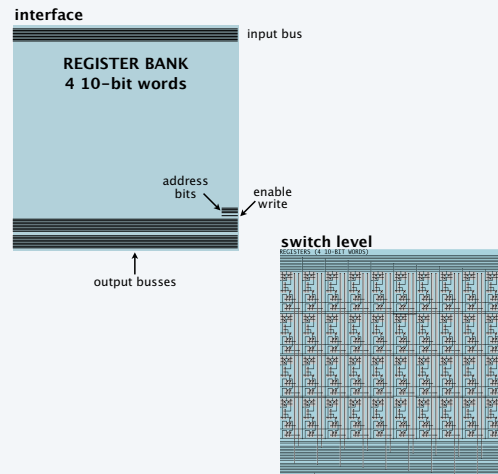- Input bus from MUX (stay tuned)
- Output busses to ALU, memory
- Address bits from IR
- *Enable write* from "control"



21


21. CPU

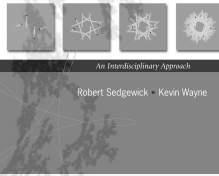

<http://introcs.cs.princeton.edu>

- Bits and registers
- **Main memory and register banks**
- Program counter
- Putting the pieces together

21. CPU

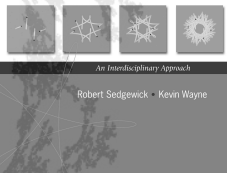

<http://introcs.cs.princeton.edu>

- Bits and registers
- Main memory and register banks
- **Program counter**
- Putting the pieces together

Designing a digital circuit: overview

Steps to design a digital (sequential) circuit

- Design **interface**: input busses, output busses, control signals.
- Determine **components**.
- Determine **datapath** requirements: "flow" of bits.
- Establish **control sequence**.




Warmup. Design tinyTOY program counter (PC).

← Three components and three control signals

Another useful combinational circuit: Multiplexer

Multiplexer (MUX). Combinational circuit that selects among input buses.

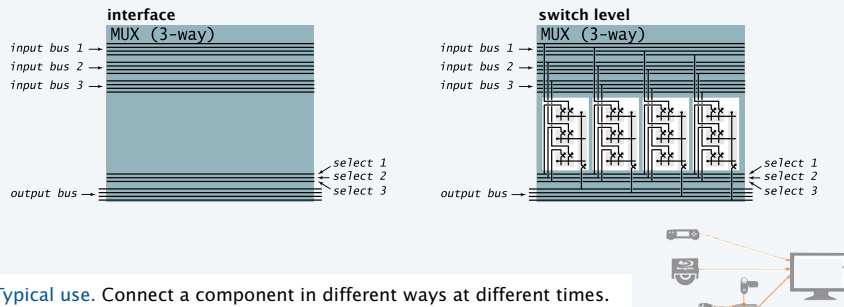- Exactly one select line i is activated. ← unary input (MUX in text takes binary input)
- Puts bit values from input bus i onto output bus.




Typical use. Connect a component in different ways at different times.

25

Counter interface

A *counter* holds a value that represents a binary integer and supports three control signals:

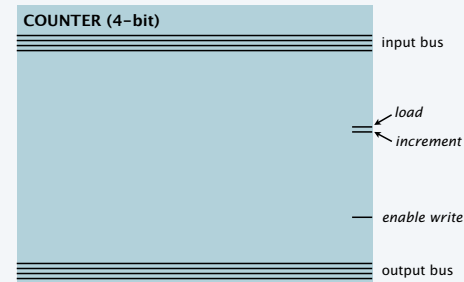- *Load*. Set value from input bus.
- *Increment*. Add one to value.
- *Enable write*. Make value available on output bus.



Components inside

- Input and output busses.
- Processor register.
- Incrementer (add 1).
- 2-way MUX.


TinyTOY PC: 4-bit counter

26


Counter layout and implementation

Layout and connections establish *data paths* where information travels.

component-level implementation

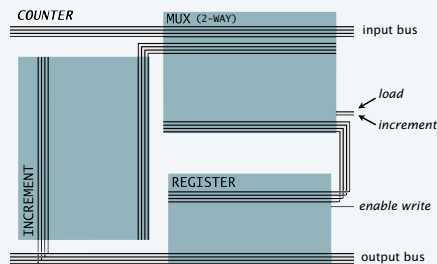

switch-level implementation

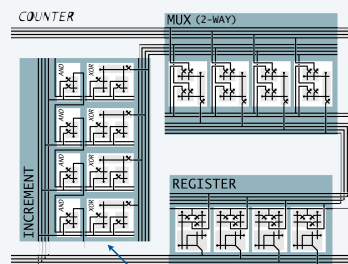


Next: Sequence of control signals that effects desired behavior

27

Control signal sequences and data paths for counter

LOAD: input bus to MUX output to register

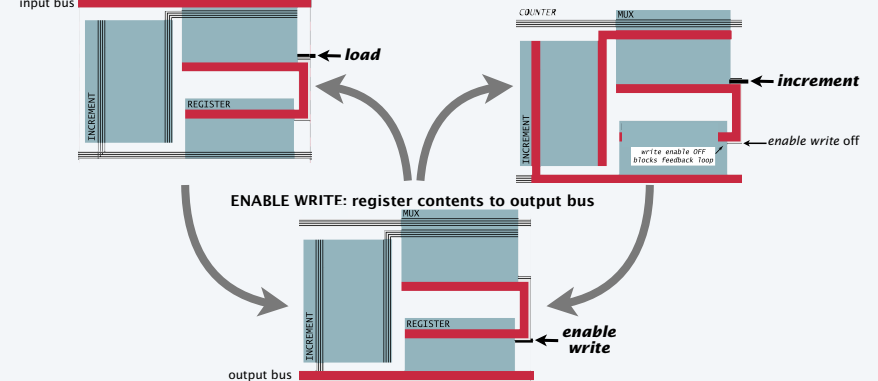INCREMENT: register output to incrementer
incrementer output to MUX
increment selects copy to register input
enable write OFF blocks feedback loop




28

Summary of TinyTOY PC circuit

The *program counter* holds an address and supports two control signal sequences:


- *Load, then enable write*. Set value from input bus (example: branch instruction).
- *Increment, then enable write*. Add one to value.

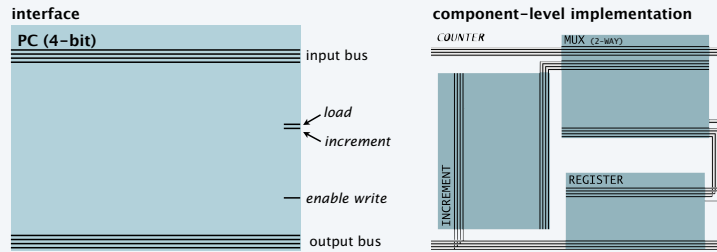Value is written to an internal processor register and available on output bus in both cases.



Next. CPU circuit (10 components, 27 control signals).

29

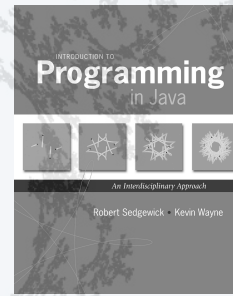


21. CPU

- Bits and registers
- Main memory and register banks
- **Program counter**
- Putting the pieces together

<http://introcs.cs.princeton.edu>

21. CPU

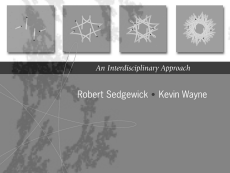

<http://introcs.cs.princeton.edu>

- Bits and registers
- Main memory and register banks
- Program counter
- **Putting the pieces together**

TinyTOY: Interface

CPU is a circuit inside the machine



Interface to outside world

- Switches and lights
- ON/OFF
- RUN

Connections (omitted)

- ADDR to PC
- DATA to memory bank input bus
- Buttons to control signals that implement memory load/store


TinyTOY
A computing machine

32

TinyTOY CPU components and layout

Components

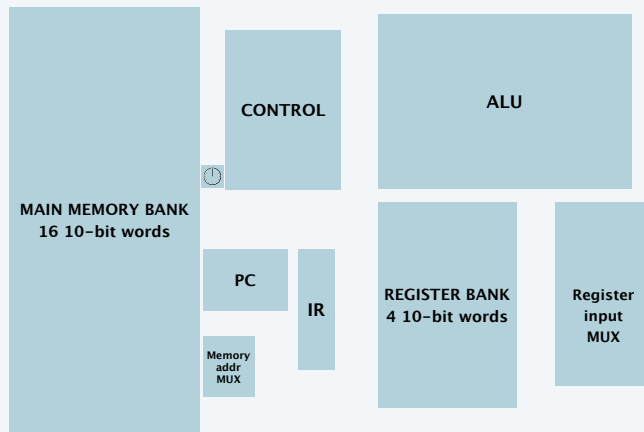- ALU
- Main memory
- Registers
- PC
- IR
- MUX switches
- Control
- Clock



33

Review: Program counter and instruction register


TOY operates by executing a sequence of *instructions*.

Critical abstractions in making this happen

- Program Counter (PC). Memory address of next instruction.
- Instruction Register (IR). Instruction being executed.

Fetch-increment-execute cycle

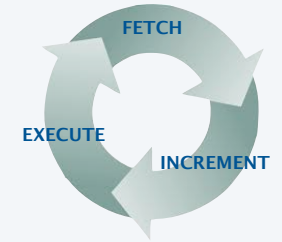- Fetch: Get instruction from memory into IR.
- Increment: Update PC to point to *next* instruction.
- Execute: Move data to or from memory, change PC, or perform calculations, as specified by IR.




34

TinyTOY control lines and data paths

Control lines

- PC to MA MUX
 - IR enable write
 - increment PC
 - PC enable write
 - memory enable write
 - reg bank enable write
 - ...
- [20-30 additional lines]

control lines ———
data paths ———

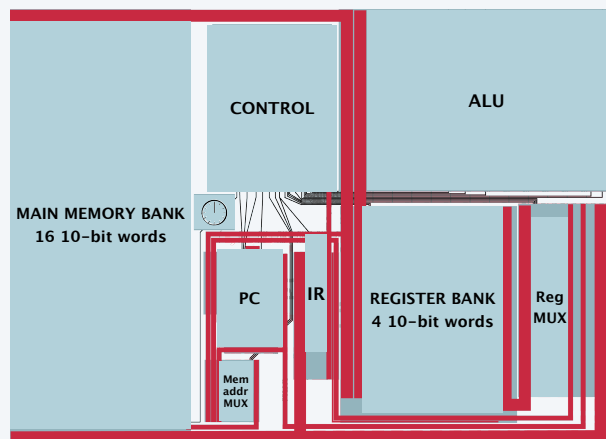


35

TinyTOY control sequences

Control sequences choreograph the flow of information through the CPU.

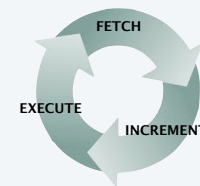
- Example 1: Fetch
 - Example 2: Increment
 - Example 3: ALU instruction
- [small sequence for each instruction]



Sequence	Instruction	Control Sequence	Control Action
FETCH			PC to mem addr MUX IR enable write
			PC increment PC enable write
EXECUTE	0	halt	...
	1	add	...
	2	subtract	...
	3	and	[IR opcode to decoder] [decoder to ALU select]
	4	xor	switch reg input MUX to ALU reg bank enable write
	5	shift left	...
	6	shift right	...
	7	load address	...
	8	load	...
	9	store	...
A	load indirect	...	
B	store indirect	...	
C	branch zero	...	
D	branch positive	...	
E	jump register	...	
F	jump and link	...	


36

Datapath for an add instruction

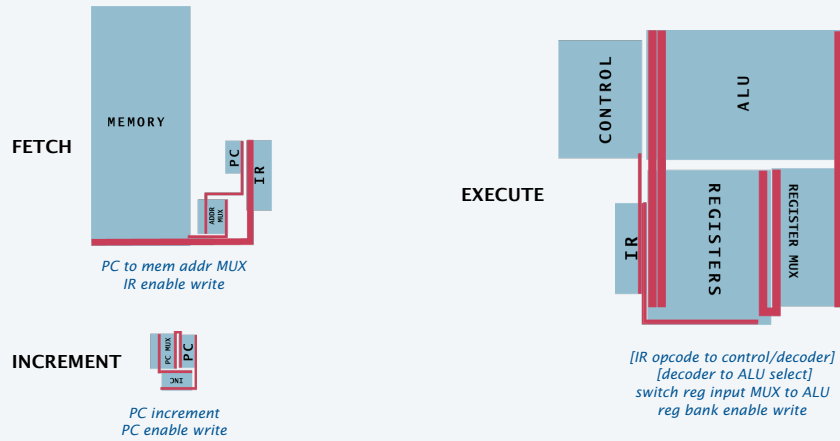

37

Datapath for a load instruction

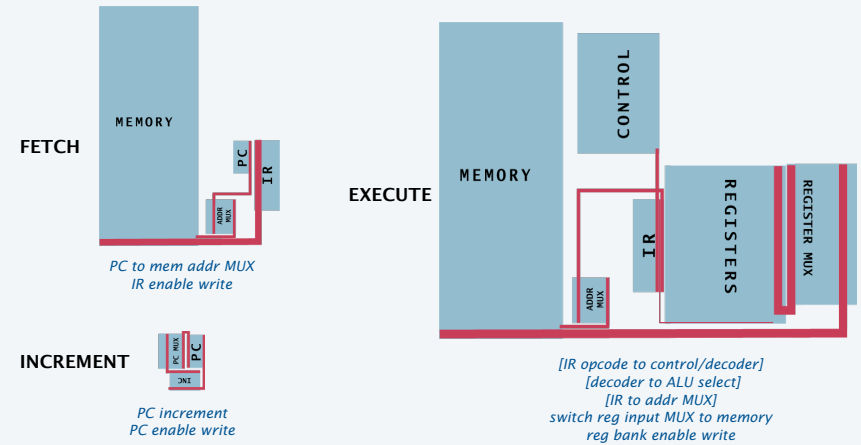

38

Clock



A **CLOCK** provides a regular ON-OFF pulse.

Requirement. Clock cycle longer than max switching time.

Q. How to implement a clock?

A. Use an external device.

A. Use a *buzzer*.

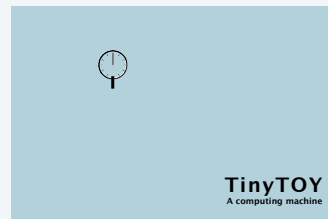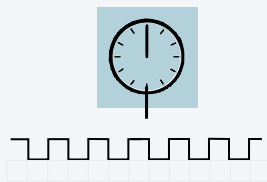

39


Last step

Use a clock to raise a **sequence** of signals.

Brute force approach

- Connect clock to simple counter.
 - Connect counter to decoder.
- Result: A *sequence* of (control) signals.

input bus
and MUX not
needed

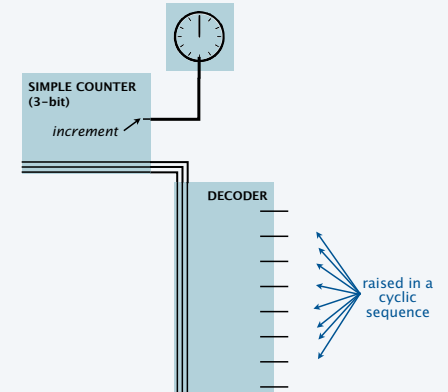


Note. TinyTOY circuit (and your computer) uses a more efficient clocking scheme.

40

One final combinational circuit: Control

Control. The circuit that determines *control line sequencing*.

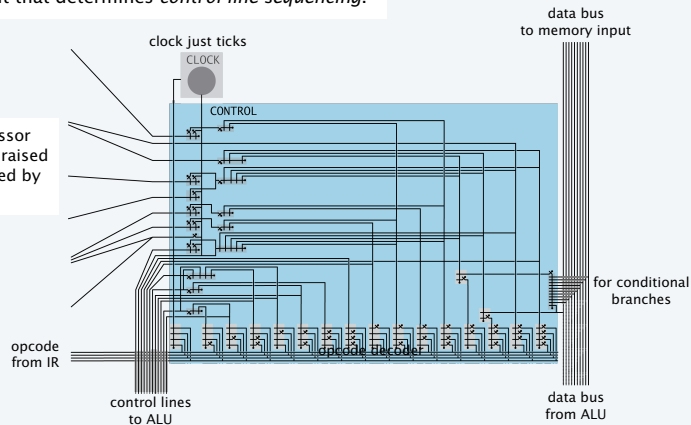Control lines to processor registers and ALU are raised in sequence determined by clock and opcode.



41


Tick-Tock

CPU is a circuit, driven by a clock.

Initialize via console switches.


Press RUN: clock starts ticking

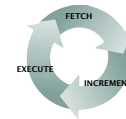- PC to mem addr MUX
- IR enable write
- PC increment
- PC enable write
- .
- .



[details of instruction execution differ]

Faster clock? Faster computer!

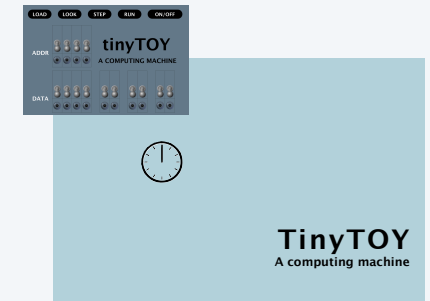


TinyTOY
A computing machine

And THAT . . . is how your computer works!


42

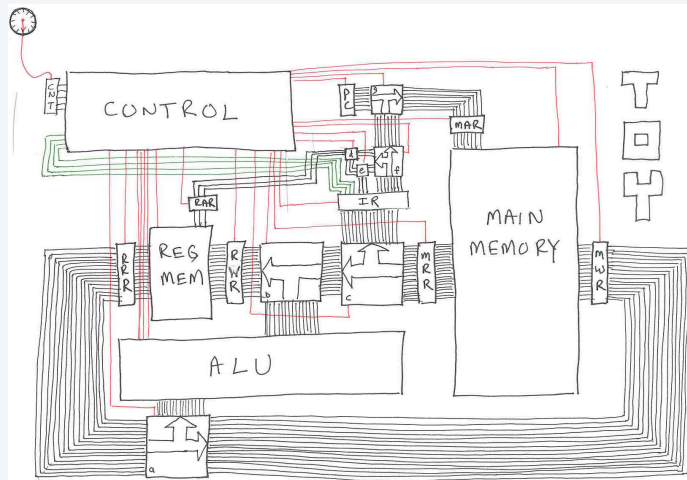TOY "Classic", back-of-envelope design (circa 2005)




43

TinyTOY CPU component-level view

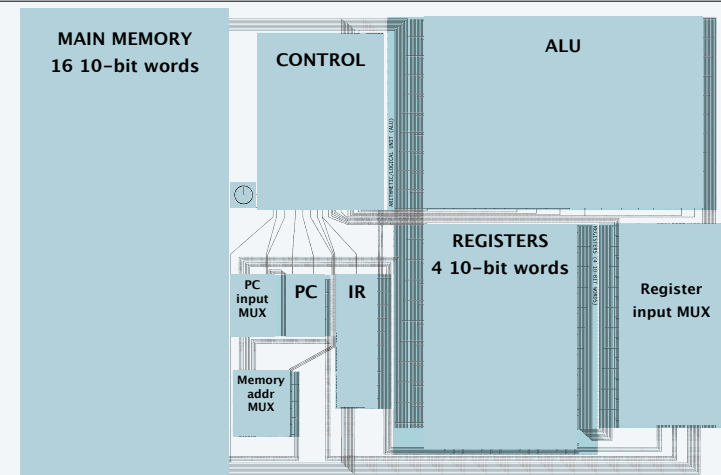


44

TinyTOY CPU switch-level view

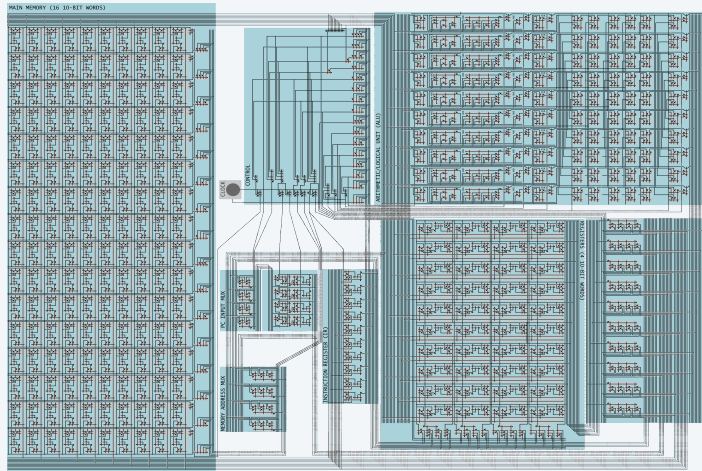

45


A real microprocessor (MIPS R10000)

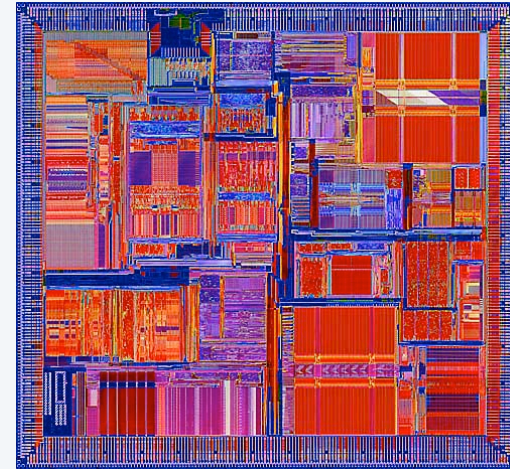

46

COMPUTER SCIENCE
SEDEGWICK / WAYNE


COMPUTER SCIENCE
SEDEGWICK / WAYNE

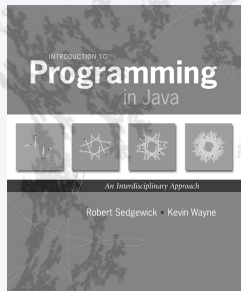

21. CPU

- Bits and registers
- Main memory and register banks
- Program counter
- Putting the pieces together

<http://introcs.cs.princeton.edu>

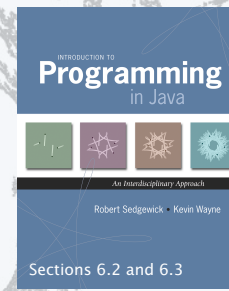

21. Central Processing Unit

Sections 6.2 and 6.3

<http://introcs.cs.princeton.edu>