

21. Central Processing Unit

<http://introc.cs.princeton.edu>

21. CPU

- Overview
- Bits, registers, and memory
- Program counter
- Components and connections

CS. 21.A.CPU.Overview

Let's build a computer!

CPU = Central Processing Unit

Computer

- Display
- Touchpad
- Battery
- Keyboard
- ...
- CPU (difference between a TV set and a computer)

Previous lecture

- Combinational circuits
- ALU (calculator)

This lecture

- Sequential circuits with *memory*
- CPU (computer)




A smaller computing machine: TinyTOY

TOY instruction-set architecture.

- 256 16-bit words of memory.
- 16 16-bit registers.
- 1 8-bit program counter.
- 2 instruction types
- 16 instructions.



Type 1 instruction

 

Type 2 instruction




TinyTOY instruction-set architecture.

- 32 8-bit words of memory.
- 1 8-bit register.
- 1 5-bit program counter.
- 1 instruction type
- 8 instructions.



TinyTOY instruction

 


Purpose of TinyTOY. Illustrate CPU circuit design for a "typical" computer.

TinyTOY instruction set architecture

TinyTOY instructions.

- Halt
- Add
- AND
- XOR
- LOAD ADDRESS
- LOAD
- STORE
- BRANCH NEGATIVE

TinyTOY instruction

 

5 bits to specify one of 32 memory words
4 bits and 16 words in prototype machine

TinyTOY instruction-set architecture.

- 16 8-bit words of memory (expandable to 32).
- 1 8-bit register (R0).
- 1 4-bit program counter (expandable to 5).
- 8 instructions (only one type).

5

Review: the state of the machine

Contents of memory, registers, and PC at a particular time

- Provide a *record* of what a program has done.
- **Completely determines** what the machine will do.

ALU and IR hold intermediate states of computation




6

CPU circuit components for TinyTOY

TinyTOY CPU

- ALU (adder, AND, XOR)
- Memory
- Register (R0)
- PC (with incrementer)
- IR
- MUXes (switch circuits)
- Control
- Clock

stay tuned (this lecture)

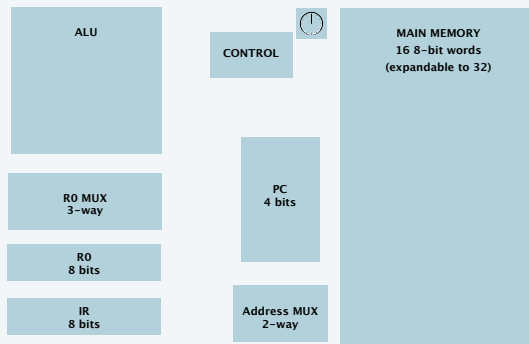


Goal. Complete CPU circuit for TinyTOY (same design extends to TOY and to your computer).

7

Perspective

Q. Why TinyTOY?

 A. TOY circuit width would be about 5 times TinyTOY circuit width.



Sobering fact. The circuit for your computer is *hundreds to thousands* of times wider.

Reassuring fact. Design of all three is based on the same fundamental ideas.

8

21. CPU

- Overview
- **Bits, registers, and memory**
- Program counter
- Connections

CS.21.B.CPU.Memory

Sequential circuits

Q. What is a sequential circuit?

A. A digital circuit (all signals are 0 or 1) *with feedback* (loops).

Q. Why sequential circuits?

A. *Memory* (difference between a DFA and a Turing machine).

Basic abstractions

- On and off.
- Wire: Propagates an on/off value.
- Switch: Controls propagation of on/off values through wires.
- Flip-flop: *Remembers* a value.

10


Simple circuits with feedback

Loops in circuits lead to time-varying behavior

- *Sequence* of switch operation matters.
- Need tight control (see next slide).

Example 1. Two switches, each blocked by the other.

- State determined by whichever switches first.
- Stable (once set, state never changes).
- *Basic building block for memory circuits.*

 

Example 2. Three switches, blocked in a cycle.

- State determined by whichever switches first.
- *Not stable* (cycles through states).




11


A new ingredient: Circuits with memory

An SR flip-flop controls feedback.

 - Add control lines to switches in simple feedback loop.
- R (reset) sets state to 0.
- S (set) sets state to 1.
- Q (state) is always available.



examples

 


Caveat. Timing of switch vs. propagation delay.

12

One bit in a register

Add logic to an SR flip-flop for more precise control

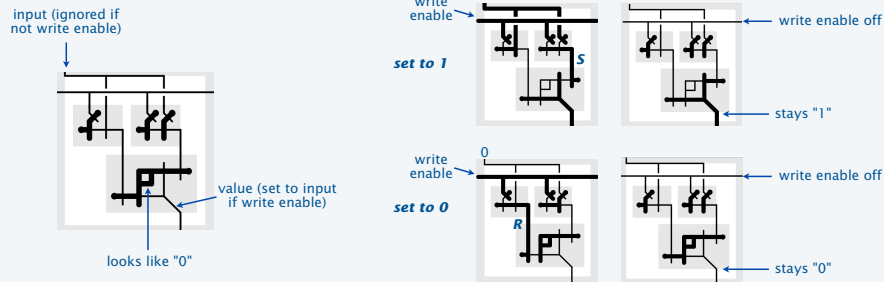- Provide data value on an input wire instead of using S and R controls.
- Use *enable write* signal to control timing of write.
- Flip-flop value is always available.




13

Registers


Register

 - Holds W bits.
- Input and output on W -wire busses.
- Register contents always available on output bus.
- Enable write puts W input bits into register.



component level

examples

 

TinyTOY registers


- PC holds 4-bit address.
- IR holds 8-bit instruction.
- R0 holds 8-bit data value.

14

One bit in main memory

Add a selection mechanism

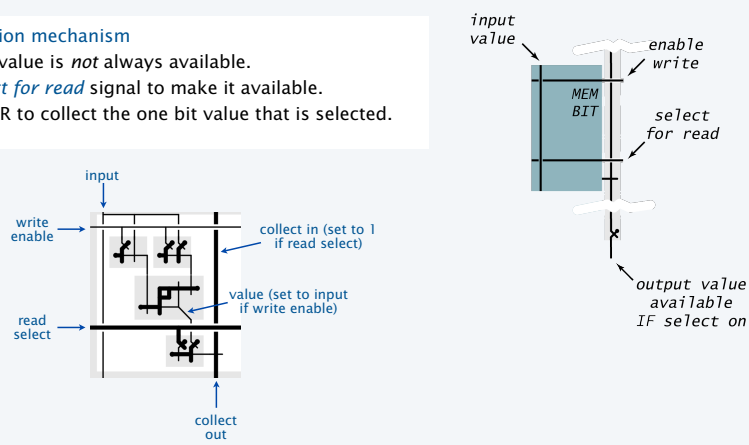- Flip-flop value is *not* always available.
- Use *select for read* signal to make it available.
- "1-hot" OR to collect the one bit value that is selected.




15

Main memory: interface

Main memory.

- N words; each stores W bits.
- Read and write data to one of N words.
- Address inputs select one word.
- Addressed word always on output bus.
- When write enabled, W input bits are copied into addressed word.

	number of words	bits per word	address bits
this slide	4	6	2
tinyTOY	16 or 32	8	4 or 5
TOY	256	16	8
your computer	1 billion	64	32

 

16

Main memory bank: component level


Main memory.

- N words; each stores W bits.
- Read and write data to one of N words.
- Address inputs select one word.
- Addressed word always on output bus.
- When write enabled, W input bits are copied into addressed word.

Basic mechanisms

- A decoder uses address to switch on one line (through the addressed word)
- "1-hot" OR gates at each bit position take word contents to the output bus.

Example: Read word 2 (10)

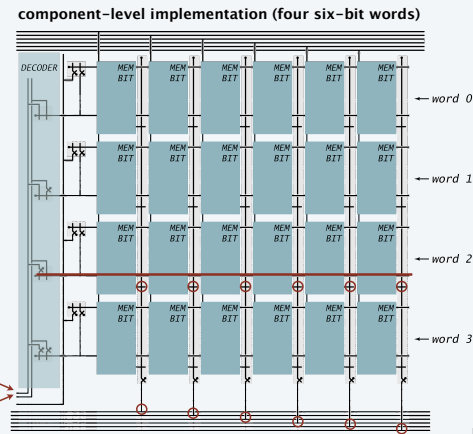


17

Main memory bank: switch level

Main memory.

- N words; each stores W bits.
- Read and write data to one of N words.
- Address inputs select one word.
- Addressed word always on output bus.
- When write enabled, W input bits are copied into addressed word.

switch-level implementation

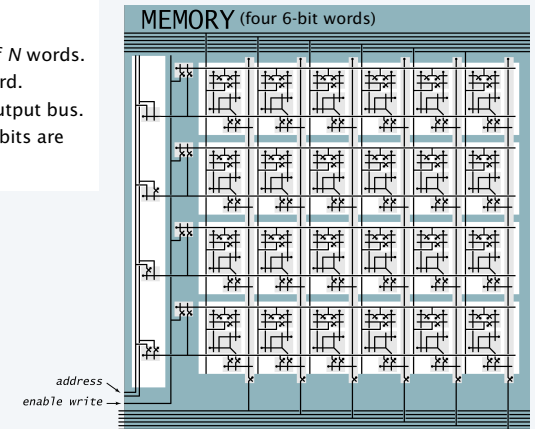

18


TinyTOY main memory bank

Interface

- Input bus for "store"
- Output bus for "load"
- Address bits to select a word
- *Enable write* control signal

Connections

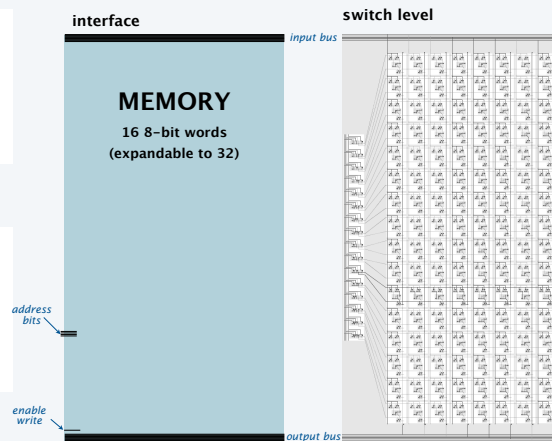- Input bus from registers
- Output bus to IR and R0
- Address bits from PC, IR, R0
- *Enable write* from "control"



19

21. CPU

- Overview
- Bits, registers, and memory
- Program counter
- Components and connections

Designing a digital circuit: overview

Steps to design a digital (sequential) circuit

- Design **interface**: input busses, output busses, control signals.
- Determine **components**.
- Determine **datapath** requirements: "flow" of bits.
- Establish **control sequence**.




Warmup. Design TinyTOY program counter (PC). ← Three components and three control signals

21

Another useful combinational circuit: Multiplexer


Bus multiplexer (MUX).

 - Combinational circuit to select among input busses.
- Exactly one select line i is activated.
- Puts bit values from input bus i onto output bus.



Note: MUX in text takes binary select specification

example

 


Typical use. Connect a component in different ways at different times.

22

Counter interface

A **Counter** holds a value and supports 3 control signals:

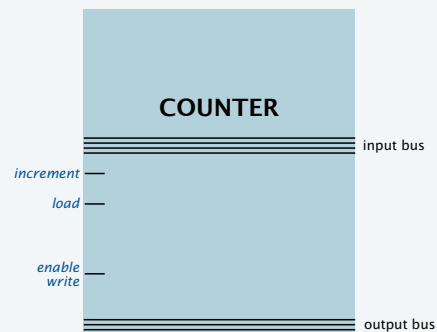- **Increment**. Add 1 to value.
- **Load**. Set value from input bus.
- **Enable write**. Make value available on output bus.



Components inside

- Register.
- Incrementer (add 1).
- 2-way MUX.


TinyTOY PC: 4-bit counter

23

Counter layout and implementation


Layout and connections establish

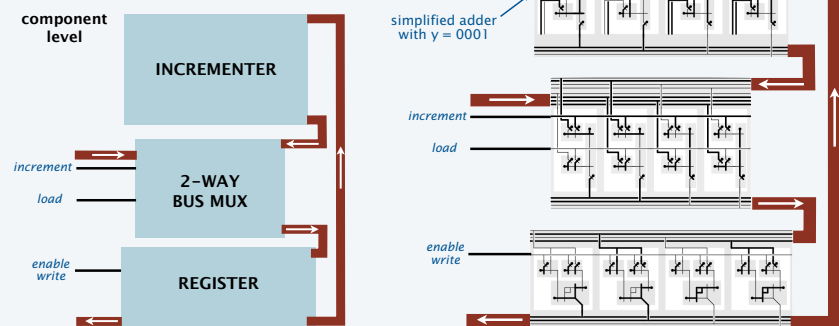- data paths (busses) =
- control signals



24

Counter operation

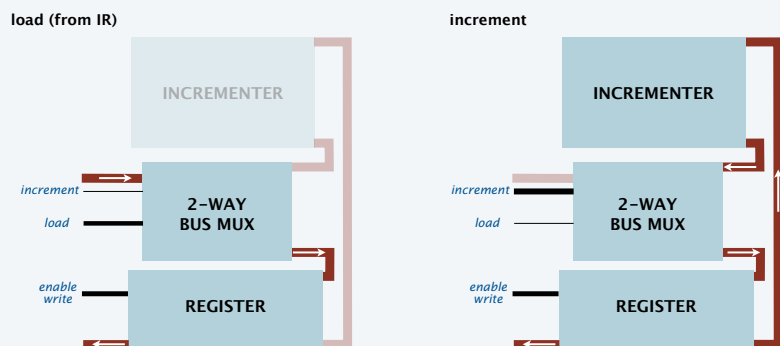

Important note: *Enable write* is a pulse, to avoid feedback (stay tuned)


25

Summary of TinyTOY PC (counter) circuit

The *PC* is three components and supports three control signals:

- *Load, then enable write*. Set value from input bus (example: branch instruction).
- *Increment, then enable write*. Add one to value.

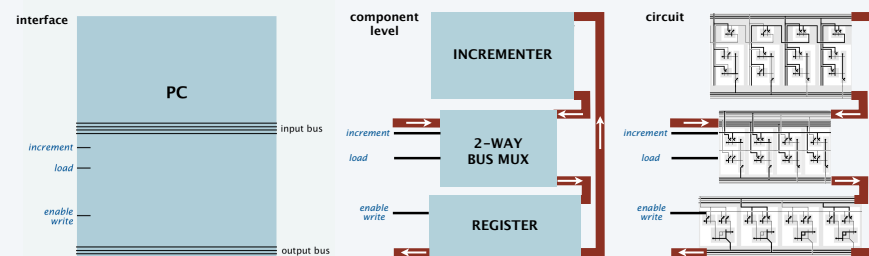Value is written to the *PC* and available on output bus in both cases.



Next. CPU circuit (10 components, 20+ control signals).

26

21. CPU

- Overview
- Bits, registers, and memory
- Program counter
- **Components and connections**

TinyTOY: Interface

CPU is a circuit inside the machine



Interface to outside world

- Switches and lights
- ON/OFF
- RUN

Connections to outside (omitted)

- ADDR to PC
- DATA to memory bank input bus
- Buttons to control lines that activate memory load/store


TinyTOY
A computing machine

28

Review: CPU circuit components for TinyTOY

TinyTOY CPU

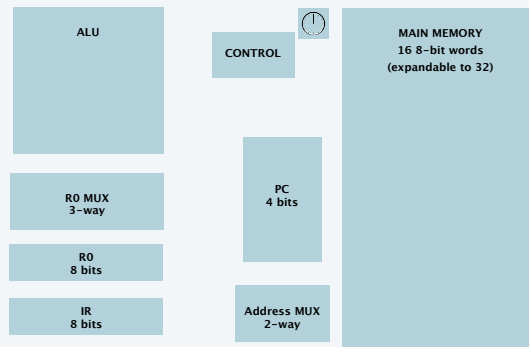- ALU (adder, AND, XOR)
- Memory
- Register (R0)
- PC (with incrementer)
- IR
- MUXes (switch circuits)
- Control
- Clock



29

Review: Program counter and instruction register


TOY operates by executing a sequence of *instructions*.

Critical abstractions in making this happen

- Program Counter (PC). Memory address of next instruction.
- Instruction Register (IR). Instruction being executed.


Fetch-increment-execute cycle

 - Fetch: Get instruction from memory into IR.
- Increment: Update PC to point to *next* instruction.
- Execute: Move data to or from memory, change PC, or perform calculations, as specified by IR.




30

TinyToy data paths and control lines

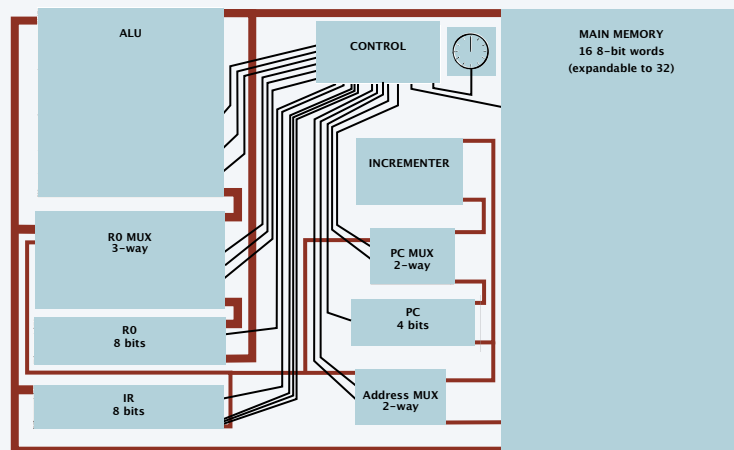

31

Fetch (every instruction)

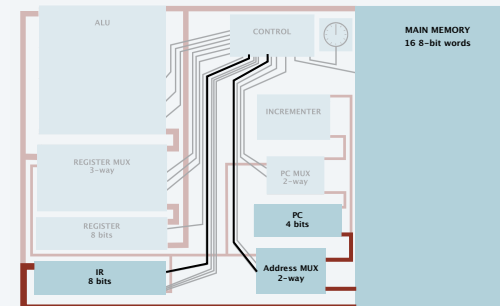

Data paths

- PC to Address MUX
- Address MUX to memory
- Memory to IR

Control signals

- Address MUX select 1
- IR Write Enable


32

One final combinational circuit: Control

Control. Circuit that determines *control line sequencing*.

Control line sequencing

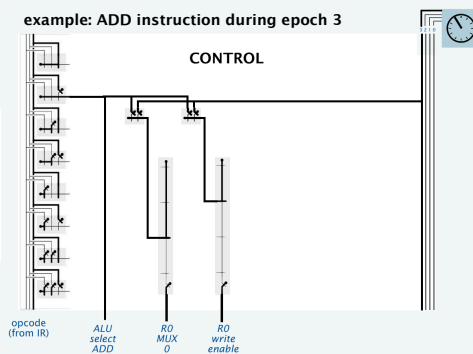- Clock through four epochs, raising one line at a time
- Determines sequence of at most 4 sets of control lines for each instruction



Key feature. A simple combinatorial circuit.

37

Tick-Tock

CPU is a circuit, driven by a clock.



Initialize via console switches.

Press RUN: clock starts ticking

- PC to mem addr MUX
- IR enable write
- PC increment
- PC enable write
- .
- .
- .

[details of instruction execution differ]


Faster clock? Faster computer!

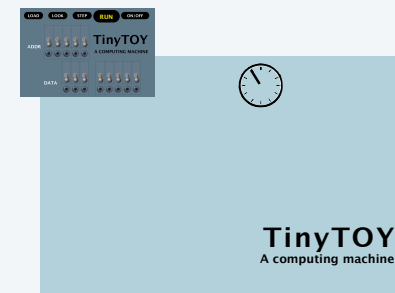 

And THAT . . . is how your computer works!


38

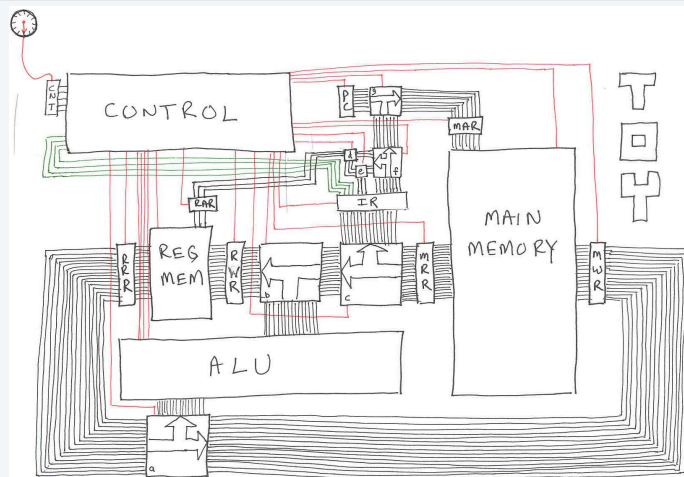TOY "Classic", back-of-envelope design (circa 2005)





39

TinyTOY CPU

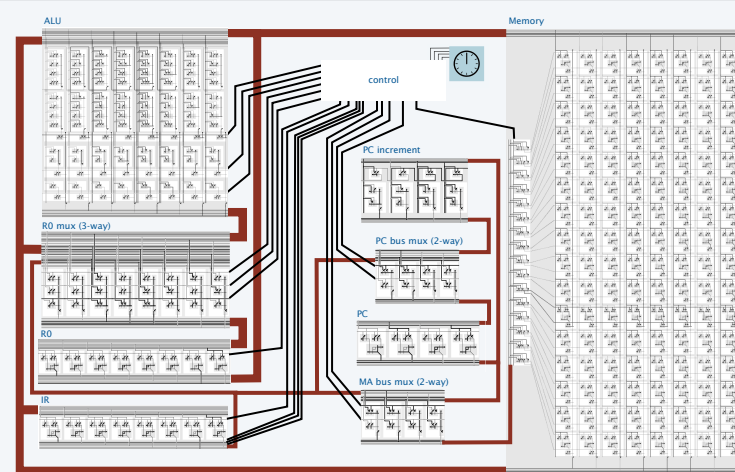

40

A real microprocessor (MIPS R10000)

  

21. Central Processing Unit