 


# CS 126 Lecture A4: Sequential Circuits

## Midterm Statistics



## Outline

- **Introduction**
- An S-R Flip-flop
- More flip-flops
- Registers and register files
- Counters
- Conclusions


## Where We Are At

- We have learned the abstract **interface** presented by a machine: the instruction set architecture
- What we are learning: the **implementation** behind the interface:
  - ~~Start with switching devices (such as transistors)~~
  - ~~Build logic gates with transistors~~
  - ~~Build combinational circuit (memory-less) devices using gates~~
  - **Today: build sequential circuit (memory) devices**
  - Thursday: glue these devices into a computer

## Memory-less Devices vs. Devices with Memory

- What we we have learned in the last lecture
  - Devices that can carry out one step of operation
- What they can't do
  - “Remember” history of operations
  - Carry out a sequence of operations in which later operations depend on results of previous ones

## Combinational vs. Sequential Circuits

 


- Combinational circuits
  - Outputs determined solely by inputs
- Sequential Circuits
  - Characterized by feedbacks
  - Outputs determined by inputs and previous outputs

## Outline


- Introduction
- **An S-R Flip-flop**
- More flip-flops
- Registers and register files
- Counters
- Conclusions

## Set-Reset Flip-flop

 

- A flip-flop
  - A smallest sequential circuit
  - Can “remember” a bit of information
- An S-R flip-flop
  - Pulse on Set (S) line turns flip-flop on
  - Pulse on Reset (R) line turns flip-flop off
  - If  $S=R=0$ , nothing happens
  - $S=R=1$  not allowed

## Timing Diagram (for S-R Flip-flop)

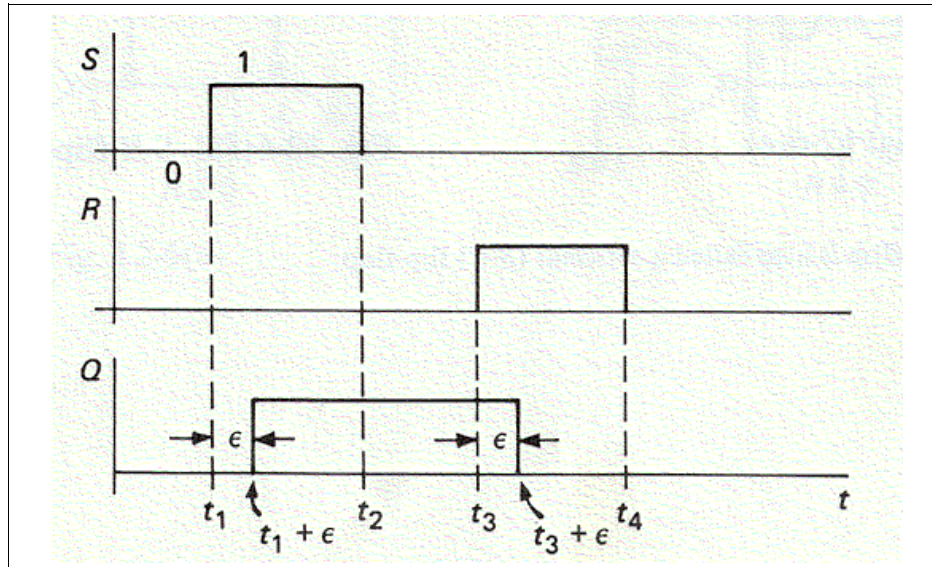

- Because sequential circuits are functions of time, a timing diagram is one of the ways of describing them

## Truth Table (for S-R Flip-flop)

previous state		next state	
$S(t)$	$R(t)$	$Q(t)$	$Q(t + \epsilon)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-

0  
1  
2  
3  
4  
5

} inputs not allowed

- Previous states become “input variables” in truth table

## Characteristic Equation (for S-R Flip-flop)


$$Q^+ = S + R'Q \quad (SR=0)$$

- An equation that expresses the next state of a flip-flop in terms of its present state and inputs (also called next state equations)
- Timing diagrams, truth tables, and next-state equations are important tools for understanding and constructing more sophisticated sequential circuits as well

## Outline

- Introduction
- ~~An S-R Flip-flop~~
- **More flip-flops**
- Registers and memory
- Counters
- Conclusions

## The Clock

 


CS126


12-12

Randy Wang


## A Clocked S-R Flip-flop

 

interface

 

implementation

 

timing  
diagram


- In large sequential networks, there are many flip-flops
- Need to synchronize operations of different flip-flops
- Synchronization provided by a common clock (pulse)

CS126


12-13

Randy Wang

## A D Flip-flop

 

Interface

 


Implementation

On clock pulse

$D = 1$  set

$D = 0$  reset

## Behavior of D Flip-flop

 

Timing Diagram

$D$	$Q$	$Q^+$
0	0	0
0	1	0
1	0	1
1	1	1


Truth Table

$$Q^+ = D$$

Characteristic Equation




## Rising vs. Falling Edge

 


- So far, all the clocked flip-flops “flip-flop” on the rising edge of a clock signal
- When we cram a lot of actions into a single cycle, we sometimes need them to change state on the falling edge
 
## Master-Slave D Flip-flop


On rising edge, input copied into master;  
On falling edge, master copies data into slave.



Implementation

 

Interface

 


Timing Diagram

- Input sampled on rising edge, and must remain stable during the pulse, output changes on falling edge
- Question: why don't we just invert the clock using a NOT?
- Another type: “edge-triggered”, allows input change during clock pulse

## Outline

- Introduction
- ~~An S-R Flip-flop~~
- ~~More flip-flops~~
- **Registers and register files**
- Counters
- Conclusions


## Stand-alone Register Interface

 

LOAD line (and clock)  
controls when new values are loaded

Use registers for  
PC  
memory addresses  
memory buffer  
arithmetic

## Stand-alone Register Implementation

 


CS126

12-20

Randy Wang

## Register File Interface (Bits)

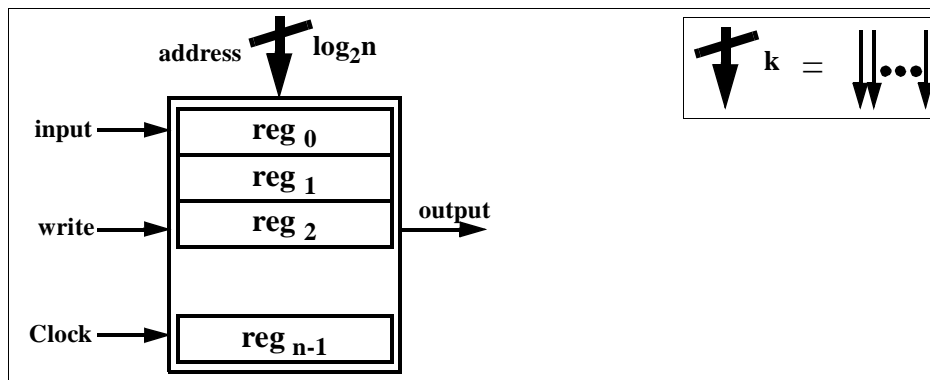


- bunch of bits to choose from
- “address” specifies which bit
- if “write” is 1, “input” gets copied into the chosen bit on clock pulse
- if “write” is 0, chosen bit appears on “output”

CS126

12-21



Randy Wang

## Register File Implementation (Bits)

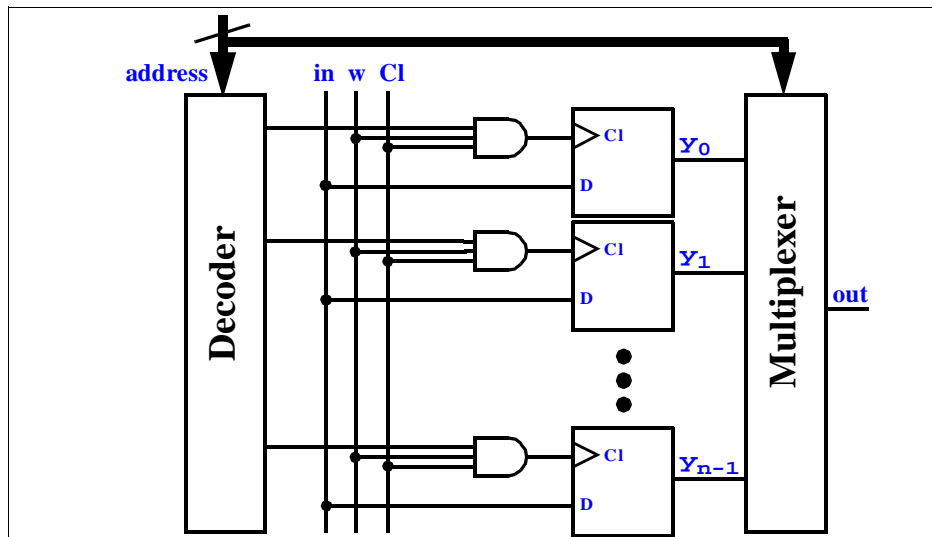


- Decoder chooses exactly one bit to write into
- Multiplexer chooses exactly one bit to copy out

## 3-State Logic

  

- Can't connect outputs together (even if they are zero)
- Must use multiplexer (or its equivalent: [**3-state logic**])

## Register File Implementation 2 (Bits)

 


- Red things are new: replace MUX with 3-state logic
- Less Complex than MUX version

CS126

12-24

Randy Wang

## Register File Interface (Words)

 


- Register file of  $k$ -bit words
- **red** things show the differences between word case and bit case

CS126

12-25

Randy Wang

## Register File Implementation (Words)

 

- **red** things show the differences between word case and bit case
- Multiply the number of flip-flops and MUXes by bits per register ( $k$ )
- May replace MUXes with 3-state logic (see previous slides)

CS126

12-26

Randy Wang

## Correcting Lecture Notes in Your Course Reader


- Memory vs. register files
  - Lecture notes use the term “memory”
  - Meant to say register files (or SRAM)
  - DRAM made differently--no flip-flops
  - DRAM: one transistor per bit!
  - Much higher density than flip-flops, but slower

CS126

12-27


Randy Wang
 
## Correting Lecture Notes in Your Course Reader (cont.)



- Can't connect outputs together (even if they are zero)
- Must use multiplexer (or its equivalent: [3-state logic])
 
## Correting Lecture Notes in Your Course Reader (cont.)




- Don't need decoder
- But even if you remove it, still not quite right for TOY register file: no need to replicate decoders for each bit

# Outline

- Introduction
- ~~An S-R Flip-flop~~
- ~~More flip-flops~~
- ~~Registers and register files~~
- **Counters**
- Conclusions



## 1-Bit Counter

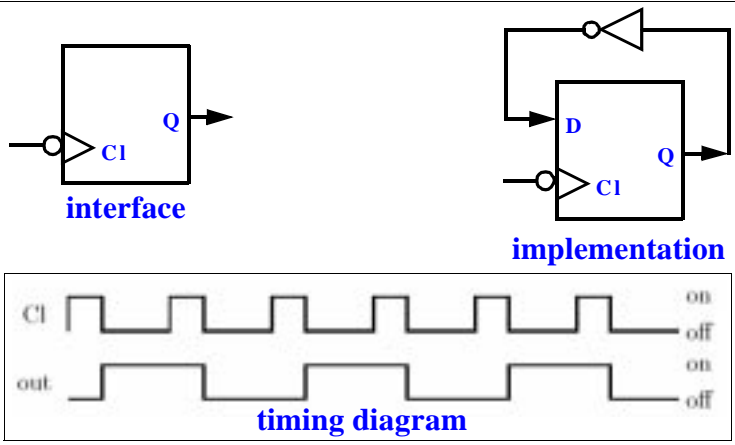

- The behavior of a 1-bit binary counter is a clock whose cycle is twice as long as the input clock



# N-bit Counter

  


- n-bit counter: chaining n 1-bit counters together
- Recursive! An n-bit counter is made by gluing one extra bit to an (n-1) bit counter

# Outline

- Introduction
- An S-R Flip-flop
- More flip-flops
- Registers and register files
- Counters
- Conclusions

## High-Level View of Computer

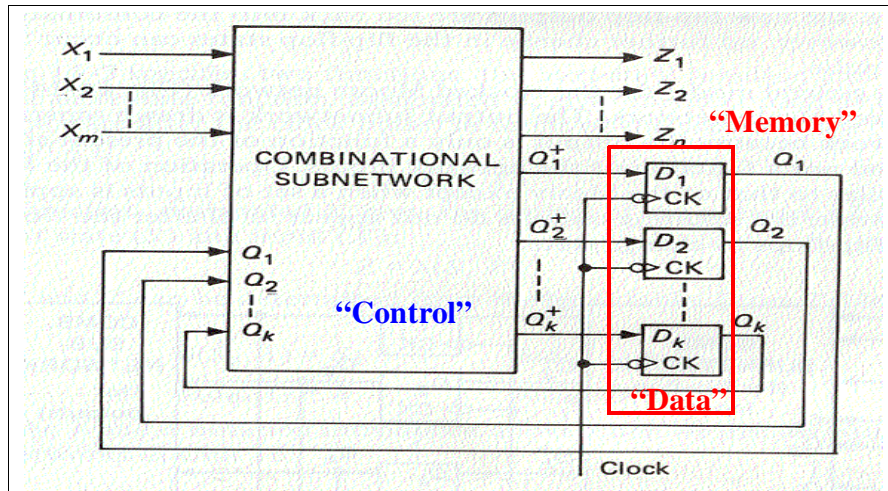

- Computer: “memory” state with feedback, clocked
- Each clock enables changes in memory state
- Combinational logic (topic of last lecture) employed to specify what changes to make in response to inputs and past history

## What We Have Learned Today

- Flip-flops ([S-R, D], [unlocked, clocked, master-slave, edge triggered])
  - Their behavior (timing diagrams, truth tables, characteristic equations)
  - How they are made
- Some sequential devices (registers, register files, counters)
  - Their behavior
  - How they are made