




Memory; Sequential & Clocked Circuits; Finite State Machines

COS 116: 3/25/2008

Sanjeev Arora

 COS 116 Midterm - March 13, 2008 - Histogram



Midterm grade
Criterion:


58-65: A	40-44: B-
55-57: A-	33-39: C
50-54: B+	26--32: D
45-49: B	25 and below: F

Recap: Boolean Logic

Boolean Expression

$$E = S \text{ AND } \bar{D}$$

Boolean Circuit

 

Truth table:


Value of E for every possible D, S.

TRUE=1; FALSE= 0.

D	S	E
0	0	0
0	1	1
1	0	0
1	1	0

Truth table has 2^k rows if the number of variables is k

 Boole's reworking of Clarke's "proof" of existence of God (see handout)



- General idea: Try to prove that Boolean expressions E_1, E_2, \dots, E_k cannot simultaneously be true
- Method: Show $E_1 \cdot E_2 \cdot \dots \cdot E_k = 0$
- Discussion: What exactly does Clarke's "proof" prove? How convincing is such a proof to you?

Also: Do Google search for "Proof of God's Existence."

Combinational circuit for binary addition?

$$\begin{array}{r} 25 \qquad 11001 \\ + 29 \qquad 11101 \\ \hline 54 \qquad 110110 \end{array}$$

- Want to design a circuit to add any two N -bit integers.

Is the truth table method useful for $N=64$?

Modular design

Have small number
of basic components.

Put them together to achieve
desired functionality

Basic principle of modern industrial design;
recurring theme in next few lectures.




Modular design for N-bit adder

$$\begin{array}{cccccc} & \mathbf{c}_{N-1} & \mathbf{c}_{N-2} & \dots & \mathbf{c}_1 & \mathbf{c}_0 & \text{Carry bits} \\ & \mathbf{a}_{N-1} & \mathbf{a}_{N-2} & \dots & \mathbf{a}_1 & \mathbf{a}_0 & \\ + & \mathbf{b}_{N-1} & \mathbf{b}_{N-2} & \dots & \mathbf{b}_1 & \mathbf{b}_0 & \\ \hline & \mathbf{s}_N & \mathbf{s}_{N-1} & \mathbf{s}_{N-2} & \dots & \mathbf{s}_1 & \mathbf{s}_0 \end{array}$$


Suffices to use N 1-bit adders!

1-bit adder

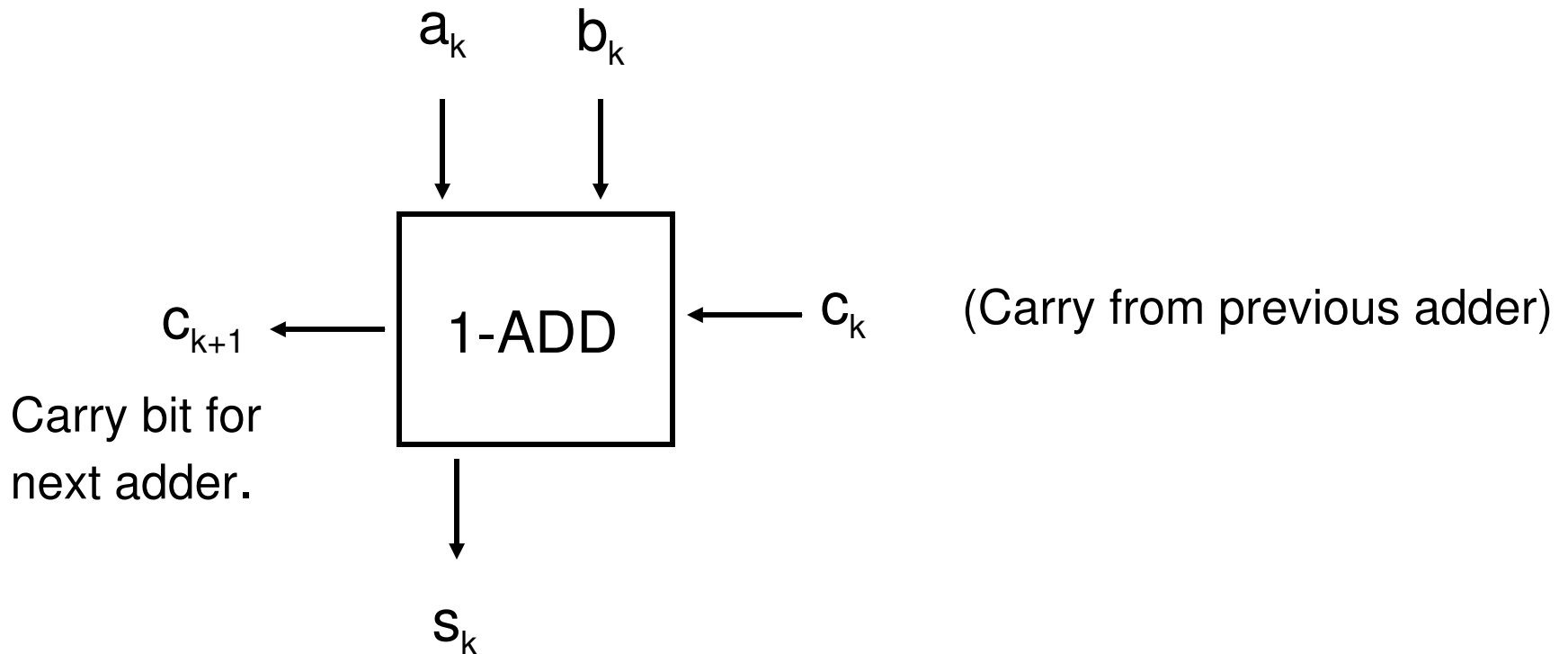



Do yourself: Write truth table, circuit.

A Full Adder (from handout)

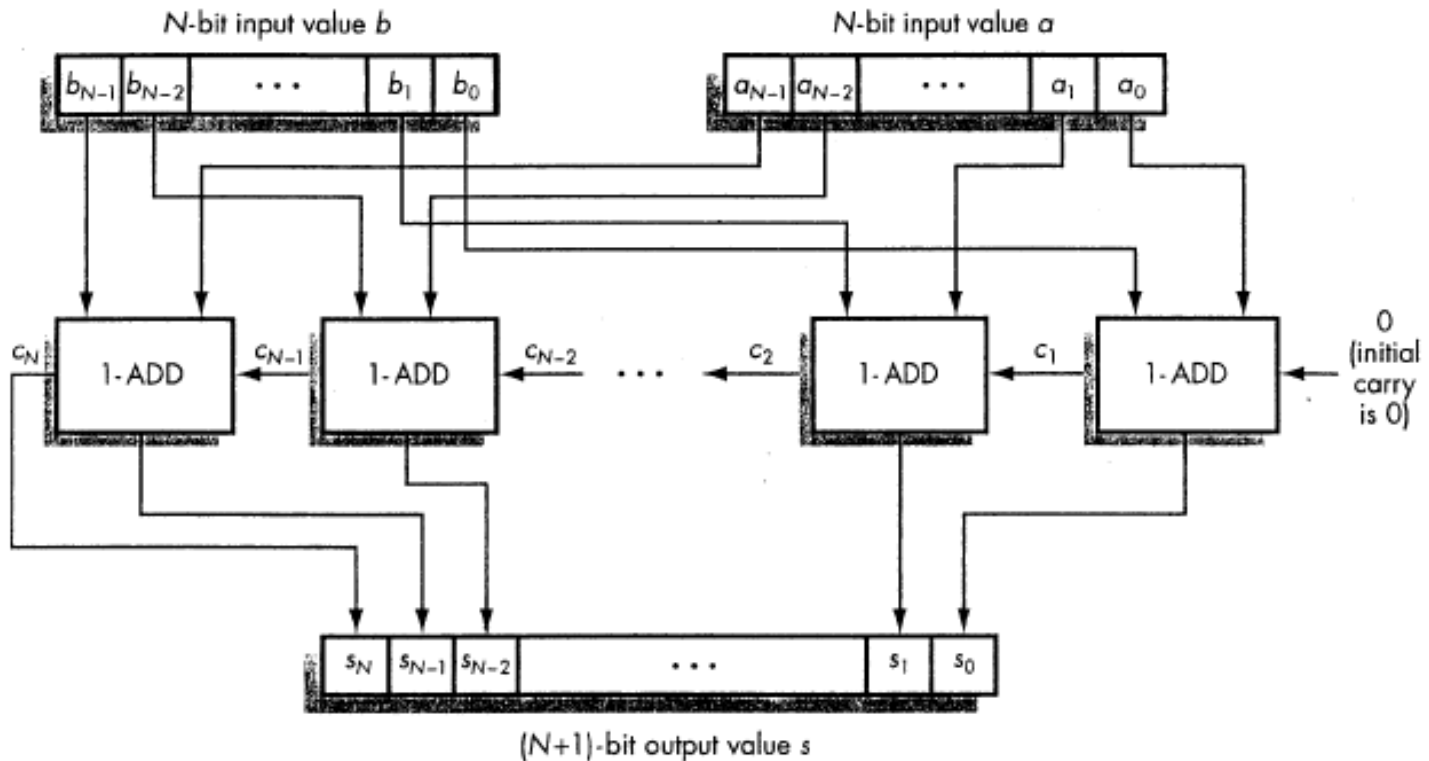

Timing Diagram


NOT gate

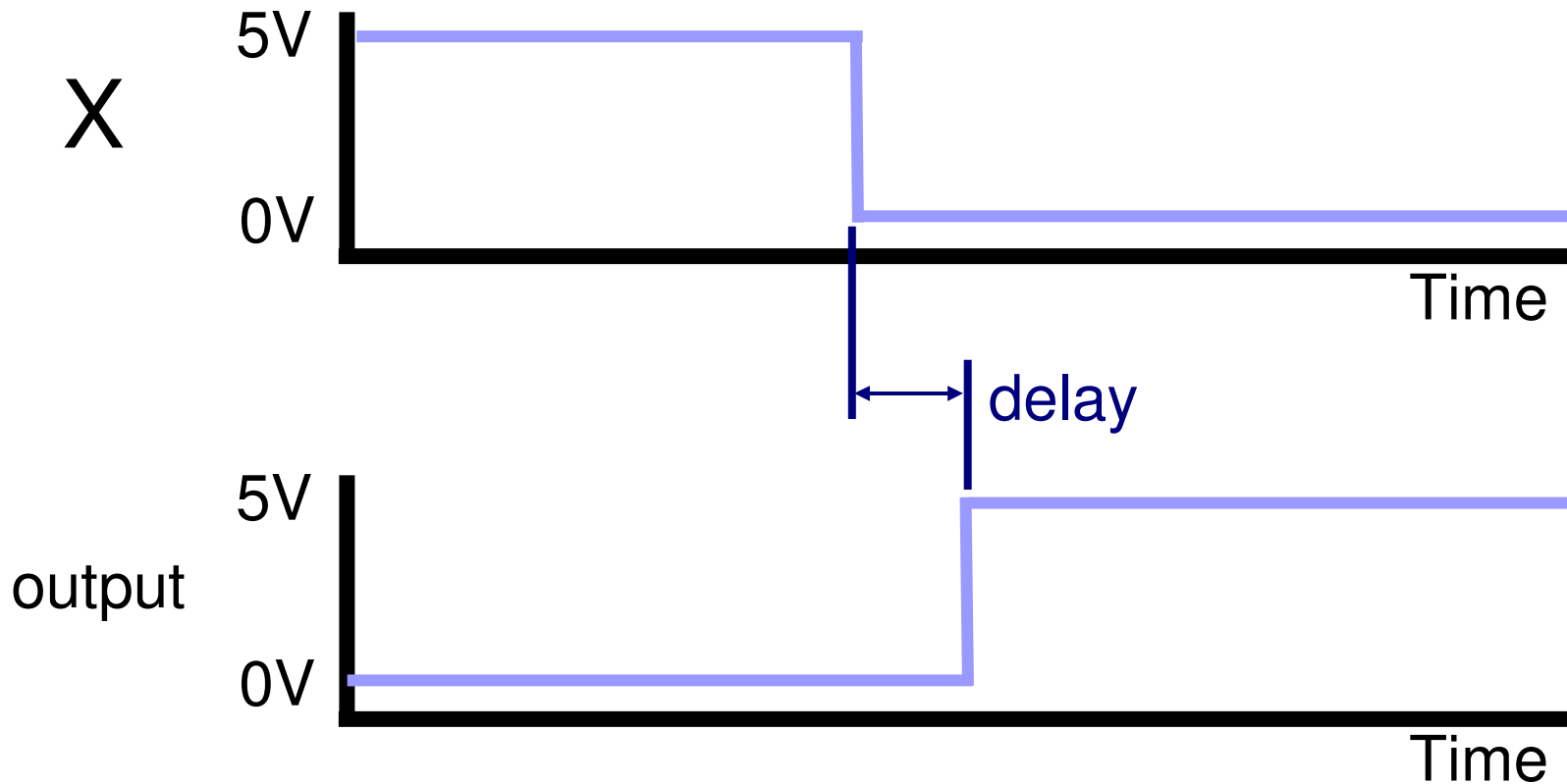 



Memory

 Rest of this lecture:
How boolean circuits can have
“memory”.



What do you understand by ‘memory’?”?




How can you tell that a 1-year old child has it?

Behaviorist's answer:
His/her actions depend upon past events.




Why combinational circuits have no “memory”

- Boolean gates connected by wires

 

Wires: transmit voltage
(and hence value)

- Important: no loops allowed

 


Output is determined by current inputs;
no “memory” of past values of the inputs.

Today: Circuits with loops; aka “Sequential Circuits”

Matt likes Sue but he doesn't like changing his mind

 - Represent with a circuit:
Matt will go to the party if Sue goes or if he already wanted to go





Is this well-defined?

Sequential Circuits

- Circuits with AND, OR and NOT gates.
- Cycles **are** allowed (ie outputs can feed back into inputs)
- Can exhibit “memory”.
- Sometimes may have “undefined” values

Enter Rita

 
 
- Matt will go to the party if Sue goes OR if the following holds: if Rita does not go *and* he already wanted to go.



R, S: **“control”** inputs


What combination of R, S changes M?

R-S Flip-Flop

  

- M becomes 1 if Set is turned on
- M becomes 0 if Reset is turned on
- Otherwise (if both are 0), M just remembers its value

A more convenient form of memory

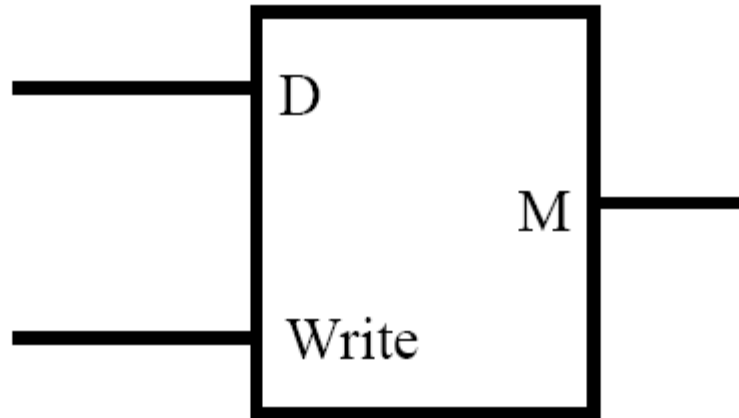


No
“undefined”
outputs ever!

- If $Write = 0$, M just keeps its value. (It ignores D .)
- If $Write = 1$, then M becomes set to D

“Data Flip-Flop” or “D flip flop”;
Can be implemented using R-S flip flop.

“Register” with 4 bits of memory

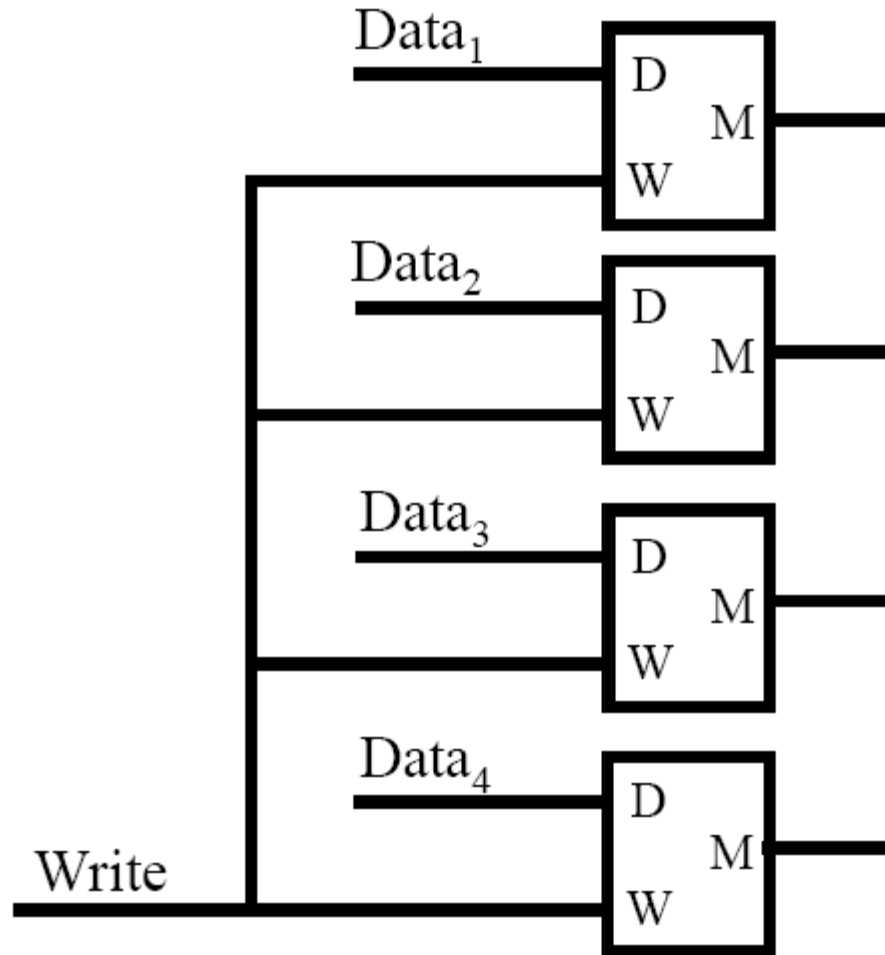

What controls the “Write” signal?

- Often, the system clock!
- “clock” = device that sends out a fluctuating voltage signal that looks like this




“Computer speed” often refers to the clock frequency (e.g. 2.4GHz)

The “symphony” inside a computer




Clock

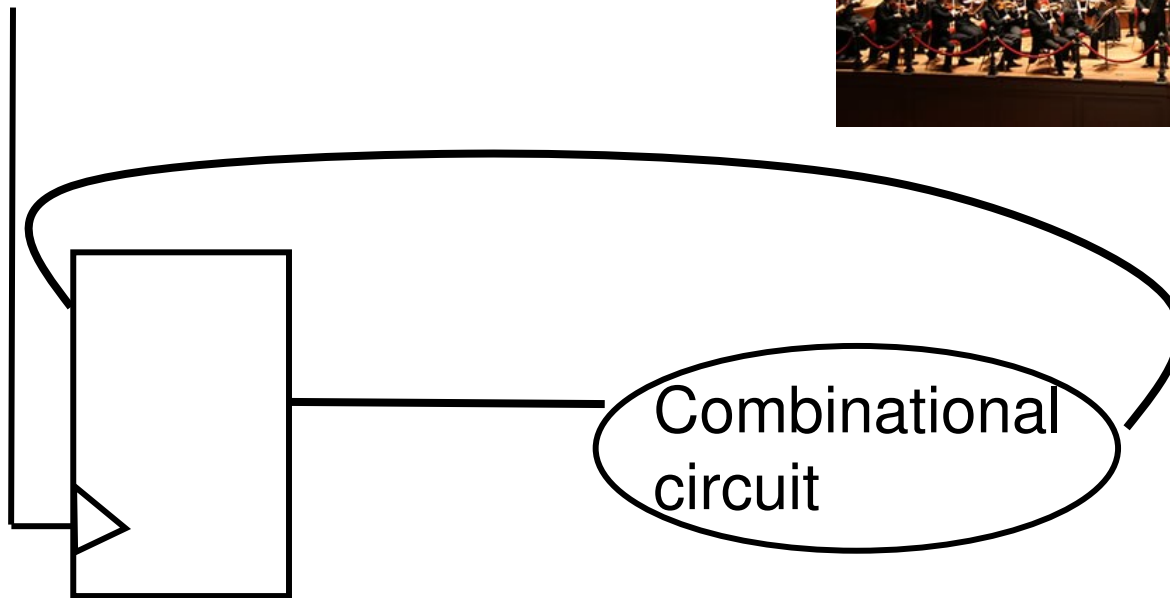

Memory

Combinational
circuit

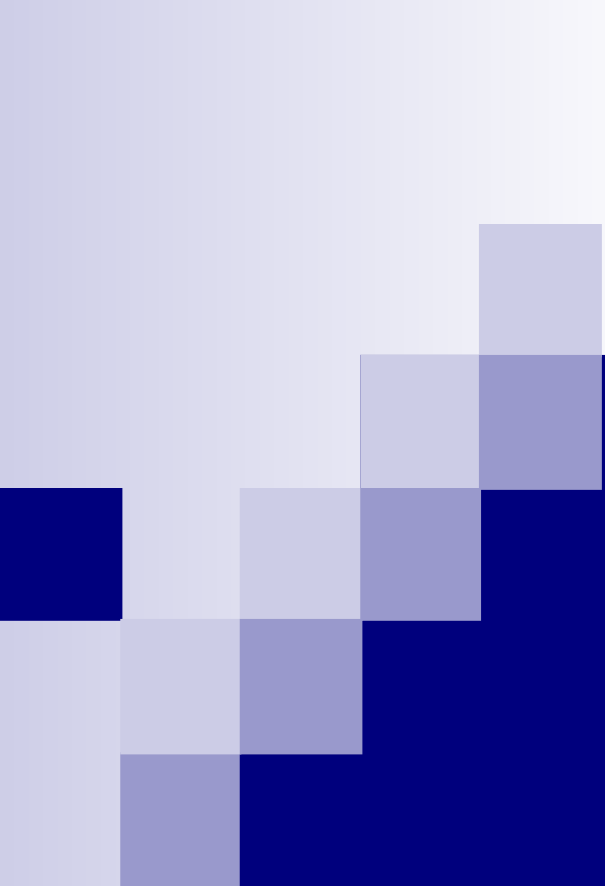
Clocked
Sequential
Circuit
(aka
Synchronous
Circuits)




Clocked Sequential Circuits

Synchronous Sequential Circuit

(aka Clocked Sequential Circuit)

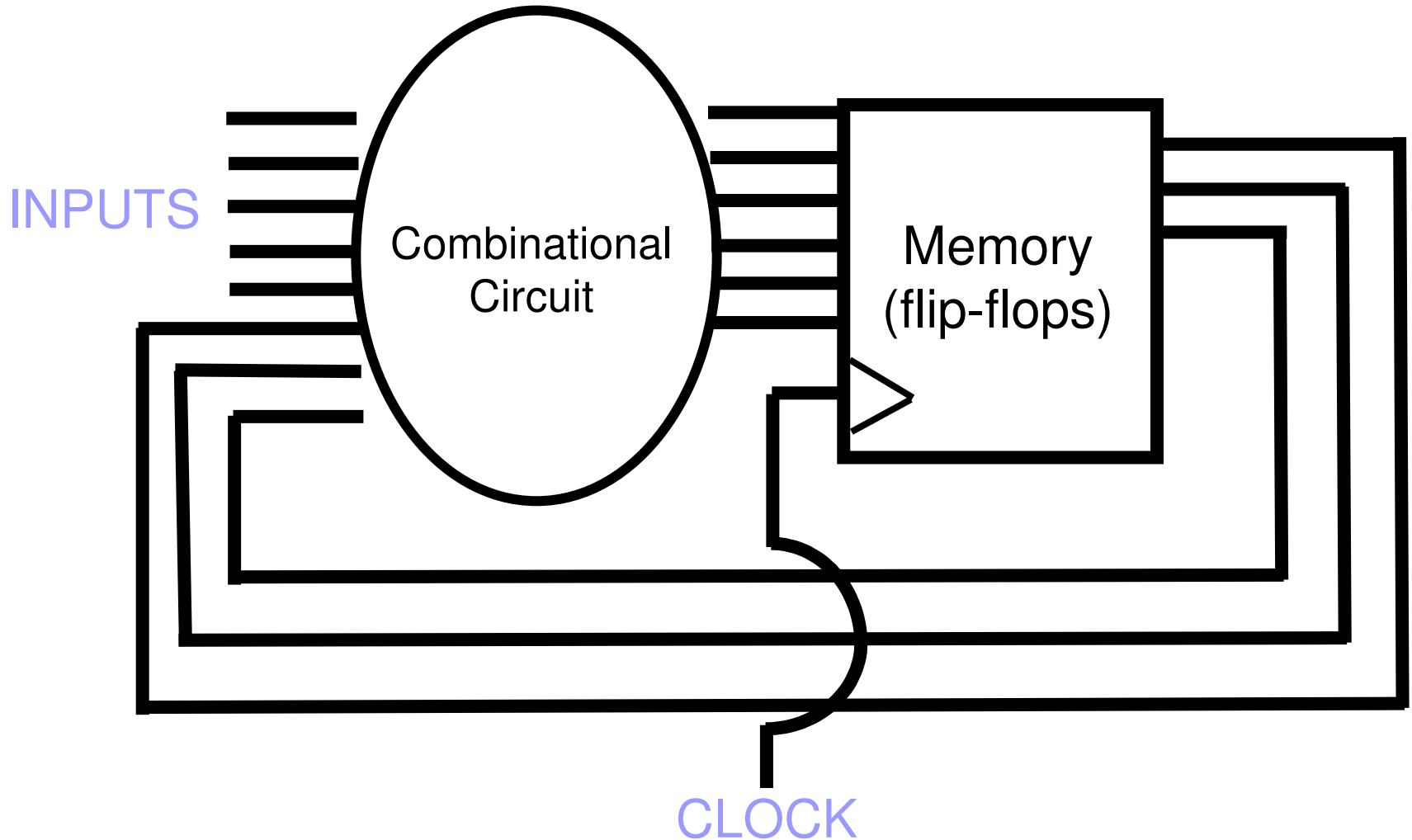


Shorthand

 

This stands for "lots of wires"


Clock Speeds

1974	Intel 8080	2 MHz (Mega = Million)
1981	Original IBM PC	4.77 MHz
1993	Intel Pentium	66 MHz
2005	Pentium 4	3.4 GHz (Giga = Billion)

 

Heinrich Hertz
1857-94

What limits clock speed?

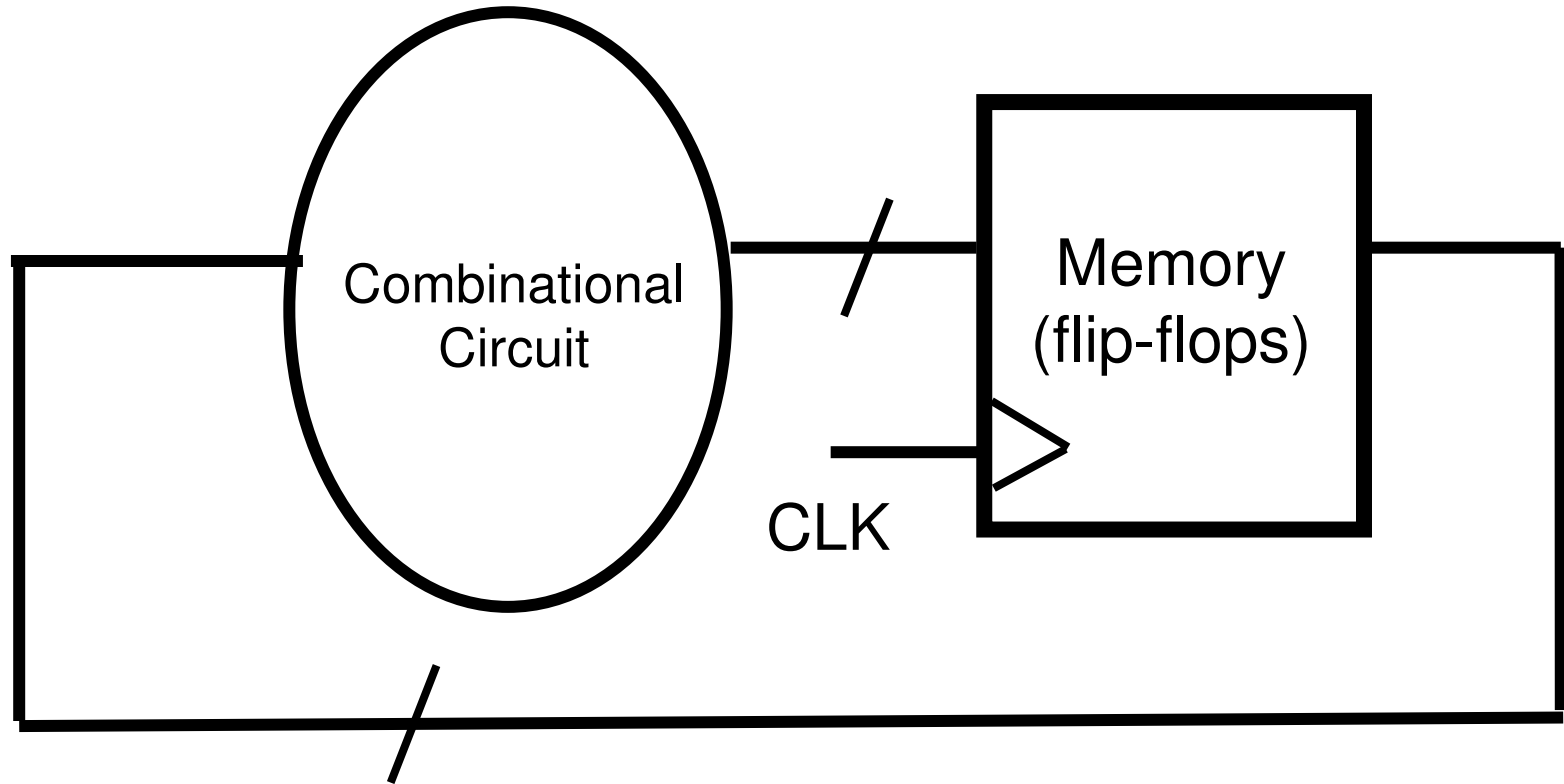

Delays in combinational logic (remember the adder)

During 1 clock cycle of Pentium 4, light travels: **4 inches**



Finite State Machines

Read handout (Brian Hayes article) for next time.

Example: State diagram for automatic door

