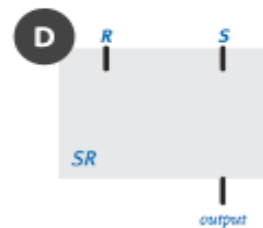
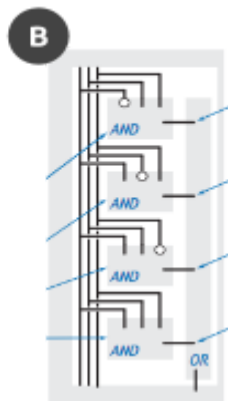
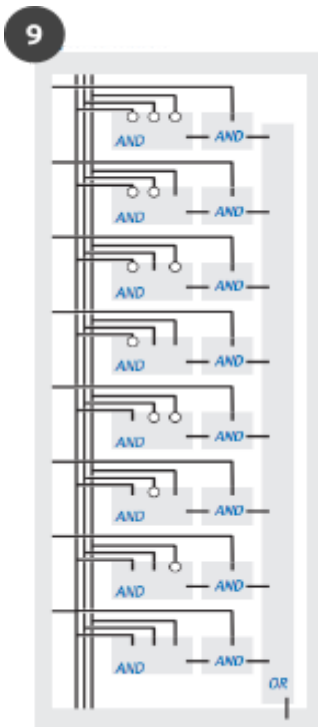
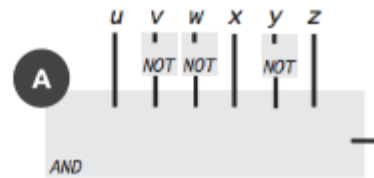
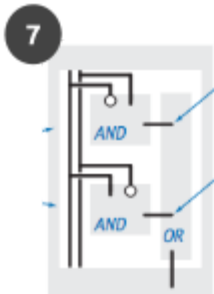
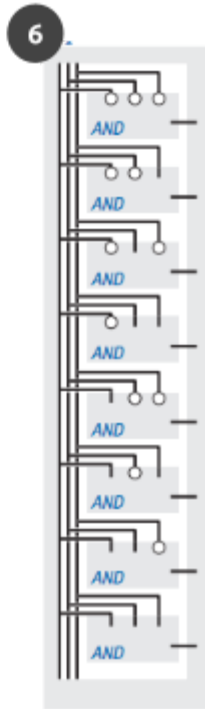
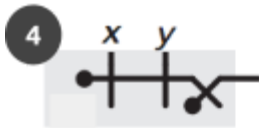
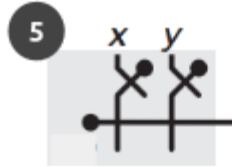
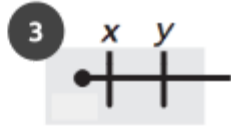
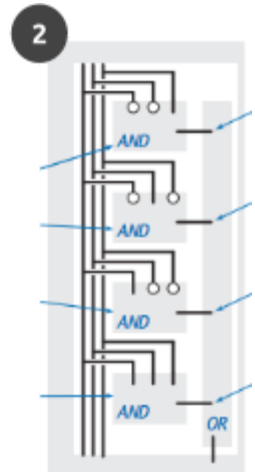
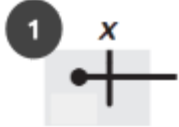


For each circuit below, find its matching boolean algebraic expression on the second page, then find its matching description on the third page.



0  $(u + v + w + x + y + z)'$

1  $x'$

3 3-bit value selects one of eight input wires

2  $x'yz + xy'z + xyz' + xyz$

6 can be used to store one bit of memory

4  $(x + y)'$

8 3-bit value turns on one of eight output wires

5  $uvwxyz$

A  $uv'w'xy'z$

9  $x'y + xy'$

7  $x + y$

B  $u + v + w + x + y + z$

D  $xy$

C  $x'y'z + x'yz' + xy'z' + xyz$

0 6-INPUT AND

1 NOR

3 XOR

2 NOT

6 OR

8 MULTIPLEXER

4 MAJ

5 DECODER

9 6-INPUT OR

A AND

B ODD

7 6-INPUT  
GENERAL  
BOOLEAN  
FUNCTION

D FLIP-FLOP

C 6-INPUT NOR

Write the matching numbers/letters in the empty cells below.

PAGE 1 CIRCUIT	PAGE 2 BOOLEAN ALG.	PAGE 3 DESCRIPTION
0		
1		
2		
3		
4		
5		
6		
7		
8		
9		
A		
B		
C		
D		