
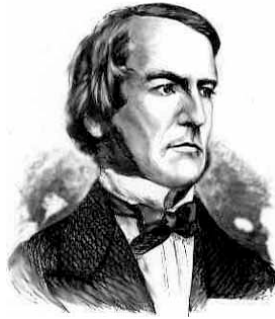


Lecture 10: Combinational Circuits

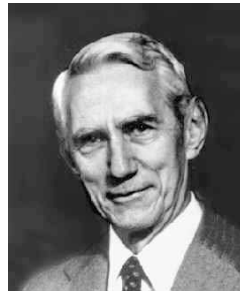

George Boole (1815 - 1864)




Claude Shannon (1916 - 2001)

Computer Architecture

Previous two lectures.

- TOY machine.

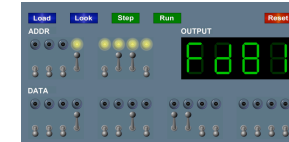

Next two lectures.

- Digital circuits.



Culminating lecture.

- Putting it all together and building a TOY machine.

Digital Circuits

What is a digital system?

- Digital: signals are 0 or 1.
- Analog: signals vary continuously.

Why digital systems?

- Accuracy and reliability.
- Staggeringly fast and cheap.

Basic abstractions.

- On, off.
- Switch that can turn something on or off.


Digital circuits and you.

- ➔ ▪ Computer microprocessors.
- Antilock brakes.
- Cell phones.

Wires


Wires.

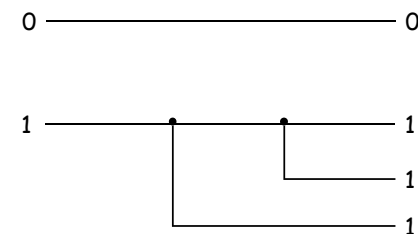- Propagate logical values from place to place.
- Signals "flow" from left to right.



Input


Output

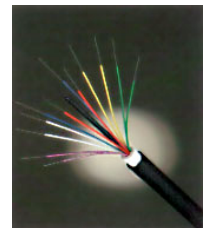

Logic Gates

Logical gates.

- Fundamental building blocks.

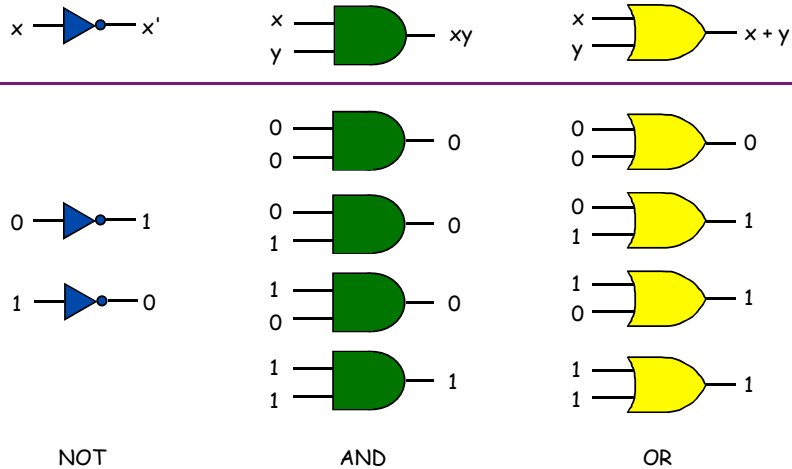


5

Multiway AND Gates

$AND(x_0, x_1, x_2, x_3, x_4, x_5, x_6, x_7)$.

- 1 if all inputs are 1.
- 0 otherwise.

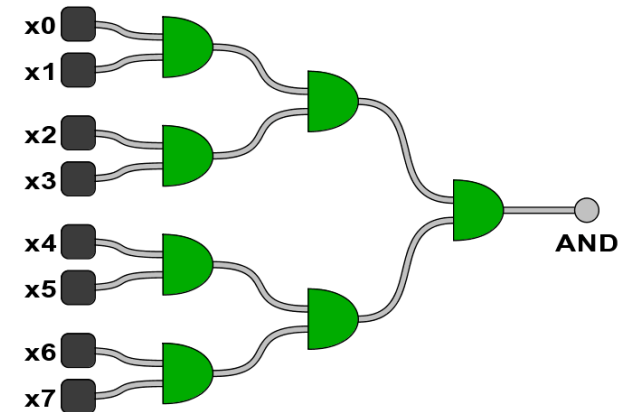


6

Multiway OR Gates

$OR(x_0, x_1, x_2, x_3, x_4, x_5, x_6, x_7)$.

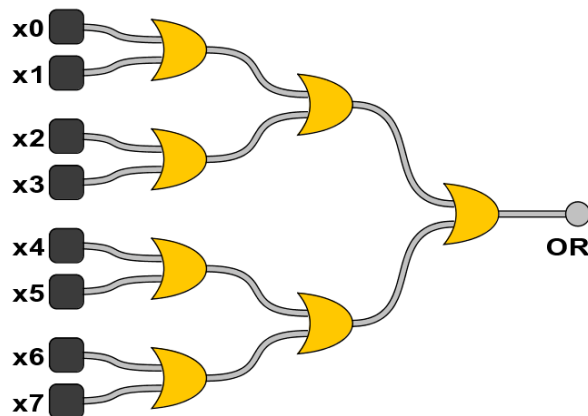- 1 if at least one input is 1.
- 0 otherwise.



7

Boolean Algebra

History.


- Developed by Boole to solve mathematical logic problems (1847).
- Shannon first applied to digital circuits (1937).

Basics.

- Boolean variable: value is 0 or 1.
- Boolean function: function whose inputs and outputs are 0, 1.

Relationship to circuits.

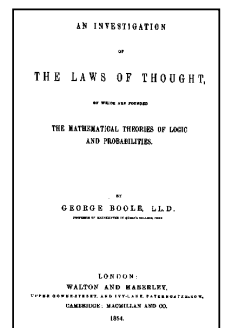- Boolean variables: signals.
- Boolean functions: circuits.




8

Truth Table

Truth table.

- Systematic method to describe Boolean function.
- One row for each possible input combination.
- N inputs $\Rightarrow 2^N$ rows.

AND Truth Table		
x	y	AND(x, y)
0	0	0
0	1	0
1	0	0
1	1	1

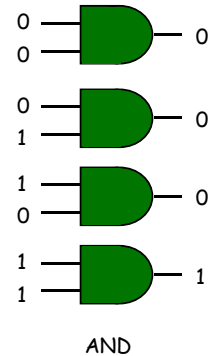

9

Truth Table for Functions of 2 Variables

Truth table.

- 16 Boolean functions of 2 variables.
- every 4-bit value represents one

Truth Table for All Boolean Functions of 2 Variables									
x	y	ZERO	AND		x		y	XOR	OR
0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1

Truth Table for All Boolean Functions of 2 Variables									
x	y	NOR	EQ	y'		x'		NAND	ONE
0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1

10

Truth Table for Functions of 3 Variables

Truth table.

- 16 Boolean functions of 2 variables.
- every 4-bit value represents one
- 256 Boolean functions of 3 variables.
- every 8-bit value represents one
- $2^{(2^N)}$ Boolean functions of N variables!

Some Functions of 3 Variables						
x	y	z	AND	OR	MAJ	ODD
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	0	1	0	1
0	1	1	0	1	1	0
1	0	0	0	1	0	1
1	0	1	0	1	1	0
1	1	0	0	1	1	0
1	1	1	1	1	1	1



11

Universality of AND, OR, NOT

Any Boolean function can be expressed using AND, OR, NOT.

- "Universal."
- $XOR(x,y) = xy' + x'y$

Expressing XOR Using AND, OR, NOT							
x	y	x'	y'	x'y	xy'	x'y + xy'	XOR
0	0	1	1	0	0	0	0
0	1	1	0	1	0	1	1
1	0	0	1	0	1	1	1
1	1	0	0	0	0	0	0

Notation	Meaning
x'	NOT x
x y	x AND y
x + y	x OR y

Exercise: {AND, NOT}, {OR, NOT}, {NAND}, {AND, XOR} are universal.

12

Sum-of-Products

Any Boolean function can be expressed using AND, OR, NOT.

- Sum-of-products is systematic procedure.
 - form AND term for each 1 in Boolean function
 - OR terms together


Expressing MAJ Using Sum-of-Products									
x	y	z	MAJ	$x'yz$	$xy'z$	xyz'	xyz	$x'yz + xy'z + xyz' + xyz$	
0	0	0	0	0	0	0	0	0	
0	0	1	0	0	0	0	0	0	
0	1	0	0	0	0	0	0	0	
0	1	1	1	1	0	0	0	1	
1	0	0	0	0	0	0	0	0	
1	0	1	1	0	1	0	0	1	
1	1	0	1	0	0	1	0	1	
1	1	1	1	0	0	0	1	1	

13

Translate Boolean Formula to Boolean Circuit

Use sum-of-products form.

- $XOR(x, y) = xy' + x'y$.

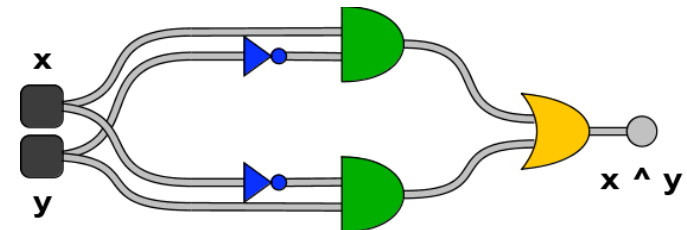


14

Translate Boolean Formula to Boolean Circuit

Use sum-of-products form.

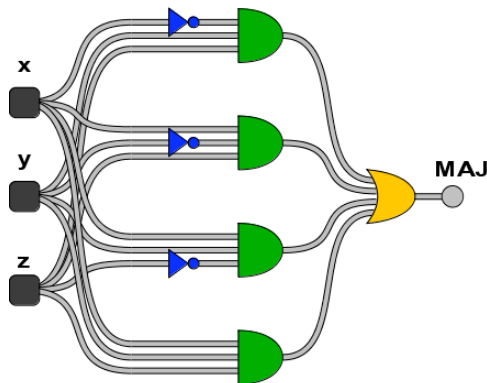- $MAJ(x, y, z) = x'yz + xy'z + xyz' + xyz$.




15


Simplification Using Boolean Algebra

Many possible circuits for each Boolean function.

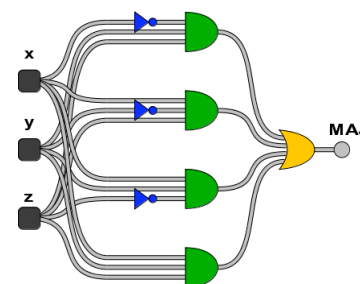- Sum-of-products not necessarily optimal in:
 - number of gates (space)
 - depth of circuit (time)
- $MAJ(x, y, z) = x'yz + xy'z + xyz' + xyz = xy + yz + xz$.



size = 8, depth = 3

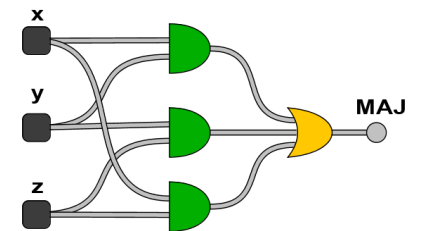

size = 4, depth = 2

16

Expressing a Boolean Function Using AND, OR, NOT

Ingredients.

- AND gates.
- OR gates.
- NOT gates.
- Wire.

Instructions.

- Step 1: represent input and output signals with Boolean variables.
- Step 2: construct truth table to carry out computation.
- Step 3: derive (simplified) Boolean expression using sum-of products.
- Step 4: transform Boolean expression into circuit.

17

ODD Parity Circuit

ODD(x, y, z).

- 1 if odd number of inputs are 1.
- 0 otherwise.


Expressing ODD Using Sum-of-Products								
x	y	z	ODD	$x'y'z$	$x'yz'$	$xy'z'$	xyz	$x'y'z + x'yz' + xy'z' + xyz$
0	0	0	0	0	0	0	0	0
0	0	1	1	1	0	0	0	1
0	1	0	1	0	1	0	0	1
0	1	1	0	0	0	0	0	0
1	0	0	1	0	0	1	0	1
1	0	1	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0
1	1	1	1	0	0	0	1	1

18

ODD Parity Circuit

ODD(x, y, z).

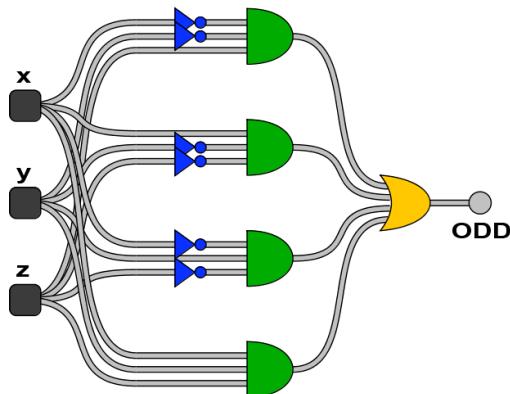- 1 if odd number of inputs are 1.
- 0 otherwise.



19


Let's Make an Adder Circuit

Goal: $x + y = z$ for 4-bit integers.

- We build 4-bit adder: 9 inputs, 4 outputs.
- Same idea scales to 128-bit adder.
- Key computer component.

Step 1.

- Represent input and output in binary.

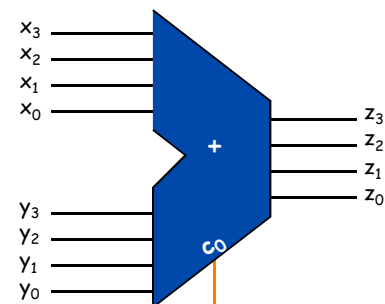

	1	1	1	0
	2	4	8	7
+	3	5	7	9
	6	0	6	6

	1	1	0	0
	0	0	1	0
+	0	1	1	1
	1	0	0	1

	x_3	x_2	x_1	x_0
	y_3	y_2	y_1	y_0
+	y_3	y_2	y_1	y_0
	z_3	z_2	z_1	z_0

20

Let's Make an Adder Circuit

Goal: $x + y = z$ for 4-bit integers.

Step 2. (first attempt)

- Build truth table.
- Why is this a bad idea?
 - 128-bit adder: 2^{256+1} rows > # electrons in universe!

				c_0
x_3	x_2	x_1	x_0	
+	y_3	y_2	y_1	y_0
	z_3	z_2	z_1	z_0

4-Bit Adder Truth Table												
c_0	x_3	x_2	x_1	x_0	y_3	y_2	y_1	y_0	z_3	z_2	z_1	z_0
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	0	0	0	1	1	0	0	1	1
0	0	0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	0	1	0	1	0	1	0	1
0	0	0	0	0	0	1	1	0	0	1	1	0
0	0	0	0	0	1	0	0	0	0	1	0	0
0	0	0	0	0	1	0	1	0	1	1	0	1
0	0	0	0	0	1	1	0	0	0	1	1	0
0	0	0	0	0	1	1	1	0	1	1	1	1
1	1	1	1	1	1	1	1	1	1	1	1	1

$2^{8+1} = 512$ rows!

21

Let's Make an Adder Circuit

Goal: $x + y = z$ for 4-bit integers.

Step 2. (do one bit at a time)

- Build truth table for carry bit.
- Build truth table for summand bit.

	c_3	c_2	c_1	$c_0 = 0$
x_3	x_2	x_1	x_0	
+	y_3	y_2	y_1	y_0
	z_3	z_2	z_1	z_0

Carry Bit			
x_i	y_i	c_i	c_{i+1}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Summand Bit			
x_i	y_i	c_i	z_i
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

22

Let's Make an Adder Circuit

Goal: $x + y = z$ for 4-bit integers.

Step 3.

- Derive (simplified) Boolean expression.

	c_3	c_2	c_1	$c_0 = 0$
x_3	x_2	x_1	x_0	
+	y_3	y_2	y_1	y_0
	z_3	z_2	z_1	z_0

Carry Bit				
x_i	y_i	c_i	c_{i+1}	MAJ
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Summand Bit				
x_i	y_i	c_i	z_i	ODD
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


23

Let's Make an Adder Circuit

Goal: $x + y = z$ for 4-bit integers.

Step 4.

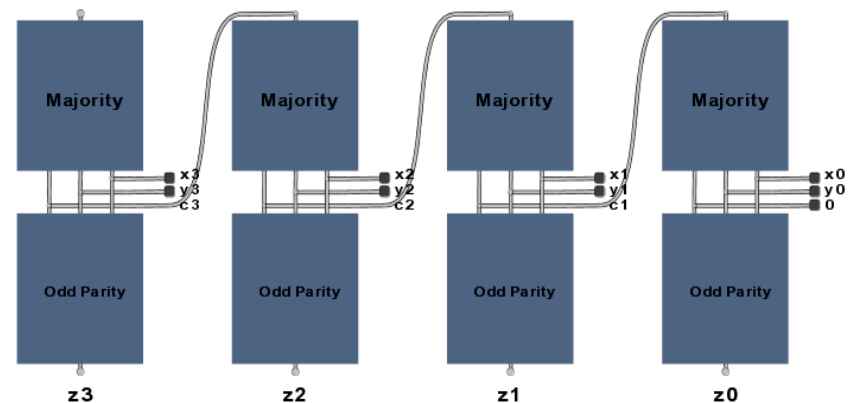- Transform Boolean expression into circuit.
- Chain together 1-bit adders.




24

Let's Make an Adder Circuit

Goal: $x + y = z$ for 4-bit integers.

Step 4.

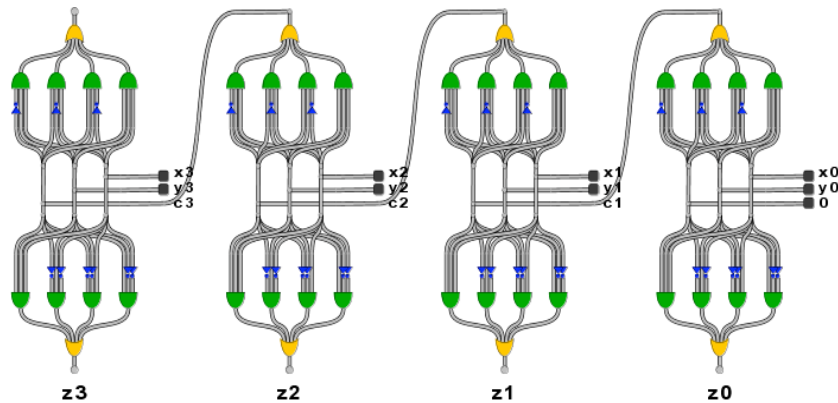- Transform Boolean expression into circuit.
- Chain together 1-bit adders.




25


Subtractor

Subtractor circuit: $z = x - y$.

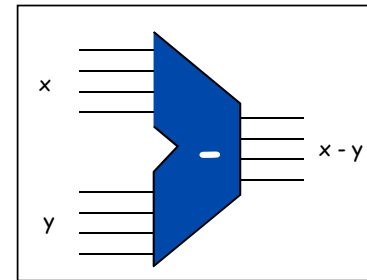- One approach: design like adder circuit.
- Better idea: reuse adder circuit.
 - 2's complement: to negate an integer, flip bits, then add 1



4-Bit Subtractor Interface

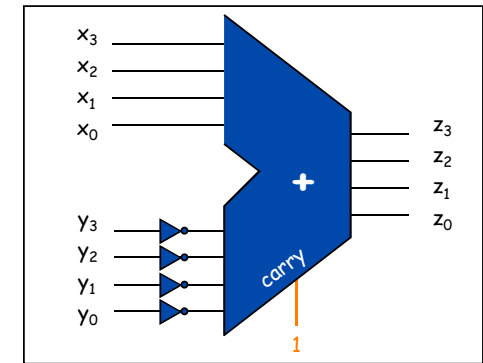

4-Bit Subtractor Implementation


26

Arithmetic Logic Unit: Interface

ALU Interface.


- Add, subtract, bitwise and, bitwise xor, shift left, shift right, copy.
- Associate 3-bit integer with 5 primary ALU operations.
 - ALU performs operations in parallel
 - control wires select which result ALU outputs

op	2	1	0
+, -	0	0	0
&	0	0	1
^	0	1	0
<<, >>	0	1	1
input 2	1	0	0

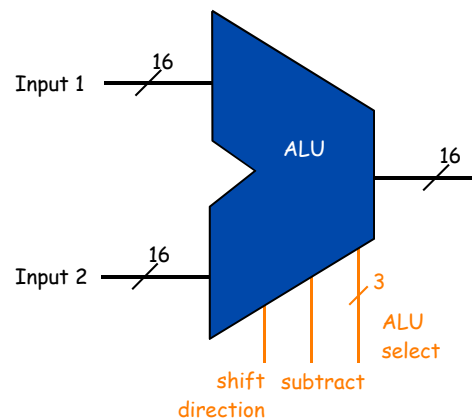

27

Arithmetic Logic Unit: Implementation

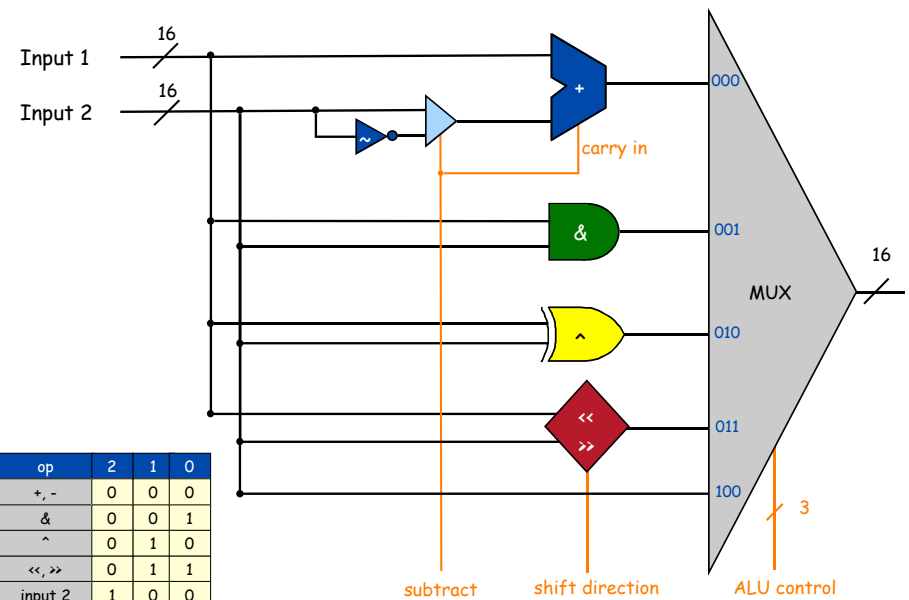

op	2	1	0
+, -	0	0	0
&	0	0	1
^	0	1	0
<<, >>	0	1	1
input 2	1	0	0

28

Summary

Lessons for software design apply to hardware design!

- Interface describes behavior of circuit.
- Implementation gives details of how to build it.

Layers of abstraction apply with a vengeance!

- On/off.
- Controlled switch (transistor).
- Gates (AND, OR, NOT).
- Boolean circuit (MAJ, ODD).
- Adder.
- . . .
- Arithmetic logic unit.
- . . .
- TOY machine.