



Memory; Sequential & Clocked Circuits; Finite State Machines

COS 116: 3/27/2007

Adam Finkelstein

Combinational circuit: addition

$$\begin{array}{r} 25 \qquad 11001 \\ + 29 \qquad 11101 \\ \hline 54 \qquad 110110 \end{array}$$


- Want to add any two N -bit integers

Modular design

$$\begin{array}{rcccccc} & & \mathbf{c}_{N-1} & \mathbf{c}_{N-2} & \dots & \mathbf{c}_1 & \mathbf{c}_0 & \text{Carry bits} \\ & & \mathbf{a}_{N-1} & \mathbf{a}_{N-2} & \dots & \mathbf{a}_1 & \mathbf{a}_0 & \\ + & & \mathbf{b}_{N-1} & \mathbf{b}_{N-2} & \dots & \mathbf{b}_1 & \mathbf{b}_0 & \\ \hline & \mathbf{s}_N & \mathbf{s}_{N-1} & \mathbf{s}_{N-2} & \dots & \mathbf{s}_1 & \mathbf{s}_0 & \end{array}$$


Need N 1-bit adders

1-bit adder

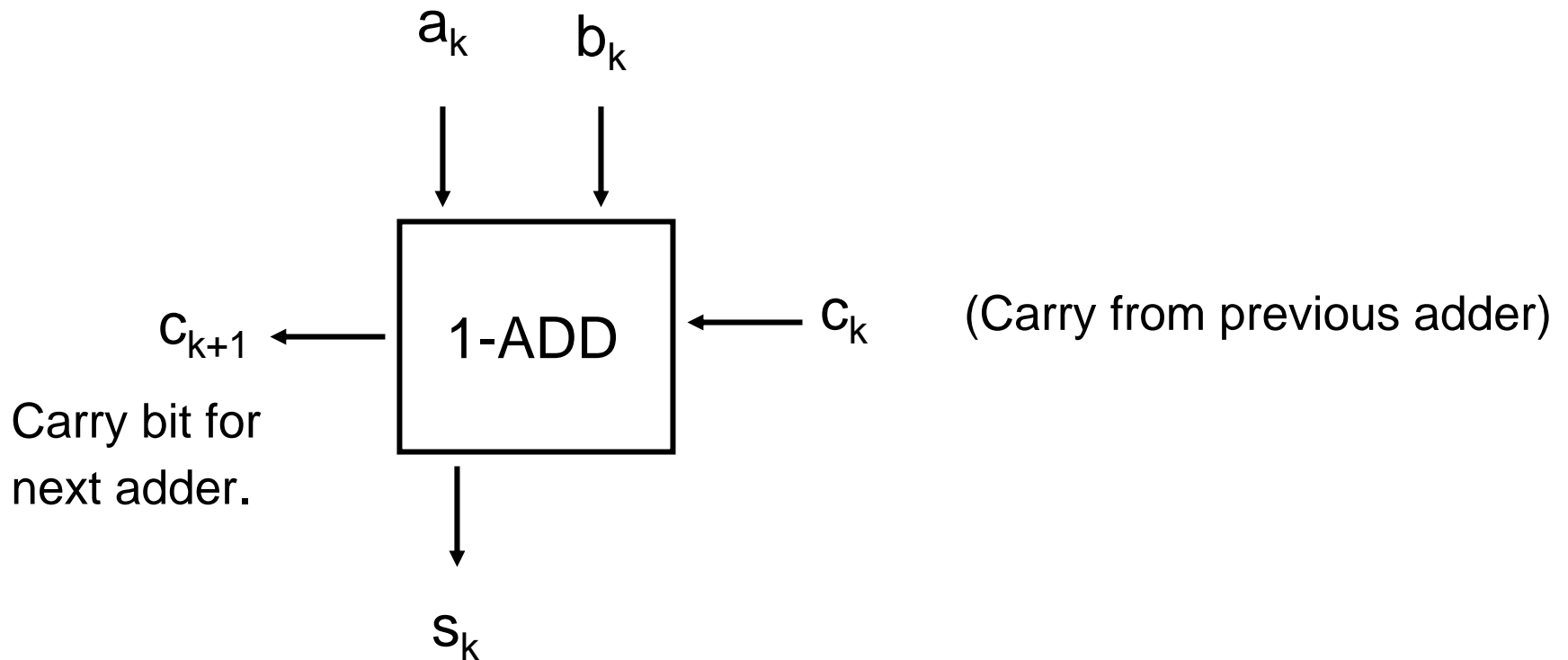



Do yourself: Write truth table, circuit.

A Full Adder (from handout)

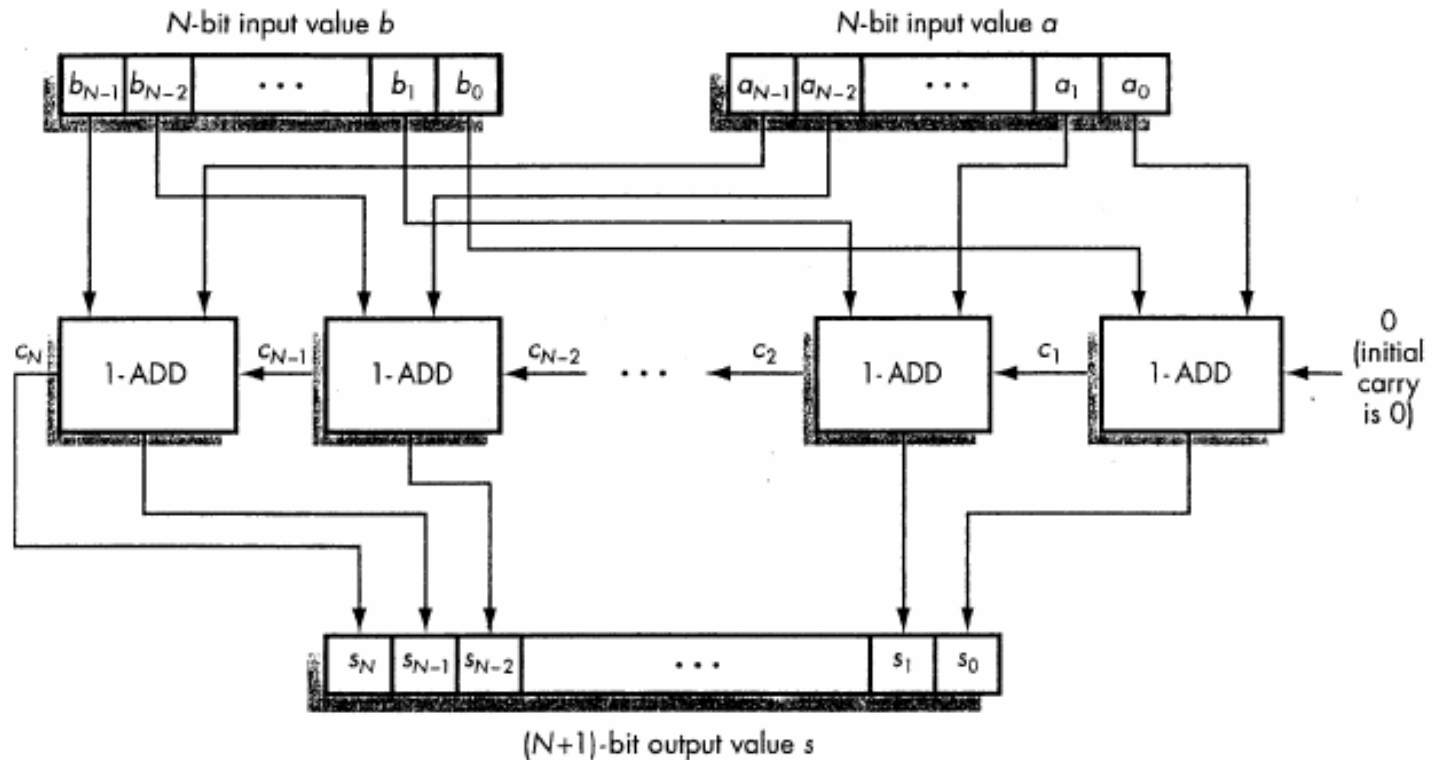

Timing Diagram

NOT gate

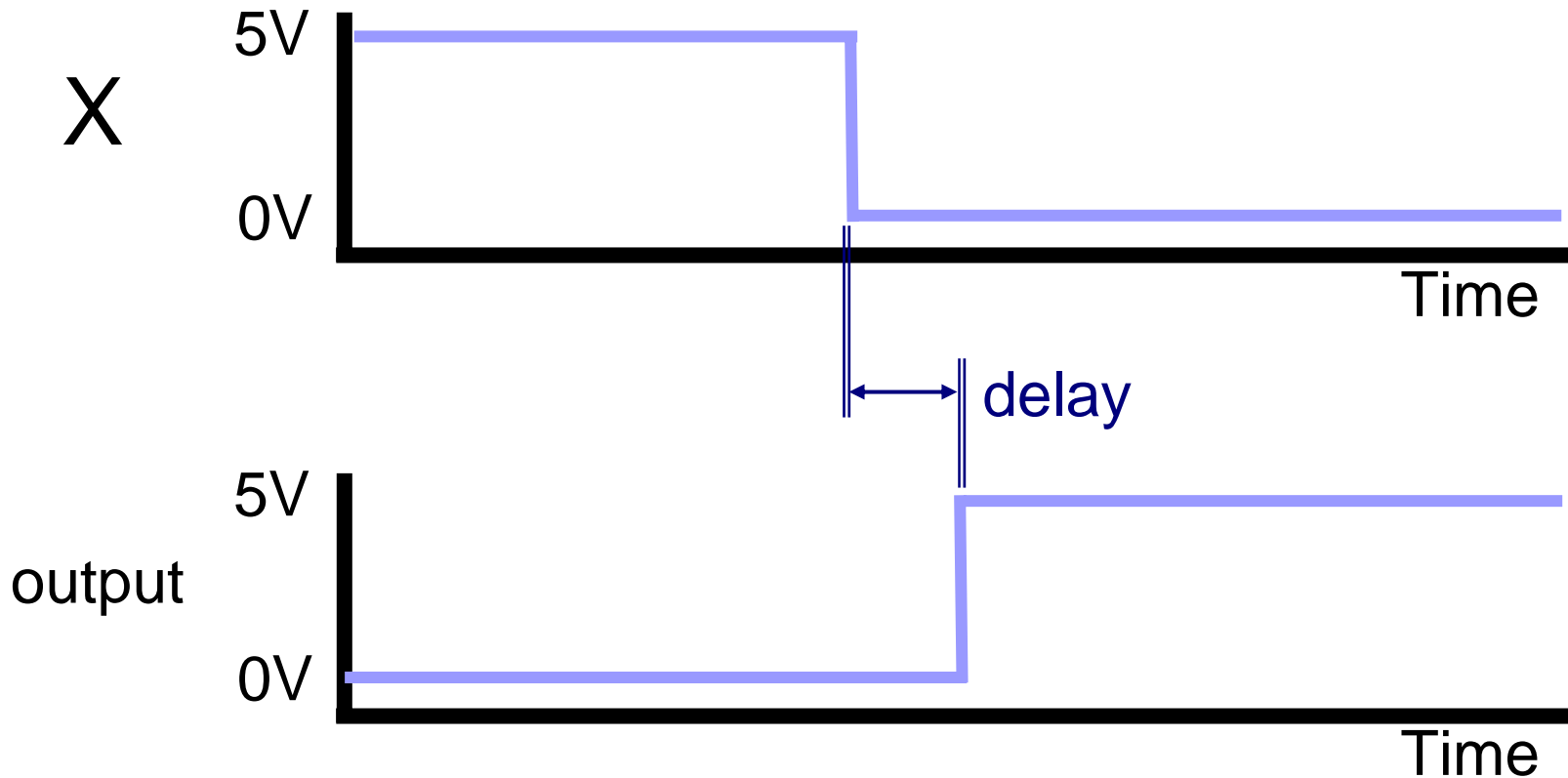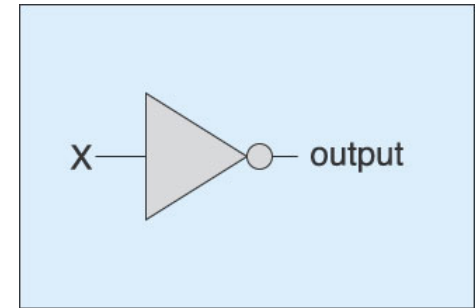




Memory

Going beyond combinational circuits

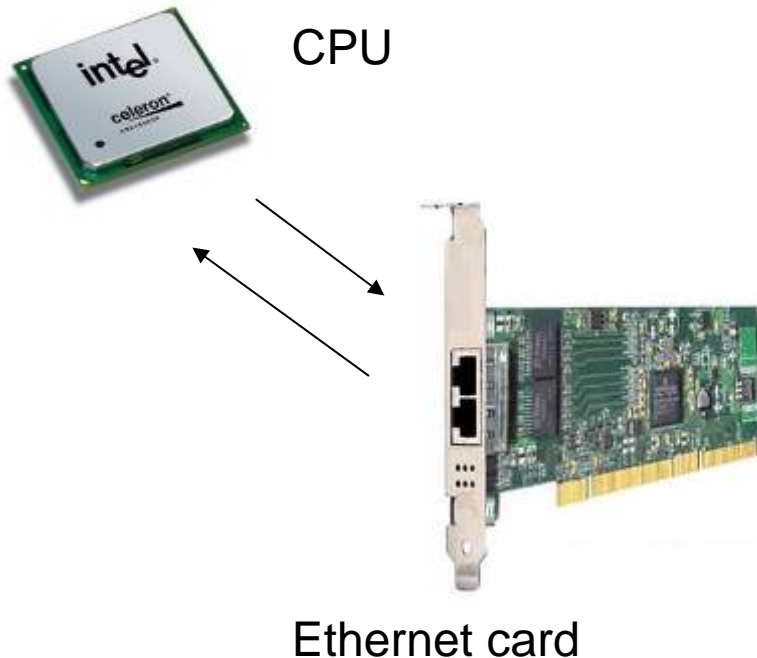- Need 2-way communication between circuits (i.e. need cycles!)



- Need memory (scratchpad)



What do you understand by ‘memory’?”?




How can you tell that a 1-year old child has it?

Behaviorist's answer:
His/her actions depend upon past events.



Matt likes Sue but he doesn't like changing his mind


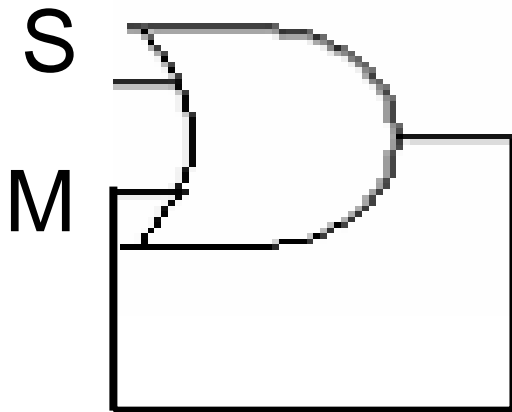
- Represent with a circuit:
Matt will go to the party if Sue goes or if he already wanted to go



Is this well-defined?

Enter Rita

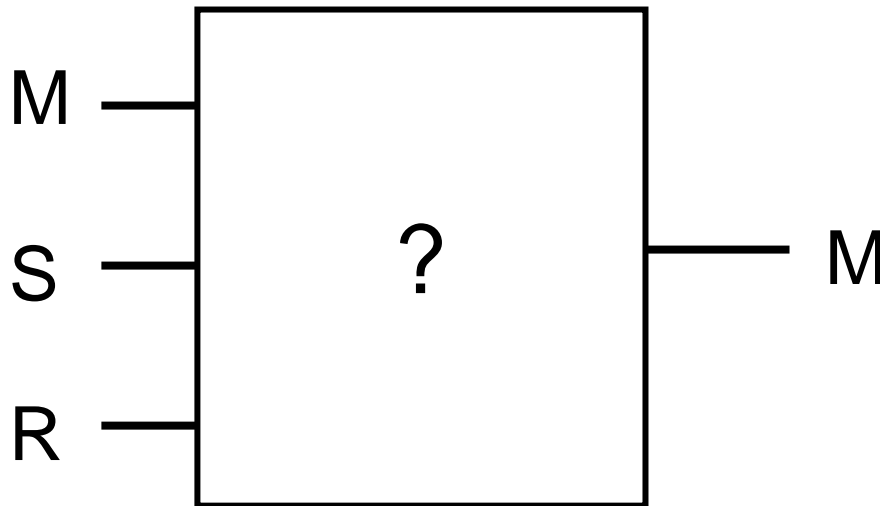
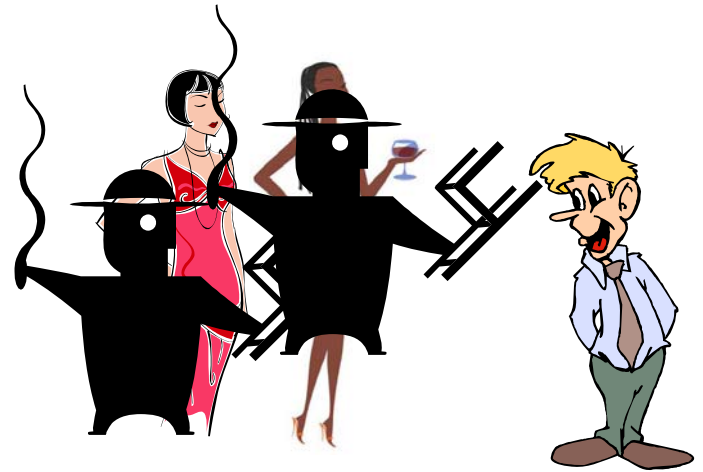
- Matt will go to the party if Sue goes OR if the following holds: if Rita does not go *and* he already wanted to go.



R, S: “**control**” inputs


What combination of R, S changes M?

Flip-Flop

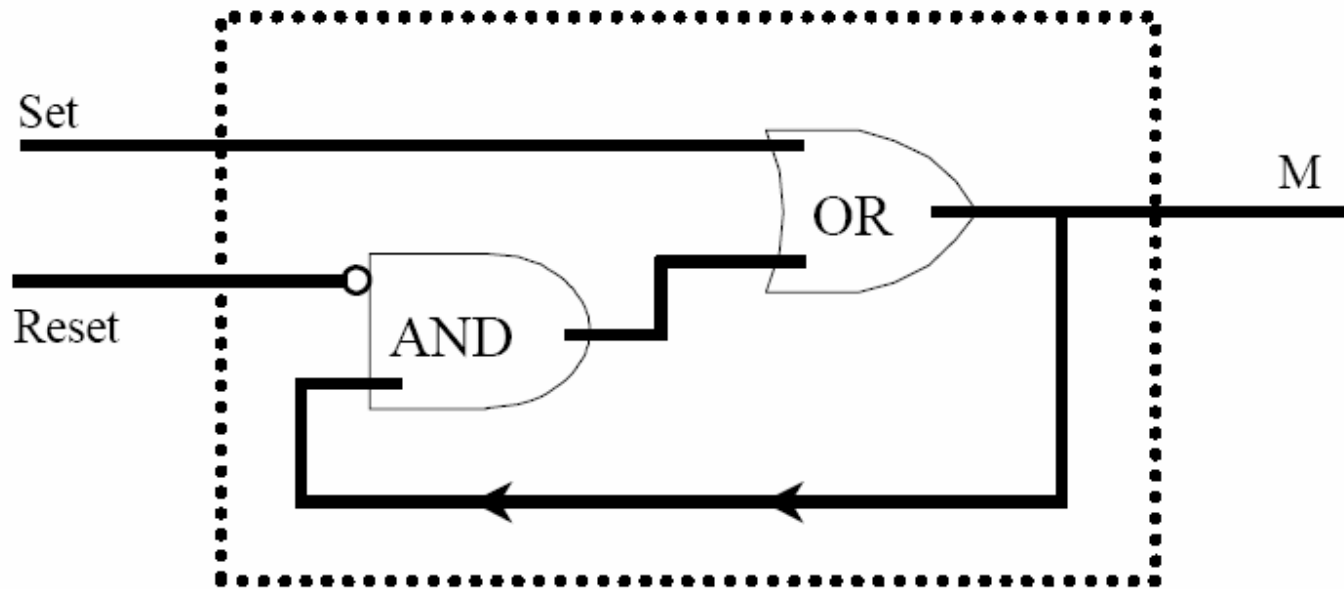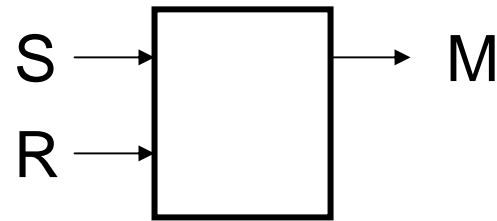

- M becomes 1 if Set is turned on
- M becomes 0 if Reset is turned on
- Otherwise (if both are 0), M just remembers its value

A more convenient form of memory

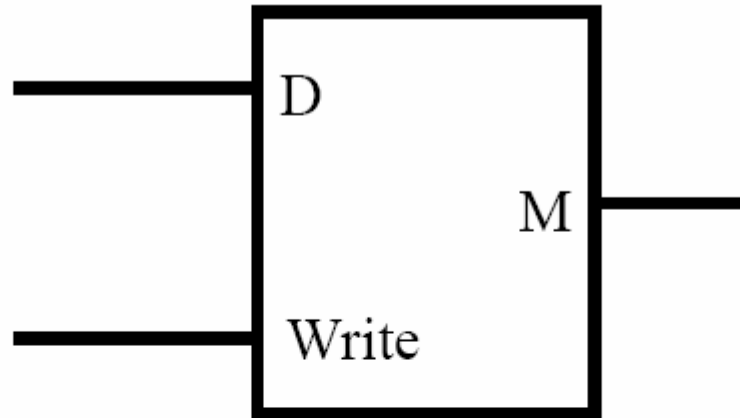

- If $\text{Write} = 0$, M just keeps its value. (It ignores D .)
- If $\text{Write} = 1$, then M becomes set to D

“Data Flip-Flop” or “D flip flop.”


What controls the “Write” signal?


- Often, the system clock!
- “clock” = device that sends out a fluctuating voltage signal that looks like this



“Computer speed” often refers to the clock frequency (e.g. 2.4GHz)

Memory “Register”: 4 bits

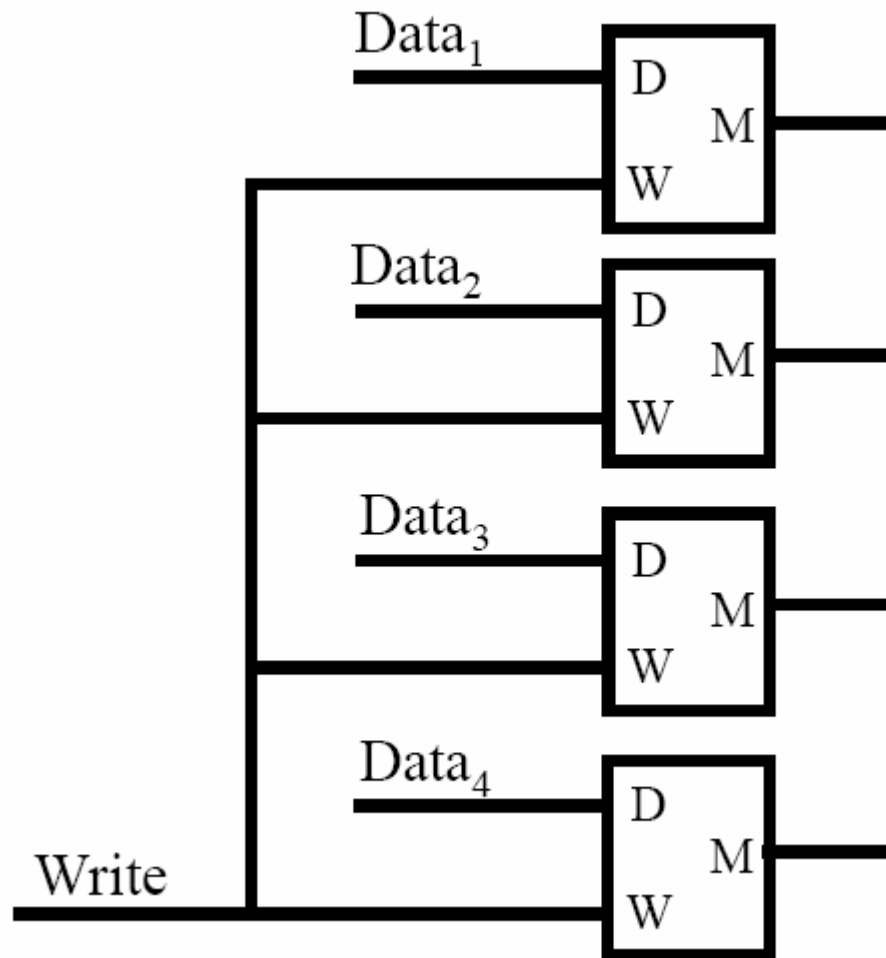


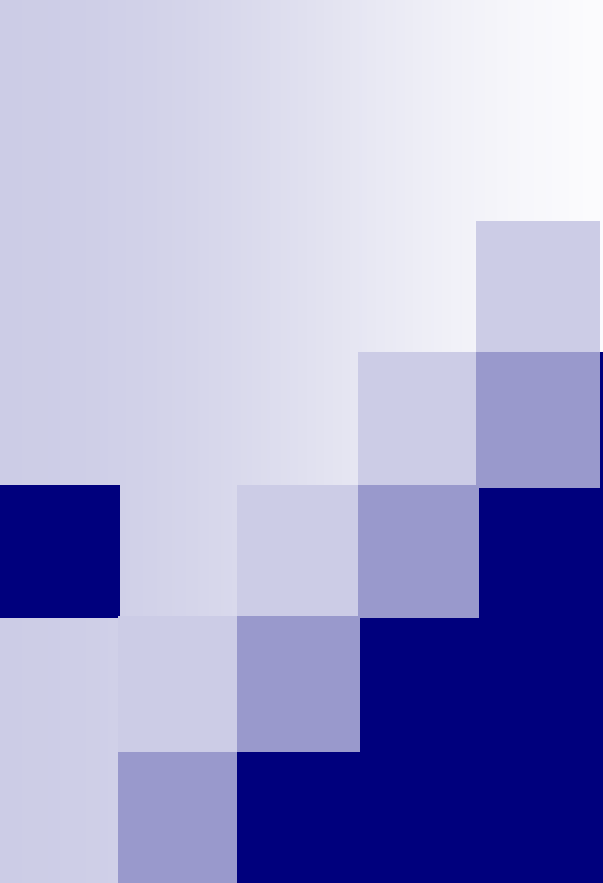


Clocked Sequential Circuits

Synchronous Sequential Circuit

(aka Clocked Sequential Circuit)

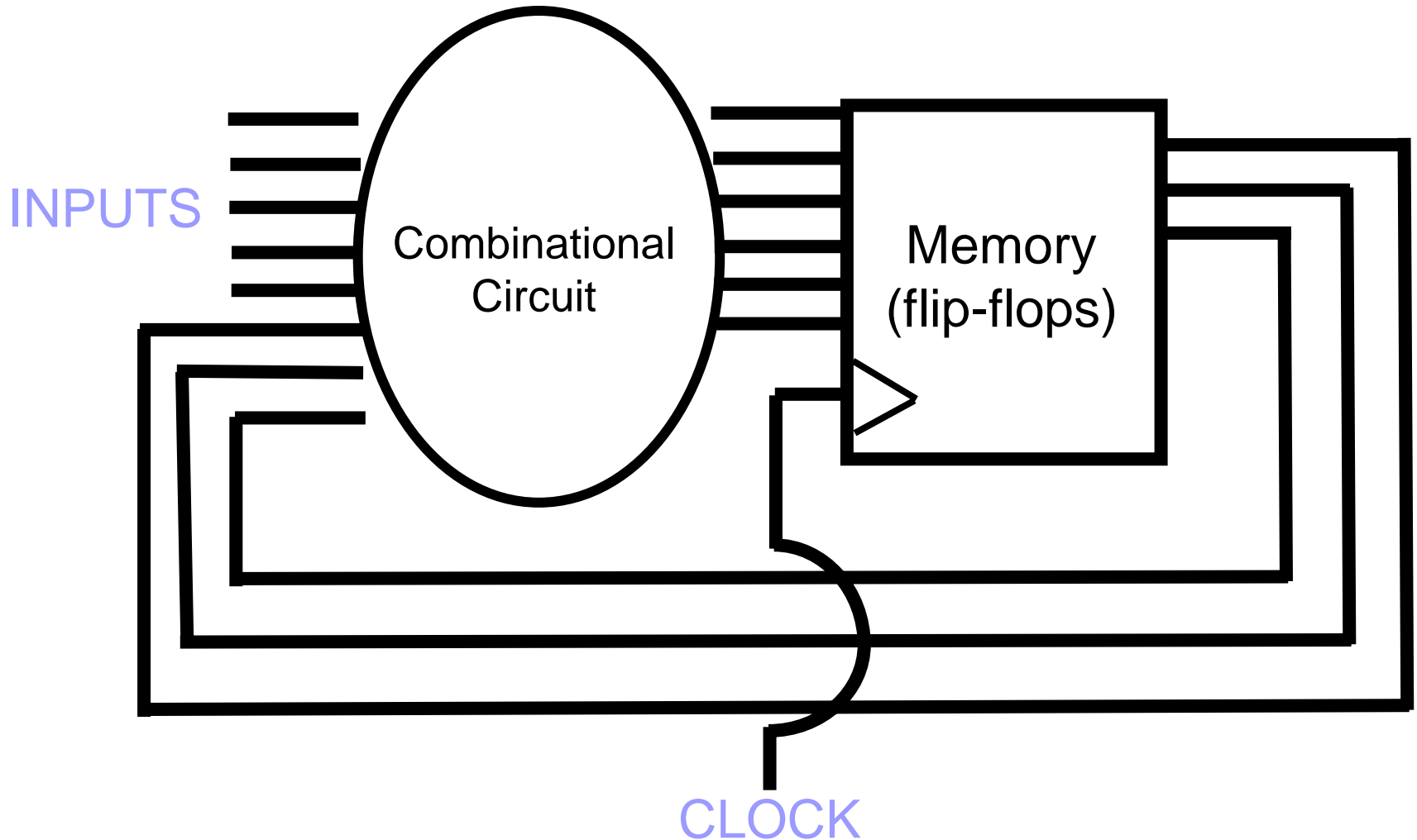

Shorthand

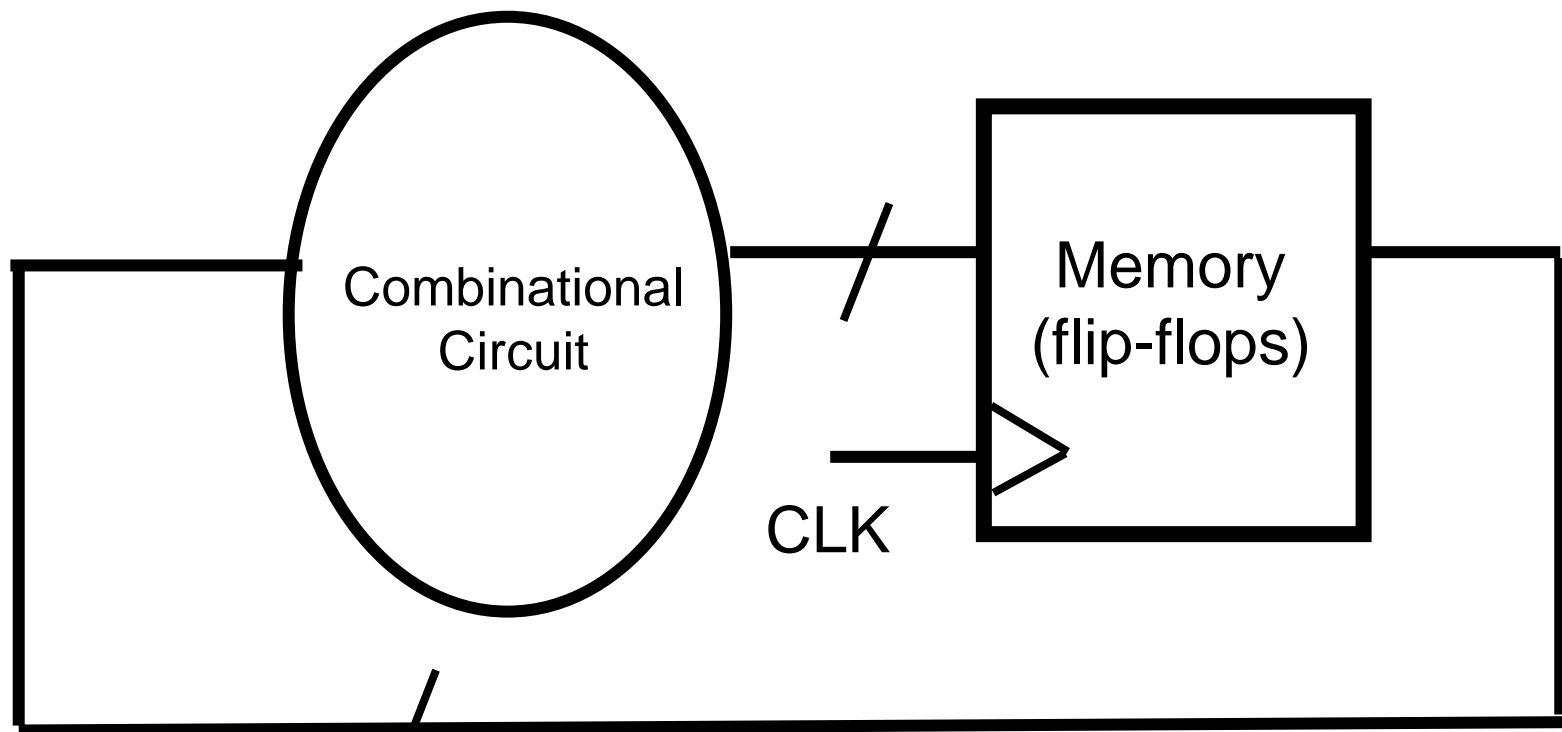

This stands for "lots of wires"


Clock Speeds



Heinrich Hertz
1857-94

1974	Intel 8080	2 MHz (Mega = Million)
1981	Original IBM PC	4.77 MHz
1993	Intel Pentium	66 MHz
2005	Pentium 4	3.4 GHz (Giga = Billion)

What limits clock speed?

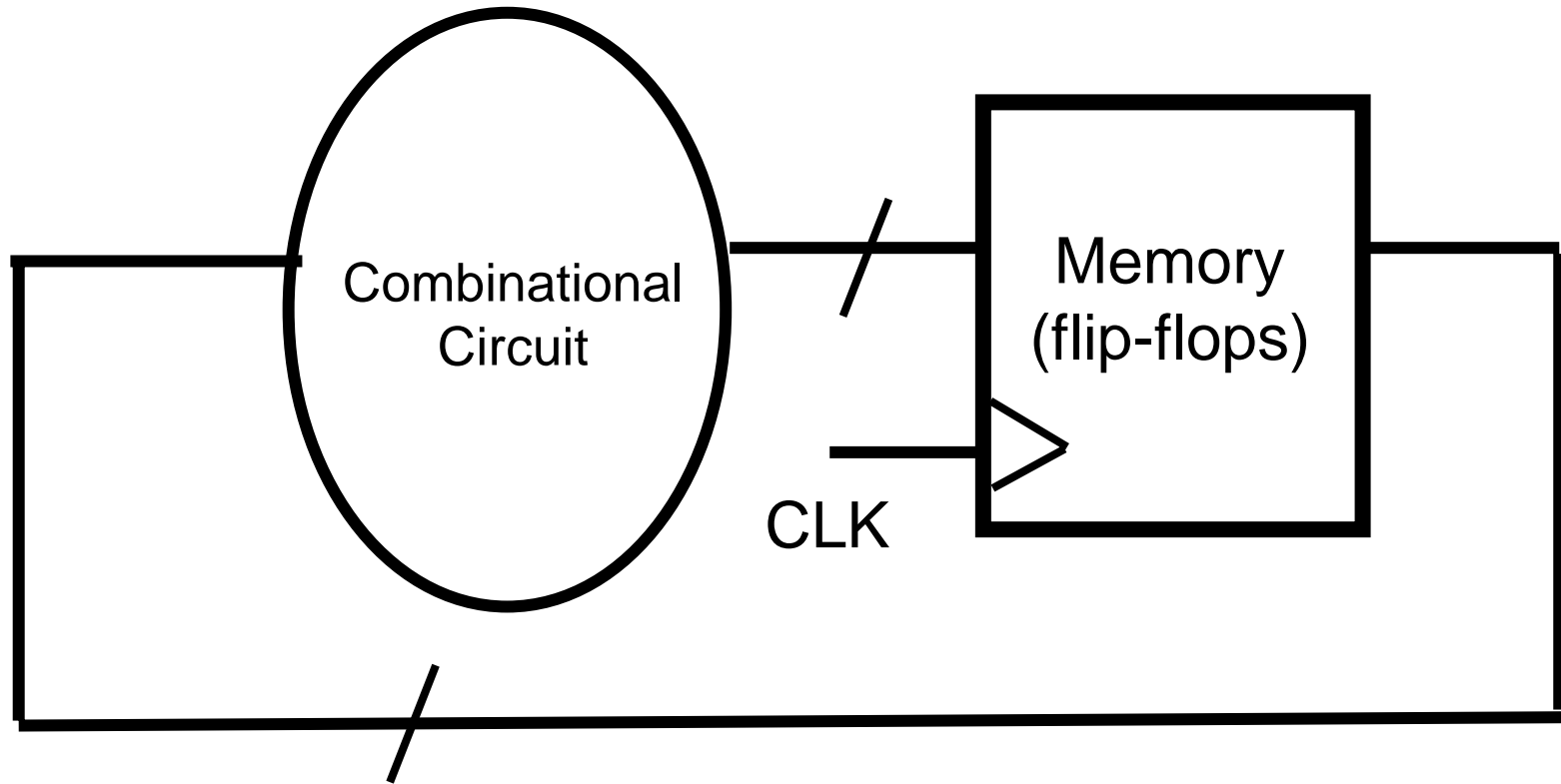

Delays in combinational logic (remember the adder)

During 1 clock cycle of Pentium 4, light travels: **4 inches**


Sequential Circuits (Recap.)

- Circuits with AND, OR and NOT gates.
- Cycles *are* allowed.
- Can exhibit “memory”.




Finite State Machines

State diagram for automatic door

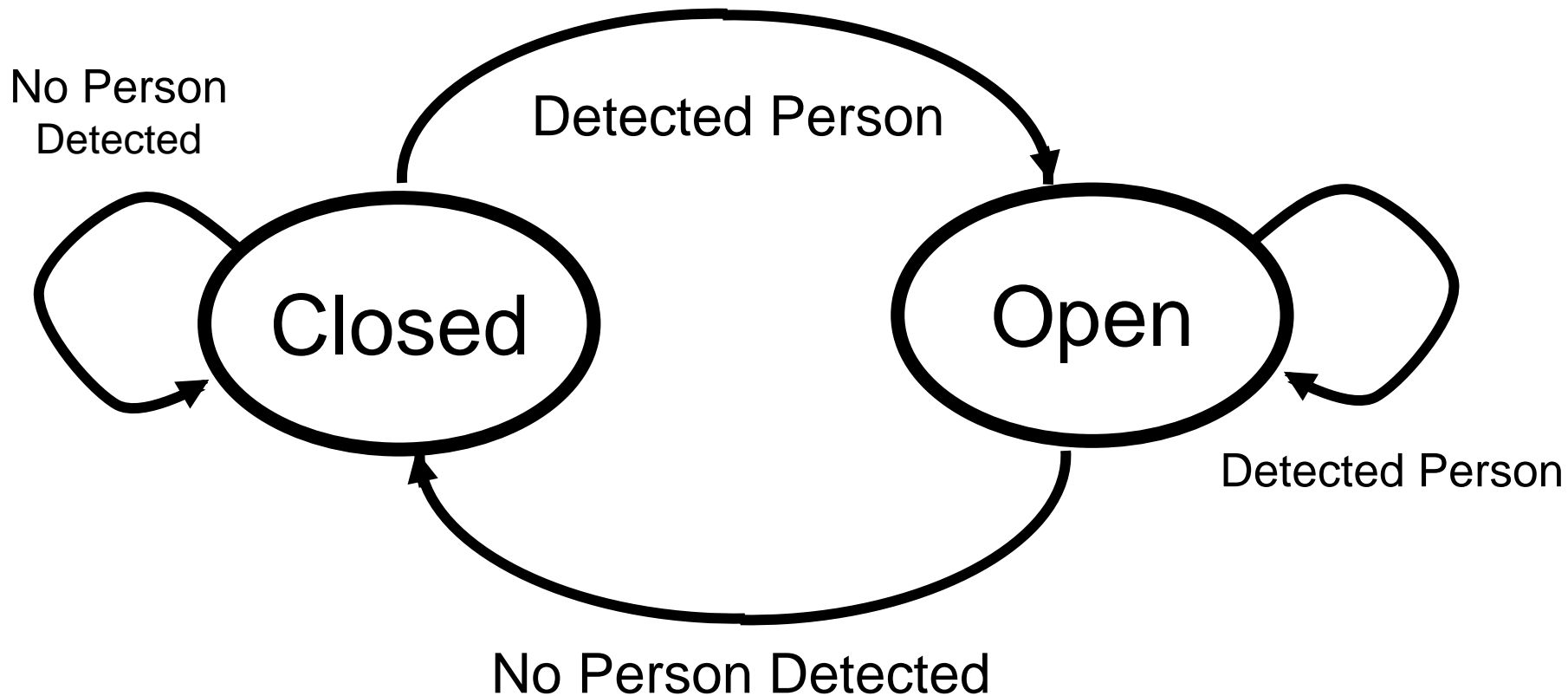

Implementing as synchronous circuit

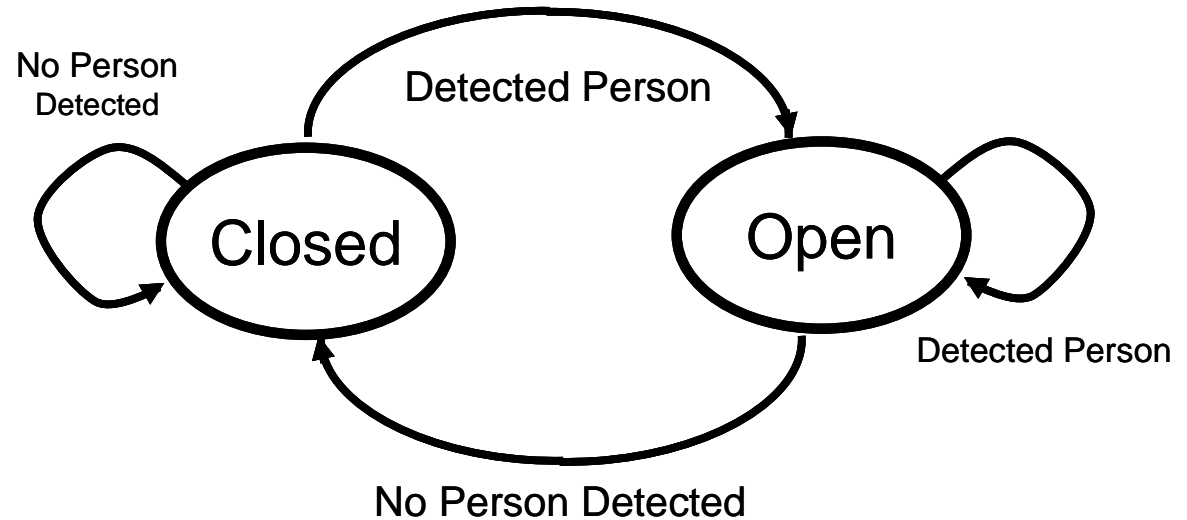

INPUT


0 = No Person Detected
1 = Person Detected

STATE

0 = Door Closed
1 = Open

Input	Present State	Next State
0	0	0
1	0	1
0	1	0
1	1	1

Implementation

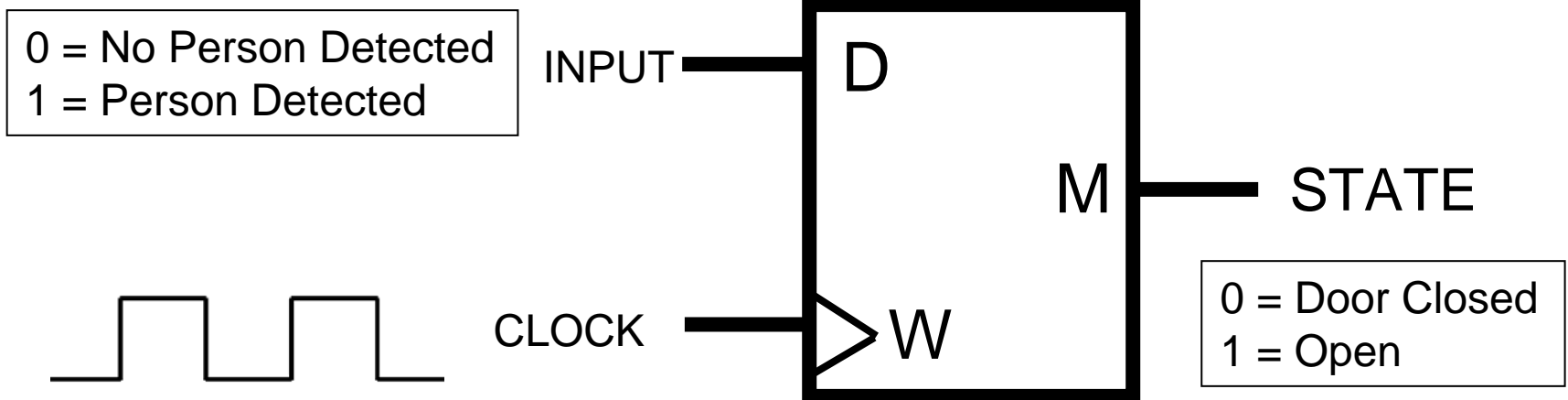

Other examples of FSMs

- Sisyphus




- Brook's Genghis (51 FSMs) (see p. 46 in our text)



- Human Soul a la Aquinas (see Handout)

Portion of Genghis AFSM Network

[Parker'94]

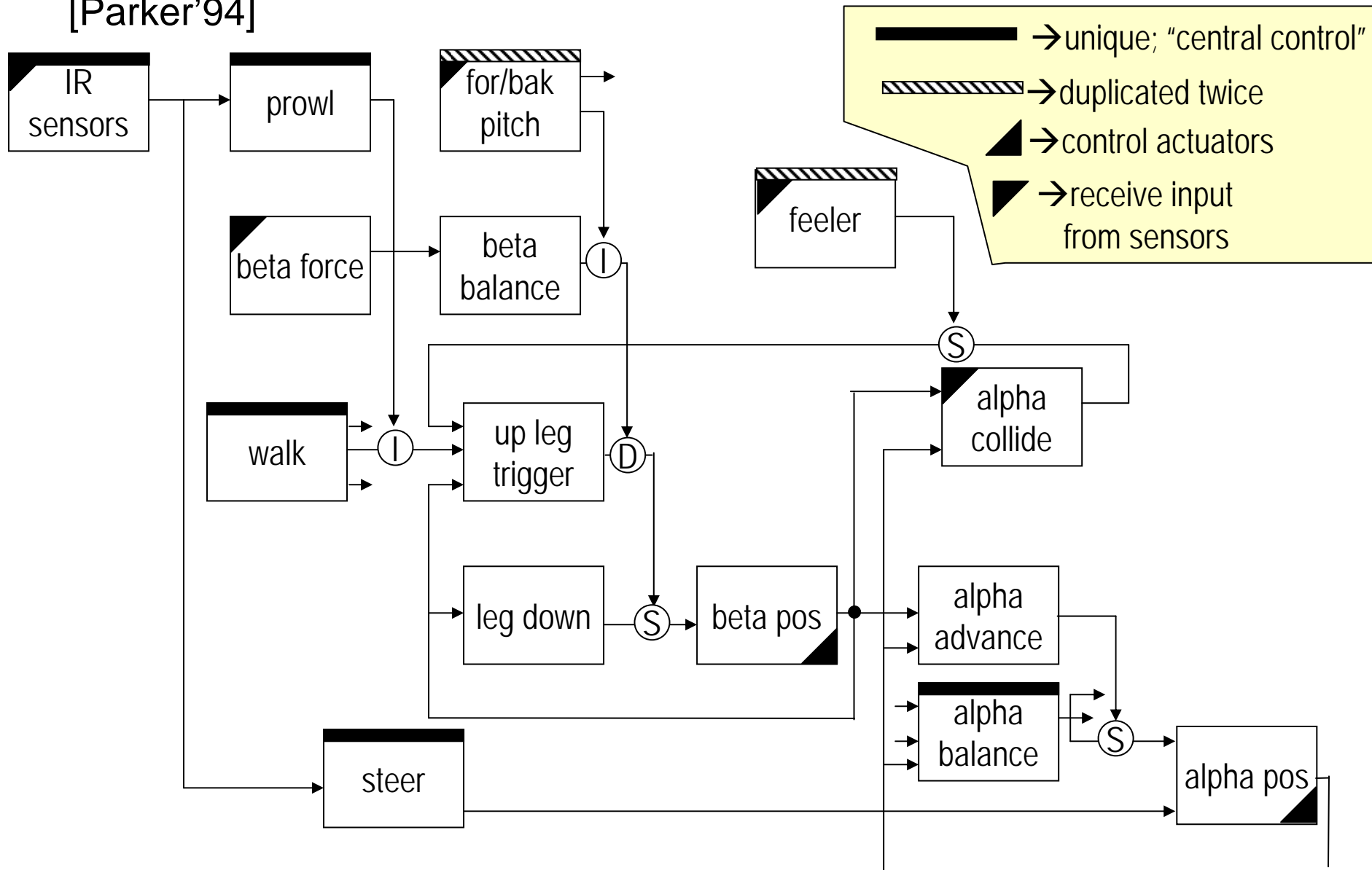



Next time...

- How computers execute programs.
- Discuss Boole/Clarke “proof” of the existence of God.