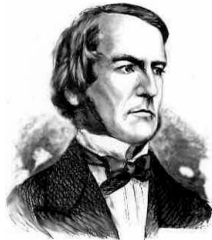


6. Combinational Circuits



George Boole (1815 - 1864)



Claude Shannon (1916 - 2001)

TOY lectures. von Neumann machine.



This lecture. Boolean circuits.

Digital Circuits

Q. What is a digital system?

A. Digital: signals are 0 or 1.

← analog: signals vary continuously

Q. Why digital systems?

A. Accurate, reliable, fast, cheap.

Basic abstractions.

- On, off.
- Wire: propagates on/off value.
- Switch: controls propagation of on/off values through wires.

Applications. Cell phone, iPod, antilock breaks, **microprocessors**, ...




Building Blocks

Wires

Wires.

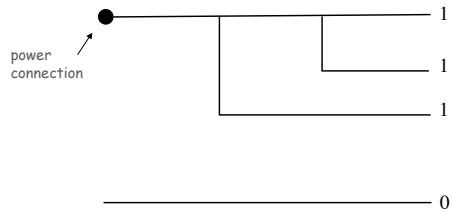
- On (1): connected to power.
- Off (0): not connected to power.
- If a wire is connected to a wire that is on, that wire is also on.
- Typical drawing convention: "flow" from top, left to bottom, right.



Logic Gates



$$NOT = x'$$

x	NOT
0	1
1	0

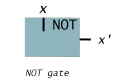


$$OR = x+y$$

x	y	OR
0	0	0
0	1	1
1	0	1
1	1	1

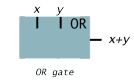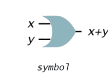

$$AND = xy$$

x	y	AND
0	0	0
0	1	0
1	0	0
1	1	1

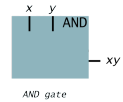


5

6

Logic Gates



$$NOT = x'$$

x	NOT
0	1
1	0

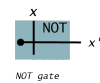



$$OR = x+y$$

x	y	OR
0	0	0
0	1	1
1	0	1
1	1	1

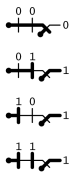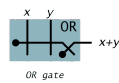

$$AND = xy$$

x	y	AND
0	0	0
0	1	0
1	0	0
1	1	1

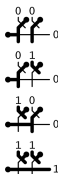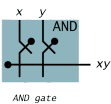







implementations with switches

7

Multiway Gates

Multiway gates.

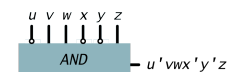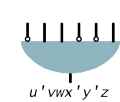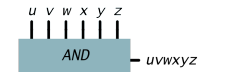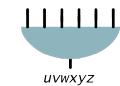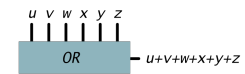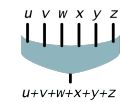- OR: 1 if any input is 1; 0 otherwise.
- AND: 1 if all inputs are 1; 0 otherwise.
- Generalized: negate some inputs.



symbol


gate

8

Multiway Gates

Multiway gates.

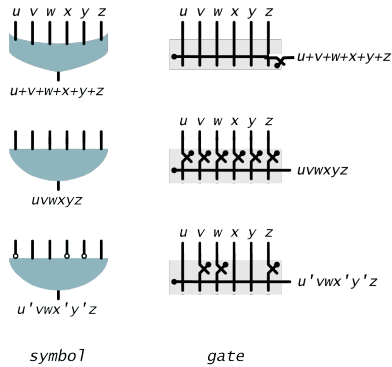- OR: 1 if any input is 1; 0 otherwise.
- AND: 1 if all inputs are 1; 0 otherwise.
- Generalized: negate some inputs.



9

Boolean Algebra

Boolean Algebra

History.

- Developed by Boole to solve mathematical logic problems (1847).
- Shannon master's thesis applied it to digital circuits (1937).


"possibly the most important, and also the most famous, master's thesis of the [20th] century" — Howard Gardner

Boolean algebra.

- Boolean variable: value is 0 or 1.
- Boolean function: function whose inputs and outputs are 0, 1.

Relationship to circuits.

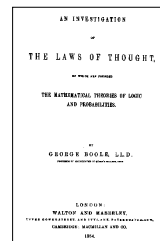- Boolean variable: signal.
- Boolean function: circuit.



11


Truth Table

Truth table.

- Systematic method to describe Boolean function.
- One row for each possible input combination.
- n inputs $\Rightarrow 2^n$ rows.

x	y	xy
0	0	0
0	1	0
1	0	0
1	1	1

AND truth table

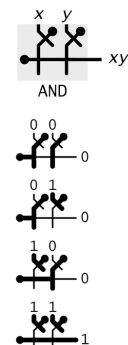

10

13

Truth Table for Functions of 2 Variables

Truth table.

- 16 Boolean functions of 2 variables.

← every 4-bit value represents one

x	y	ZERO	AND		x	y	XOR	OR
0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	1	1	1
1	0	0	0	1	1	0	0	1
1	1	0	1	0	1	0	1	1

truth table for all Boolean functions of 2 variables

x	y	NOR	EQ	y'		x'		NAND	ONE
0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1

truth table for all Boolean functions of 2 variables

Truth Table for Functions of 3 Variables

Truth table.

- 16 Boolean functions of 2 variables.
- 256 Boolean functions of 3 variables.
- 2^{2^n} Boolean functions of n variables!

← every 4-bit value represents one

← every 8-bit value represents one

← every 2^n -bit value represents one

x	y	z	AND	OR	MAJ	ODD
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	0	1	0	1
0	1	1	0	1	1	0
1	0	0	0	1	0	1
1	0	1	0	1	1	0
1	1	0	0	1	1	0
1	1	1	1	1	1	1

some functions of 3 variables

14

15

Universality of AND, OR, NOT

Fact. Any Boolean function can be expressed using AND, OR, NOT.

- {AND, OR, NOT} are **universal**.
- Ex: $XOR(x, y) = xy' + x'y$.

notation	meaning
x'	NOT x
$x y$	x AND y
$x + y$	x OR y

Expressing XOR Using AND, OR, NOT

x	y	x'	y'	x'y	xy'	x'y + xy'	x XOR y
0	0	1	1	0	0	0	0
0	1	1	0	1	0	1	1
1	0	0	1	0	1	1	1
1	1	0	0	0	0	0	0

Exercise. Show {AND, NOT}, {OR, NOT}, {NAND} are universal.

Hint. DeMorgan's law: $(x'y)' = x + y$.

16

Sum-of-Products

Sum-of-products. Systematic procedure for representing a Boolean function using AND, OR, NOT.

- Form AND term for each 1 in Boolean function.
- OR terms together.

proves that {AND, OR, NOT} are universal

x	y	z	MAJ	x'y'z	xy'z'	xyz'	xyz	x'y'z + xy'z' + xyz' + xyz
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0
0	1	1	1	1	0	0	0	1
1	0	0	0	0	0	0	0	0
1	0	1	1	0	1	0	0	1
1	1	0	1	0	0	1	0	1
1	1	1	1	0	0	0	1	1

expressing MAJ using sum-of-products

17

Translate Boolean Formula to Boolean Circuit

Sum-of-products. XOR.

$$XOR = x'y + xy'$$

x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0

Truth table



Circuit


Translate Boolean Formula to Boolean Circuit

Sum-of-products. XOR.


$$XOR = x'y + xy'$$

x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0

Truth table

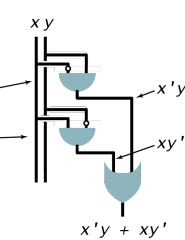

Abstract circuit

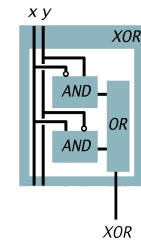

Circuit


Translate Boolean Formula to Boolean Circuit

Sum-of-products. XOR.


$$XOR = x'y + xy'$$

x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0

Truth table

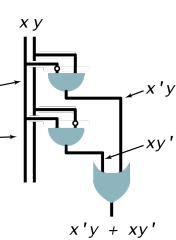

Abstract circuit

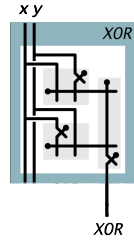

Circuit

Translate Boolean Formula to Boolean Circuit

Sum-of-products. Majority.

$$MAJ = x'yz + xy'z + xyz' + xyz$$

x	y	z	MAJ
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Truth table




Circuit

Translate Boolean Formula to Boolean Circuit

Sum-of-products. Majority.

$$MAJ = x'yz + xy'z + xyz' + xyz$$

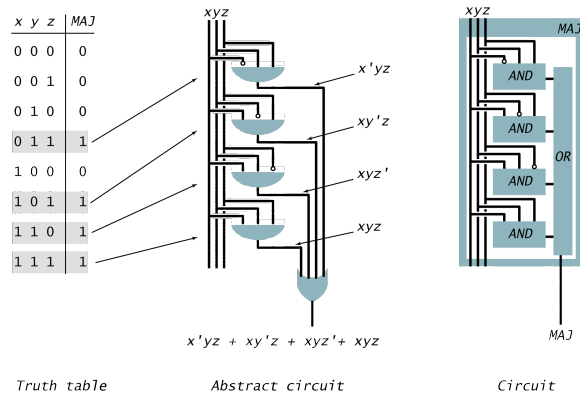


22

Translate Boolean Formula to Boolean Circuit

Sum-of-products. Majority.

$$MAJ = x'yz + xy'z + xyz' + xyz$$

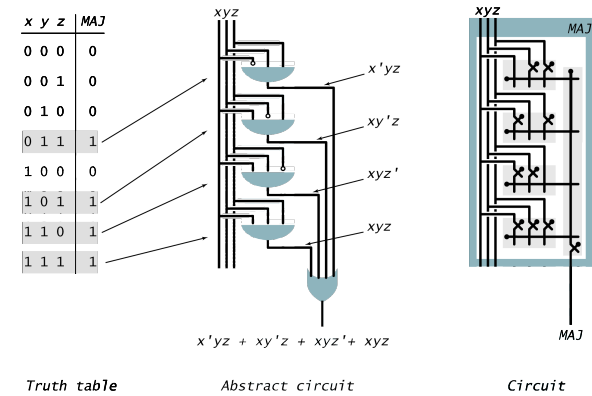


23

Simplification Using Boolean Algebra

Many possible circuits for each Boolean function.

- Sum-of-products not necessarily optimal in:
 - number of switches (space)
 - depth of circuit (time)

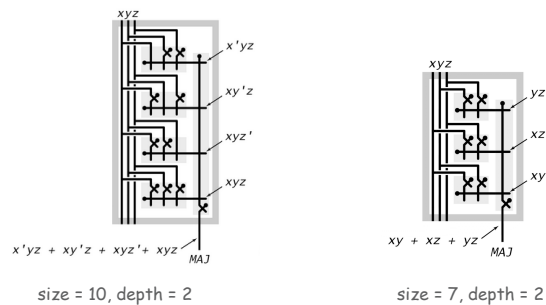Ex. $MAJ(x, y, z) = x'yz + xy'z + xyz' + xyz = xy + yz + xz$.



24

Expressing a Boolean Function Using AND, OR, NOT

Ingredients.

- AND gates.
- OR gates.
- NOT gates.
- Wire.

Instructions.

- Step 1: represent input and output signals with Boolean variables.
- Step 2: construct truth table to carry out computation.
- Step 3: derive (simplified) Boolean expression using sum-of products.
- Step 4: transform Boolean expression into circuit.

25

ODD Parity Circuit

$ODD(x, y, z)$.

- 1 if odd number of inputs are 1.
- 0 otherwise.

x	y	z	ODD	$x'y'z$	$x'y'z'$	$xy'z'$	xyz	$x'y'z + x'y'z' + xy'z' + xyz$
0	0	0	0	0	0	0	0	0
0	0	1	1	1	0	0	0	1
0	1	0	1	0	1	0	0	1
0	1	1	0	0	0	0	0	0
1	0	0	1	0	0	1	0	1
1	0	1	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0
1	1	1	1	0	0	0	1	1

Expressing ODD using sum-of-products

26


ODD Parity Circuit

$ODD(x, y, z)$.

- 1 if odd number of inputs are 1.
- 0 otherwise.

$$MAJ = x'y'z + xy'z + xyz' + xyz$$

$$ODD = x'y'z + x'y'z' + xy'z' + xyz$$

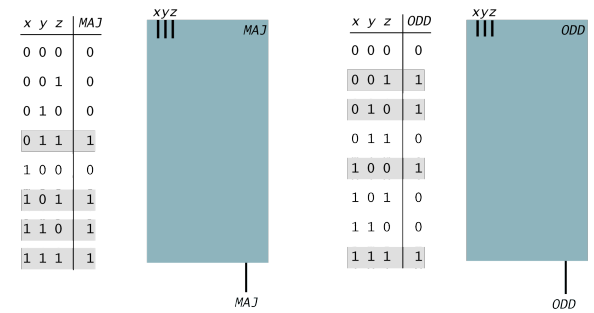

27


ODD Parity Circuit

$ODD(x, y, z)$.

- 1 if odd number of inputs are 1.
- 0 otherwise.

$$MAJ = x'y'z + xy'z + xyz' + xyz$$

$$ODD = x'y'z + x'y'z' + xy'z' + xyz$$

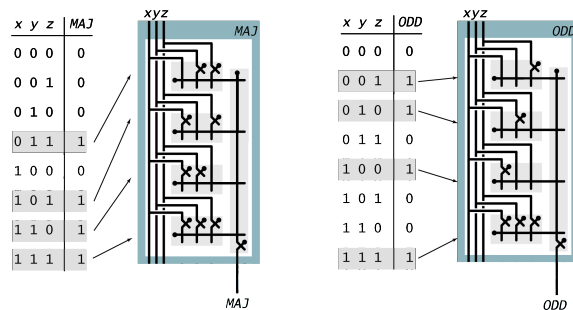

28

Adder Circuit

29


Let's Make an Adder Circuit

Goal. $x + y = z$ for 4-bit integers.

- We build 4-bit adder: 9 inputs, 4 outputs.
- Same idea scales to 128-bit adder.
- Key computer component.

	1	1	1	0
	2	4	8	7
+	3	5	7	9
	6	0	6	6

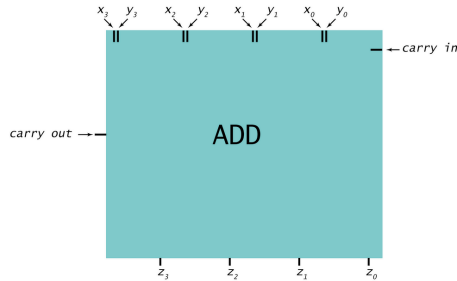Step 1. Represent input and output in binary.



	1	1	0	0
	0	0	1	0
+	0	1	1	1
	1	0	0	1

	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
	z_3	z_2	z_1	z_0

Let's Make an Adder Circuit

Goal. $x + y = z$ for 4-bit integers.

Step 2. [first attempt]

- Build truth table.

	c_{out}			c_{in}
	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
	z_3	z_2	z_1	z_0

4-bit adder truth table

c_0	x_3	x_2	x_1	x_0	y_3	y_2	y_1	y_0	z_3	z_2	z_1	z_0
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	0	0	0	1	1	0	0	1	1
0	0	0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	0	1	0	0	0
0	0	0	0	1	0	0	0	0	1	1	0	0
0	0	0	1	0	0	0	0	0	1	1	1	0
0	0	1	0	0	0	0	0	0	1	1	1	1
0	1	0	0	0	0	0	0	0	1	1	1	1
1	1	1	1	1	1	1	1	1	1	1	1	1

2⁸⁺¹ = 512 rows!

Q. Why is this a bad idea?

A. 128-bit adder: 2²⁵⁶⁺¹ rows >> # electrons in universe!

Let's Make an Adder Circuit

Goal. $x + y = z$ for 4-bit integers.

Step 2. [do one bit at a time]

- Build truth table for carry bit.
- Build truth table for summand bit.

	c_{out}	c_3	c_2	c_1	$c_0 = 0$
	x_3	x_2	x_1	x_0	
+	y_3	y_2	y_1	y_0	
	z_3	z_2	z_1	z_0	

carry bit

x_i	y_i	c_i	c_{i+1}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

summand bit

x_i	y_i	c_i	z_i
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Let's Make an Adder Circuit

Goal. $x + y = z$ for 4-bit integers.

Step 3.

- Derive (simplified) Boolean expression.

	c_{out}	c_3	c_2	c_1	$c_0 = 0$
	x_3	x_2	x_1	x_0	
+	y_3	y_2	y_1	y_0	
	z_3	z_2	z_1	z_0	

carry bit

x_i	y_i	c_i	c_{i+1}	MAJ
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

summand bit


x_i	y_i	c_i	z_i	ODD
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Let's Make an Adder Circuit

Goal. $x + y = z$ for 4-bit integers.


Step 4.

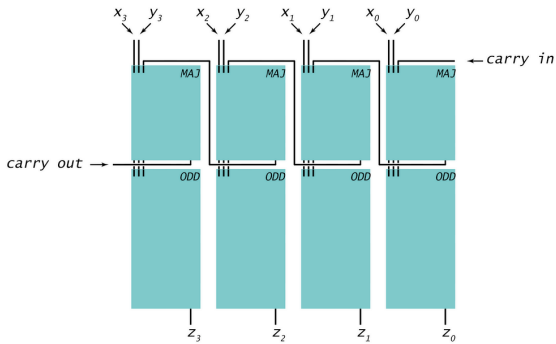- Transform Boolean expression into circuit.
- Chain together 1-bit adders.




34

Adder: Interface

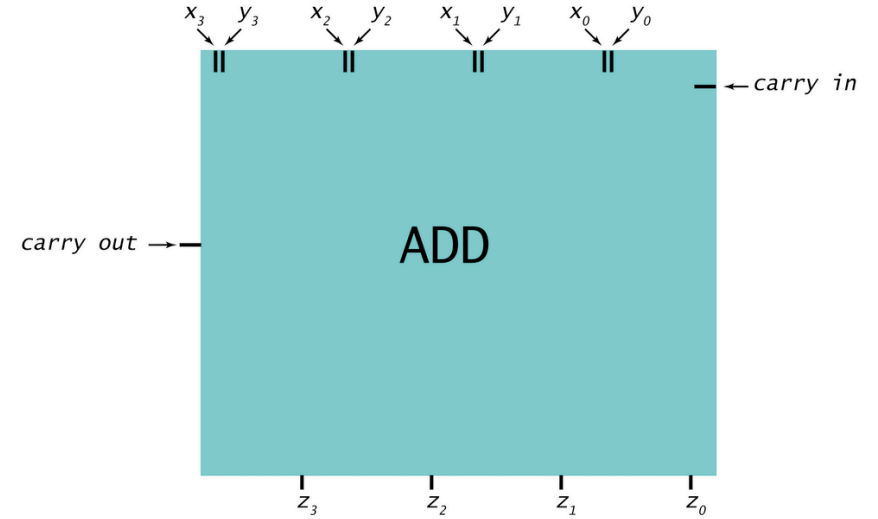


35

Adder: Component Level View

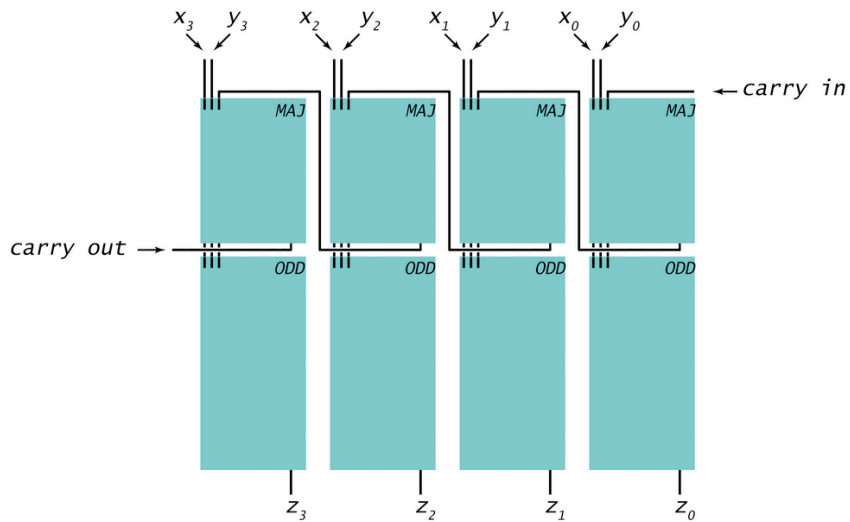

36

Adder: Switch Level View

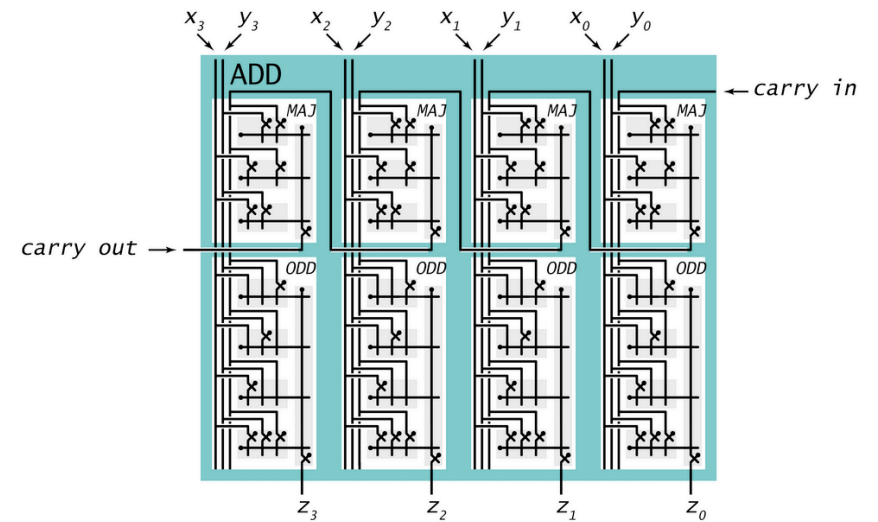

37