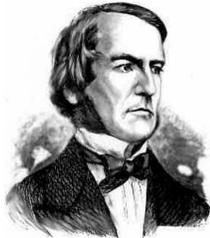


6. Combinational Circuits



George Boole (1815 - 1864)



Claude Shannon (1916 - 2001)

TOY lectures. von Neumann machine.



This lecture. Boolean circuits.

Ahead. Putting it all together and building a TOY machine.

Digital Circuits

What is a digital system?

- Digital: signals are 0 or 1.
- Analog: signals vary continuously.

Why digital systems?

- Accuracy and reliability.
- Staggeringly fast and cheap.

Basic abstractions.

- On, off.
- Wire: propagates on/off value.
- Switch: controls propagation of on/off values through wires.


Digital circuits and you.

- Computer microprocessors.
- Antilock brakes, cell phones, iPods, etc.

Wires

Wires.

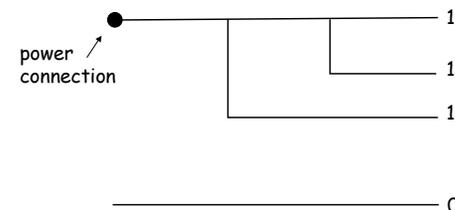
- On (1): connected to power.
- Off (0): not connected to power.
- If a wire is connected to a wire that is on, that wire is also on.
- Typical drawing convention: "flow" from top, left to bottom, right.



Controlled Switch


Controlled switch. [relay implementation]

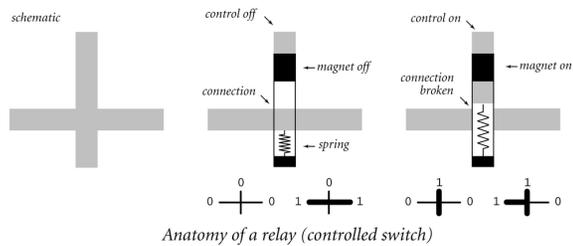- 3 connections: input, output, control.
- Magnetic force pulls on a contact that cuts electrical flow.
- Control wire affects output wire, but output does not affect control; establishes forward flow of information over time.



5

Circuit Anatomy

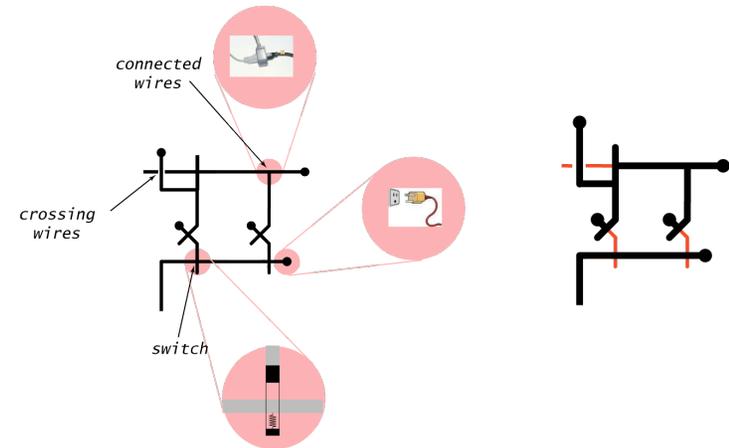


6

Layers of Abstraction

Layers of abstraction.

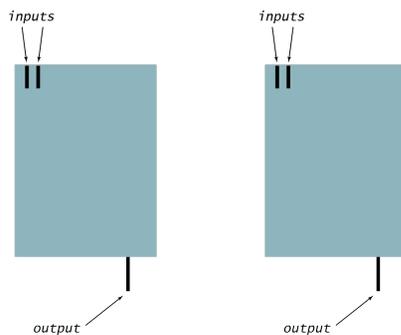- Build a circuit from wires and switches. [implementation]
- Define a circuit by its inputs and outputs. [interface]
- To control complexity, encapsulate circuits. [ADT]




7

Layers of Abstraction

Layers of abstraction.

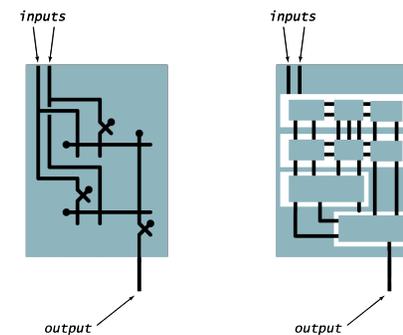
- Build a circuit from wires and switches. [implementation]
- Define a circuit by its inputs and outputs. [interface]
- To control complexity, encapsulate circuits. [ADT]




8

Logic Gates: Fundamental Building Blocks


$$NOT = x'$$

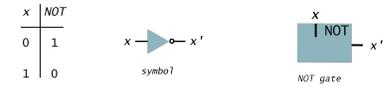

$$OR = x+y$$

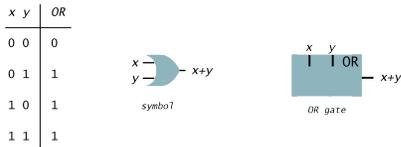

$$AND = xy$$

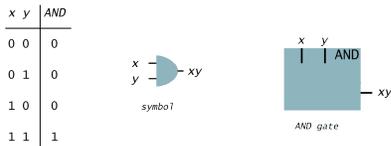


Logic Gates: Fundamental Building Blocks


$$NOT = x'$$



$$OR = x+y$$

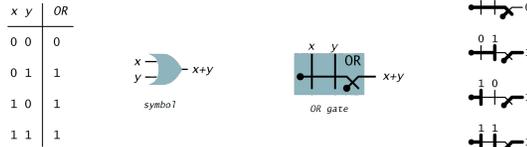

$$AND = xy$$

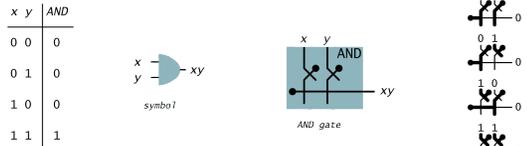

implementations with switches


9

10

Multiway Gates

Multiway gates.

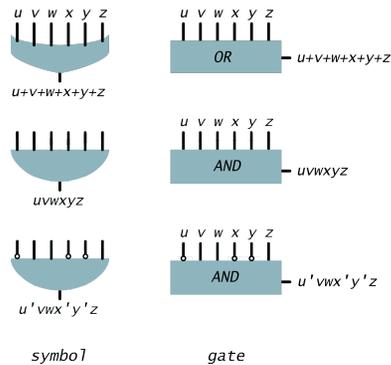
- OR: 1 if any input is 1; 0 otherwise.
- AND: 1 if all inputs are 1; 0 otherwise.
- Generalized: negate some inputs.



Multiway Gates

Multiway gates.

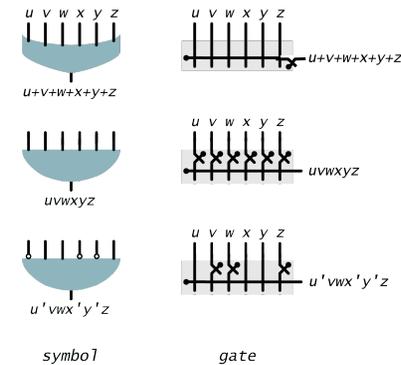- OR: 1 if any input is 1; 0 otherwise.
- AND: 1 if all inputs are 1; 0 otherwise.
- Generalized: negate some inputs.



11

12

Boolean Algebra

History.

- Developed by Boole to solve mathematical logic problems (1847).
- Shannon master's thesis applied it to digital circuits (1937).


"possibly the most important, and also the most famous, master's thesis of the [20th] century" --Howard Gardner

Basics.

- Boolean variable: value is 0 or 1.
- Boolean function: function whose inputs and outputs are 0, 1.

Relationship to circuits.

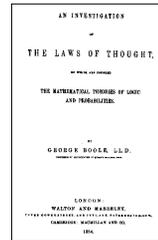- Boolean variables: signals.
- Boolean functions: circuits.



Boole Orders Lunch



Copyright 2004, Sidney Harris, <http://www.sciencecartoonsplus.com/>

13

14


Truth Table

Truth table.

- Systematic method to describe Boolean function.
- One row for each possible input combination.
- N inputs $\Rightarrow 2^N$ rows.

x	y	x y
0	0	0
0	1	0
1	0	0
1	1	1

AND Truth Table

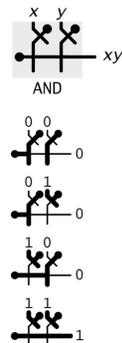

Truth Table for Functions of 2 Variables

Truth table.

- 16 Boolean functions of 2 variables.

← every 4-bit value represents one

x	y	ZERO	AND	x	y	XOR	OR
0	0	0	0	0	0	0	0
0	1	0	0	0	1	1	1
1	0	0	0	1	0	0	1
1	1	0	1	0	1	0	1

Truth table for all Boolean functions of 2 variables

x	y	NOR	EQ	y'	x'	NAND	ONE
0	0	1	1	1	1	1	1
0	1	0	0	0	1	1	1
1	0	0	0	1	0	0	1
1	1	0	1	0	0	1	0

Truth table for all Boolean functions of 2 variables

15

16

Truth Table for Functions of 3 Variables

Truth table.

- 16 Boolean functions of 2 variables. ← every 4-bit value represents one
- 256 Boolean functions of 3 variables. ← every 8-bit value represents one
- 2^{2^n} Boolean functions of n variables! ← every 2^n -bit value represents one

x	y	z	AND	OR	MAJ	ODD
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	0	1	0	1
0	1	1	0	1	1	0
1	0	0	0	1	0	1
1	0	1	0	1	1	0
1	1	0	0	1	1	0
1	1	1	1	1	1	1

Some Functions of 3 Variables

Universality of AND, OR, NOT

Fact. Any Boolean function can be expressed using AND, OR, NOT.

- {AND, OR, NOT} are **universal**.
- Ex: $XOR(x,y) = xy' + x'y$.

Notation	Meaning
x'	NOT x
$x y$	x AND y
$x + y$	x OR y

Expressing XOR Using AND, OR, NOT

x	y	x'	y'	$x'y$	xy'	$x'y + xy'$	x XOR y
0	0	1	1	0	0	0	0
0	1	1	0	1	0	1	1
1	0	0	1	0	1	1	1
1	1	0	0	0	0	0	0

Exercise. Show {AND, NOT}, {OR, NOT}, {NAND}, {NOR} are universal.

Hint. DeMorgan's law: $(x'y')' = x + y$.

17

18

Sum-of-Products

Sum-of-products. Systematic procedure for representing a Boolean function using AND, OR, NOT.

- Form AND term for each 1 in Boolean function.
 - OR terms together.
- proves that {AND, OR, NOT} are universal

x	y	z	MAJ	$x'yz$	$xy'z$	xyz'	xyz	$x'yz + xy'z + xyz' + xyz$
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0
0	1	1	1	1	1	0	0	1
1	0	0	0	0	0	0	0	0
1	0	1	1	0	1	0	0	1
1	1	0	1	0	0	1	0	1
1	1	1	1	0	0	0	1	1

expressing MAJ using sum-of-products

19

Translate Boolean Formula to Boolean Circuit

Sum-of-products. XOR.

$$XOR = x'y + xy'$$

x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0

Truth table



Circuit

20


Translate Boolean Formula to Boolean Circuit

Sum-of-products. XOR.


$$XOR = x'y + xy'$$

x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0

Truth table

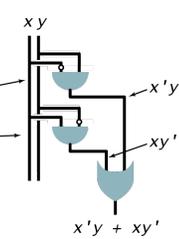

Abstract circuit

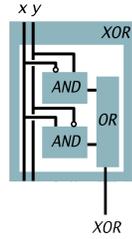

Circuit


Translate Boolean Formula to Boolean Circuit

Sum-of-products. XOR.


$$XOR = x'y + xy'$$

x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0

Truth table

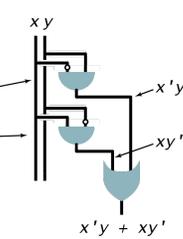

Abstract circuit

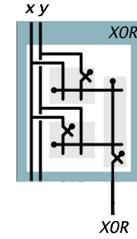

Circuit

Translate Boolean Formula to Boolean Circuit

Sum-of-products. Majority.

$$MAJ = x'yz + xy'z + xyz' + xyz$$

x	y	z	MAJ
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Truth table



Circuit


Translate Boolean Formula to Boolean Circuit

Sum-of-products. Majority.


$$MAJ = x'yz + xy'z + xyz' + xyz$$

x	y	z	MAJ
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Truth table

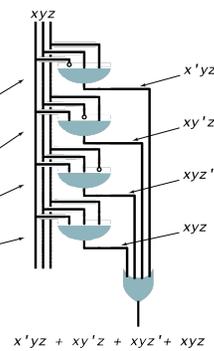

Abstract circuit

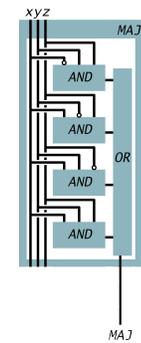


Circuit

Translate Boolean Formula to Boolean Circuit

Sum-of-products. Majority.

$$MAJ = x'yz + xy'z + xyz' + xyz$$

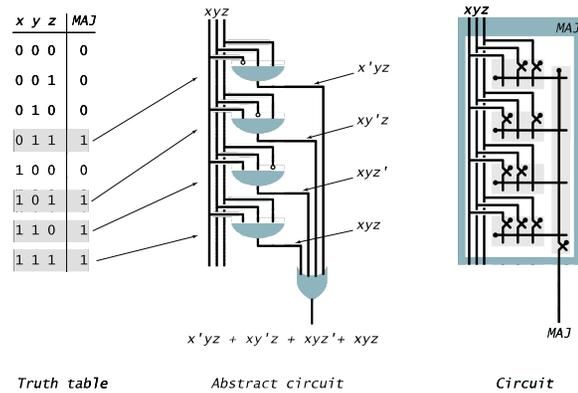


Simplification Using Boolean Algebra

Many possible circuits for each Boolean function.

- Sum-of-products not necessarily optimal in:
 - number of switches (space)
 - depth of circuit (time)

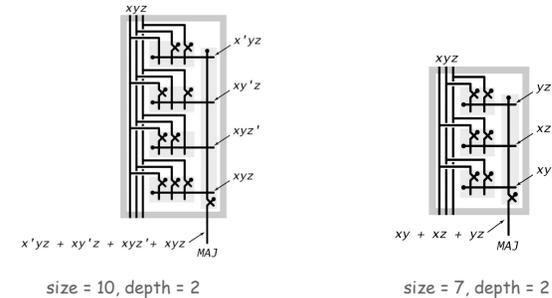Ex. $MAJ(x, y, z) = x'yz + xy'z + xyz' + xyz = xy + yz + xz$



25

26

Expressing a Boolean Function Using AND, OR, NOT

Ingredients.

- AND gates.
- OR gates.
- NOT gates.
- Wire.

Instructions.

- Step 1: represent input and output signals with Boolean variables.
- Step 2: construct truth table to carry out computation.
- Step 3: derive (simplified) Boolean expression using sum-of products.
- Step 4: transform Boolean expression into circuit.

ODD Parity Circuit

ODD(x, y, z).

- 1 if odd number of inputs are 1.
- 0 otherwise.

x	y	z	ODD	$x'y'z$	$x'yz'$	$xy'z'$	xyz	$x'y'z + x'yz' + xy'z' + xyz$
0	0	0	0	0	0	0	0	0
0	0	1	1	1	0	0	0	1
0	1	0	1	0	1	0	0	1
0	1	1	0	0	0	0	0	0
1	0	0	1	0	0	1	0	1
1	0	1	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0
1	1	1	1	0	0	0	1	1

Expressing ODD using sum-of-products

27

28

ODD Parity Circuit

ODD(x, y, z).

- 1 if odd number of inputs are 1.
- 0 otherwise.

$$MAJ = x'yz + xy'z + xyz' + xyz$$

x	y	z	MAJ
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



$$ODD = x'y'z + x'yz' + xy'z' + xyz$$

x	y	z	ODD
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1




29

ODD Parity Circuit


ODD(x, y, z).

- 1 if odd number of inputs are 1.
- 0 otherwise.

$$MAJ = x'yz + xy'z + xyz' + xyz$$

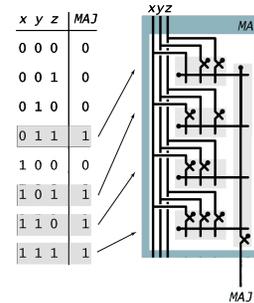

$$ODD = x'y'z + x'yz' + xy'z' + xyz$$

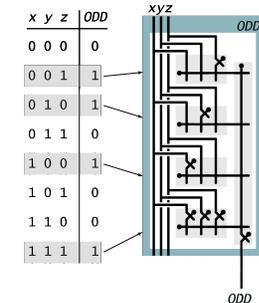

30


Let's Make an Adder Circuit

Goal. $x + y = z$ for 4-bit integers.

- We build 4-bit adder: 9 inputs, 4 outputs.
- Same idea scales to 128-bit adder.
- Key computer component.

1	1	1	0	
2	4	8	7	
+	3	5	7	9
<hr/>				
6	0	6	6	

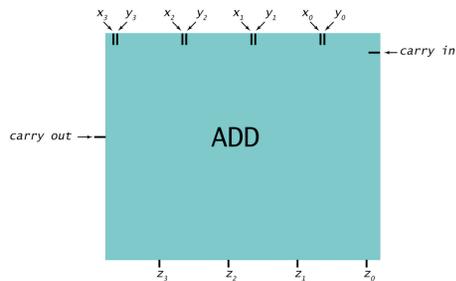Step 1. Represent input and output in binary.



1	1	0	0
0	0	1	0
+	0	1	1
<hr/>			
1	0	0	1

	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
<hr/>				
	z_3	z_2	z_1	z_0

31

Let's Make an Adder Circuit

Goal. $x + y = z$ for 4-bit integers.

Step 2. [first attempt]

- Build truth table.

c_{out}	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
<hr/>				
	z_3	z_2	z_1	z_0

4-Bit Adder Truth Table

c_0	x_3	x_2	x_1	x_0	y_3	y_2	y_1	y_0	z_3	z_2	z_1	z_0
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	0	0	0	1	1	0	0	1	1
0	0	0	0	0	0	1	0	0	0	1	0	0
.
1	1	1	1	1	1	1	1	1	1	1	1	1

$2^8 = 512$ rows!

Q. Why is this a bad idea?

A. 128-bit adder: 2^{256+1} rows \gg # electrons in universe!

32

Let's Make an Adder Circuit

Goal. $x + y = z$ for 4-bit integers.

Step 2. [do one bit at a time]

- Build truth table for carry bit.
- Build truth table for summand bit.

	c_{out}	c_3	c_2	c_1	$c_0 = 0$
	x_3	x_2	x_1	x_0	
+	y_3	y_2	y_1	y_0	
	z_3	z_2	z_1	z_0	

Carry Bit

x_i	y_i	c_i	c_{i+1}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Summand Bit

x_i	y_i	c_i	z_i
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Let's Make an Adder Circuit

Goal. $x + y = z$ for 4-bit integers.

Step 3.

- Derive (simplified) Boolean expression.

	c_{out}	c_3	c_2	c_1	$c_0 = 0$
	x_3	x_2	x_1	x_0	
+	y_3	y_2	y_1	y_0	
	z_3	z_2	z_1	z_0	

Carry Bit

x_i	y_i	c_i	c_{i+1}	MAJ
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Summand Bit


x_i	y_i	c_i	z_i	ODD
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Let's Make an Adder Circuit


Goal. $x + y = z$ for 4-bit integers.

Step 4.

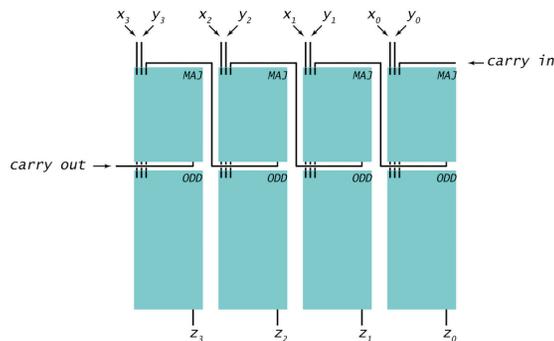
- Transform Boolean expression into circuit.
- Chain together 1-bit adders.



Adder: Interface

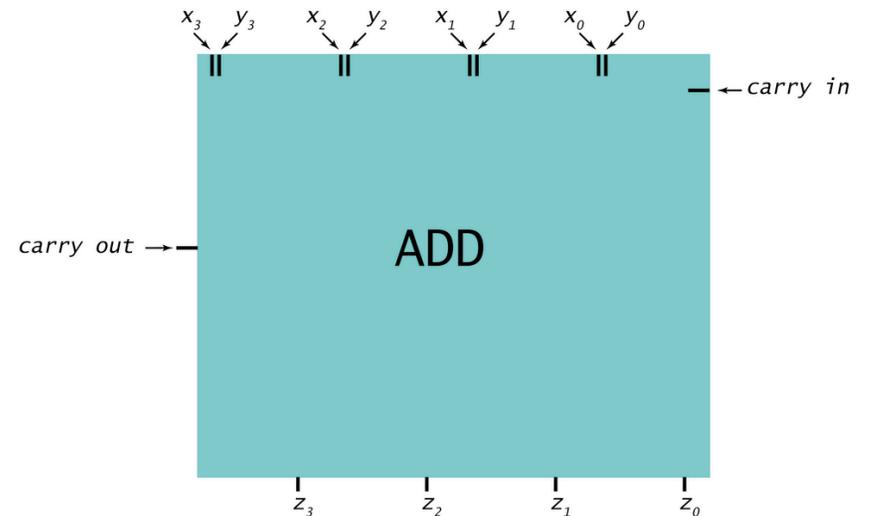


Adder: Component Level View

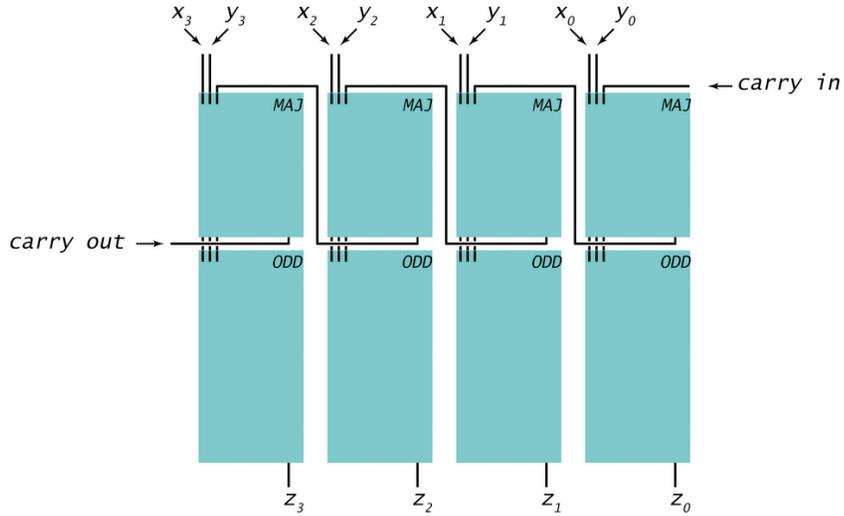


37

Adder: Switch Level View

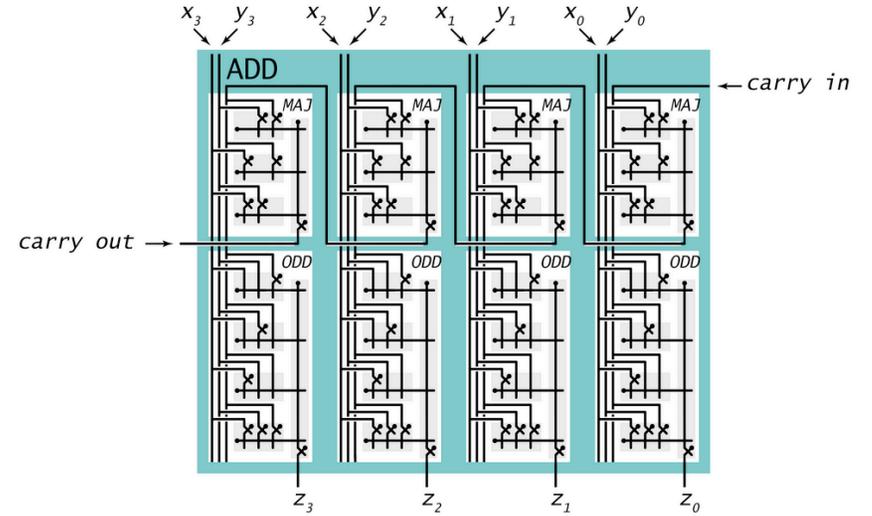

38

Shifter

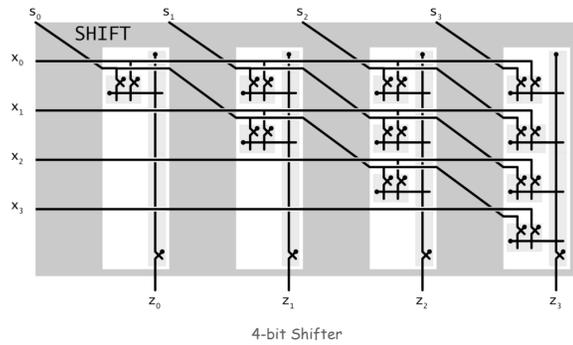


4-bit Shifter

39

Decoder

Decoder. [n-bit]

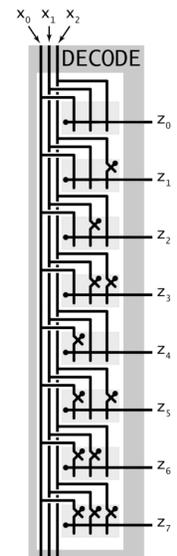- n address inputs, 2^n data outputs.
- Addressed output bit is 1; others are 0.




3-bit Decoder

40

2-Bit Decoder Controlling 4-Bit Shifter

Ex. Put in a binary amount to shift.

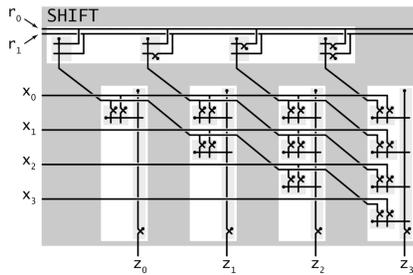


Right-shifter with decoder

1 Hot OR

1 hot OR.

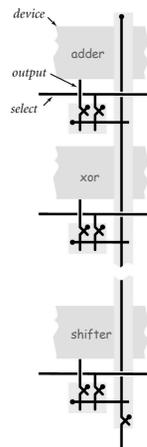- All devices compute their answer; we pick one.
- Exactly one select line is on.
- Implies exactly one output line is relevant.



Output select with one-hot OR

41

Arithmetic Logic Unit

Arithmetic logic unit (ALU). Computes all operations in parallel.

- Add and subtract.
- Xor.
- And.
- Shift left or right.

Q. How to select desired answer?

42


ALU

Arithmetic logic unit.

- Add and subtract.
- Xor.
- And.
- Shift left or right.

Arithmetic logic unit.

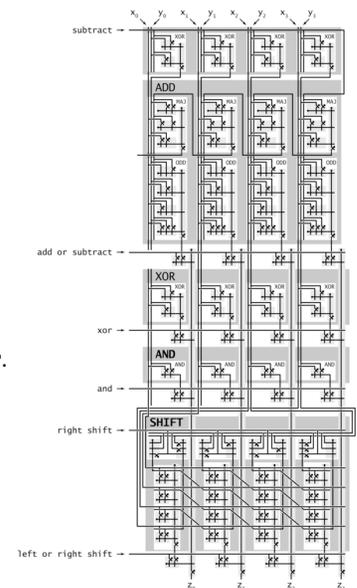- Computes all operations in parallel.
- Uses 1-hot OR to pick each bit answer.




43

44

Device Interface Using Buses

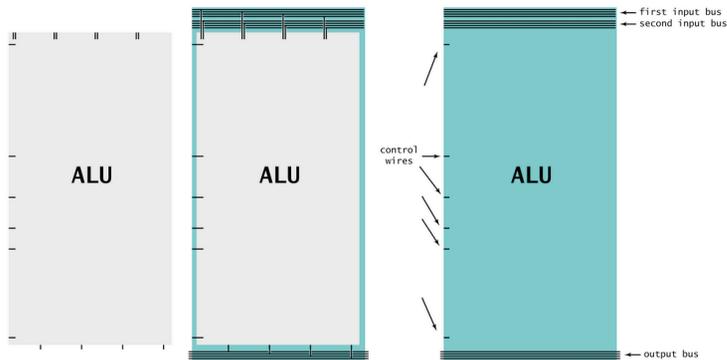- Device. Processes a word at a time. ← 16-bit words for TOY memory
- Input bus. Wires on top.
- Output bus. Wires on bottom.
- Control. Individual wires on side.



45

Summary

Lessons for software design apply to hardware design!

- Interface describes behavior of circuit.
- Implementation gives details of how to build it.

Layers of abstraction apply with a vengeance!

- On/off.
- Controlled switch. [relay, transistor]
- Gates. [AND, OR, NOT]
- Boolean circuit. [MAJ, ODD]
- Adder.
- Shifter.
- Arithmetic logic unit.
- ...
- TOY machine.

46