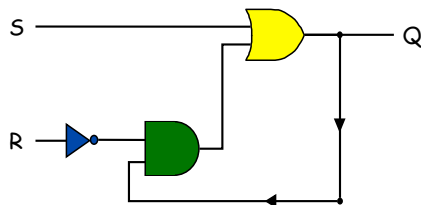


6.2: Sequential Circuits




COS126: General Computer Science · <http://www.cs.Princeton.EDU/~cos126>


SR Flip-Flop

SR Flip-Flop.

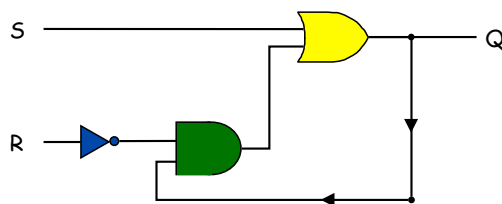- $S = 1, R = 0$ (set) \Rightarrow "Flips" bit on.
- $S = 0, R = 1$ (reset) \Rightarrow "Flips" bit off.
- $S = R = 0$ \Rightarrow Status quo.
- $S = R = 1$ \Rightarrow Not allowed.



Implementation

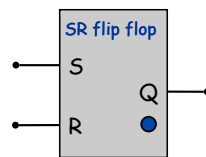


Interface

Sequential vs. Combinational Circuits


Combinational circuits.

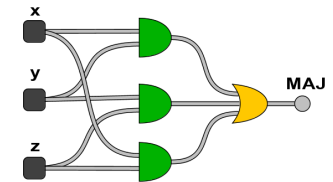- Output determined solely by inputs.
- Can draw solely with left-to-right signal paths.



Sequential circuits.

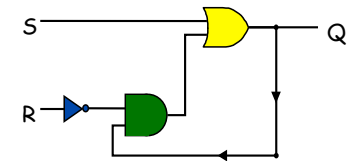- Output determined by inputs AND previous outputs.
- Feedback loop.



Memory Overview

Computers and TOY have many types of memory.

- Program counter.
- Registers.
- Main memory.

We implement each bit of memory with a clocked D flip-flop.


Need mechanism to organize and manipulate GROUPS of related bits.

- TOY has 16-bit words.
- Memory hierarchy makes architecture manageable.

Bus

16-bit bus.

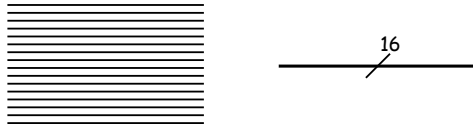- Bundle of 16 wires.
- Memory transfer, register transfer.



8-bit bus.

- Bundle of 8 wires.
- TOY memory address.



4-bit bus.

- Bundle of 4 wires.
- TOY register address.




5

Stand-Alone Register


k-bit register.

- Stores k bits.
- Register contents always available on output.
- If write enable is asserted, k input bits get copied into register.

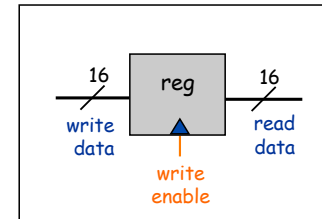Ex: Program Counter, 16 TOY registers, 256 TOY memory locations.



16-bit Register Interface

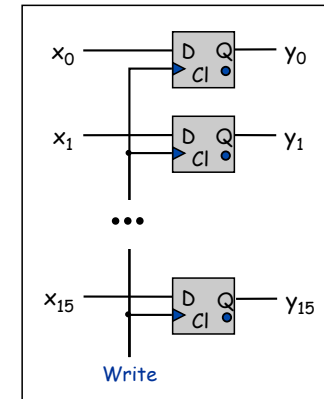

16-bit Register Implementation

6


Register File Interface

n-by-k register file.

- Bank of n registers; each stores k bits.
- Read and write information to *one* of n registers.
 - $\log_2 n$ address inputs specifies which one
- Addressed bits always appear on output.
- If write enable and clock are asserted, k input bits are copied into addressed register.

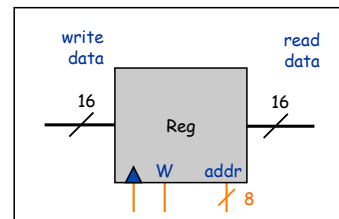Examples.

- TOY registers: $n = 16, k = 16$.
- TOY main memory: $n = 256, k = 16$.
- Real computer: $n = 256$ million, $k = 32$.
 - 1 GB memory
 - (1 Byte = 8 bits)




256 x 16 Register File Interface

7

Register File Implementation

Implementation example: TOY main memory.

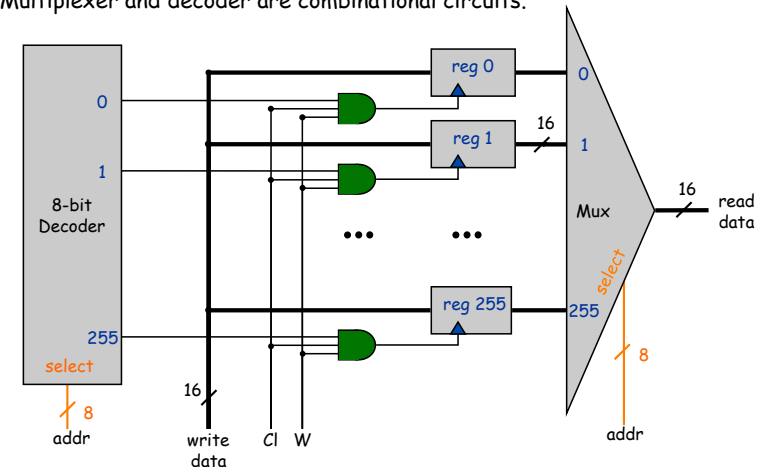- Use 256 16-bit registers.
- Multiplexer and decoder are combinational circuits.




8

Register File Implementation: Reading

Implementation example: TOY main memory.

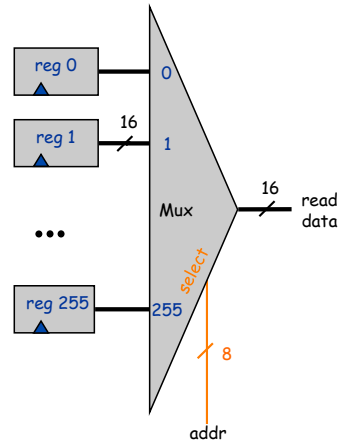- Use 256 16-bit registers.
- Multiplexer is combinational circuit.




9

2^n -to-1 Multiplexer


$n = 8$ for main memory

2^n -to-1 multiplexer.

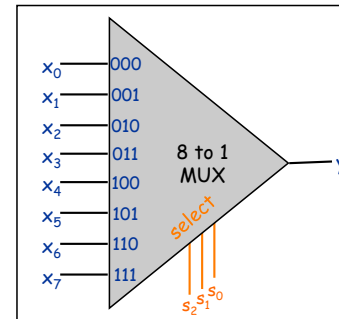- n select inputs, 2^n data inputs, 1 output.
- Copies "selected" data input bit to output.



8-to-1 Mux Interface

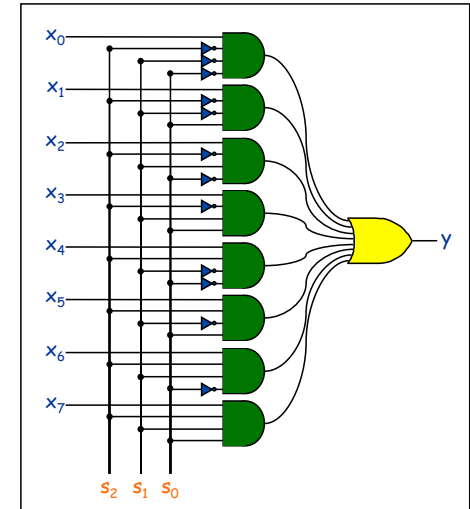

8-to-1 Mux Implementation


10

2^n -to-1 Multiplexer


$n = 8$ for main memory

2^n -to-1 multiplexer.

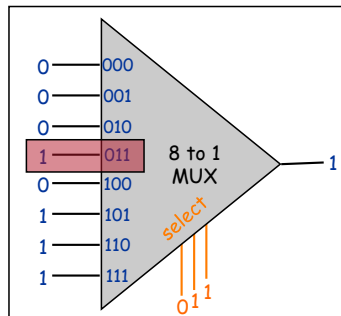- n select inputs, 2^n data inputs, 1 output.
- Copies "selected" data input bit to output.



8-to-1 Mux Interface

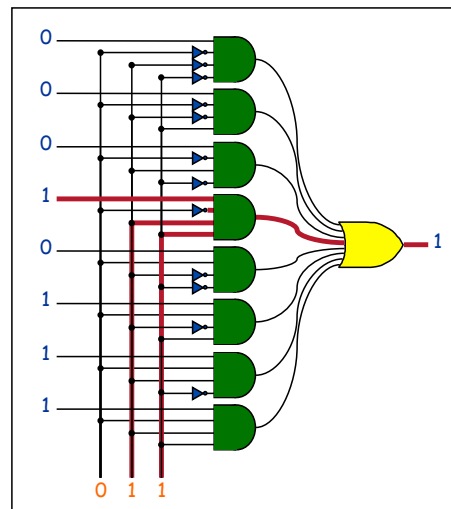

8-to-1 Mux Implementation


11

2^n -to-1 Multiplexer, Width = k


$n = 8, k = 16$ for main memory

2^n -to-1 multiplexer, width = k .

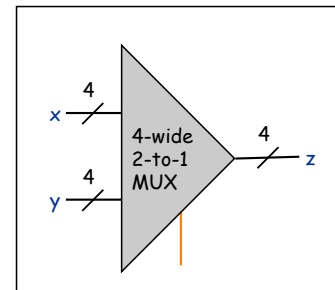- Select from one of 2^n k -bit buses.
- Copies k "selected" data bits to output.
- Layering k 2^n -to-1 multiplexers.



Interface for 2-to-1 MUX, width = 4

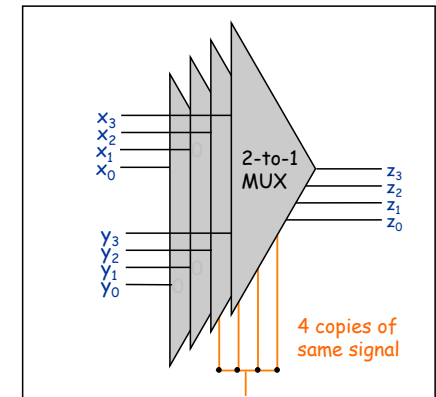


Implementation for 2-to-1 MUX, width = 4

12

Register File Implementation: Writing

Implementation example: TOY main memory.

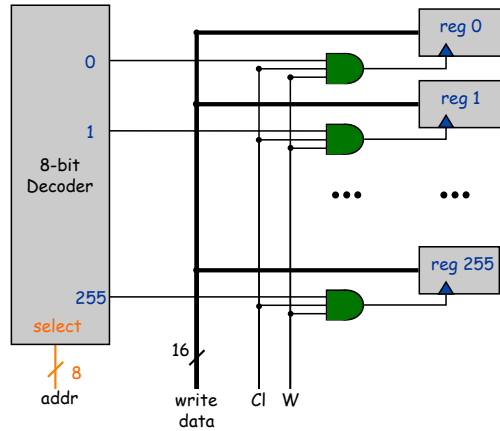- Use 256 16-bit registers.
- Decoder is combinational circuit.




13

Register File Implementation: Writing

Implementation example: TOY main memory.

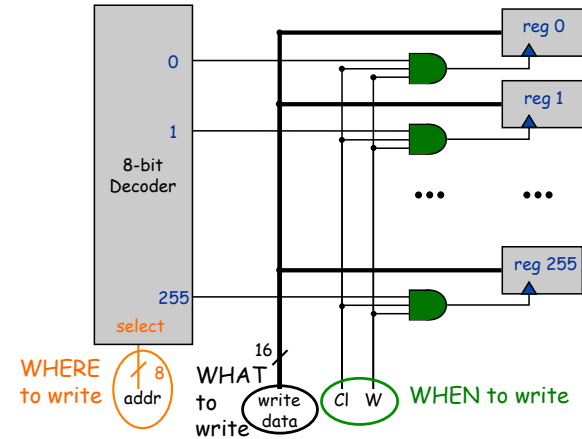- Use 256 16-bit registers.
- Decoder is combinational circuit.




14

n-Bit Decoder


n = 8 for main memory

n-bit decoder.

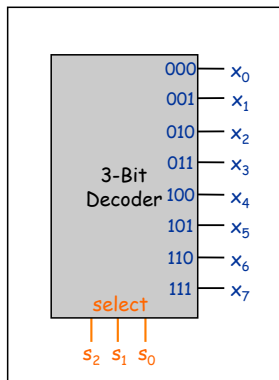- n address inputs, 2^n data outputs.
- Addressed output bit is 1; others are 0.



3-Bit Decoder Interface

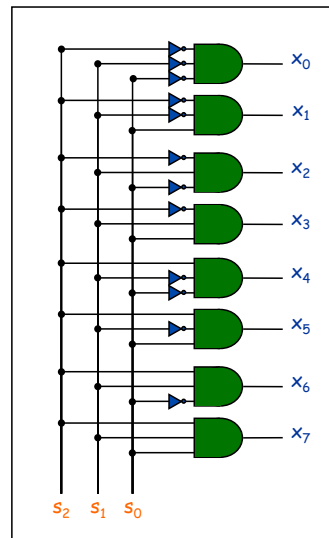

3-Bit Decoder Implementation


15

n-Bit Decoder


n = 8 for main memory

n-bit decoder.

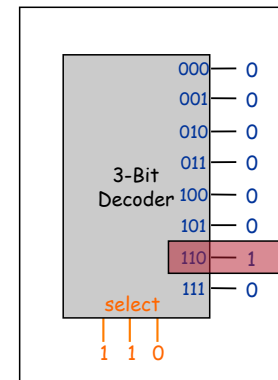- n address inputs, 2^n data outputs.
- Addressed output bit is 1; others are 0.



3-Bit Decoder Interface

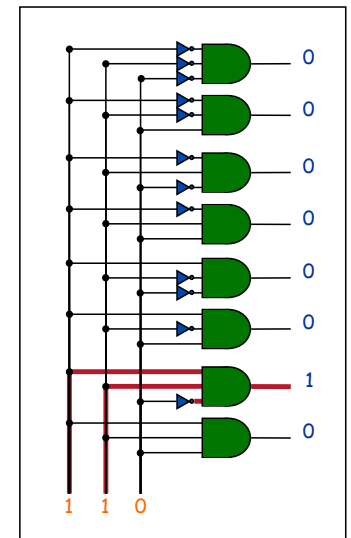


3-Bit Decoder Implementation

16

Register File Implementation: Reading and Writing

Implementation example: TOY main memory.

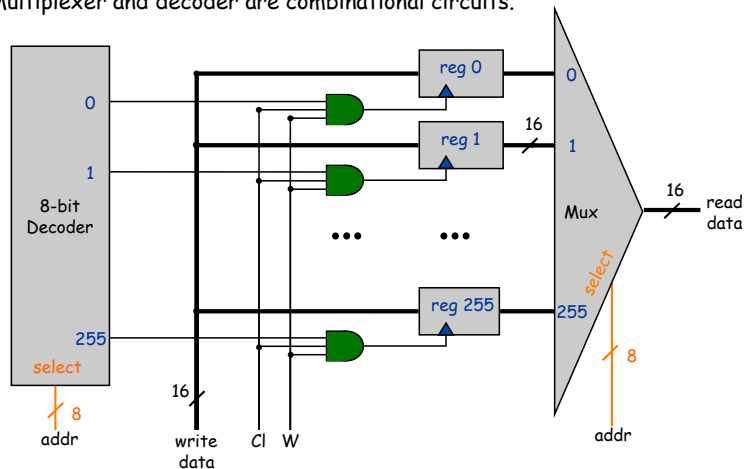- Use 256 16-bit registers.
- Multiplexer and decoder are combinational circuits.



17

Register File Variations

Read address can be different from Write address

- Not in Main Memory (one address from instruction or PC)
- But definitely in TOY registers (read from and write to different registers)


Can have multiple "ports"

- TOY registers supply TWO values per instruction
- How? Just get another set of 16-to-1, 16-wide multiplexors (and one more 4-bit address)

18

The TOY Machine

6.3: TOY Machine Architecture

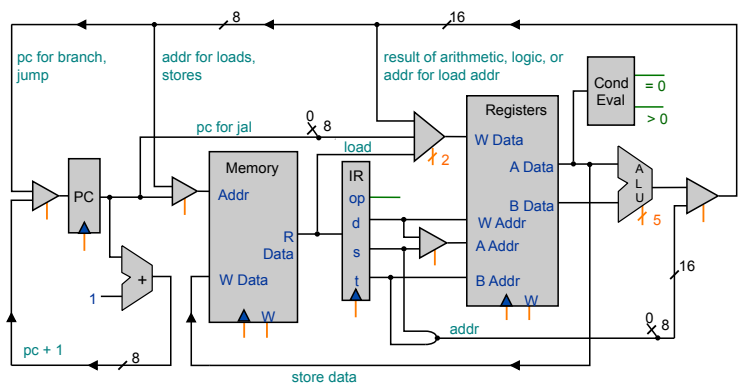

TOY machine.


- 256 16-bit words of memory.
- 16 16-bit registers.
- 1 8-bit program counter.
- 16 instructions types.

What we've done.

- Written programs for the TOY machine.
- Software implementation of fetch-execute cycle.
 - TOY simulator.

Our goal today.

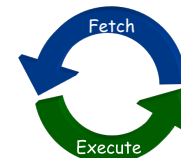- Hardware implementation of fetch-execute cycle.
 - TOY computer.



Designing a Processor

How to build a microprocessor?

- ➔
 - Develop instruction set architecture (ISA).
 - 16-bit words, 16 TOY machine instructions
 - Determine major components.
 - ALU, memory, registers, program counter
 - Determine datapath requirements.
 - "flow" of bits
 - Establish clocking methodology.
 - 2-cycle design: fetch, execute
 - Analyze how to implement each instruction.
 - determine settings of control signals

21

Instruction Set Architecture

Instruction set architecture (ISA).

- 16-bit words, 256 words of memory, 16 registers.
- Determine set of primitive instructions.
 - too narrow ⇒ cumbersome to program
 - too broad ⇒ cumbersome to build hardware
- TOY machine: 16 instructions.

Instructions	
0:	halt
1:	add
2:	subtract
3:	and
4:	xor
5:	shift left
6:	shift right
7:	load address

Instructions	
8:	load
9:	store
A:	load indirect
B:	store indirect
C:	branch zero
D:	branch positive
E:	jump register
F:	jump and link

22

Designing a Processor

How to build a microprocessor?

- ➔
 - Develop instruction set architecture (ISA).
 - 16-bit words, 16 TOY machine instructions
 - Determine major components.
 - ALU, memory, registers, program counter
 - Determine datapath requirements.
 - "flow" of bits
 - Establish clocking methodology.
 - 2-cycle design: fetch, execute
 - Analyze how to implement each instruction.
 - determine settings of control signals


23

Arithmetic Logic Unit

TOY ALU.


- Big combinational circuit.
- 16-bit bus.
- Add, subtract, and, xor, shift left, shift right, copy input 2.

op	2	1	0
+, -	0	0	0
&	0	0	1
^	0	1	0
<<, >>	0	1	1
input 2	1	0	0

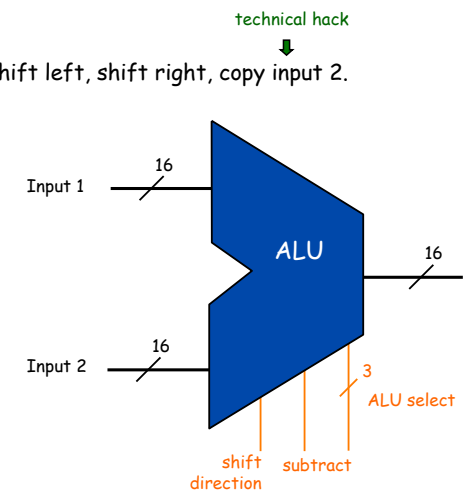

24


Arithmetic Logic Unit: Implementation

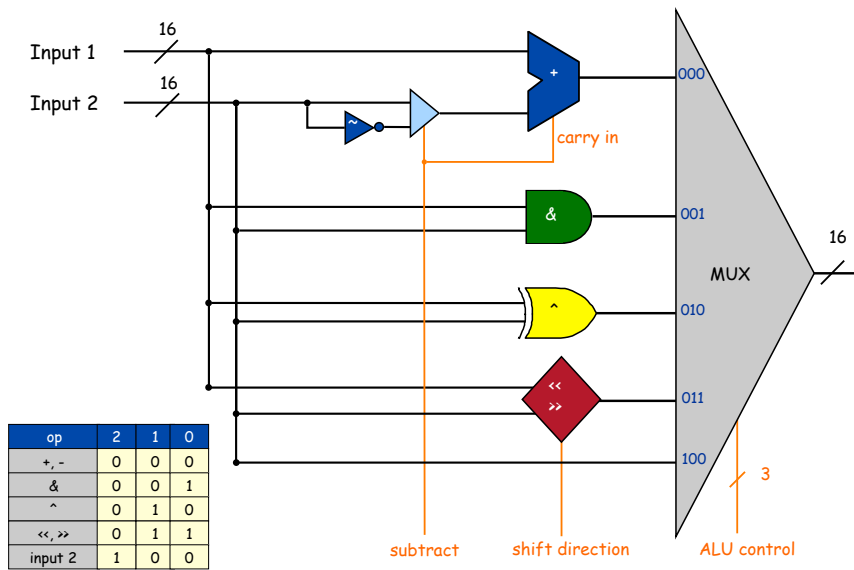

25

Main Memory

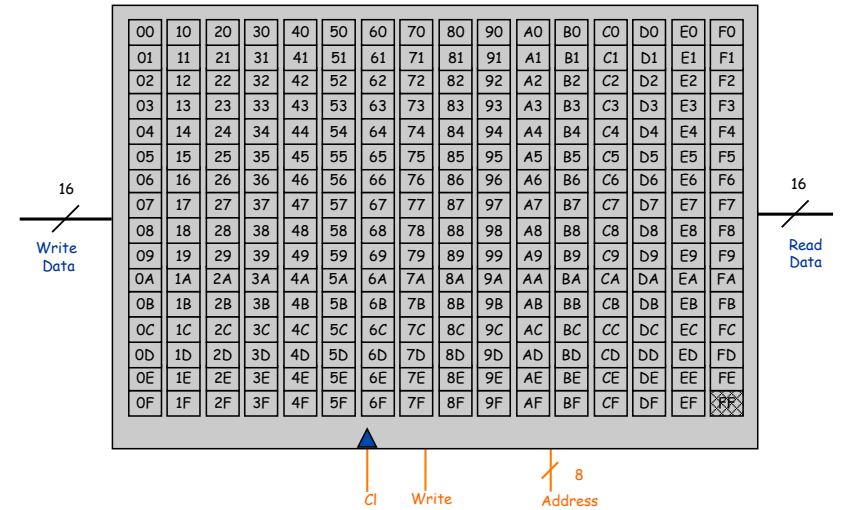TOY main memory: 256 x 16-bit register file.




26

Registers

TOY registers: fancy 16 x 16-bit register file.

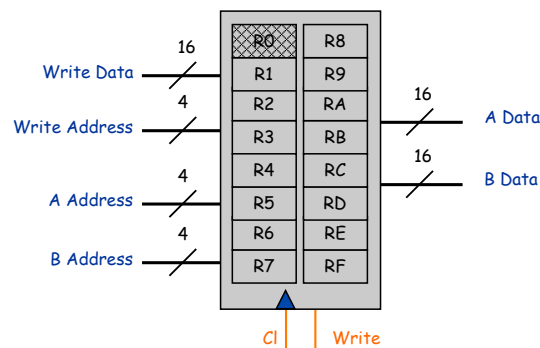- Want to be able to read two registers, and write to a third in the same instructions: $R1 \leftarrow R2 + R3$.
- 3 address inputs, 1 data input, 2 data outputs.
- Add decoders and muxes for additional ports.



27

Designing a Processor

How to build a microprocessor?

- Develop instruction set architecture (ISA).
 - 16-bit words, 16 TOY machine instructions
- Determine major components.
 - ALU, memory, registers, program counter
- Determine datapath requirements.
 - "flow" of bits
- Establish clocking methodology.
 - 2-cycle design: fetch, execute
- Analyze how to implement each instruction.
 - determine settings of control signals

28


Datapath and Control

Datapath.

- Layout and interconnection of components.
- Must accommodate all instruction types.

Control.

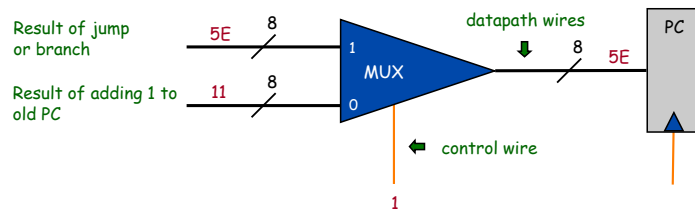- Choreographs the "flow" of information on the datapath.
- Depending on instruction, different control wires are turned on.



29


Datapath and Control

Datapath.

- Layout and interconnection of components.
- Must accommodate all instruction types.


Control.

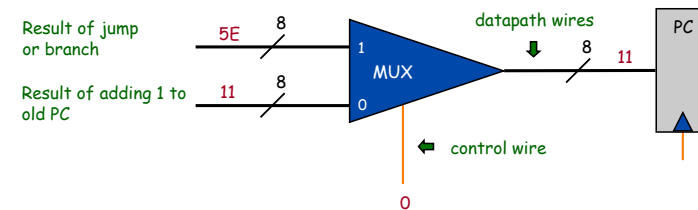- Choreographs the "flow" of information on the datapath.
- Depending on instruction, different control wires are turned on.




30

TOY "Classic", Back Of Envelope Design

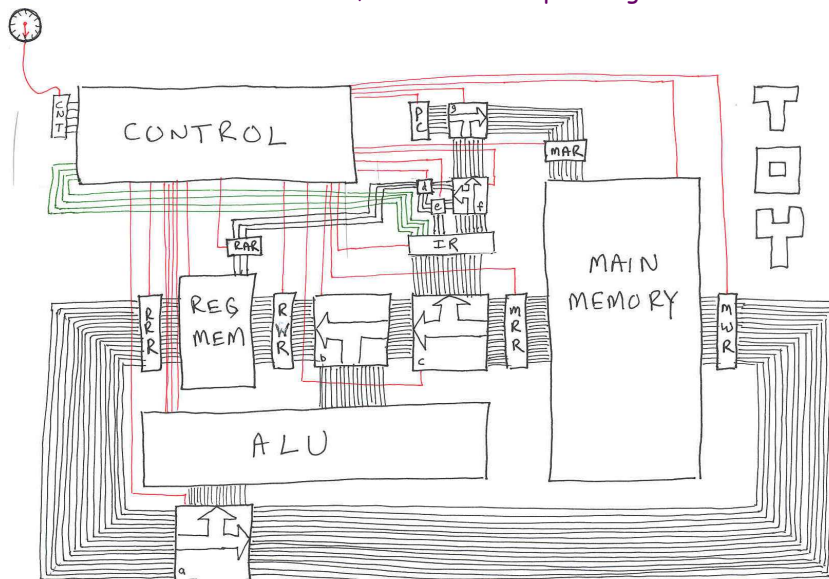


31

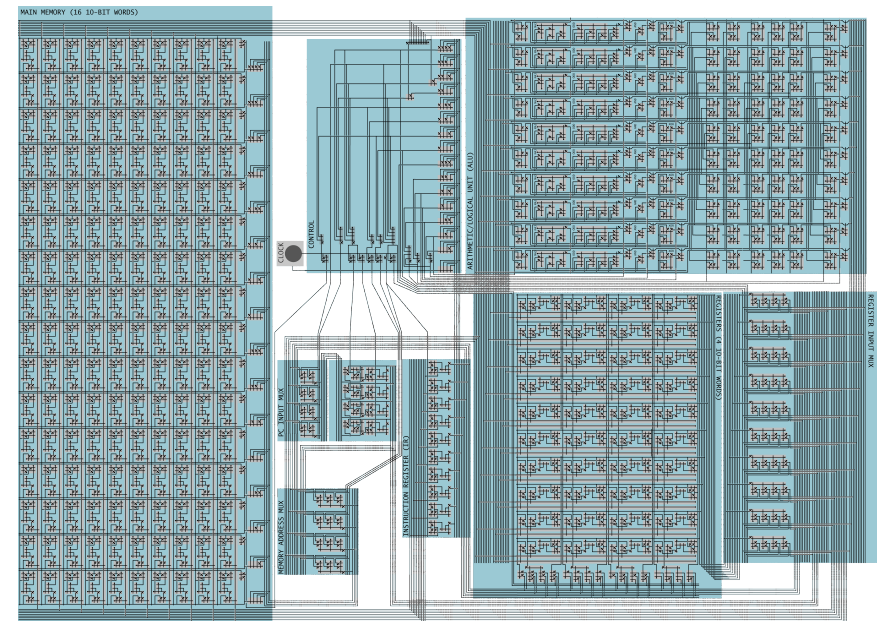


32

Real Microprocessor Chip (Intel Nehalem)

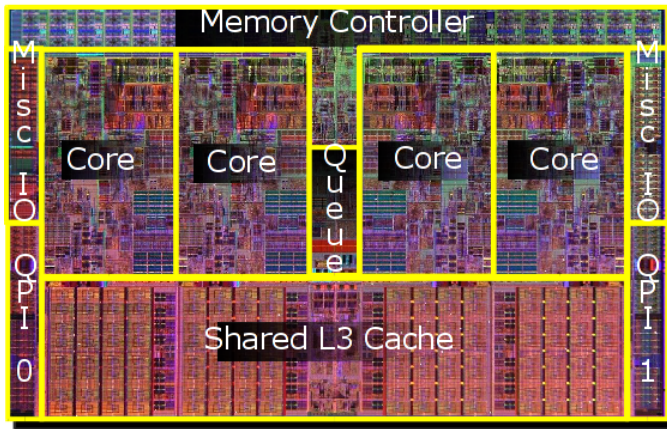


The TOY Datapath

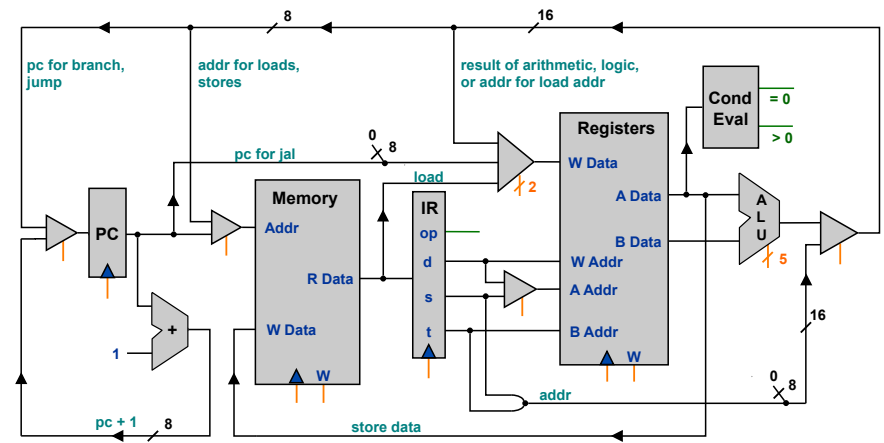

33

34


The TOY Datapath: Add

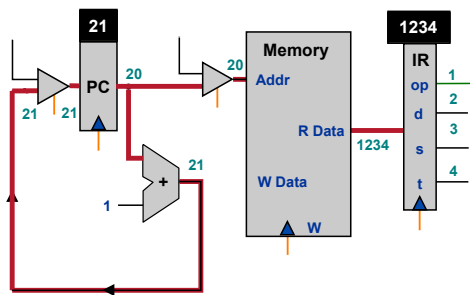

Before fetch:
 $pc = 20, mem[20] = 1234$

After fetch:
 $pc = 21$
 $IR = 1234: R[2] \leftarrow R[3] + R[4]$

The TOY Datapath: Add

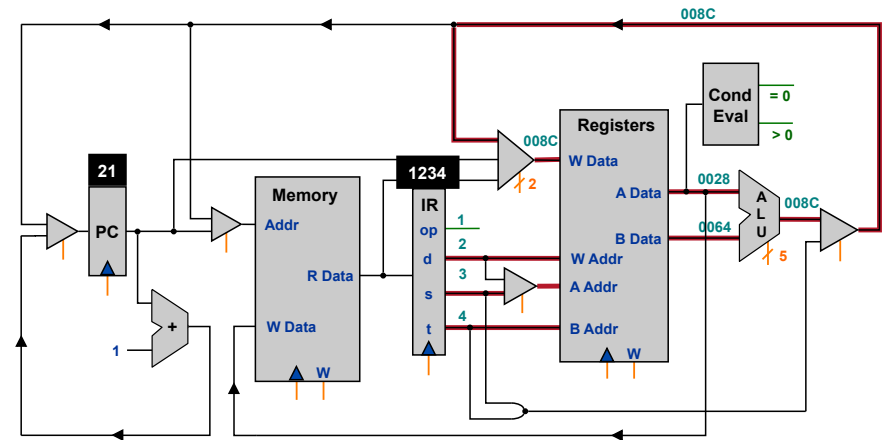


Before execute:
 $pc = 21$
 $IR = 1234: R[2] \leftarrow R[3] + R[4]$
 $R[3] = 0028, R[4] = 0064$

After execute:
 $pc = 21$
 $R[2] = 008C$

35

36

Do Try This At Home

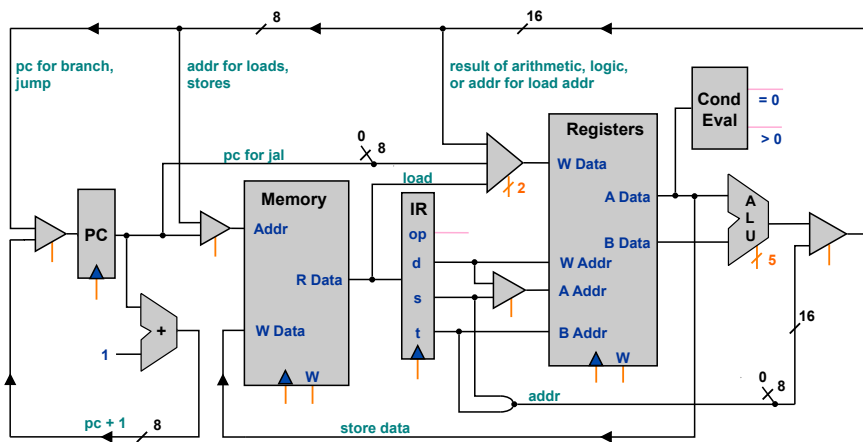

Trace the flow of some other instructions through the datapath picture.

37

Designing a Processor

How to build a microprocessor?



- Develop instruction set architecture (ISA).
 - 16-bit words, 16 TOY machine instructions
- Determine major components.
 - ALU, memory, registers, program counter
- Determine datapath requirements.
 - "flow" of bits
- ➔ ▪ Establish clocking methodology.
 - 2-cycle design: fetch, execute
- Analyze how to implement each instruction.
 - determine settings of control signals

38

Clocking Methodology

Two cycle design (fetch and execute).

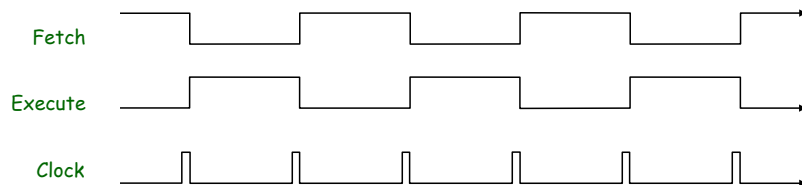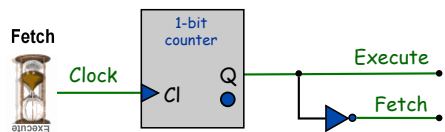- Use 1-bit counter to distinguish between 2 cycles.
- Use two cycles since fetch and execute phases each access memory and alter program counter.



39


Clocking Methodology

4 distinguishable epochs.

- During fetch phase.
- At very end of execute phase.
- During execute phase.
- At very end of fetch phase.

Ex: can only write at very end of execute phase.

- $R1 \leftarrow R1 + R1$

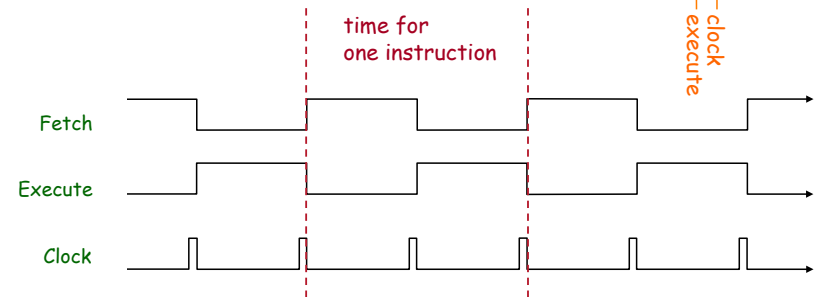

40

Designing a Processor


How to build a microprocessor?

- Develop instruction set architecture (ISA).
 - 16-bit words, 16 TOY machine instructions
- Determine major components.
 - ALU, memory, registers, program counter
- Determine datapath requirements.
 - "flow" of bits
- Establish clocking methodology.
 - 2-cycle design: fetch, execute
- Analyze how to implement each instruction.
 - determine settings of control signals

Control

Control: controls components, enables connections.

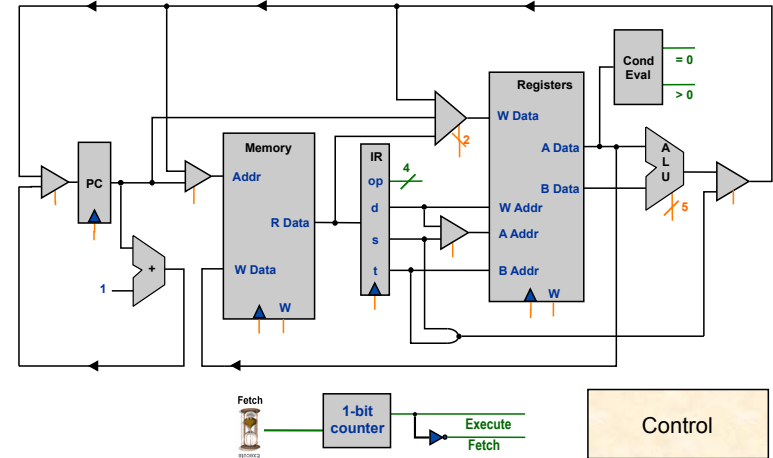- Input: opcode, clock, conditional evaluation. (green)
- Output: control wires. (orange)




41

42

Control


Control: controls components, enables connections.

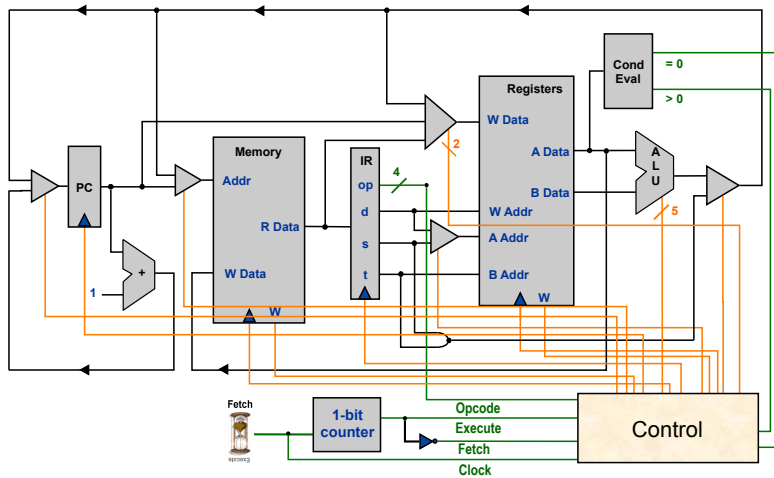- Input: opcode, clock, conditional evaluation. (green)
- Output: control wires. (orange)




43

Implementation of Control

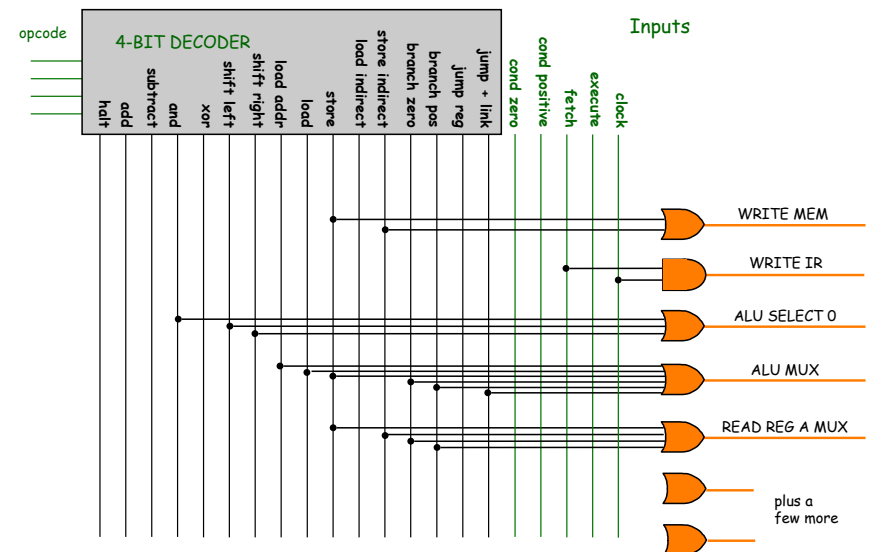


44

Implementation of Control: Store

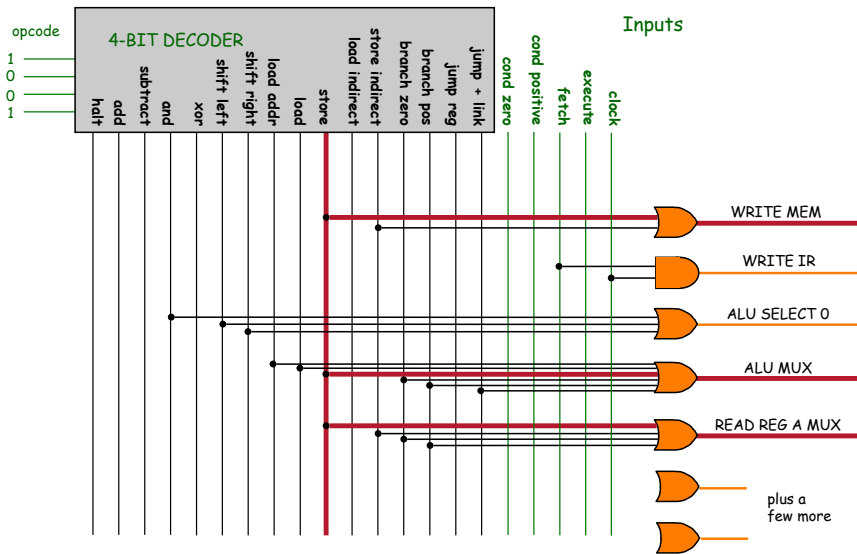


45

Control: Execute Phase of Store

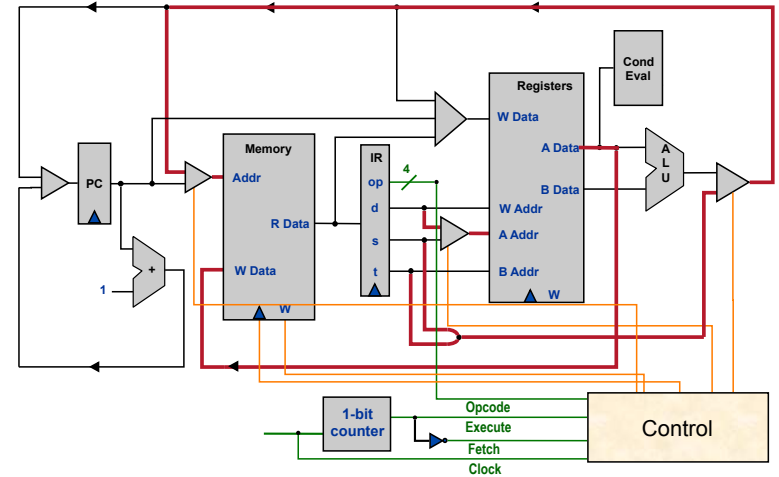

46

Stand-Alone Registers

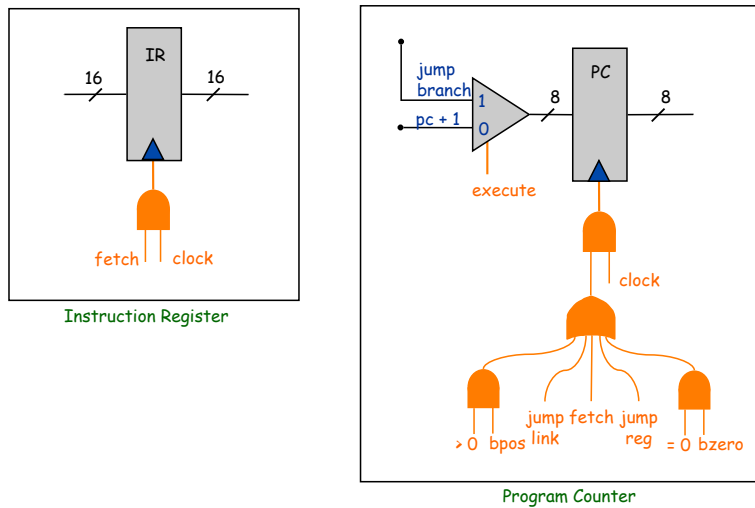

47

Pipelining

Pipelining.

- At any instant, processor is either fetching instructions or executing them (and so half of circuitry is idle).
- Why not fetch next instruction while current instruction is executing?
 - Analogy: washer / dryer.

Issues.


- Jump and branch instructions change PC.
 - "Prefetch" next instruction.
- Fetch and execute cycles may need to access same memory.
 - Solution: use two memory "caches".

Result.


- Better utilization of hardware.
- Can double speed of processor.

48

Goodbye, TOY

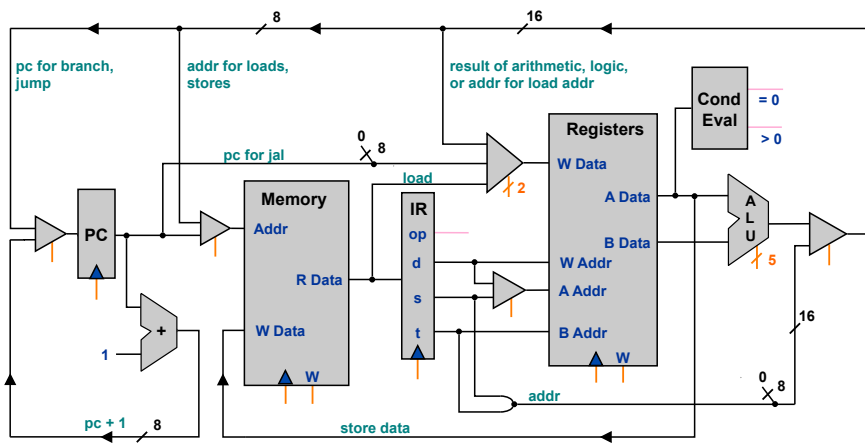

The final secret

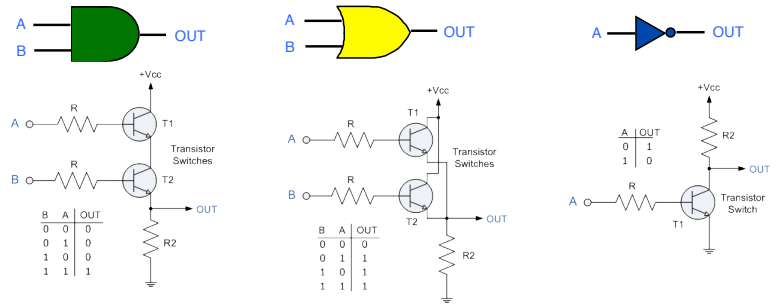

All three of our logic primitives can be made using a *single** type of electronic primitive: the *transistor*!