 


# More Sequential Circuits, plus Architecture


---



## Sequential vs. Combinational Circuits

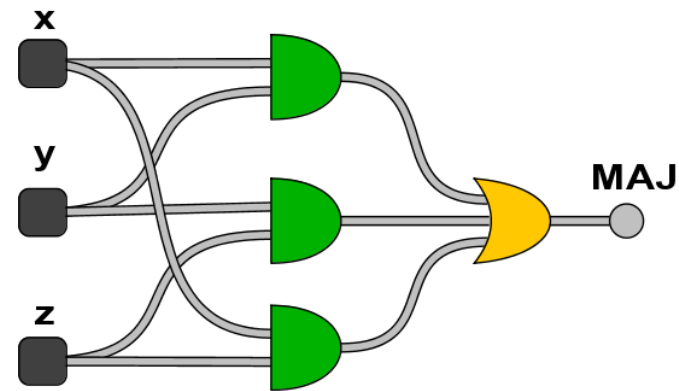
### Combinational circuits.

- Output determined solely by inputs.
- Can draw solely with left-to-right signal paths.


 
### Sequential circuits.


- Output determined by inputs AND previous outputs.
- Feedback loop.




# SR Flip-Flop
 
## SR Flip-Flop.

- $S = 1, R = 0$  (set)  $\Rightarrow$  "Flips" bit on.
- $S = 0, R = 1$  (reset)  $\Rightarrow$  "Flips" bit off.
- $S = R = 0$   $\Rightarrow$  Status quo.
- $S = R = 1$   $\Rightarrow$  Not allowed.



Implementation

 


Interface


# Clocked SR Flip-Flop
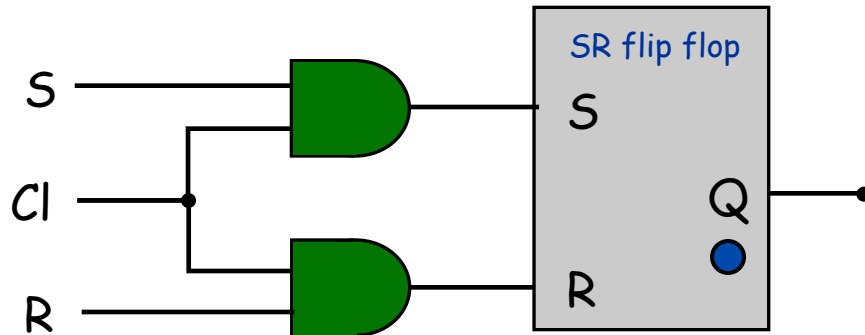
## Clocked SR Flip-Flop.


- Same as SR flip-flop except S and R only active when clock is 1.



Implementation

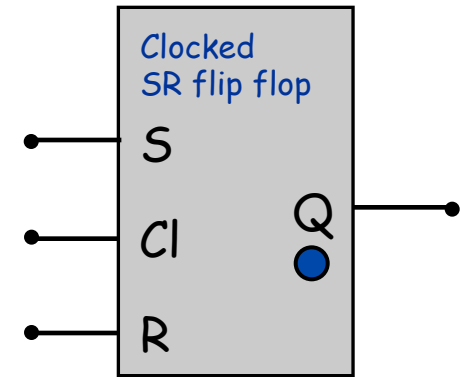


Interface

 


# Clocked D Flip-Flop
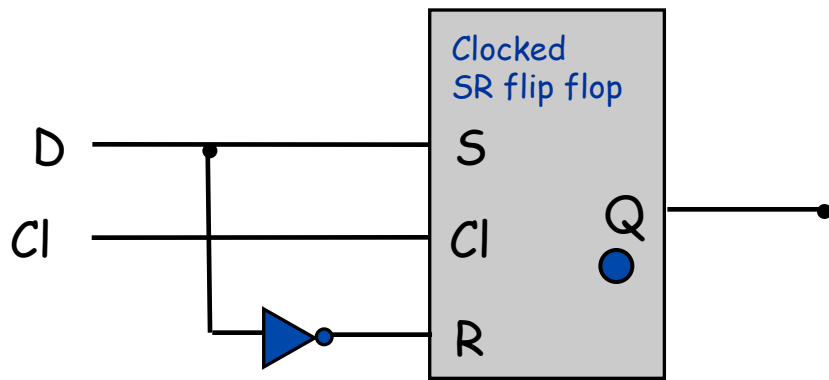
## Clocked D Flip-Flop.


- Output follows D input while clock is 1.
- Output is remembered while clock is 0.



Implementation

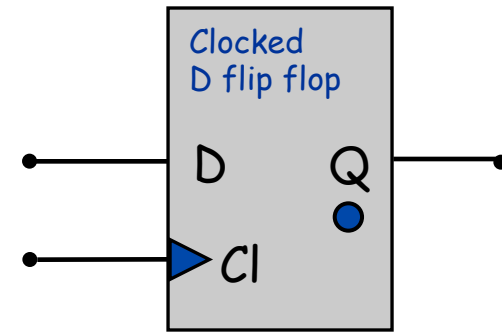

Interface

 

## Memory Overview

Computers and TOY have many types of memory.

- Program counter.
- Registers.
- Main memory.

We implement each bit of memory with a clocked D flip-flop.



Need mechanism to organize and manipulate *GROUPS* of related bits.

- TOY has 16-bit words.
- Memory hierarchy makes architecture manageable.

## Bus

 
 
### 16-bit bus.

- Bundle of 16 wires.
- Memory transfer, register transfer.



 
 
### 8-bit bus.

- Bundle of 8 wires.
- TOY memory address.


  
### 4-bit bus.

- Bundle of 4 wires.
- TOY register address.




# Stand-Alone Register


k-bit register.

- Stores k bits.
- Register contents always available on output.
- If write enable is asserted, k input bits get copied into register.

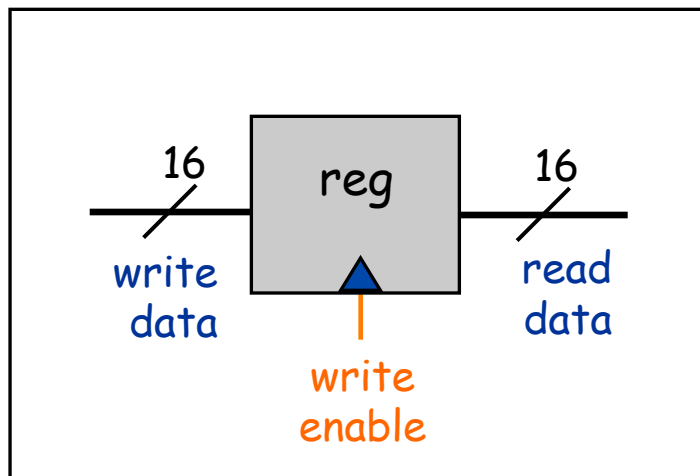Ex: Program Counter, 16 TOY registers, 256 TOY memory locations.



16-bit Register Interface

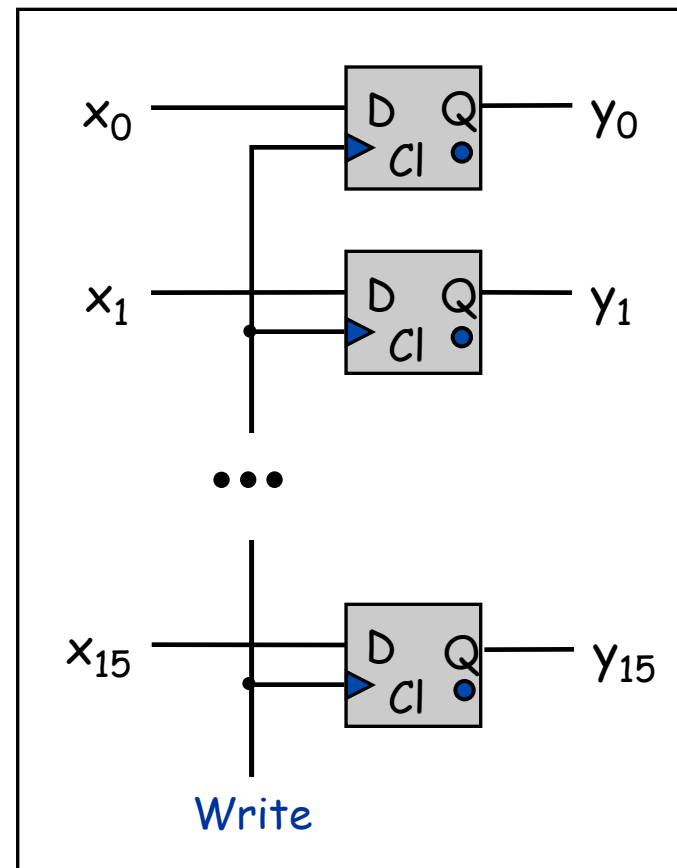

16-bit Register Implementation




# Register File Interface

## n-by-k register file.

- Bank of  $n$  registers; each stores  $k$  bits.
- Read and write information to *one* of  $n$  registers.
  - $\log_2 n$  address inputs specifies which one
- Addressed bits always appear on output.
- If write enable and clock are asserted,  $k$  input bits are copied into addressed register.
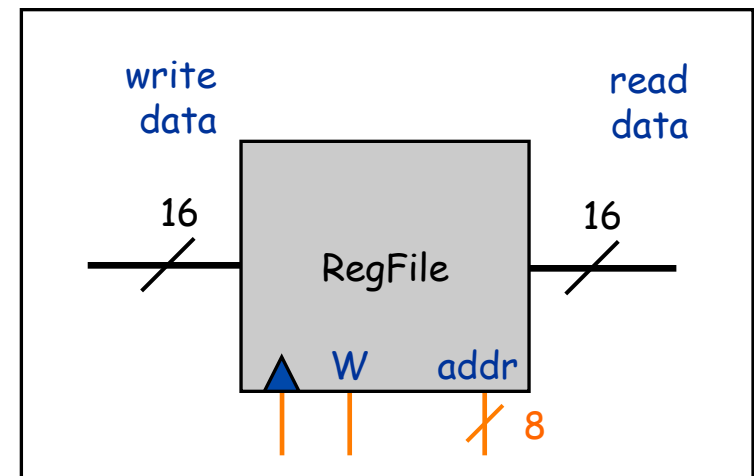
## Examples.

- TOY registers:  $n = 16, k = 16$ .
- TOY main memory:  $n = 256, k = 16$ .
- Real computer:  $n = 256$  million,  $k = 32$ .
  - 1 GB memory
  - (1 Byte = 8 bits)




256 x 16 Register File Interface
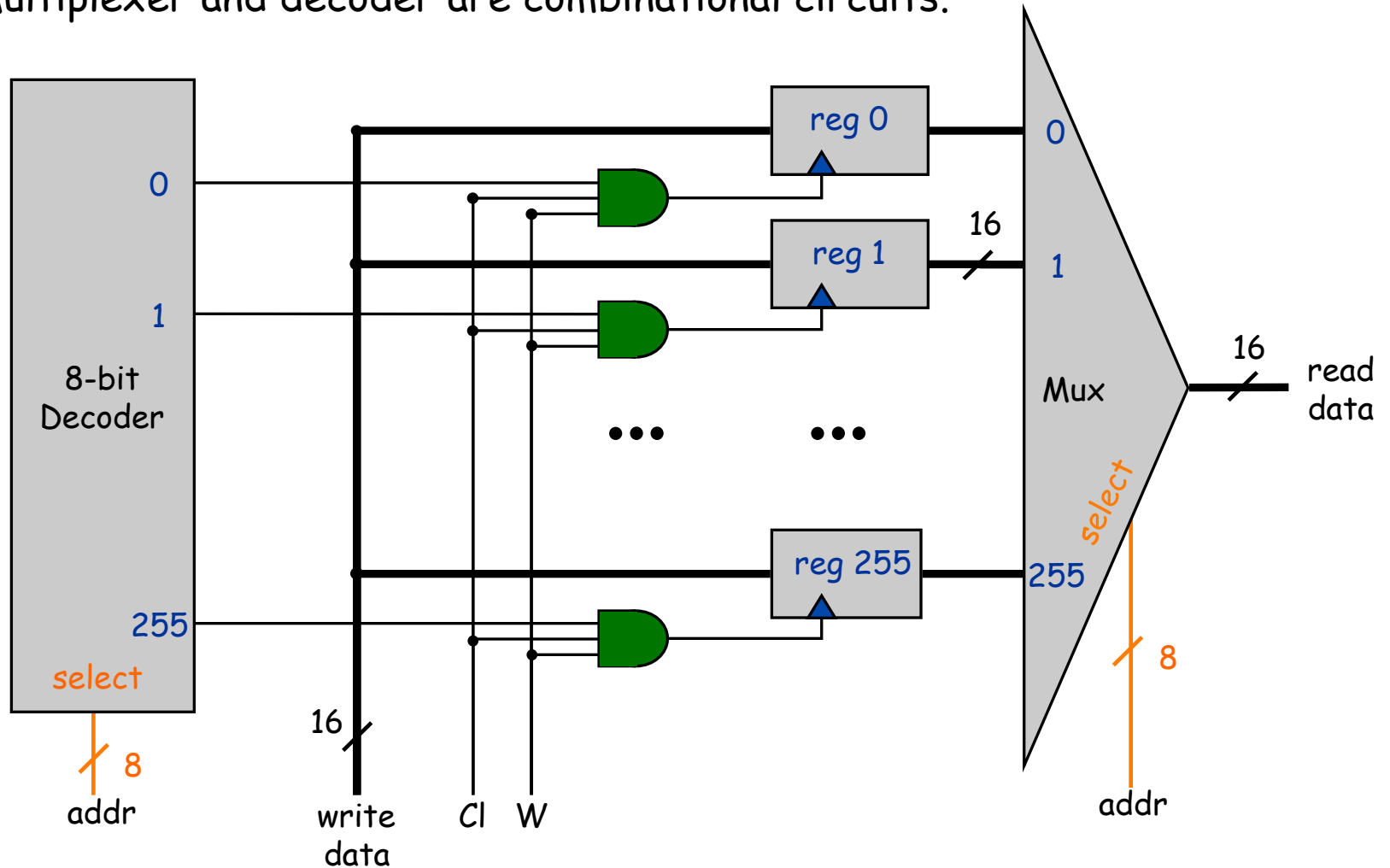
# Register File Implementation

Implementation example: TOY main memory.


- Use 256 16-bit registers.
- Multiplexer and decoder are combinational circuits.


 
## Register File Implementation: Reading

Implementation example: TOY main memory.

- Use 256 16-bit registers.
- Multiplexer is combinational circuit.




# 2<sup>n</sup>-to-1 Multiplexer


↙ n = 8 for main memory

2<sup>n</sup>-to-1 multiplexer.

 - n select inputs, 2<sup>n</sup> data inputs, 1 output.
- Copies "selected" data input bit to output.



8-to-1 Mux Interface

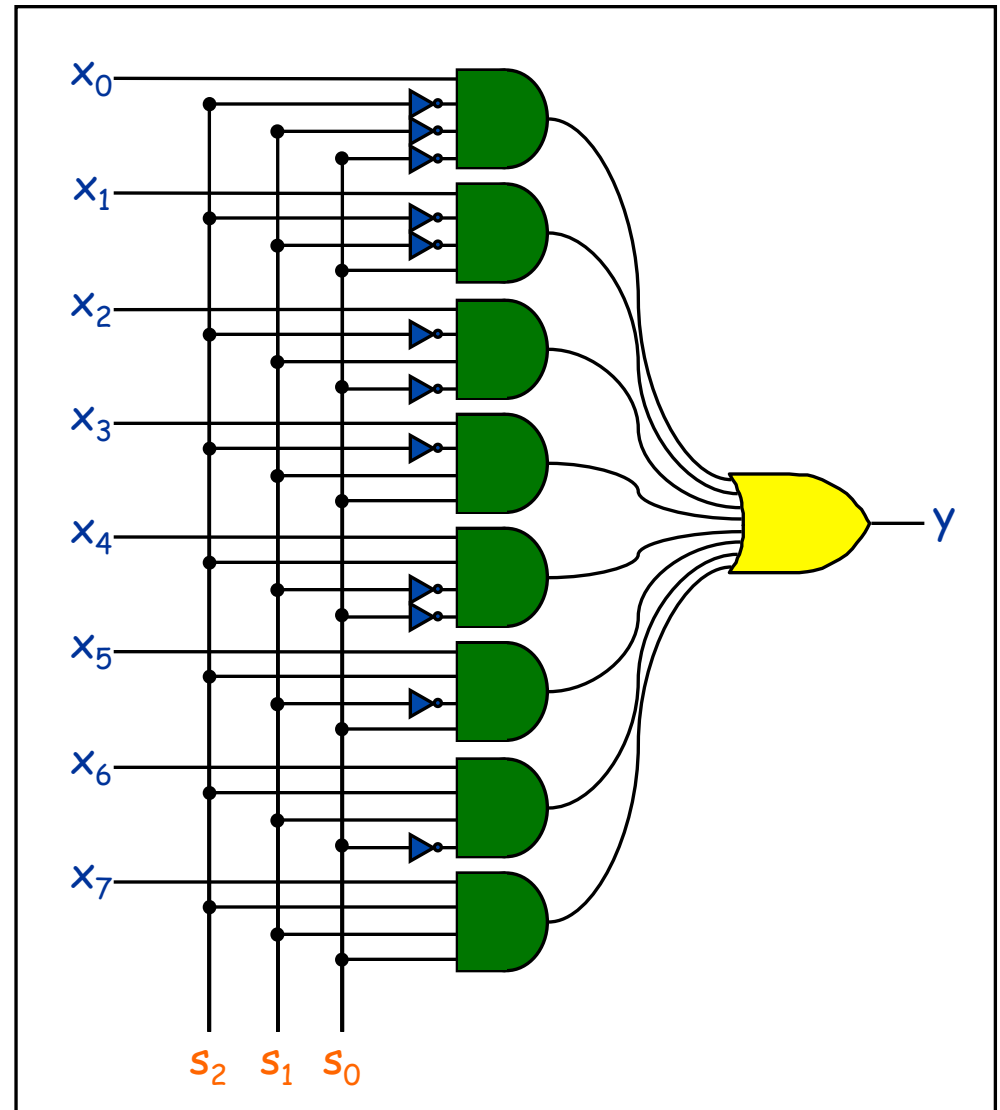


8-to-1 Mux Implementation

# 2<sup>n</sup>-to-1 Multiplexer


↙ n = 8 for main memory

2<sup>n</sup>-to-1 multiplexer.

 - n select inputs, 2<sup>n</sup> data inputs, 1 output.
- Copies "selected" data input bit to output.



8-to-1 Mux Interface

 


8-to-1 Mux Implementation

## 2<sup>n</sup>-to-1 Multiplexer, Width = k


↙ n = 8, k = 16 for main memory

2<sup>n</sup>-to-1 multiplexer, width = k.

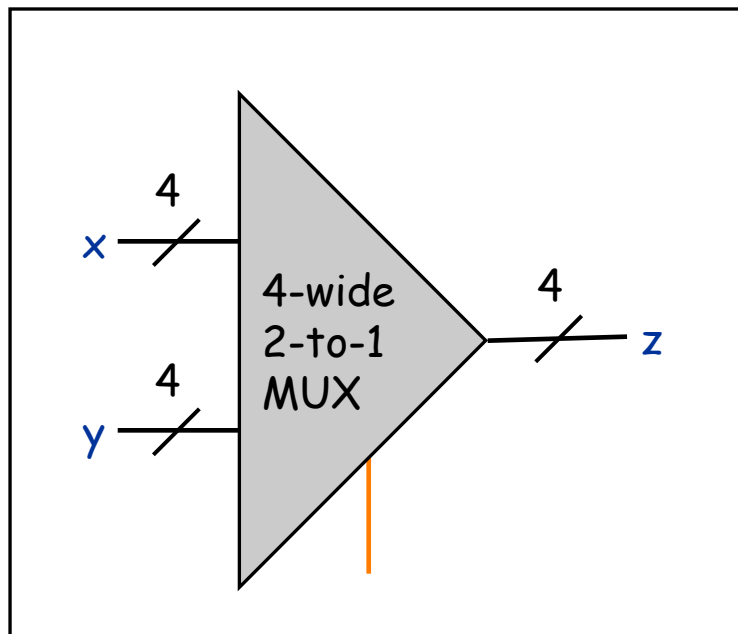- Select from one of 2<sup>n</sup> k-bit buses.
- Copies k "selected" data bits to output.
- Layering k 2<sup>n</sup>-to-1 multiplexers.



Interface for 2-to-1 MUX, width = 4

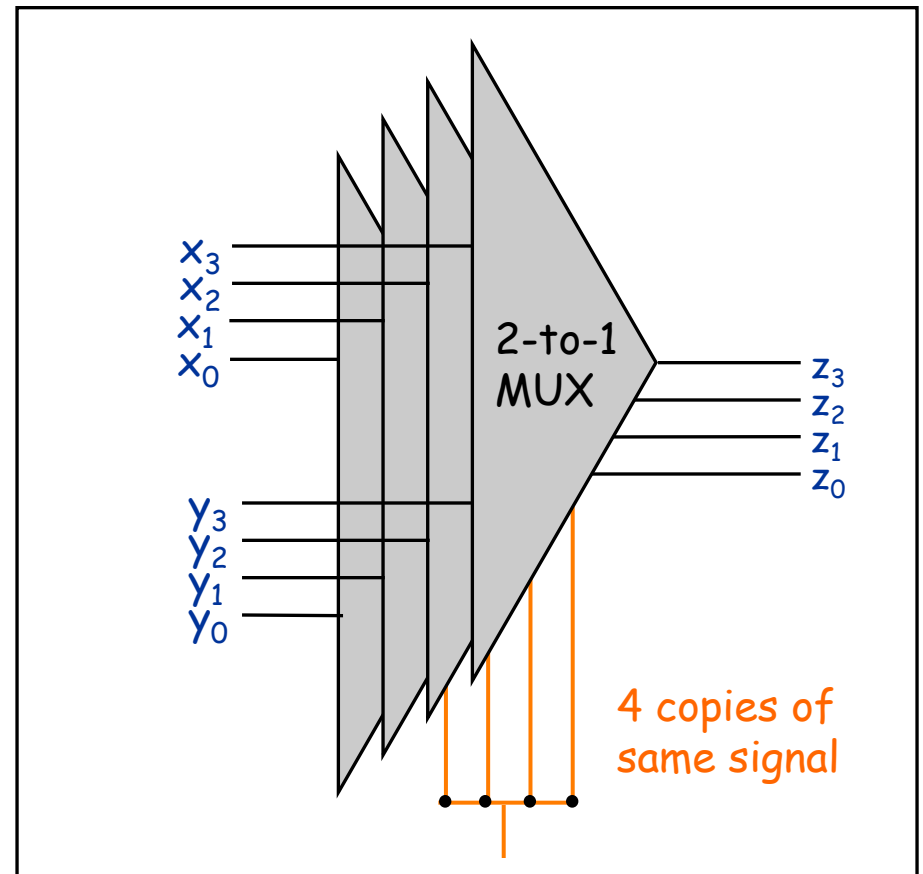


Implementation for 2-to-1 MUX, width = 4
 
# Register File Implementation: Writing

Implementation example: TOY main memory.


- Use 256 16-bit registers.
- Decoder is combinational circuit.


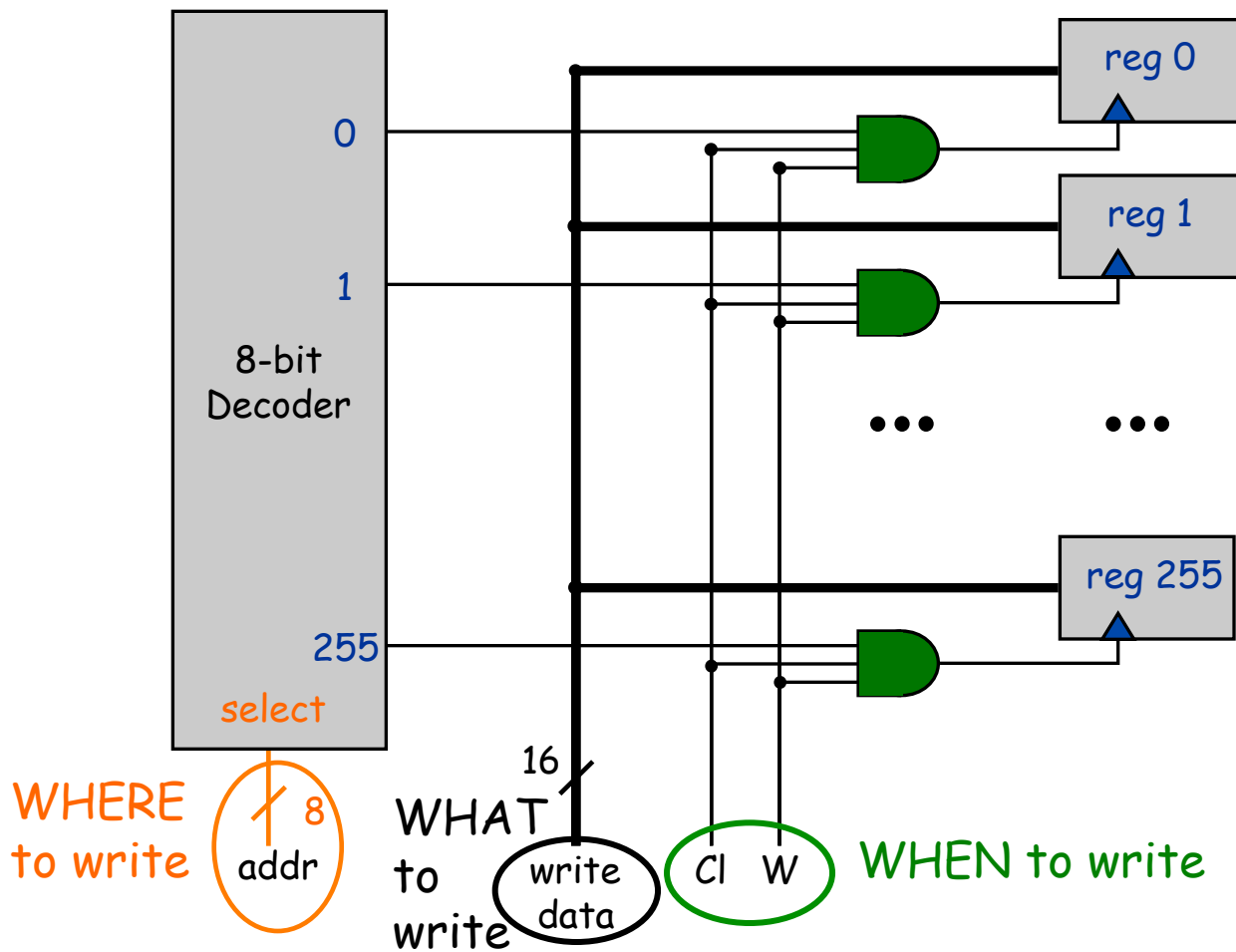
# Register File Implementation: Writing

Implementation example: TOY main memory.

- Use 256 16-bit registers.
- Decoder is combinational circuit.






# n-Bit Decoder


↙ n = 8 for main memory

n-bit decoder.

 - n address inputs,  $2^n$  data outputs.
- Addressed output bit is 1; others are 0.



3-Bit Decoder Interface

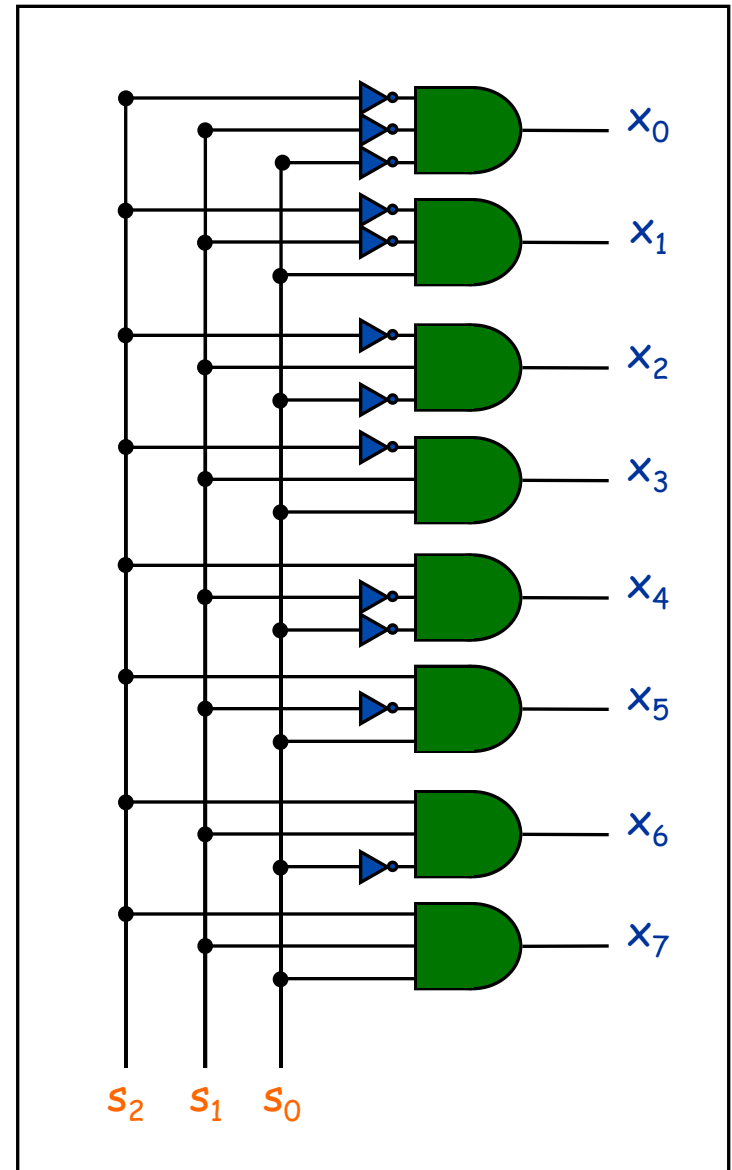


3-Bit Decoder Implementation

# n-Bit Decoder


↙ n = 8 for main memory

n-bit decoder.

 - n address inputs,  $2^n$  data outputs.
- Addressed output bit is 1; others are 0.



3-Bit Decoder Interface

 


3-Bit Decoder Implementation
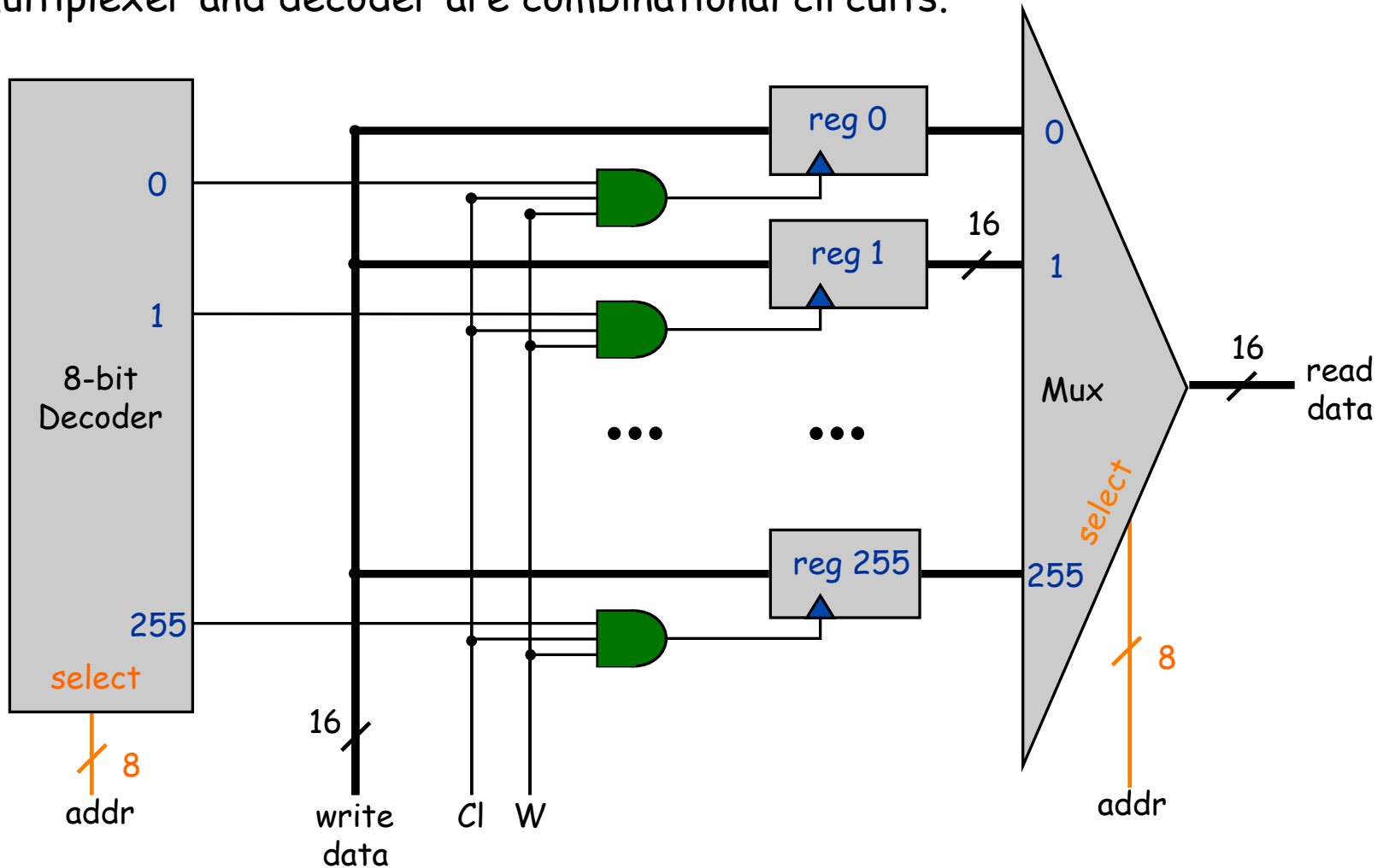
# Register File Implementation: Reading and Writing

Implementation example: TOY main memory.

- Use 256 16-bit registers.
- Multiplexer and decoder are combinational circuits.



## Register File Variations

Read address can be different from Write address

- ◆ Not in Main Memory (one address from instruction or PC)
- ◆ But definitely in TOY registers (read from and write to different registers)


Can have multiple "ports"

- ◆ TOY registers supply TWO values per instruction
- ◆ How? Just get another set of 16-to-1, 16-wide multiplexors (and one more 4-bit address)

Actual technologies for register and memory are different.

- ◆ Register files are relatively small and very fast (expensive per bit)
- ◆ Memories are relatively large and pretty fast (very cheap per bit)
- ◆ Drastic evolution of technology over time (Moore's Law)

## 6.3: TOY Machine Architecture

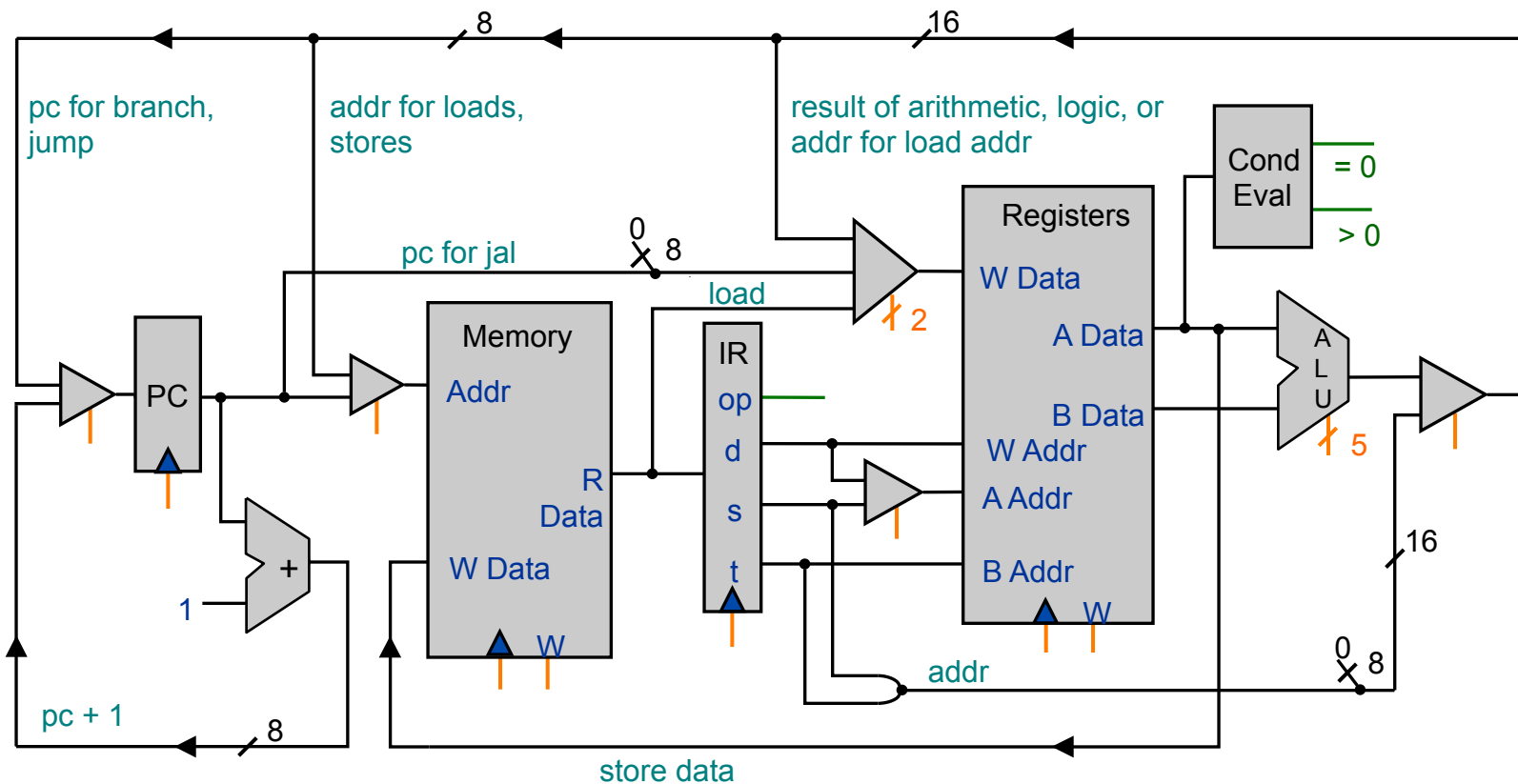

# The TOY Machine

## TOY machine.


- 256 16-bit words of memory.
- 16 16-bit registers.
- 1 8-bit program counter.
- 16 instructions types.

## What we've done.

- Written programs for the TOY machine.
- Software implementation of fetch-execute cycle.
  - TOY simulator.
 
## Our goal today.

- Hardware implementation of fetch-execute cycle.
  - TOY computer.



# Designing a Processor

## How to build a microprocessor?

- ➔ ■ Develop instruction set architecture (ISA).
  - 16-bit words, 16 TOY machine instructions
  
- Determine major components.
  - ALU, memory, registers, program counter
  
- Determine datapath requirements.
  - "flow" of bits
  
- Establish clocking methodology.
  - 2-cycle design: fetch, execute
  
- Analyze how to implement each instruction.
  - determine settings of control signals

# Instruction Set Architecture

## Instruction set architecture (ISA).

- 16-bit words, 256 words of memory, 16 registers.
- Determine set of primitive instructions.
  - too narrow  $\Rightarrow$  cumbersome to program
  - too broad  $\Rightarrow$  cumbersome to build hardware
- TOY machine: 16 instructions.

Instructions	
0:	halt
1:	add
2:	subtract
3:	and
4:	xor
5:	shift left
6:	shift right
7:	load address

Instructions	
8:	load
9:	store
A:	load indirect
B:	store indirect
C:	branch zero
D:	branch positive
E:	jump register
F:	jump and link



# Designing a Processor

## How to build a microprocessor?


- Develop instruction set architecture (ISA).
  - 16-bit words, 16 TOY machine instructions
- ➔ ▪ Determine major components.
  - ALU, memory, registers, program counter
- Determine datapath requirements.
  - "flow" of bits
- Establish clocking methodology.
  - 2-cycle design: fetch, execute
- Analyze how to implement each instruction.
  - determine settings of control signals

# Arithmetic Logic Unit


## TOY ALU.

- Big combinational circuit.
- 16-bit buses for inputs and output.
- Add, subtract, and, xor, shift left, shift right, copy input 2.

op	2	1	0
+, -	0	0	0
&	0	0	1
^	0	1	0
<<, >>	0	1	1
input 2	1	0	0

 


# Arithmetic Logic Unit: Implementation

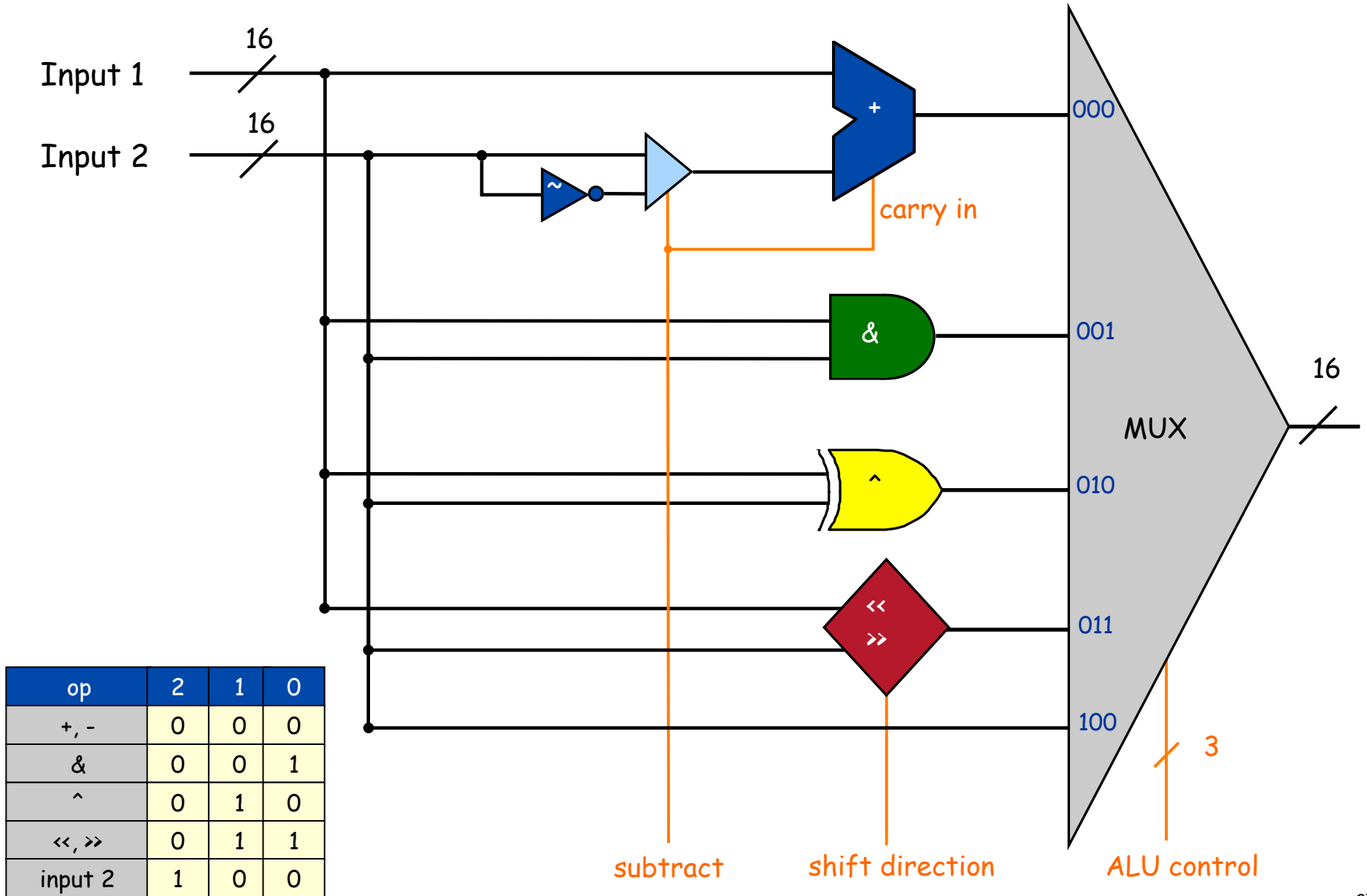
 
# Main Memory


TOY main memory: 256 x 16-bit register file.


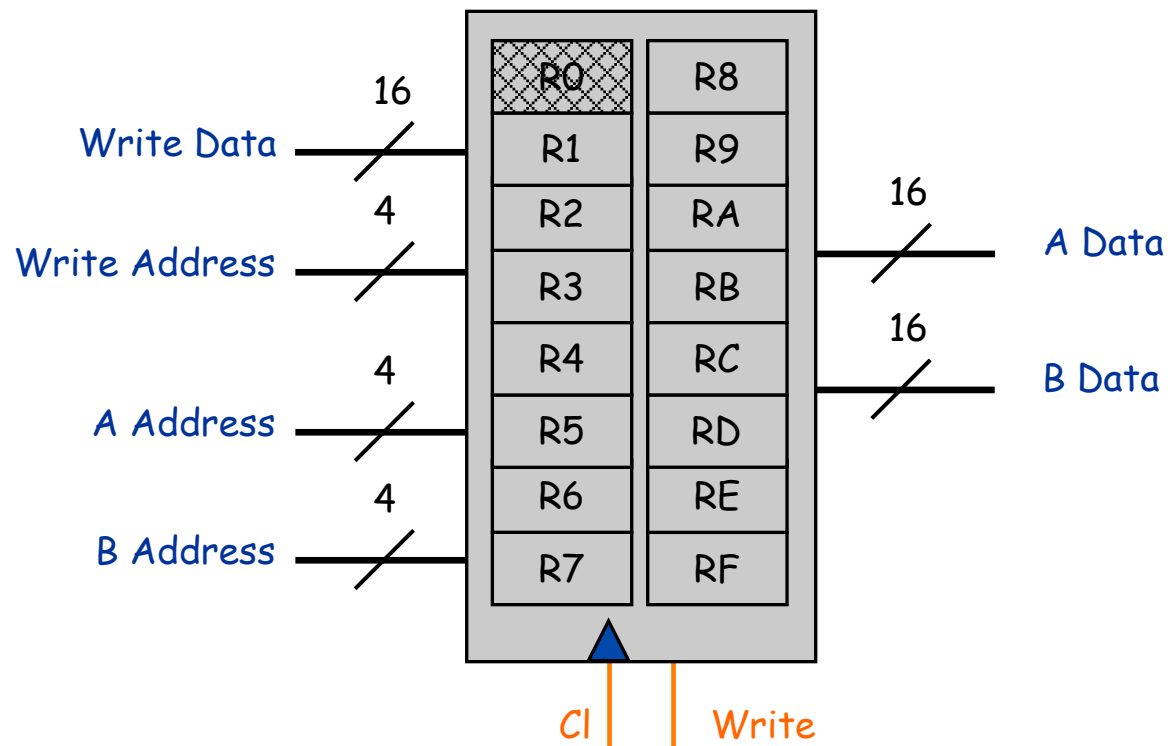
# Registers

TOY registers: fancy 16 x 16-bit register file.

- Want to be able to read two registers, and write to a third in the same instructions:  $R1 \leftarrow R2 + R3$ .
- 3 address inputs, 1 data input, 2 data outputs.
- Add decoders and muxes for additional ports.



# Designing a Processor

## How to build a microprocessor?

- Develop instruction set architecture (ISA).
  - 16-bit words, 16 TOY machine instructions
- Determine major components.
  - ALU, memory, registers, program counter
- ➔ ▪ Determine datapath requirements.
  - "flow" of bits
- Establish clocking methodology.
  - 2-cycle design: fetch, execute
- Analyze how to implement each instruction.
  - determine settings of control signals


# Datapath and Control

## Datapath.

- Layout and interconnection of components.
- Must accommodate all instruction types.
 
## Control.

- Choreographs the "flow" of information on the datapath.
- Depending on instruction, different control wires are turned on.




# Datapath and Control

## Datapath.

- Layout and interconnection of components.
- Must accommodate all instruction types.

 
## Control.

- Choreographs the "flow" of information on the datapath.
- Depending on instruction, different control wires are turned on.






MAIN MEMORY (16 10-BIT WORDS)

 


REGISTER INPUT MUX

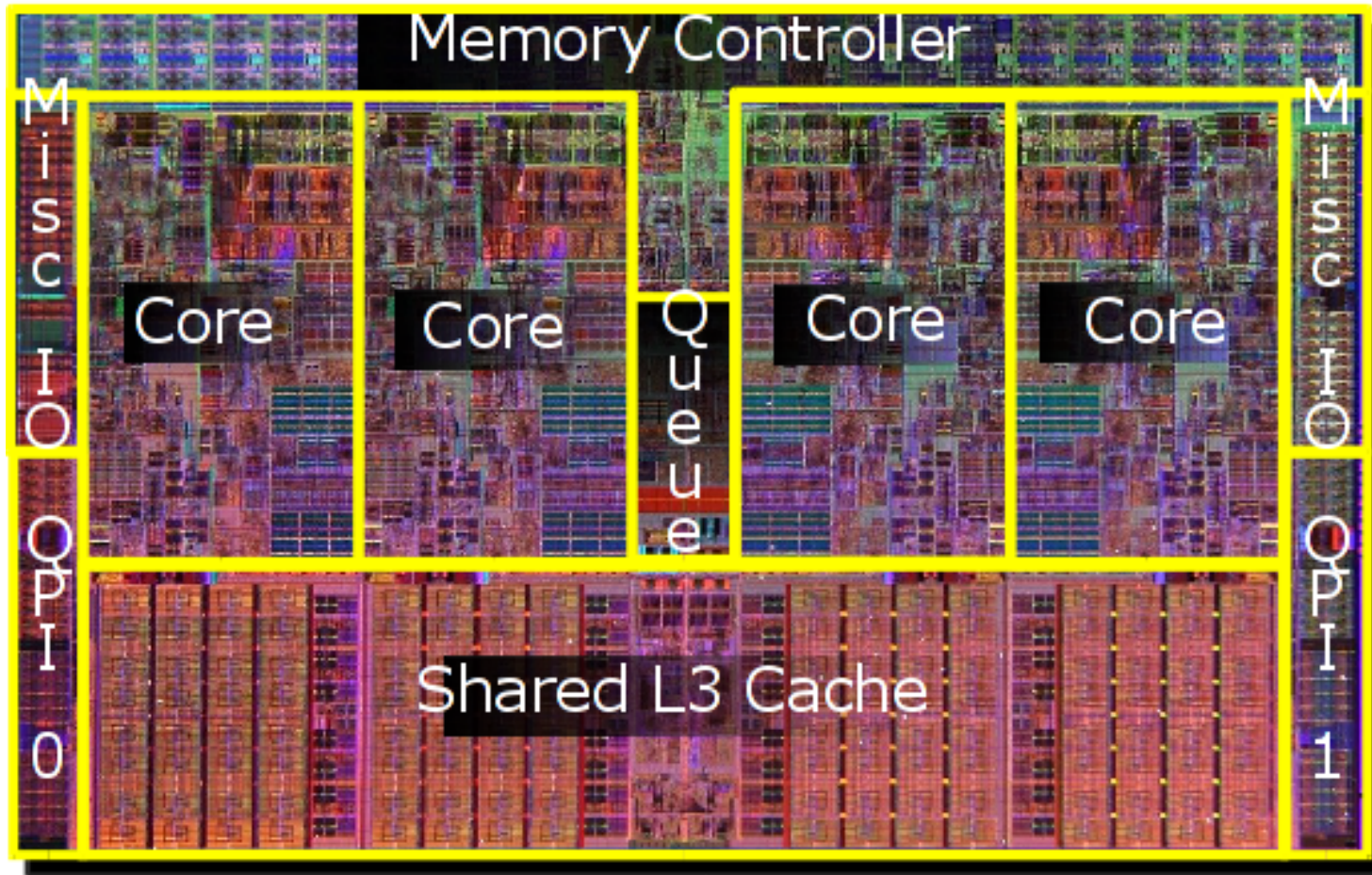
# Real Microprocessor Chip (Intel Nehalem)



# The TOY Datapath

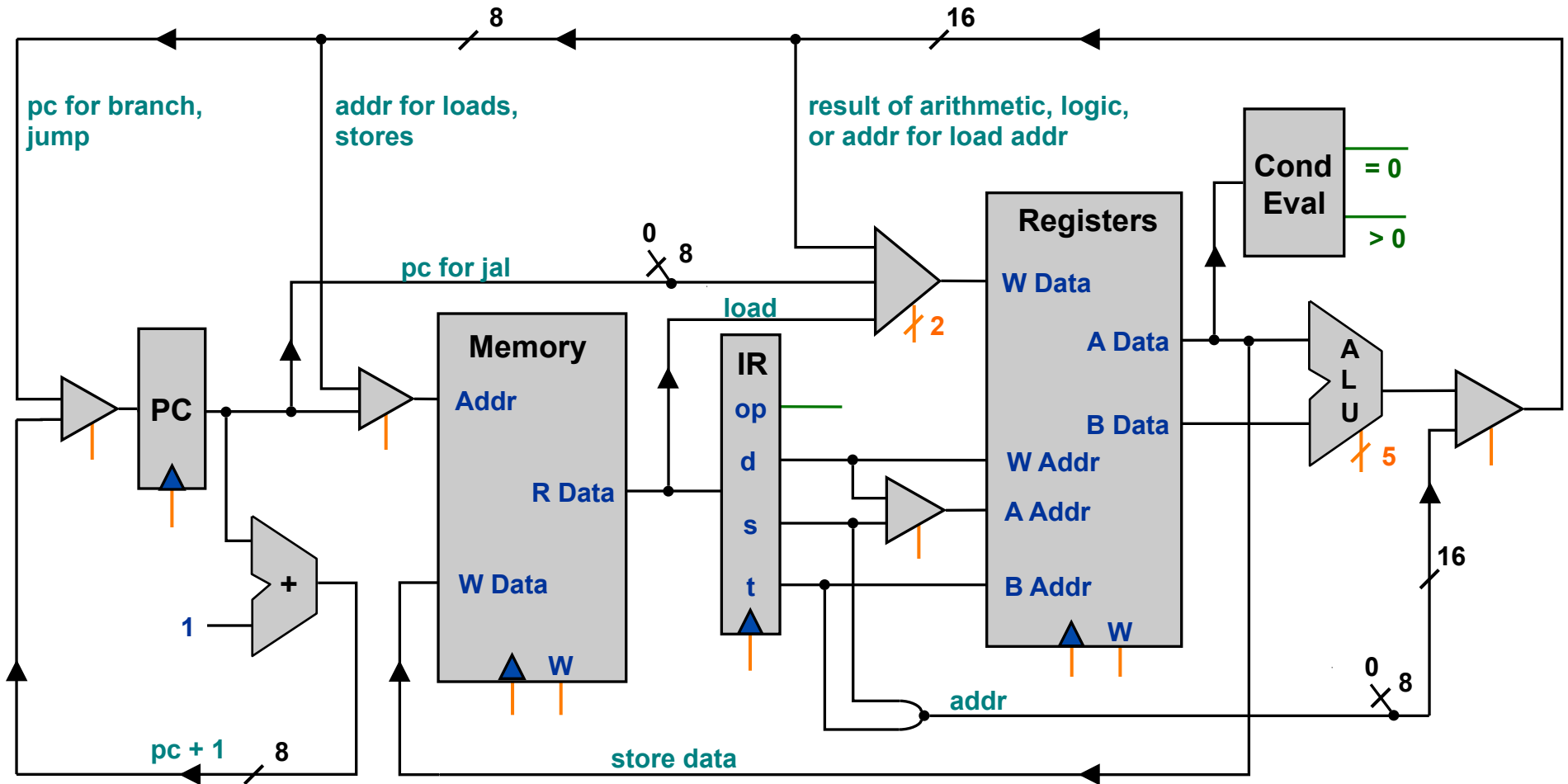

# The TOY Datapath: Add

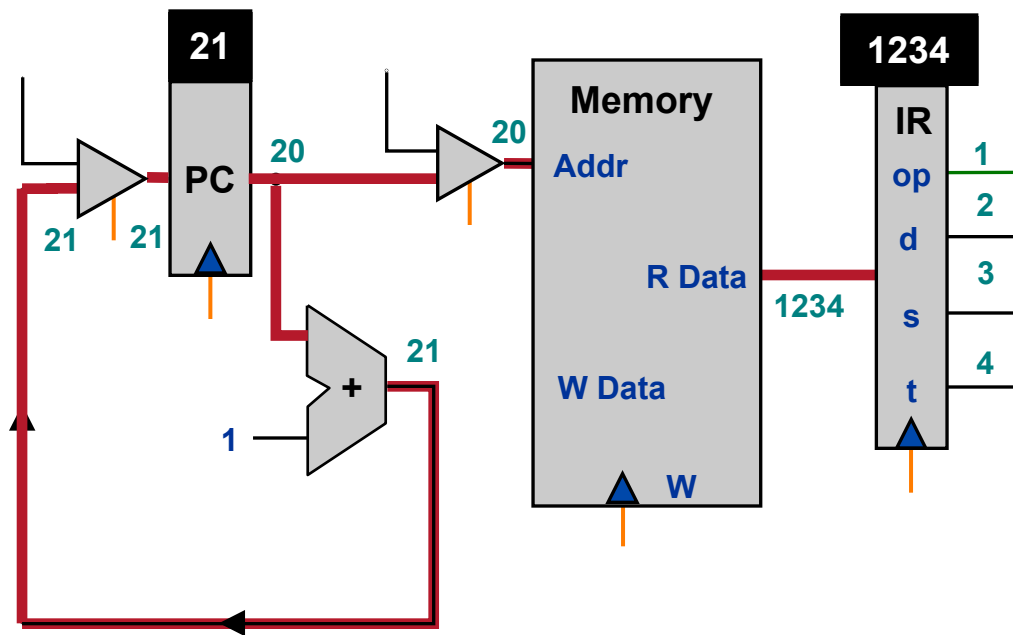

Before fetch:


pc = 20, mem[20] = 1234

After fetch:

pc = 21

IR = 1234: R[2] ← R[3] + R[4]

# The TOY Datapath: Add

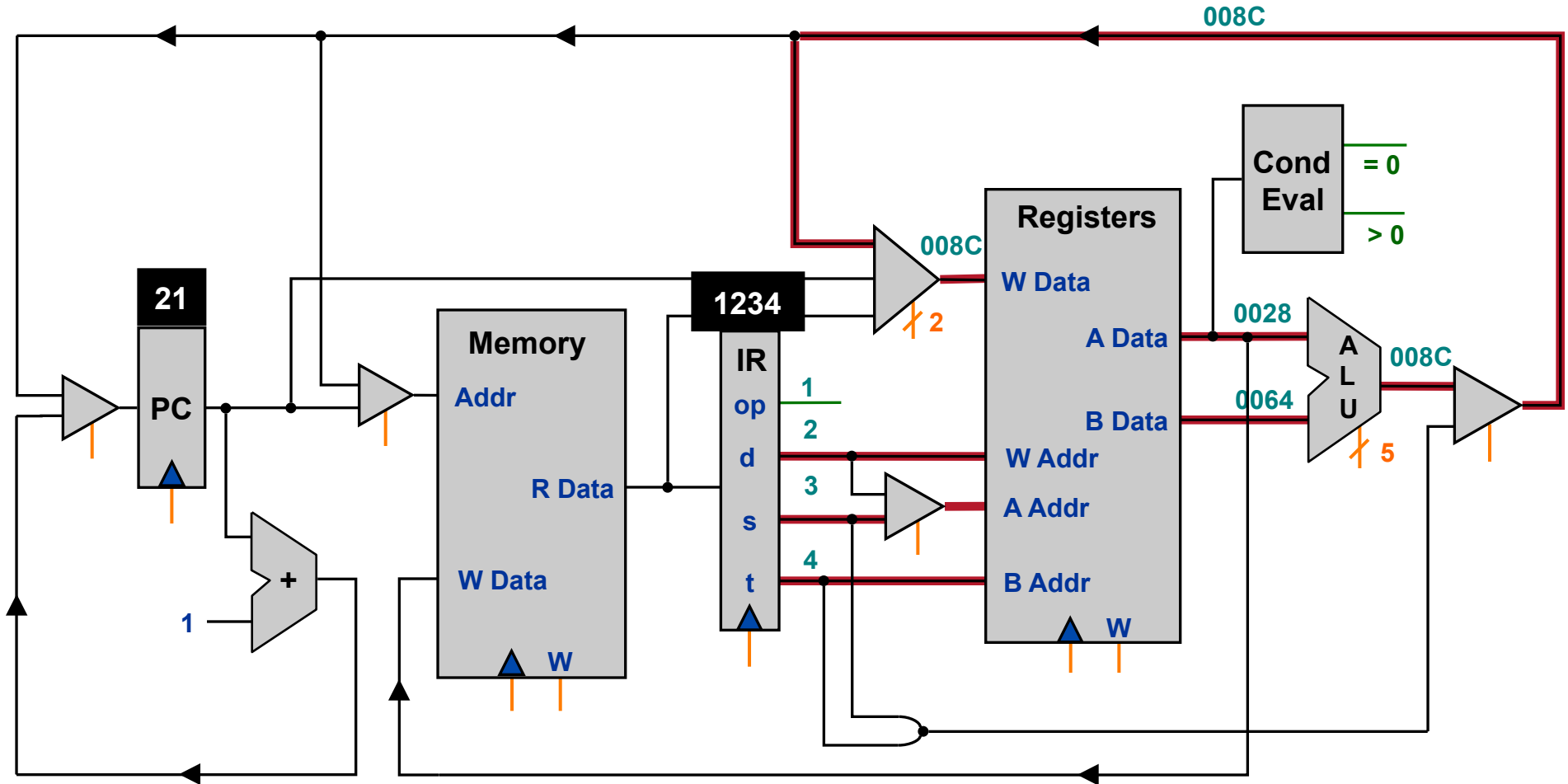

Before execute:

pc = 21

IR = 1234: R[2] ← R[3] + R[4]


R[3] = 0028, R[4] = 0064

After execute:

pc = 21

R[2] = 008C

# Do Try This At Home

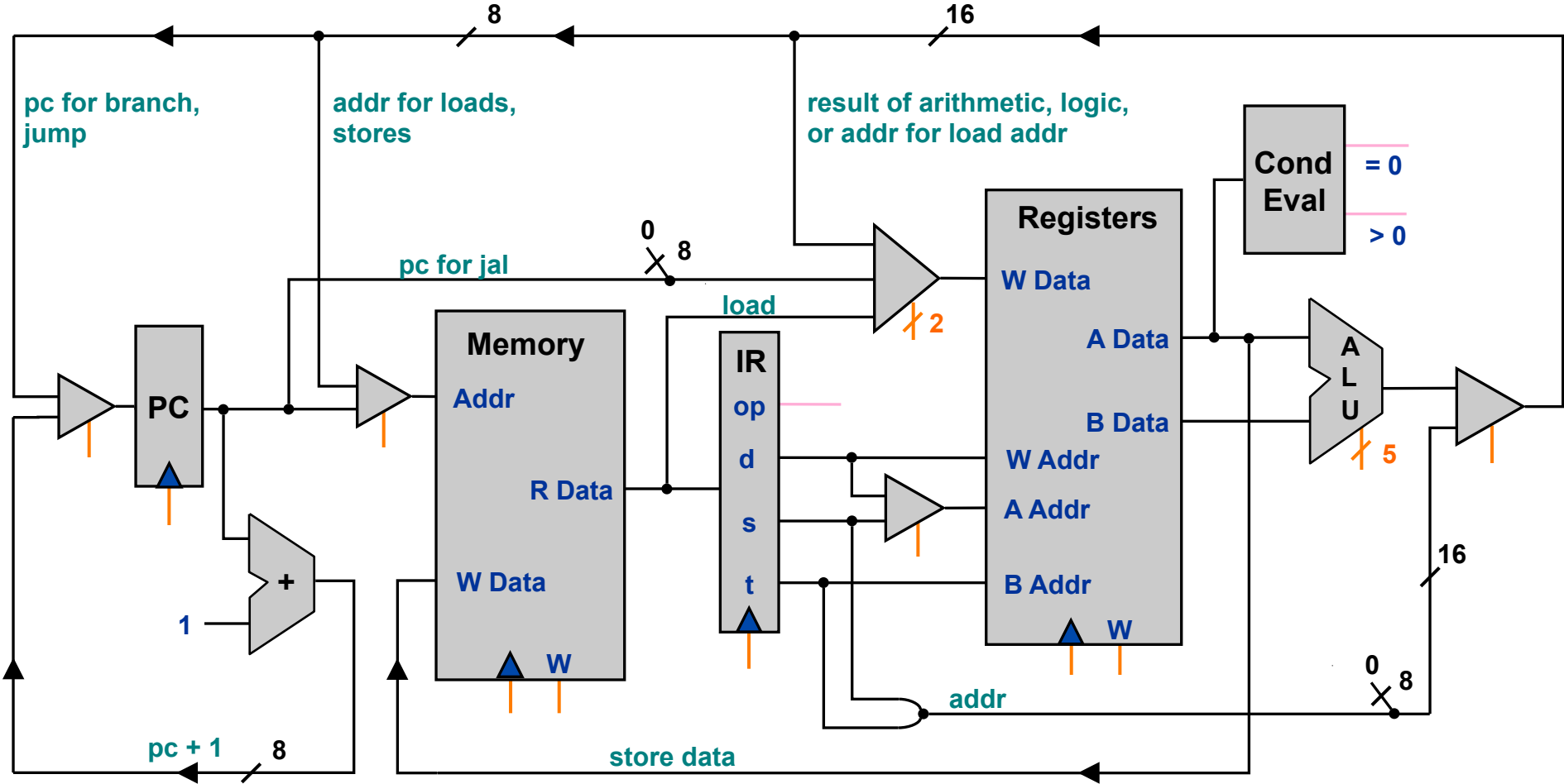

Trace the flow of some other instructions through the datapath picture.

# Designing a Processor



## How to build a microprocessor?

- Develop instruction set architecture (ISA).
  - 16-bit words, 16 TOY machine instructions
- Determine major components.
  - ALU, memory, registers, program counter
- Determine datapath requirements.
  - "flow" of bits
- ➔ ▪ Establish clocking methodology.
  - 2-cycle design: fetch, execute
- Analyze how to implement each instruction.
  - determine settings of control signals
  
# Clocking Methodology

Two cycle design (fetch and execute).

- Use 1-bit counter to distinguish between 2 cycles.
- Use two cycles since fetch and execute phases each access memory and alter program counter.






# Clocking Methodology

4 distinguishable epochs.

- During fetch phase.
- At very end of fetch phase.
- During execute phase.
- At very end of execute phase.

Ex: can only write at very end of execute phase.

- $R1 \leftarrow R1 + R1$

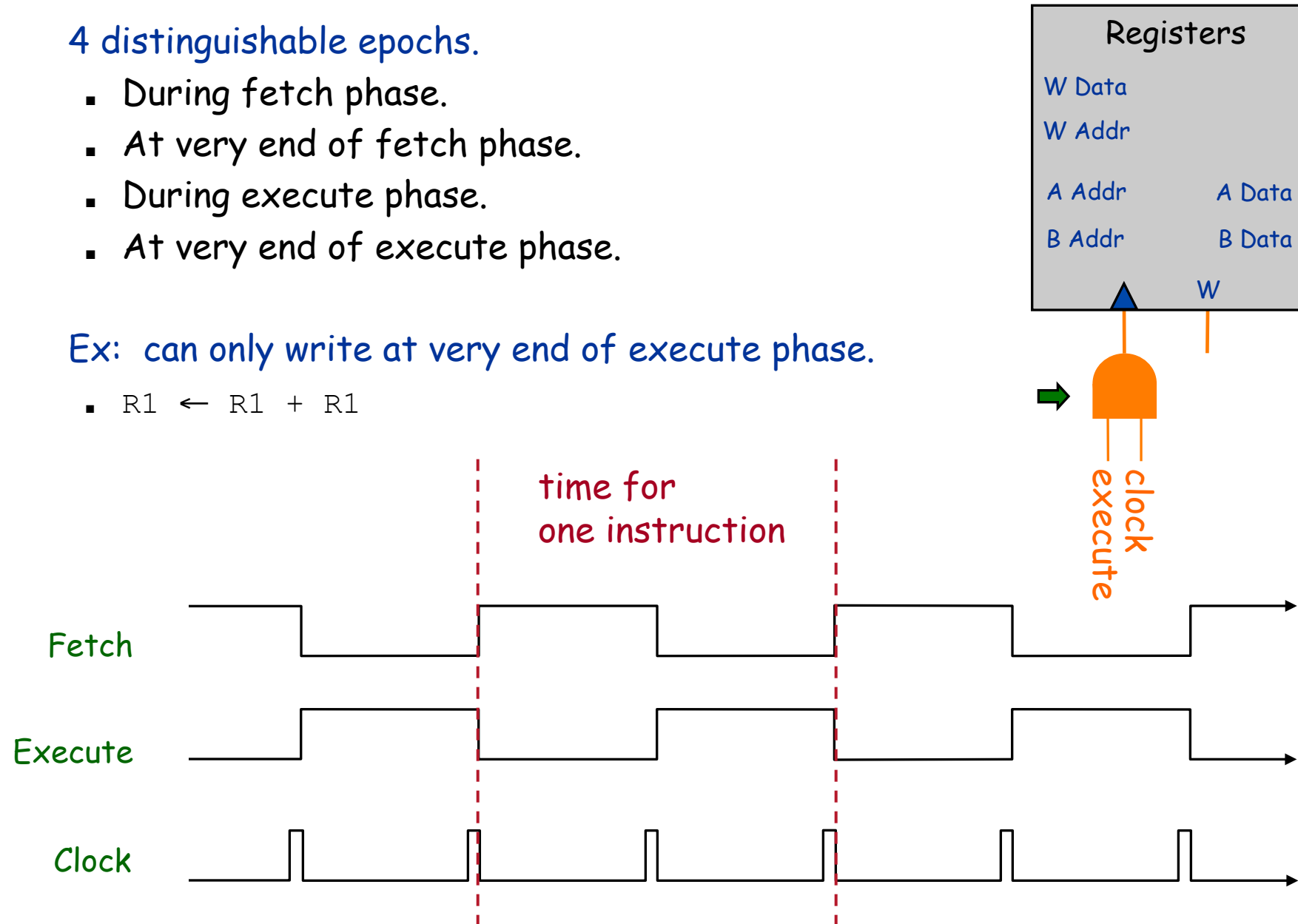

# Designing a Processor


## How to build a microprocessor?

- Develop instruction set architecture (ISA).
  - 16-bit words, 16 TOY machine instructions
- Determine major components.
  - ALU, memory, registers, program counter
- Determine datapath requirements.
  - "flow" of bits
- Establish clocking methodology.
  - 2-cycle design: fetch, execute
- ➔ ▪ Analyze how to implement each instruction.
  - determine settings of control signals
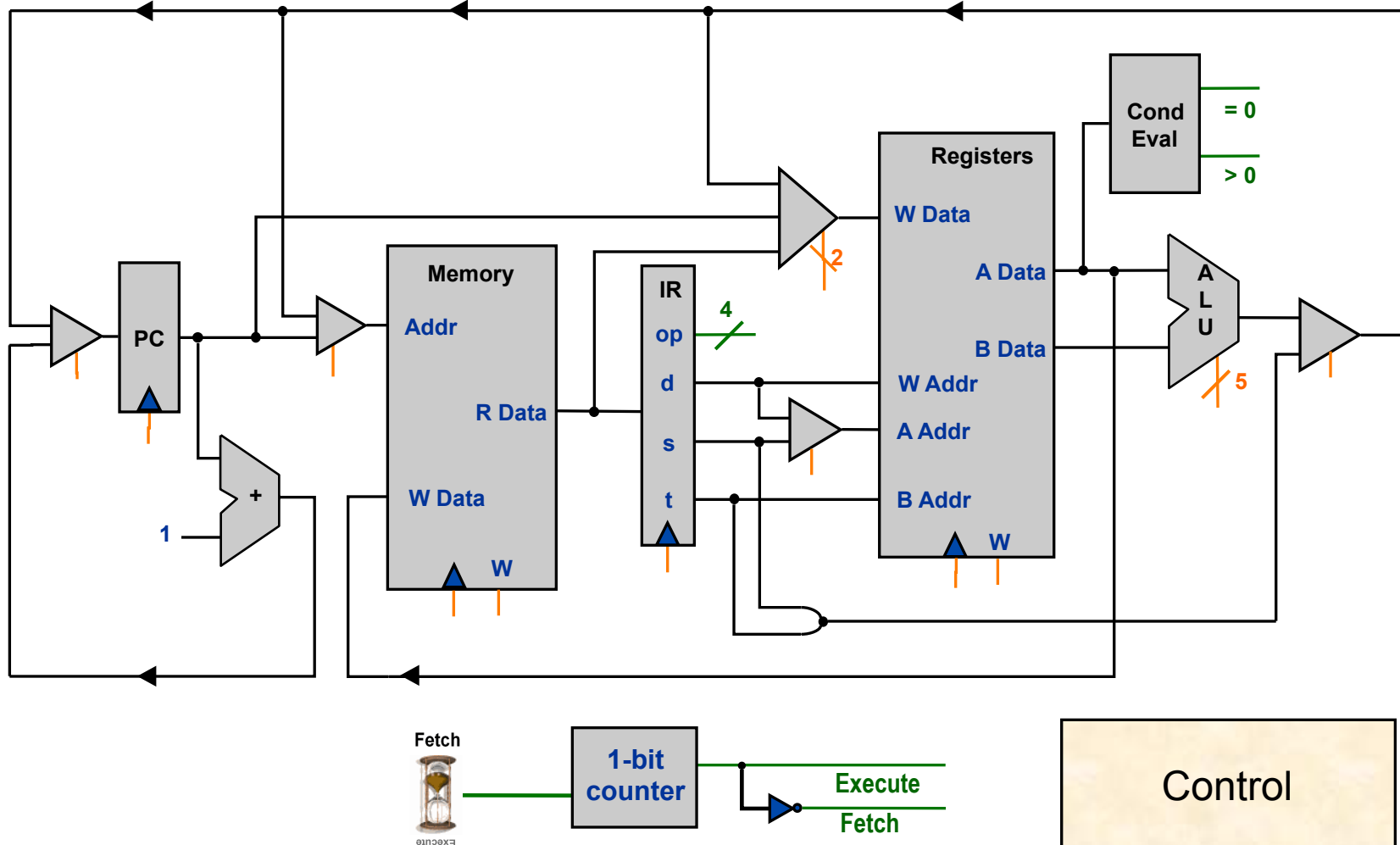
# Control

Control: controls components, enables connections.


- Input: opcode, clock, conditional evaluation. (green)
- Output: control wires. (orange)



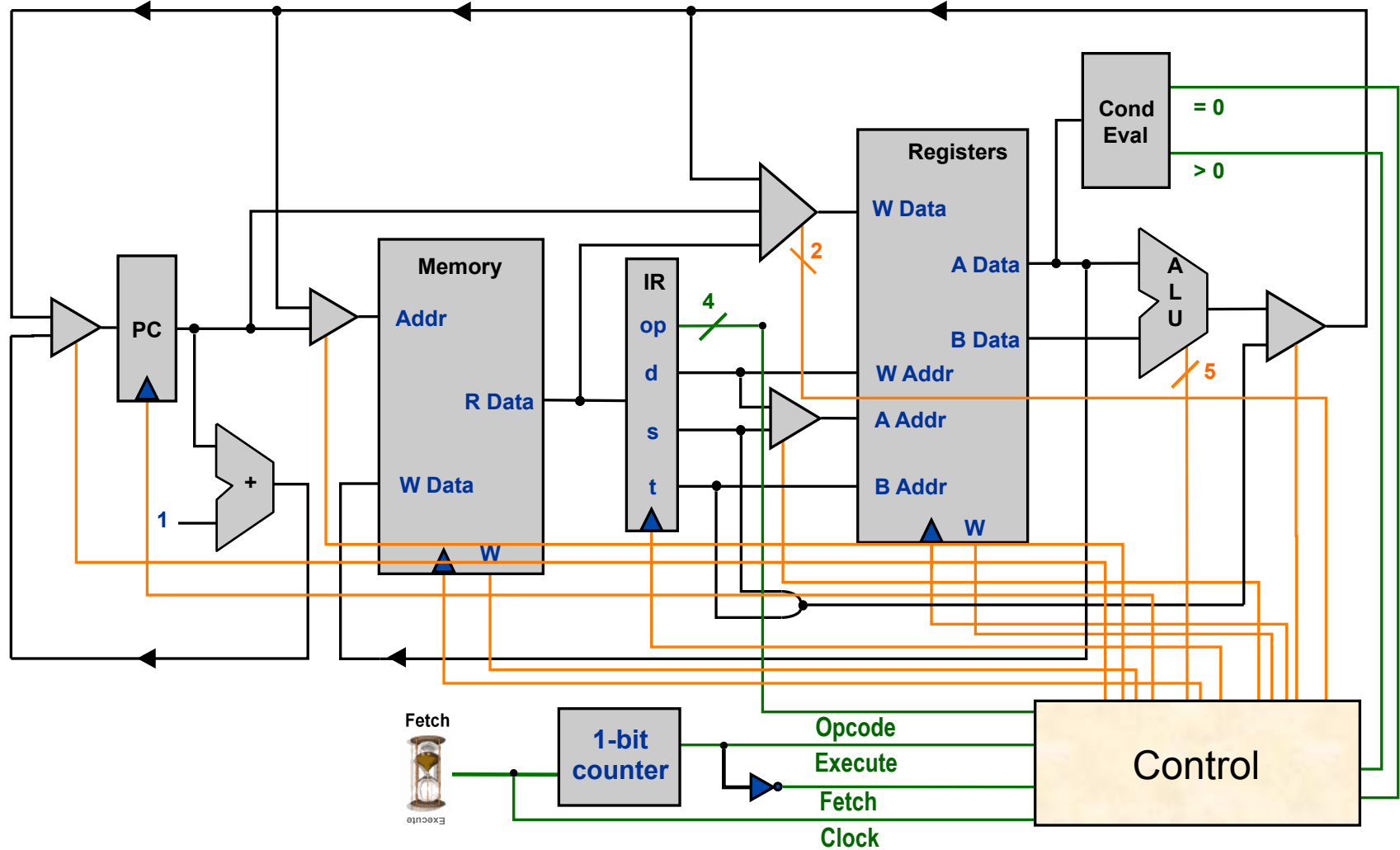
# Control

Control: controls components, enables connections.


- Input: opcode, clock, conditional evaluation. (green)
- Output: control wires. (orange)




# Implementation of Control

 


# Implementation of Control: Store

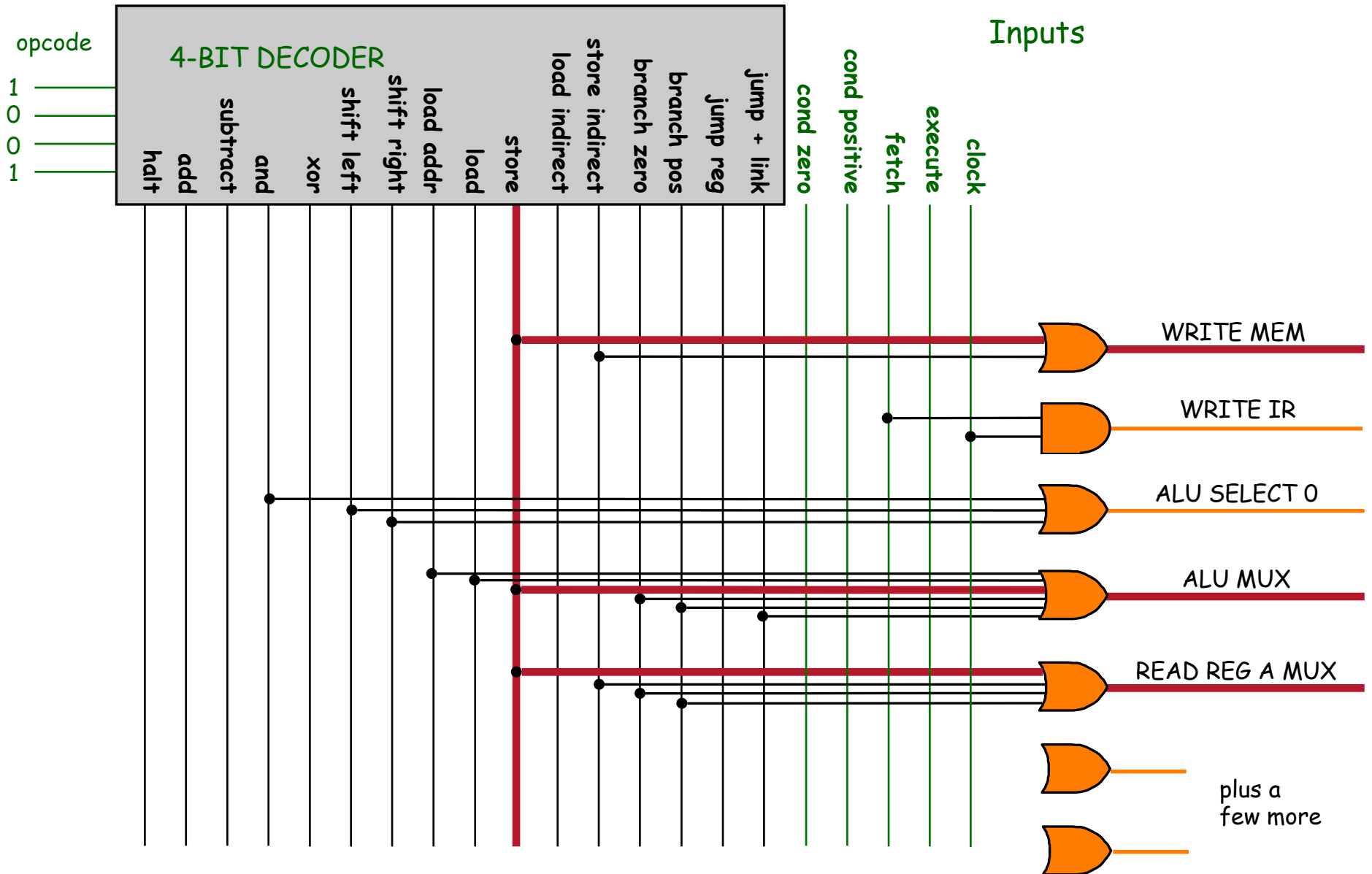


# Control: Execute Phase of Store

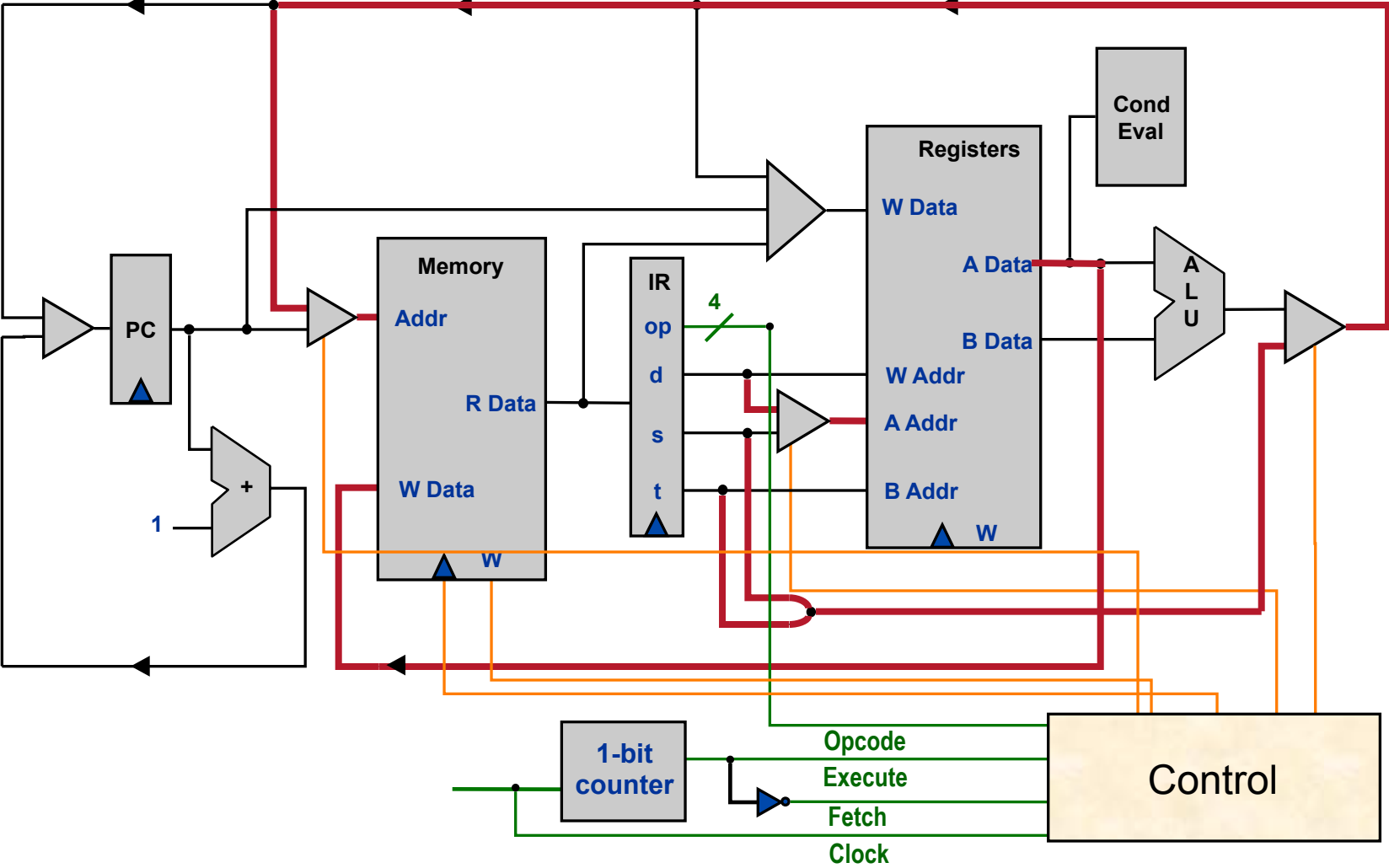

# Stand-Alone Registers

 

Instruction Register

 

Program Counter



# Pipelining

## Pipelining.

- At any instant, processor is either fetching instructions or executing them (and so half of circuitry is idle).
- Why not fetch next instruction while current instruction is executing?
  - Analogy: washer / dryer.


## Issues.

- Jump and branch instructions change PC.
  - "Prefetch" next instruction.
- Fetch and execute cycles may need to access same memory.
  - Solution: use two memory "caches".







## Result.

- Better utilization of hardware.
- Can double speed of processor.

# Goodbye, TOY

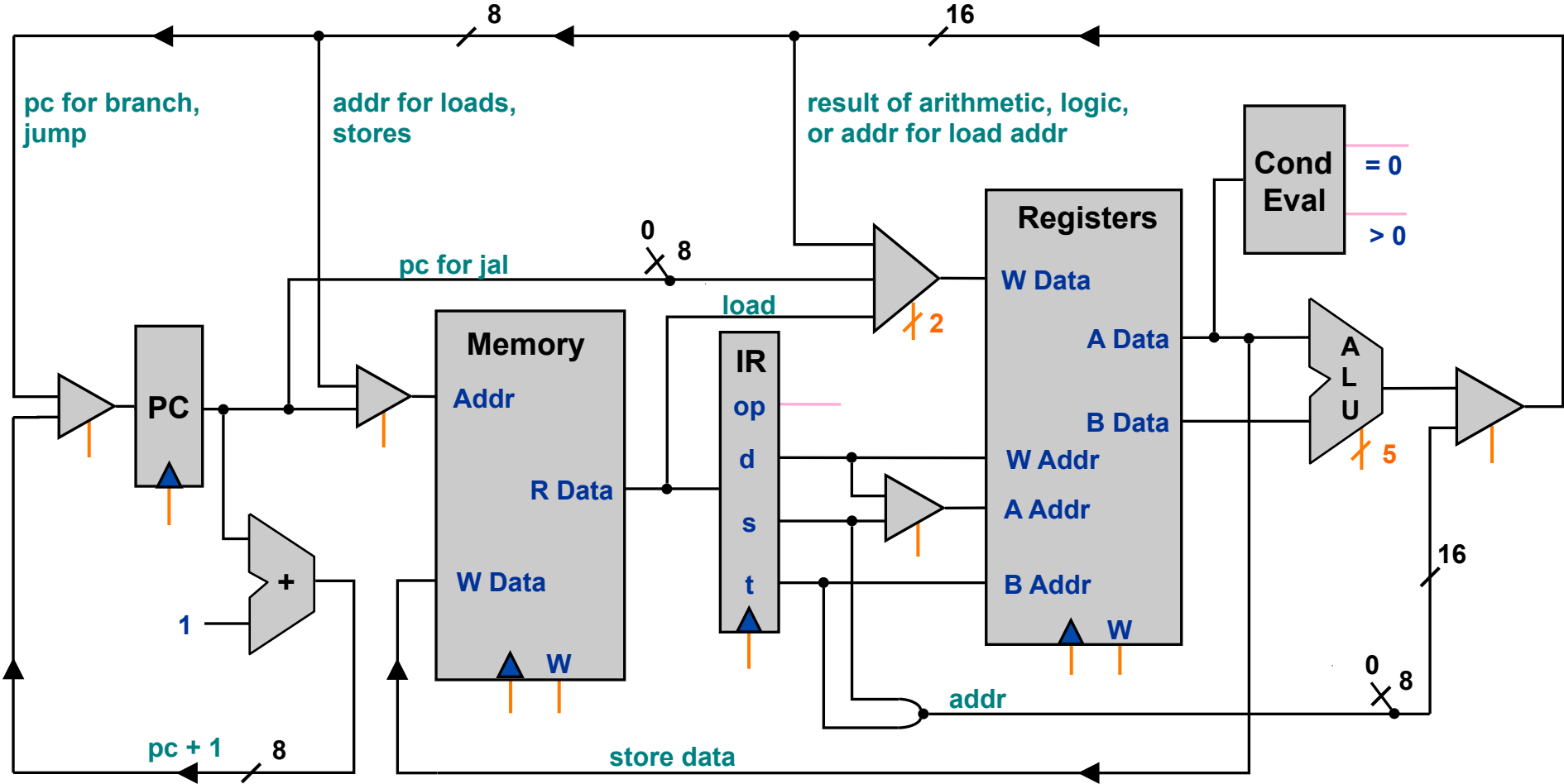

## The final secret

      

All three of our logic primitives can be made using a *single*\* type of electronic primitive: the *transistor*!

\*not counting the passive resistors