 


CS 126 Lecture A4: Sequential Circuits

Midterm Statistics



Outline

- **Introduction**
- An S-R Flip-flop
- More flip-flops
- Registers and register files
- Counters
- Conclusions



Where We Are At

- We have learned the abstract **interface** presented by a machine: the instruction set architecture
- What we are learning: the **implementation** behind the interface:
 - ~~Start with switching devices (such as transistors)~~
 - ~~Build logic gates with transistors~~
 - ~~Build combinational circuit (memory-less) devices using gates~~
 - **Today: build sequential circuit (memory) devices**
 - Thursday: glue these devices into a computer

Memory-less Devices vs. Devices with Memory

- What we we have learned in the last lecture
 - Devices that can carry out one step of operation
- What they can't do
 - “Remember” history of operations
 - Carry out a sequence of operations in which later operations depend on results of previous ones

Combinational vs. Sequential Circuits

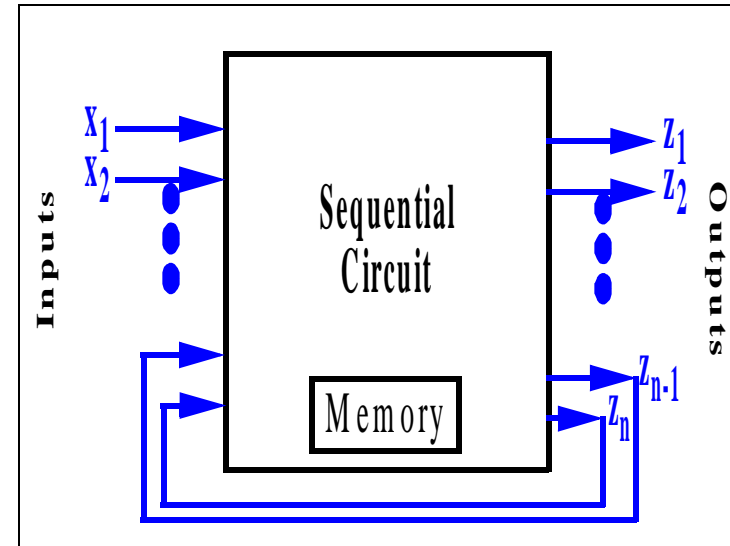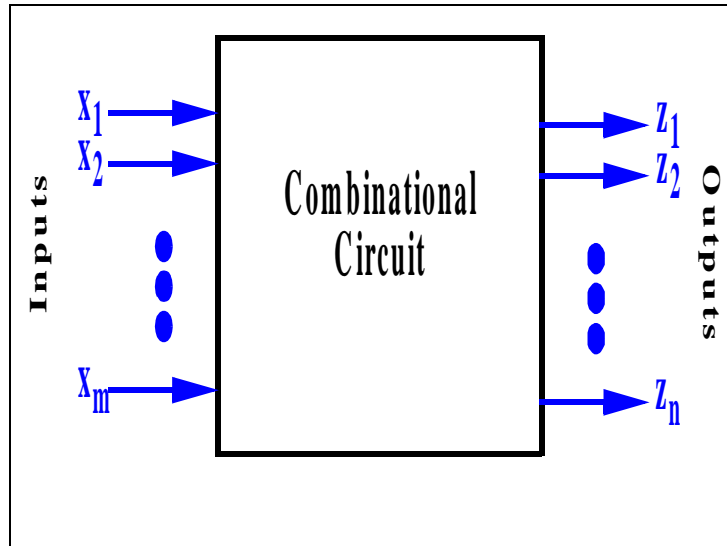


- Combinational circuits
 - Outputs determined solely by inputs
- Sequential Circuits
 - Characterized by feedbacks
 - Outputs determined by inputs and previous outputs

Outline


- Introduction
- **An S-R Flip-flop**
- More flip-flops
- Registers and register files
- Counters
- Conclusions

Set-Reset Flip-flop

 

- A flip-flop
 - A smallest sequential circuit
 - Can “remember” a bit of information
- An S-R flip-flop
 - Pulse on Set (S) line turns flip-flop on
 - Pulse on Reset (R) line turns flip-flop off
 - If $S=R=0$, nothing happens
 - $S=R=1$ not allowed

Timing Diagram (for S-R Flip-flop)

 

- Because sequential circuits are functions of time, a timing diagram is one of the ways of describing them

Truth Table (for S-R Flip-flop)

previous state			next state
$S(t)$	$R(t)$	$Q(t)$	$Q(t + \epsilon)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	—
1	1	1	—

} inputs not allowed

- Previous states become “input variables” in truth table

Characteristic Equation (for S-R Flip-flop)


$$Q^+ = S + R'Q \quad (SR=0)$$

- An equation that expresses the next state of a flip-flop in terms of its present state and inputs (also called next state equations)
- Timing diagrams, truth tables, and next-state equations are important tools for understanding and constructing more sophisticated sequential circuits as well


Outline

- Introduction
- ~~An S-R Flip-flop~~
- **More flip-flops**
- Registers and memory
- Counters
- Conclusions


The Clock

 


A Clocked S-R Flip-flop

 

interface

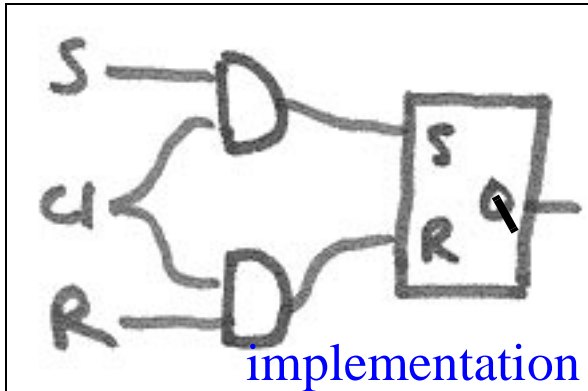


implementation

 


timing diagram

- In large sequential networks, there are many flip-flops
- Need to synchronize operations of different flip-flops
- Synchronization provided by a common clock (pulse)

A D Flip-flop

 

Interface

 


Implementation

On clock pulse

$D = 1$ set

$D = 0$ reset

Behavior of D Flip-flop

 


D	Q	Q^+
0	0	0
0	1	0
1	0	1
1	1	1

Truth Table

$$Q^+ = D$$

Characteristic Equation


Rising vs. Falling Edge

 


- So far, all the clocked flip-flops “flip-flop” on the rising edge of a clock signal
- When we cram a lot of actions into a single cycle, we sometimes need them to change state on the falling edge

Master-Slave D Flip-flop

 
On rising edge, input copied into master;
On falling edge, master copies data into slave.



Implementation

 

Interface

 


Timing Diagram

- Input sampled on rising edge, and must remain stable during the pulse, output changes on falling edge
- Question: why don't we just invert the clock using a NOT?
- Another type: "edge-triggered", allows input change during clock pulse

Outline

- Introduction
- ~~An S-R Flip-flop~~
- ~~More flip-flops~~
- **Registers and register files**
- Counters
- Conclusions

Stand-alone Register Interface

 

LOAD line (and clock)

controls when new values are loaded

Use registers for


PC

memory addresses


memory buffer

arithmetic

Stand-alone Register Implementation

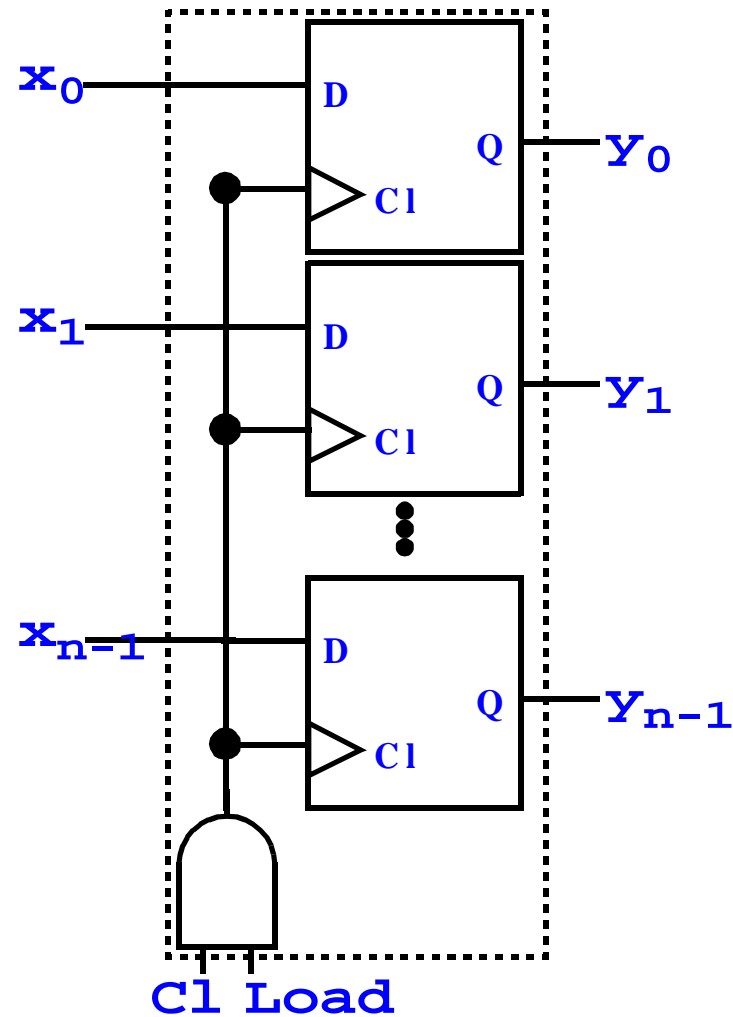


Register File Interface (Bits)

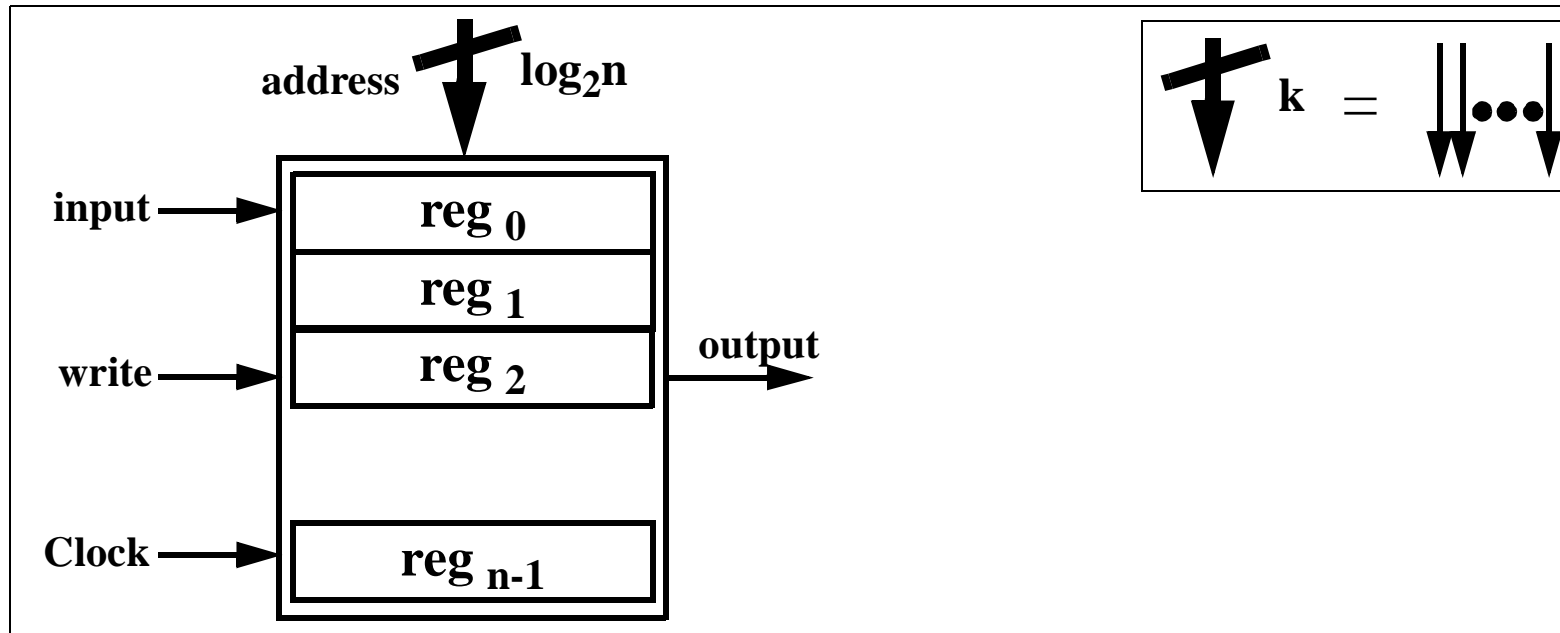


- bunch of bits to choose from
- “address” specifies which bit
- if “write” is 1, “input” gets copied into the chosen bit on clock pulse
- if “write” is 0, chosen bit appears on “output”

Register File Implementation (Bits)

 


- Decoder chooses exactly one bit to write into
- Multiplexer chooses exactly one bit to copy out

3-State Logic

 


- Can't connect outputs together (even if they are zero)
- Must use multiplexer (or its equivalent: **[3-state logic]**)

Register File Implementation 2 (Bits)

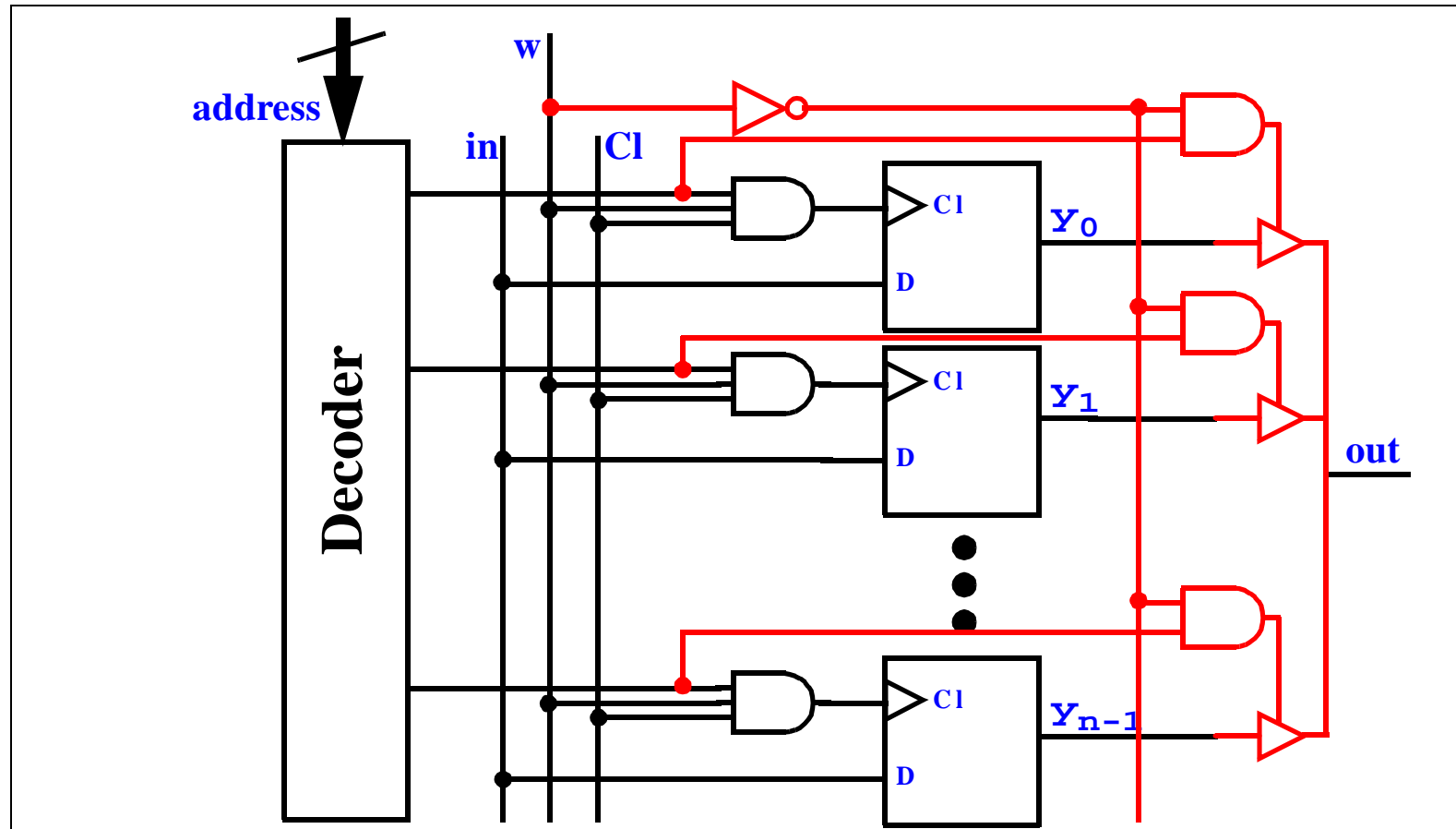


- Red things are new: replace MUX with 3-state logic
- Less Complex than MUX version

Register File Interface (Words)

 

- Register file of k -bit words
- **red** things show the differences between word case and bit case

Register File Implementation (Words)

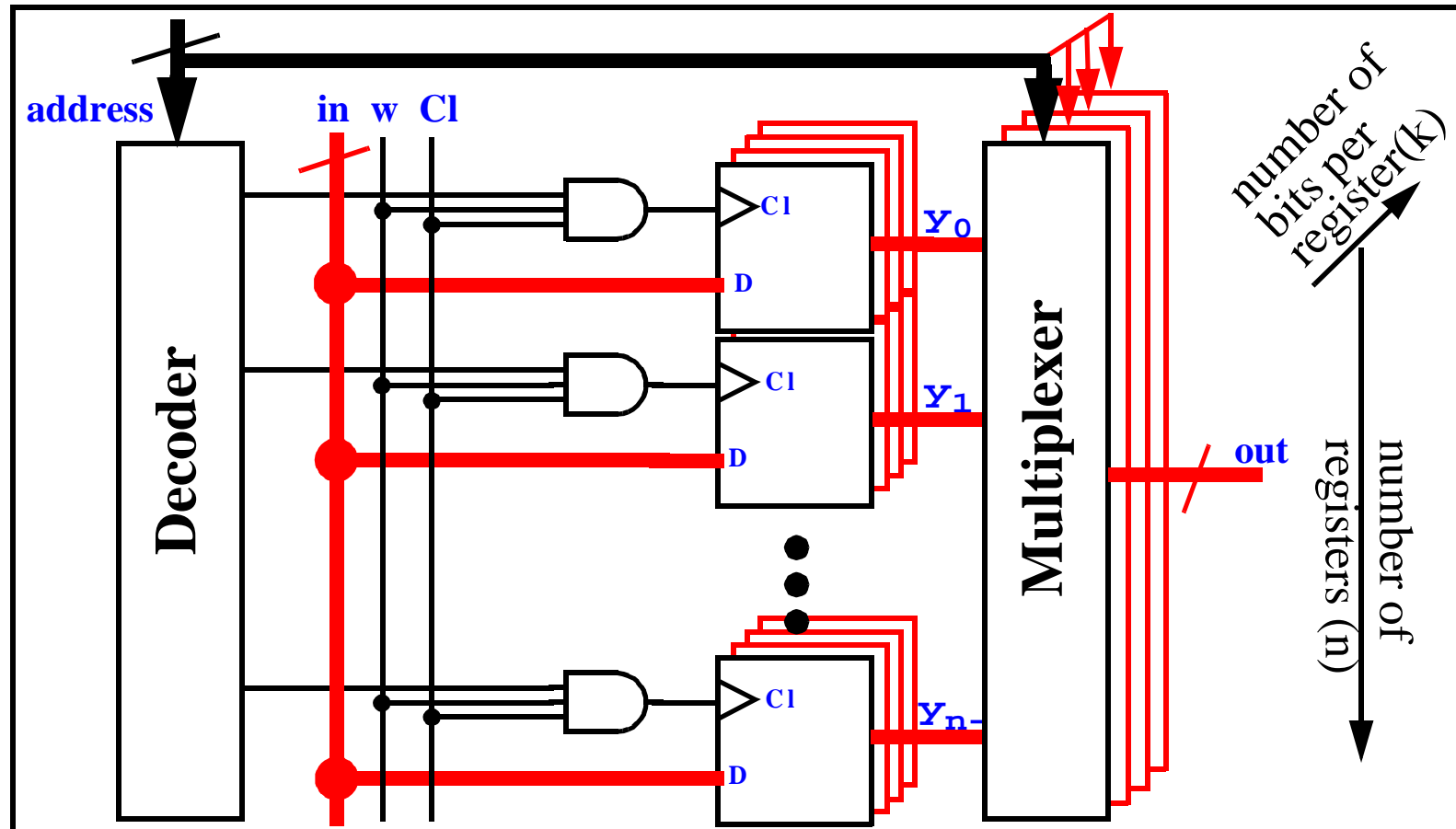


- **red** things show the differences between word case and bit case
- Multiply the number of flip-flops and MUXes by bits per register (k)
- May replace MUXes with 3-state logic (see previous slides)

Correting Lecture Notes in Your Course Reader

- Memory vs. register files
 - Lecture notes use the term “memory”
 - Meant to say register files (or SRAM)
 - DRAM made differently--no flip-flops
 - DRAM: one transistor per bit!
 - Much higher density than flip-flops, but slower

 Correting Lecture Notes in Your Course Reader (cont.)






- Can't connect outputs together (even if they are zero)
- Must use multiplexer (or its equivalent: **[3-state logic]**)

Outline



- Introduction
- ~~An S-R Flip-flop~~
- ~~More flip-flops~~
- ~~Registers and register files~~
- **Counters**
- Conclusions

1-Bit Counter

 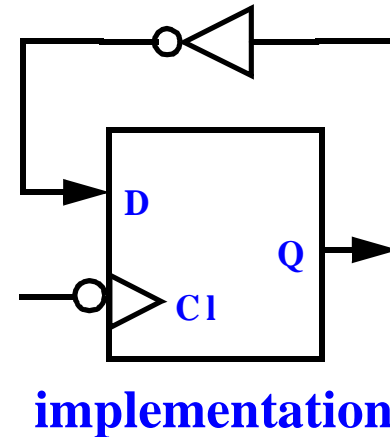 

- The behavior of a 1-bit binary counter is a clock whose cycle is twice as long as the input clock

N-bit Counter

 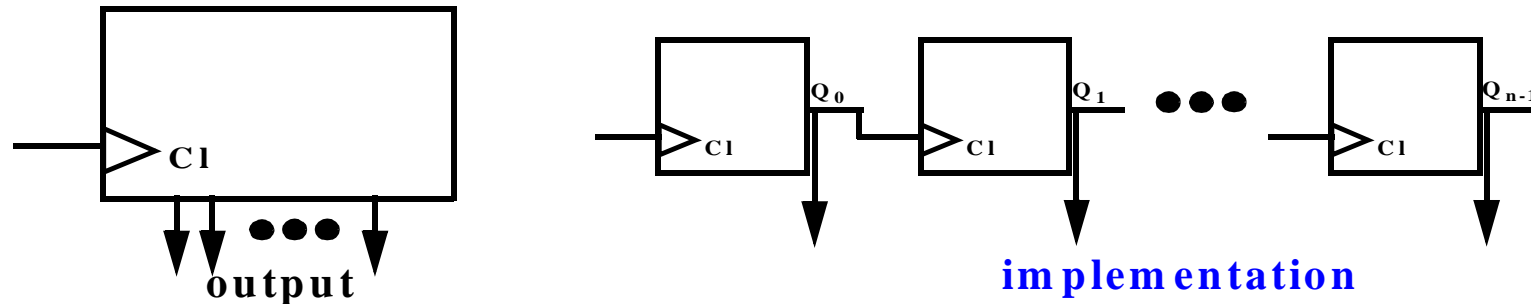


- n-bit counter: chaining n 1-bit counters together
- Recursive! An n-bit counter is made by gluing one extra bit to an (n-1) bit counter

Outline

- Introduction
- ~~An S-R Flip-flop~~
- ~~More flip-flops~~
- ~~Registers and register files~~
- ~~Counters~~
- **Conclusions**

High-Level View of Computer

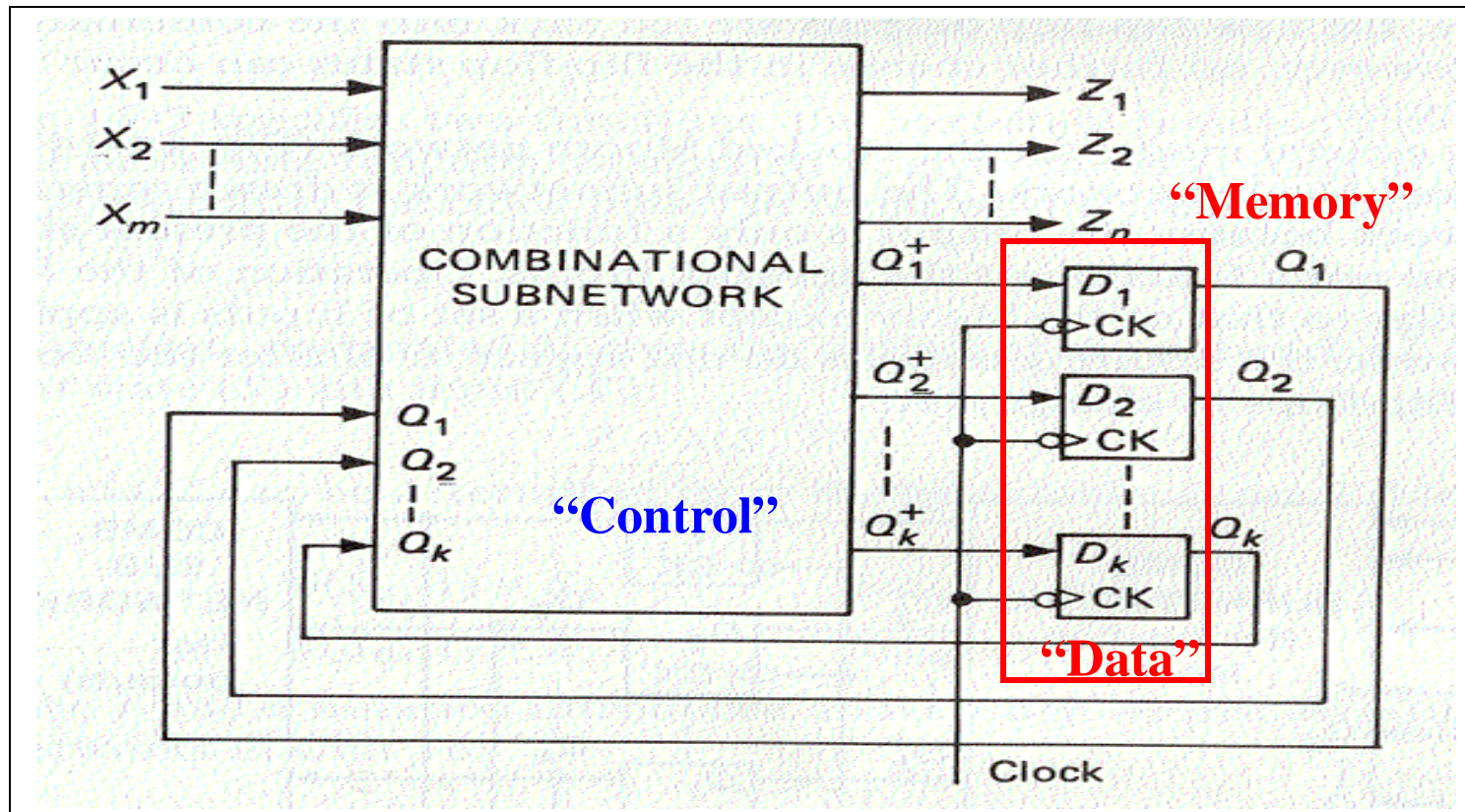

- Computer: “memory” state with feedback, clocked
- Each clock enables changes in memory state
- Combinational logic (topic of last lecture) employed to specify what changes to make in response to inputs and past history

What We Have Learned Today

- Flip-flops ([S-R, D], [unclocked, clocked, master-slave, edge triggered])
 - Their behavior (timing diagrams, truth tables, characteristic equations)
 - How they are made
- Some sequential devices (registers, register files, counters)
 - Their behavior
 - How they are made