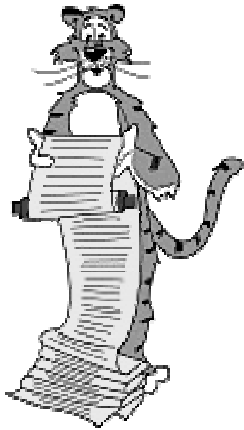


Lecture A3: Boolean Circuits



George Boole
(1815 – 1864)



Claude Shannon
(1916 – present)

Digital Circuits

What is a digital system?



Why digital systems?



Digital circuits and you.

- Computer microprocessors.
- Antilock brakes.
- VCR.
- Cell phone.

Digital Circuits

Logic gates.

- AND, OR, NOT.

Build combinational circuits from gates.

- No memory.
- Adder, multiplexer, decoder.

Lecture A4: build sequential circuits from gates.







- Memory.
- Flip-flop, register, counter.

Lecture A5: build general-purpose machine from circuits.

Logical Gates

Logical gates.

- A smallest useful circuit.

      

NOT


AND

OR

Multiway AND Gates

$AND(x_0, x_1, x_2, x_3, x_4, x_5, x_6, x_7)$.

- 1 if all inputs are 1.
- 0 otherwise.

 


6

Multiway OR Gates

$OR(x_0, x_1, x_2, x_3, x_4, x_5, x_6, x_7)$.

 - 1 if at least one input is 1.
- 0 otherwise.



7

Boolean Algebra

History.

- Developed by Boole to solve mathematical logic problems (1847).
- Shannon first applied to digital circuits (1939).

Basics.

- Boolean variable: value is 0 or 1.
- Boolean function: function whose inputs and outputs are Boolean variable.

Relationship to circuits.

- Boolean variables: signals.
- Boolean functions: circuits.


8

Truth Table

Truth table.

- Systematic method to describe Boolean function.
- One row for each possible input combination.
- N inputs $\Rightarrow 2^N$ rows.

AND Truth Table		
x	y	AND
0	0	0
0	1	0
1	0	0
1	1	1

 

9

Truth Table

Truth table.

- 16 Boolean functions of two variables.
- 2^{2^N} Boolean functions of N variables!

Truth Table for Some Functions of 2 Variables									
x	y	AND	NAND	OR	NOR	EQ	XOR	1	0
0	0	0	1	0	1	1	0	1	0
0	1	0	1	1	0	0	1	1	0
1	0	0	1	1	0	0	1	1	0
1	1	1	0	1	0	1	0	1	0

10

Truth Table

Truth table.

- 16 Boolean functions of 2 variables.
- 256 Boolean functions of 3 variables.
- 2^{2^N} Boolean functions of N variables!

Some Functions of 3 Variables							
x	y	z	AND	OR	MAJ	ODD	MUX
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	1	0	1	0
0	1	1	0	1	1	0	1
1	0	0	0	1	0	1	1
1	0	1	0	1	1	0	0
1	1	0	0	1	1	0	1
1	1	1	1	1	1	1	1

11

Universality of AND, OR, NOT

Any Boolean function can be expressed using AND, OR, NOT.

- "Universal."
- $XOR(x,y) = xy' + x'y$

Expressing XOR Using AND, OR, NOT							
x	y	x'	y'	x'y	xy'	x'y + xy'	XOR
0	0	1	1	0	0	0	0
0	1	1	0	1	0	1	1
1	0	0	1	0	1	1	1
1	1	0	0	0	0	0	0

Exercise: {AND, NOT}, {OR, NOT}, {NAND} are universal.

12

Sum-of-Products

Any Boolean function can be expressed using AND, OR, NOT.

- Sum-of-products is systematic procedure.
 - form AND term for each 1 in Boolean function
 - OR terms together


Expressing MAJ Using Sum-of-Products									
x	y	z	MAJ	x'yz	xy'z	xyz'	xyz	x'yz + xy'z + xyz' + xyz	
0	0	0	0	0	0	0	0	0	
0	0	1	0	0	0	0	0	0	
0	1	0	0	0	0	0	0	0	
0	1	1	1	1	0	0	0	1	
1	0	0	0	0	0	0	0	0	
1	0	1	1	0	1	0	0	1	
1	1	0	1	0	0	1	0	1	
1	1	1	1	0	0	0	1	1	

13

Translate Boolean Formula to Boolean Circuit

Use sum-of-products form.

- $XOR(x, y) = x'y + xy'$.

 


14

Translate Boolean Formula to Boolean Circuit

Use sum-of-products form.

 - $MAJ(x, y, z) = x'yz + xy'z + xyz' + xyz$.



15


Simplification Using Boolean Algebra

Many possible circuits for each Boolean function.


- Sum-of-products not optimal.



 - $MAJ(x, y, z) = x'yz + xy'z + xyz' + xyz = xy + yz + xz$.



size = 8, depth = 4

 

size = 4, depth = 3

16

Recipe for Making Combinational Circuit

Step 1.

- Represent input and output signals with Boolean variables.

Step 2.

- Construct truth table to carry out computation.

Step 3.

- Derive (simplified) Boolean expression using sum-of-products.

Step 4.

- Transform Boolean expression into circuit.

17

Let's Make an Adder Circuit

Goal: $x + y = z$.

Step 1.

- Represent input and output in binary.
- We build 4-bit adder: 8 inputs, 4 outputs.

	1	1	1	
	2	4	8	7
+	3	5	7	9
<hr/>				
	6	1	6	6

	1	1	0	
	0	0	1	0
+	0	1	1	1
<hr/>				
	1	0	0	1

	c_3	c_2	c_1	
	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
<hr/>				
	z_3	z_2	z_1	z_0

18

Let's Make an Adder Circuit

Goal: $x + y = z$.

Step 2.

- Build truth table.

	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
<hr/>				
	z_3	z_2	z_1	z_0

Adder Truth Table												
x_0	x_1	x_2	x_3	y_0	y_1	y_2	y_3	z_0	z_1	z_2	z_3	
0	0	0	0	0	0	0	0	0	0	0	0	
0	0	0	0	0	0	0	1	0	0	0	1	
0	0	0	0	0	0	1	0	0	0	1	0	
0	0	0	0	0	0	1	1	0	0	1	1	
0	0	0	0	0	1	0	0	0	1	0	0	
0	0	0	0	0	1	0	1	0	1	0	1	
.	
1	1	1	1	1	1	1	1	1	1	1	0	

$2^8 = 256$ rows!

19

Let's Make an Adder Circuit

Goal: $x + y = z$.

Step 2.

- Build truth table for carry bit.
- Build truth table for summand bit.

	c_3	c_2	c_1	$c_0 = 0$
	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
<hr/>				
	z_3	z_2	z_1	z_0

Carry Bit			
x_i	y_i	c_i	c_{i+1}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Summand Bit			
x_i	y_i	c_i	z_i
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

20

Let's Make an Adder Circuit

Goal: $x + y = z$.

Step 3.

- Derive (simplified) Boolean expression.

Carry Bit				
x_i	y_i	c_i	c_{i+1}	MAJ
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Summand Bit				
x_i	y_i	c_i	z_i	ODD
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


21

Let's Make an Adder Circuit

Goal: $x + y = z$.

Step 4.

 - Transform Boolean expression into circuit.




22

Let's Make an Adder Circuit

Goal: $x + y = z$.

Step 4.

 - Transform Boolean expression into circuit.



23

Lecture A1: Extra Slides



ODD Parity Circuit

$ODD(x, y, z)$.

- 1 if odd number of inputs are 1.
- 0 otherwise.


Expressing ODD Using Sum-of-Products									
x	y	z	ODD	$x'y'z$	$x'yz'$	$xy'z'$	xyz	$x'y'z + x'yz' + xy'z' + xyz$	
0	0	0	0	0	0	0	0	0	
0	0	1	1	1	0	0	0	1	
0	1	0	1	0	1	0	0	1	
0	1	1	0	0	0	0	0	0	
1	0	0	1	0	0	1	0	1	
1	0	1	0	0	0	0	0	0	
1	1	0	0	0	0	0	0	0	
1	1	1	1	0	0	0	1	1	

26

ODD Parity Circuit

ODD(x, y, z).

 - 1 if odd number of inputs are 1.
- 0 otherwise.





27

2-Bit Multiplexer Circuit

MUX(x₀, x₁, x₂, x₃, s₀, s₁).

  - x₀ if s₁ = 0, s₀ = 0.
- x₁ if s₁ = 0, s₀ = 1.
- x₂ if s₁ = 1, s₀ = 0.
- x₃ if s₁ = 1, s₀ = 1.



28

Decoder

N-bit decoder.

- N inputs.
- 2^N outputs.
- Exactly one of outputs is 1; rest are 0.
- Which one?



Ex.

- 3-bit decoder.
- Inputs: x₀, x₁, x₂.
- Outputs: Q₀, Q₁, Q₂, ..., Q₇.



I ₂	I ₁	I ₀	
0	1	1	11 ₂ = 3 ₁₀

Q ₇	Q ₆	Q ₅	Q ₄	Q ₃	Q ₂	Q ₁	Q ₀
0	0	0	0	1	0	0	0

29


3-Bit Decoder

DECODE(x, y, z).

  


30


Cheat Sheet

 


NOT

 


OR

 


AND

 

4-1 Multiplexer

 

3-8 Decoder

 

4-bit Adder