
 


Lecture A4: Sequential Circuits

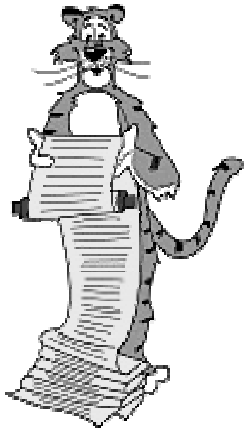

Architecture

Lecture A1 – A2: TOY machine.

Lecture A3: Boolean logic and combinational circuits.

- In principle, we could build TOY computer with one gigantic combinational circuit.



- Each circuit element used (at most) once.

Today.

- How to reuse circuit elements.
- How to store bits of information in memory.


Next time.

- Glue these components into a TOY computer.

Sequential vs. Combinational Circuits


Combinational circuits.

- Output determined solely by inputs.

 

Sequential circuits.

 - Feedback loop.
- Output determined by inputs and previous outputs.



Flip-Flop

Flip-flop.


- A smallest sequential circuit.
- Can "remember" one bit of information.

We will consider many flavors.


SR Flip-Flop

SR Flip-Flop.

 - Pulse on S (set) ⇒ line turns flip-flop on.
- Pulse on R (reset) ⇒ line turns flip-flop off.
- S = R = 0 ⇒ line
- S = R = 1 ⇒ not allowed



Implementation

 

Interface

5

Truth Table and Timing Diagram (for SR Flip-Flop)

Truth table.


- Values vary over time.
- S(t), R(t), Q(t) denote value at time t.

SR Flip Flop Truth Table			
S(t)	R(t)	Q(t)	Q(t+ε)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	
1	1	1	

Characteristic equation.

$$Q(t+\epsilon) = S(t) + R'(t)Q(t) \quad (SR = 0)$$

Sample timing diagram.

 


6

Clock

Clock.

 - Regular on-off pulse.
- Synchronize operations of different circuit elements.
- 800 MHz clock means 800 million pulses per second.




7


Clocked SR Flip-Flop

Clocked SR Flip-Flop.

 
- Like SR flip-flop but S and R only work if clock is on.



Implementation

 

Interface

 


8


Clocked D Flip-Flop

Clocked D Flip-Flop.

 
- On clock pulse: if D = 1, then set; if D = 0, then reset



Implementation

 

Interface

 


9


Master Slave Flip-Flop

Master-slave flip-flop (falling edge-trigger).

- Input can only change on falling edge.

 

Interface

 


10

Register File (bits)

Register file: n bits.

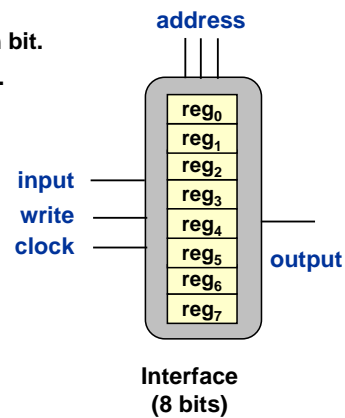- n bits to choose from.
- Address specifies which bit.
 - How many bits needed to specify address?
- If write = 1, input gets copied into chosen bit.
- If write = 0, chosen bit appears on output.




11

Register File (bits)

Register file: n bits.

 - Decoder writes input to address bit.
- Multiplexer copies address bit to output.




12

Register File (words)

Register file: n registers (words), k bits per register.

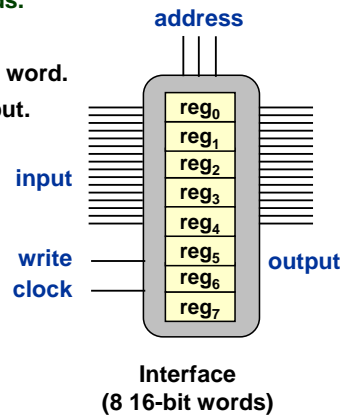- n k -bit words to choose from.
 - TOY main memory: 256 16-bit words.
 - TOY registers: 8 16-bit words.
 - Real computer: 500 million 64-bit words.
- Address specifies which word.
- If write = 1, input gets copied into chosen word.
- If write = 0, chosen word appears on output.




13

Register File (words)

Register file: n registers (words), k bits per register.

 - Single decoder writes k -bit input word to register.
- k multiplexers copy register contents to output.




14


1-Bit Counter

1-bit counter.

 
- "Clock" whose cycle is twice as long as input.



Implementation

 

Interface


 


15

N-Bit Counter


N-bit counter.

- Chain N 1-bit counters together.

  


16

Lecture A4: Extra Slides

 

Stand-Alone Register

4-bit register.

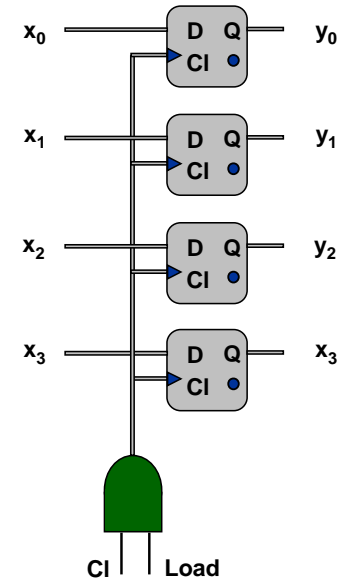

Cheat Sheet

