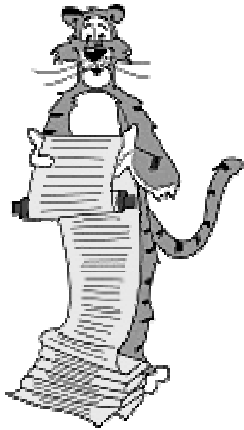


Lecture A4: Boolean Circuits



George Boole
(1815 – 1864)



Claude Shannon
(1916 – 2001)

Architecture

Lecture A1 – A3.


- TOY machine.

Lecture A4 – A5.

- Digital circuits.

Lecture A6.

- Putting it all together.

 

Digital Circuits

What is a digital system?



Why digital systems?



Basic abstraction.

- On, off.
- Switch that can turn something on or off.


Digital circuits and you.

- **Computer microprocessors.**
- Antilock brakes.
- VCR.
- Cell phone.

Abstract Switch

Abstract switch.

 - Electrical (transistor).
- Electro-mechanical (relay).
- Hydraulic (water valve).




Hydraulic valve.

- 3 connections: input, output, control.
- Pressure on control pushes on a piston that turns on water flow from input to output.
 - valve is always entirely open or closed (digital)
 - amplification, restoring logic design
- Control pipe affects output pipe, but output does not affect control.
 - establishes forward flow of information over time

Computer

Hydraulic computer. (The Pattern on the Stone)

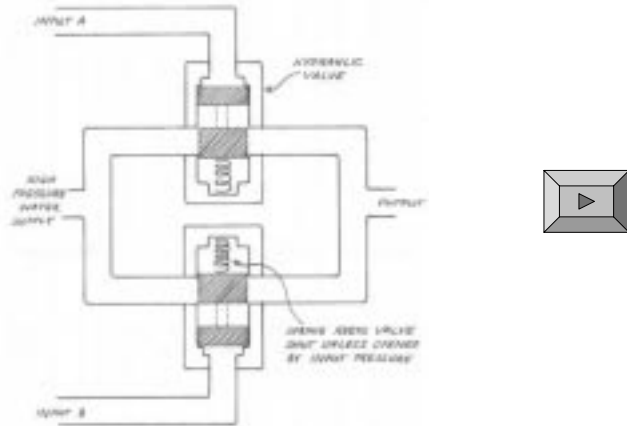- Build computer by connecting hydraulic valves and pipe.



Hydraulic OR Gate

5

Computer

Electrical computer.

- Same fundamental abstraction.


	Hydraulic Computer	Electrical Computer
Connector	Pipe	Wire
Signal	Water pressure	Voltage
Switch	Hydraulic valve	Metal-oxide transistor

6

Logic Gates

Logical gates.

- Fundamental building blocks.

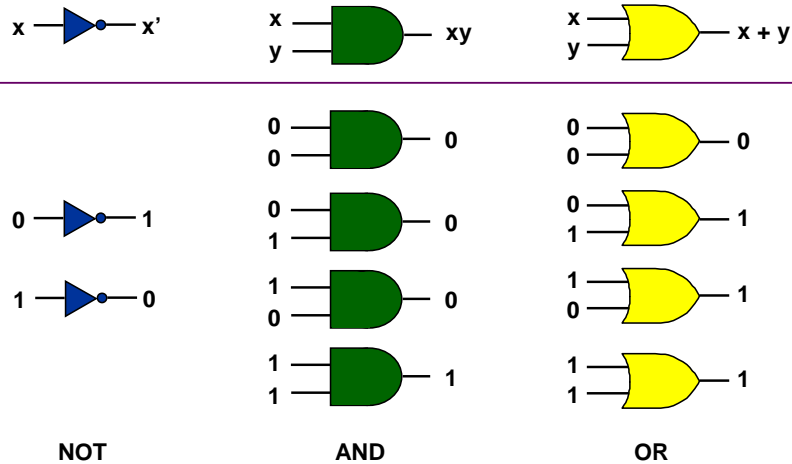


7

Multiway AND Gates

$AND(x_0, x_1, x_2, x_3, x_4, x_5, x_6, x_7)$.

- 1 if all inputs are 1.
- 0 otherwise.

 


8

Multiway OR Gates

$OR(x_0, x_1, x_2, x_3, x_4, x_5, x_6, x_7)$.

 - 1 if at least one input is 1.
- 0 otherwise.



9

Boolean Algebra

History.


- Developed by Boole to solve mathematical logic problems (1847).
- Shannon first applied to digital circuits (1937).

Basics.

- Boolean variable: value is 0 or 1.
- Boolean function: function whose inputs and outputs are 0, 1.

Relationship to circuits.

 - Boolean variables: signals.
- Boolean functions: circuits.




10

Truth Table

Truth table.

- Systematic method to describe Boolean function.
- One row for each possible input combination.
- N inputs $\Rightarrow 2^N$ rows.

AND Truth Table		
x	y	AND
0	0	0
0	1	0
1	0	0
1	1	1

 

11

Truth Table

Truth table.

- 16 Boolean functions of 2 variables.
- every 4-bit value represents one

Truth Table for All Boolean Functions of 2 Variables									
x	y	ZERO	AND		X		Y	XOR	OR
0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1

Truth Table for All Boolean Functions of 2 Variables									
x	y	NOR	EQ	Y'		X'		NAND	ONE
0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1

12

Truth Table

Truth table.

- 16 Boolean functions of 2 variables.
 - every 4-bit value represents one
- 256 Boolean functions of 3 variables.
 - every 8-bit value represents one
- 2^{2^N} Boolean functions of N variables!

Some Functions of 3 Variables							
x	y	z	AND	OR	MAJ	ODD	MUX
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	1	0	1	0
0	1	1	0	1	1	0	1
1	0	0	0	1	0	1	1
1	0	1	0	1	1	0	0
1	1	0	0	1	1	0	1
1	1	1	1	1	1	1	1

13

Universality of AND, OR, NOT

Any Boolean function can be expressed using AND, OR, NOT.

- "Universal."
- $XOR(x,y) = xy' + x'y$

Expressing XOR Using AND, OR, NOT							
x	y	x'	y'	x'y	xy'	x'y + xy'	XOR
0	0	1	1	0	0	0	0
0	1	1	0	1	0	1	1
1	0	0	1	0	1	1	1
1	1	0	0	0	0	0	0

Exercise: {AND, NOT}, {OR, NOT}, {NAND}, {AND, XOR} are universal.

14

Sum-of-Products

Any Boolean function can be expressed using AND, OR, NOT.

- Sum-of-products is systematic procedure.
 - form AND term for each 1 in Boolean function
 - OR terms together


Expressing MAJ Using Sum-of-Products								
x	y	z	MAJ	x'yz	xy'z	xyz'	xyz	x'yz + xy'z + xyz' + xyz
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0
0	1	1	1	1	0	0	0	1
1	0	0	0	0	0	0	0	0
1	0	1	1	1	0	1	0	1
1	1	0	1	1	0	0	1	1
1	1	1	1	1	0	0	1	1

15

Translate Boolean Formula to Boolean Circuit

Use sum-of-products form.

- $XOR(x, y) = xy' + x'y$.

 


16

Translate Boolean Formula to Boolean Circuit

Use sum-of-products form.

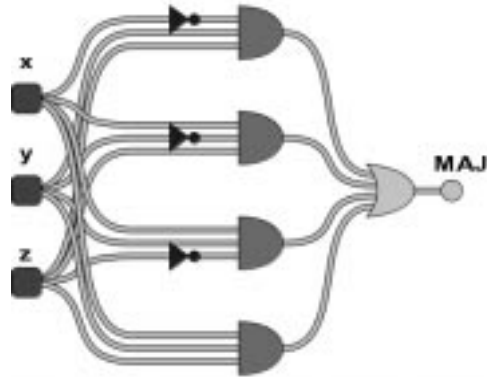- MAJ(x, y, z) = $x'yz + xy'z + xyz' + xyz$.



17


Simplification Using Boolean Algebra

Many possible circuits for each Boolean function.


- Sum-of-products not optimal.



 - MAJ(x, y, z) = $x'yz + xy'z + xyz' + xyz = xy + yz + xz$.



size = 8, depth = 4

 

size = 4, depth = 3

18

Recipe for Making Combinational Circuit

Ingredients.

- AND gates.
- OR gates.
- NOT gates.
- Wire.



White Chocolate Mousse Cake, Balducci's

Instructions.

- Step 1: represent input and output signals with Boolean variables.
- Step 2: construct truth table to carry out computation.
- Step 3: derive (simplified) Boolean expression using sum-of-products.
- Step 4: transform Boolean expression into circuit.

19

ODD Parity Circuit

ODD(x, y, z).

- 1 if odd number of inputs are 1.
- 0 otherwise.


Expressing ODD Using Sum-of-Products									
x	y	z	ODD	$x'y'z$	$x'yz'$	$xy'z'$	xyz	$x'y'z + x'yz' + xy'z' + xyz$	
0	0	0	0	0	0	0	0	0	0
0	0	1	1	1	0	0	0	0	1
0	1	0	1	0	1	0	0	0	1
0	1	1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0	0	1
1	0	1	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0
1	1	1	1	0	0	0	1	0	1

20

ODD Parity Circuit

ODD(x, y, z).

 - 1 if odd number of inputs are 1.
- 0 otherwise.



21

Let's Make an Adder Circuit


Goal: $x + y = z$.

- We build 4-bit adder: 8 inputs, 4 outputs. (Same idea scales to 128-bit adder.)
- Key computer component.

	1	1	1	0
	2	4	8	7
+	3	5	7	9
	6	1	6	6

Step 1.

- Represent input and output in binary.

 

	1	1	0	0
	0	0	1	0
+	0	1	1	1
	1	0	0	1

	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
	z_3	z_2	z_1	z_0

22

Let's Make an Adder Circuit

Goal: $x + y = z$.

Step 2.

- Build truth table.
- Why is this a bad idea?

	c_0											
	x_3	x_2	x_1	x_0								
+	y_3	y_2	y_1	y_0								
	z_3	z_2	z_1	z_0								

4-Bit Adder Truth Table												
c_0	x_3	x_2	x_1	x_0	y_3	y_2	y_1	y_0	z_3	z_2	z_1	z_0
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	0	0	1	1	0	0	1	1	1
0	0	0	0	0	1	0	0	0	0	1	0	0
0	0	0	0	0	1	0	1	0	1	0	1	1
1	1	1	1	1	1	1	1	1	1	1	1	1

$2^{8+1} = 512$ rows!

23

Let's Make an Adder Circuit

Goal: $x + y = z$.

Step 3.

- Derive (simplified) Boolean expression.

	c_3	c_2	c_1	$c_0 = 0$								
	x_3	x_2	x_1	x_0								
+	y_3	y_2	y_1	y_0								
	z_3	z_2	z_1	z_0								

Carry Bit				
x_i	y_i	c_i	c_{i+1}	MAJ
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Summand Bit				
x_i	y_i	c_i	z_i	ODD
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


25

Let's Make an Adder Circuit

Goal: $x + y = z$.

Step 4.

 - Transform Boolean expression into circuit.




Let's Make an Adder Circuit

Goal: $x + y = z$.

Step 4.

 
- Transform Boolean expression into circuit.




Subtractor

Subtractor circuit: $z = x - y$.

 - One approach: design like adder circuit.
- Better idea: reuse adder circuit.
 - 2's complement: to negate an integer, flip bits, then add 1



4-Bit Subtractor Interface

 


4-Bit Subtractor Implementation


N-Bit Decoder

N-bit decoder.

 - N address inputs, 2^N data outputs.
- Addressed output bit is 1; all others are 0.



3-Bit Decoder Interface

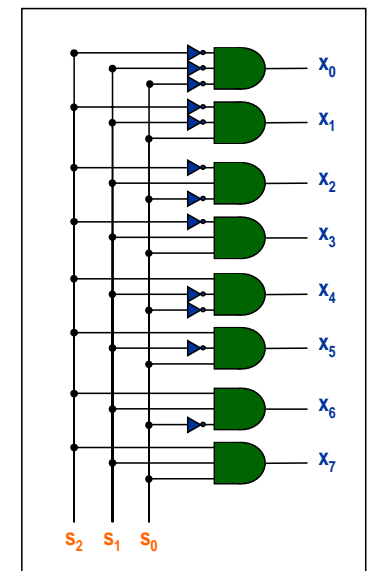


3-Bit Decoder Implementation


N-Bit Decoder

N-bit decoder.

 - N address inputs, 2^N data outputs.
- Addressed output bit is 1; all others are 0.



3-Bit Decoder Interface

 


3-Bit Decoder Implementation

30

N-Bit Decoder

Application.

 - Convert from binary to "unary."
- Decode opcode into instruction type.




31


8-to-1 Multiplexer

2^N -to-1 multiplexer.

 - N select inputs, 2^N data inputs, 1 output.
- Copies "selected" data input bit to output.



8-to-1 Mux Interface

 


8-to-1 Mux Implementation

32


8-to-1 Multiplexer

2^N -to-1 multiplexer.

 - N select inputs, 2^N data inputs, 1 output.
- Copies "selected" data input bit to output.



8-to-1 Mux Interface

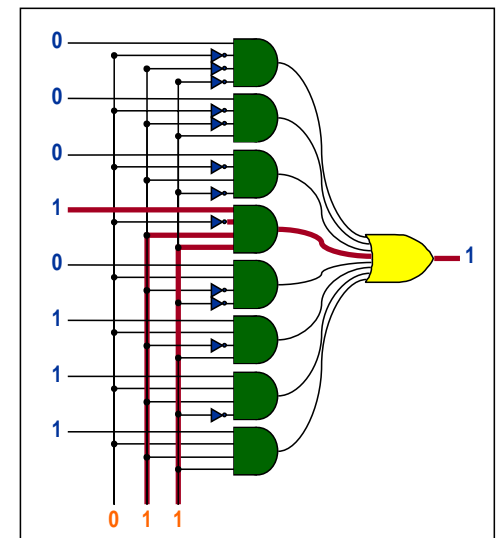

8-to-1 Mux Implementation

33

Multiplexer: Application


Use 2^N -to-1 mux to implement any Boolean function of N variables.

- N select inputs: Boolean variables.
- 2^N data inputs: truth table.

MAJ(x, y, z).

- 1 if at least two inputs are 1.
- 0 otherwise.


x	y	z	MAJ
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

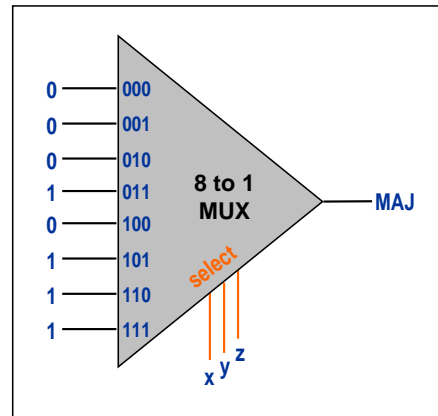

Majority Implementation


34

Sum-Of-Products Revisited

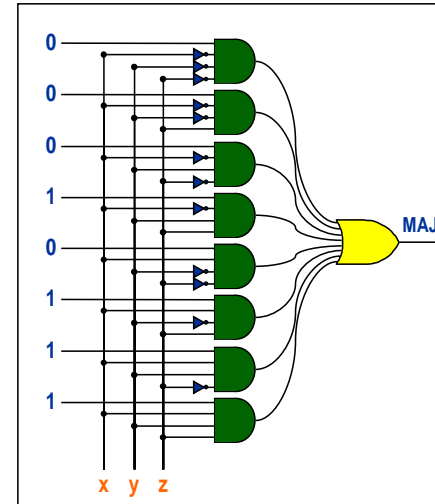

Majority Implementation with Mux

 Simplify circuit by exploiting that data inputs are fixed.




Sum of Products

35

Bus

16-bit bus.

 - Bundle of 16 wires.
- Memory transfer, register transfer.



8-bit bus.

- Bundle of 8 wires.
- Memory address.



4-bit bus.

- Bundle of 4 wires.
- Register address.




36


4-Wide 2-to-1 Multiplexer

Goal: select from one of two 4-bit buses.

 - Implement by layering 4 2-to-1 multiplexers.



Interface

 


Implementation

37

k-Wide n-to-1 Multiplexer

Goal: select from one of n k-bit buses.

- Implement by layering k n-bit muxes.

 

Interface

38


Multiplexer: Application

Program counter

- Result of jump or branch instruction.
- Adding 1 to old program counter.

Use 8-wide 2-to-1 mux to route appropriate 8-bit address to PC.

 - Unspecified detail: how to set control wire?




39

Arithmetic Logic Unit: Interface

ALU Interface.


- Add, subtract, bitwise and, bitwise xor, shift left, shift right, copy.
- Associate 3-bit integer with 5 primary ALU operations.
 - ALU performs operations in parallel
 - control wires select which result ALU outputs

op	2	1	0
+, -	0	0	0
&	0	0	1
^	0	1	0
<<, >>	0	1	1
input 2	1	0	0

 

40

Arithmetic Logic Unit: Implementation

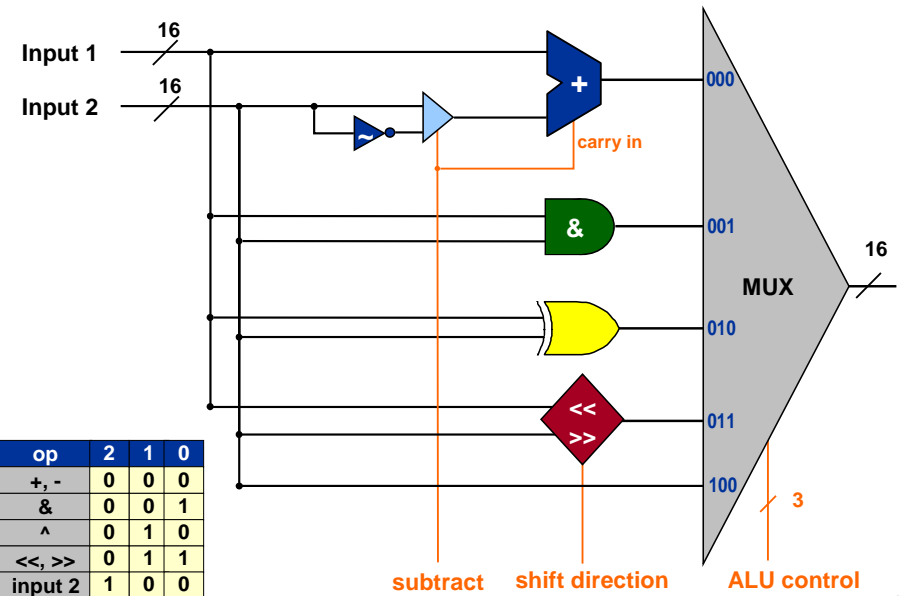


op	2	1	0
+, -	0	0	0
&	0	0	1
^	0	1	0
<<, >>	0	1	1
input 2	1	0	0

41


Bitwise AND, XOR, NOT

Bitwise logical operations.

 - Inputs x and y : n -bits each.
- Output z : n -bits.
- Apply logical operation to each corresponding pair of bits.



Bitwise And Interface

 

Bitwise And Implementation

Abstraction and Encapsulation

Lessons for ADT apply to hardware!

- Interface describes behavior of circuit.
- Implementation gives details of how to build it.