
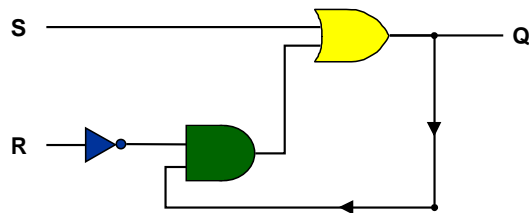


# Lecture A5: Sequential Circuits

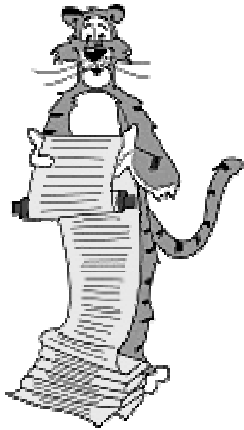

## Overview

Lecture A1 – A3: TOY machine.

Lecture A4: Boolean logic and combinational circuits.

- In principle, we could build X-TOY computer with one gigantic combinational circuit.
- Each circuit element used (at most) once.


Today: reuse circuit elements by storing bits in "memory."

Next time: glue components together to make X-TOY computer.

## Sequential vs. Combinational Circuits


Combinational circuits.

- Output determined solely by inputs.

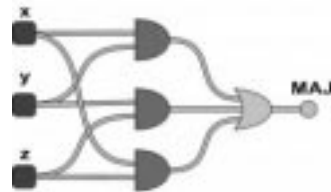

Sequential circuits.

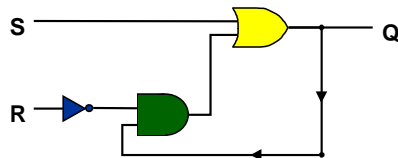- Feedback loop.
- Output determined by inputs and previous outputs.



## Flip-Flop

Flip-flop.


- A small and useful sequential circuit.
- "Remembers" one bit.

We will consider several flavors.

## SR Flip-Flop
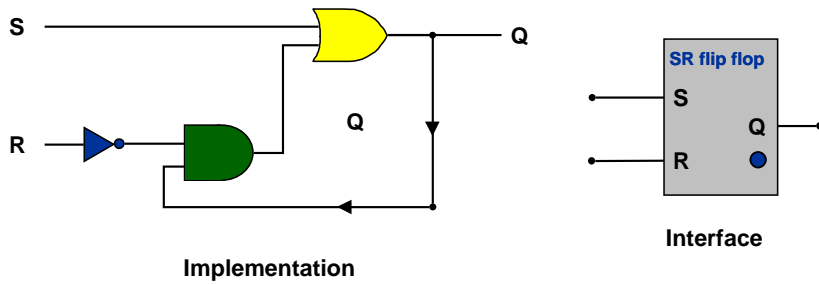
### SR Flip-Flop.

- Pulse on S (set)  $\Rightarrow$  Flips "bit" on.
- Pulse on R (reset)  $\Rightarrow$  Flips "bit" off.
- S = R = 0  $\Rightarrow$  Status quo.
- S = R = 1  $\Rightarrow$  Not allowed.



5


## Truth Table and Timing Diagram (for SR Flip-Flop)

### Truth table.

- Values vary over time.
- S(t), R(t), Q(t) denote value at time t.

SR Flip Flop Truth Table			
S(t)	R(t)	Q(t)	Q(t+ $\epsilon$ )
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	
1	1	1	

### Sample timing diagram.

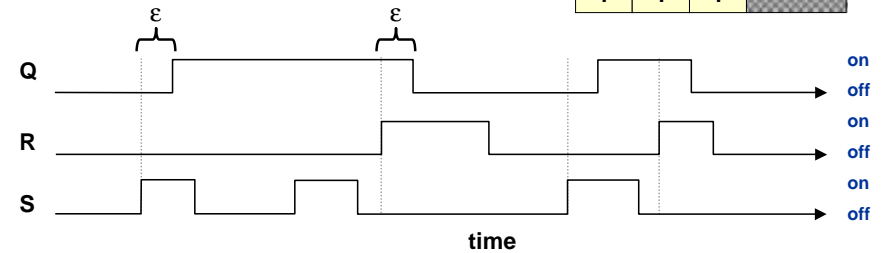


6

## Clock
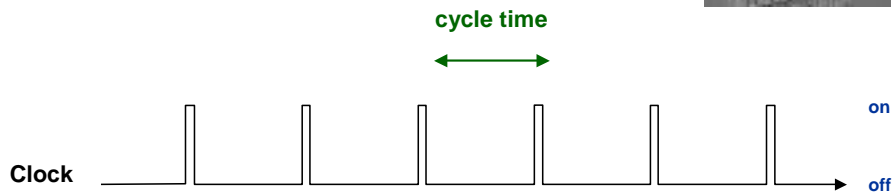
### Clock.

- Fundamental abstraction.
  - regular on-off pulse
- External analog device.
- Synchronize operations of different circuit elements.
- 800 MHz clock means 800 million pulses per second.





7

## Clocked SR Flip-Flop
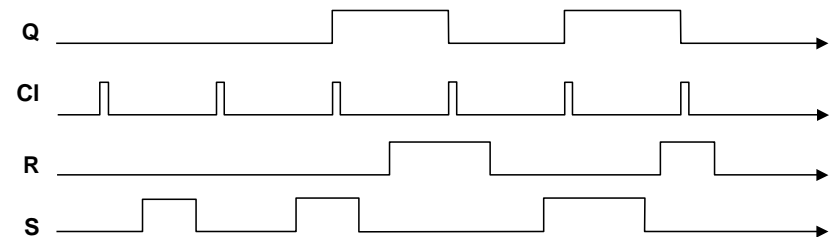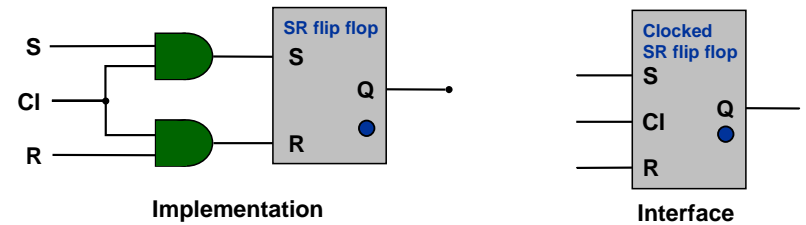
### Clocked SR Flip-Flop.

- Like SR flip-flop but S and R only work if clock is on.





8

## Clocked D Flip-Flop
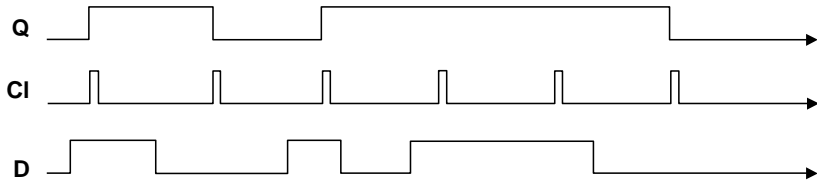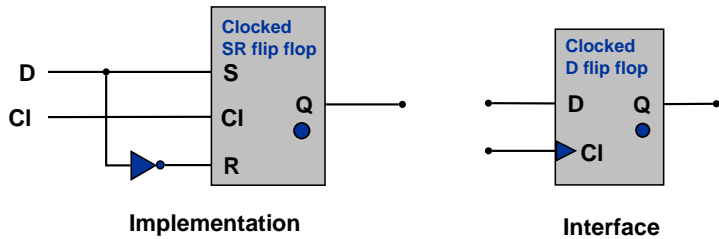
### Clocked D Flip-Flop.

- Output follows D input when clock is high.
- Output is remembered when clock is low.





9

## 1-Bit Counter
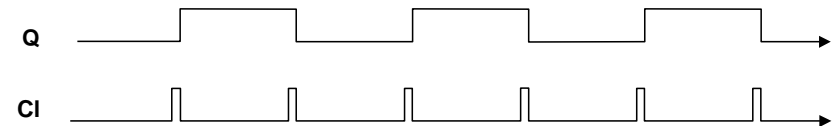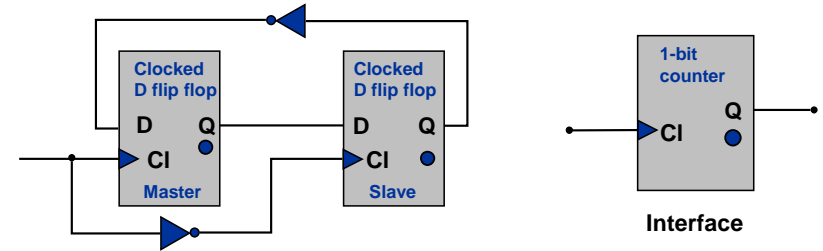
### 1-bit counter (falling edge-trigger).

- Circuit that oscillates between on and off.





10

## Fetch-Execute Cycle

### Fetch-execute cycle.

- Use 1-bit counter.

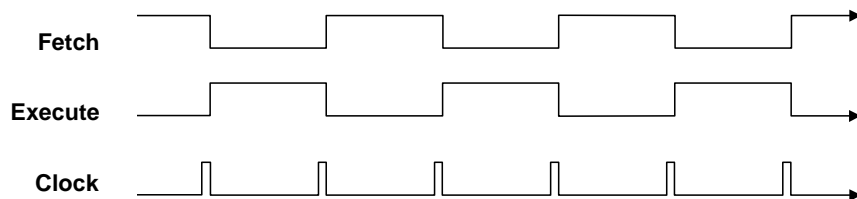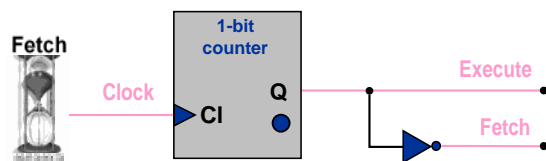

11

## Memory Overview

### Computers have many types of memory.

- PC.
- Registers.
- Main memory.

### We implement 1 bit of memory with clocked D flip-flop.

### Need mechanism to organize and manipulate groups of related bits.

- X-TOY has 16-bit words.
- Memory hierarchy make architecture cleaner.


12

## Stand-Alone Register

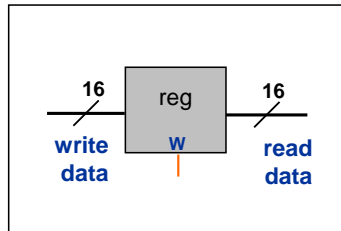
### k-bit register.

- Stores k bits.
- Register contents always available on output.
- If write enable is asserted, k input bits get copied into register.

Ex: PC, 16 TOY registers,  
256 TOY memory locations.



16-bit Register Interface

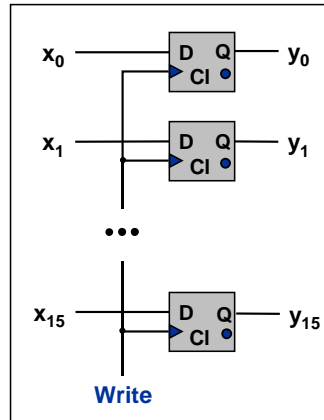

16-bit Register Implementation

13


## Register File Interface

### n x k register file.

- Bank of n registers; each stores k bits.
- Read and write information to ONE of n registers.
  - address inputs specifies which one
  - how many bits needed to specify address?
- Addressed bits always appear on output.
- If write enable and clock are asserted, k input bits get copied into addressed register.
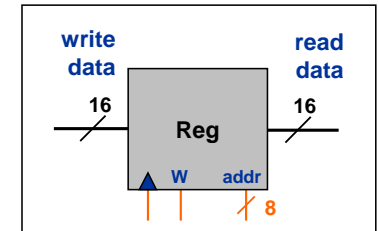
### Examples.

- X-TOY registers: n = 16, k = 16.
- X-TOY main memory: n = 256, k = 16.




256 x 16 Register File Interface

14

## Register File Implementation
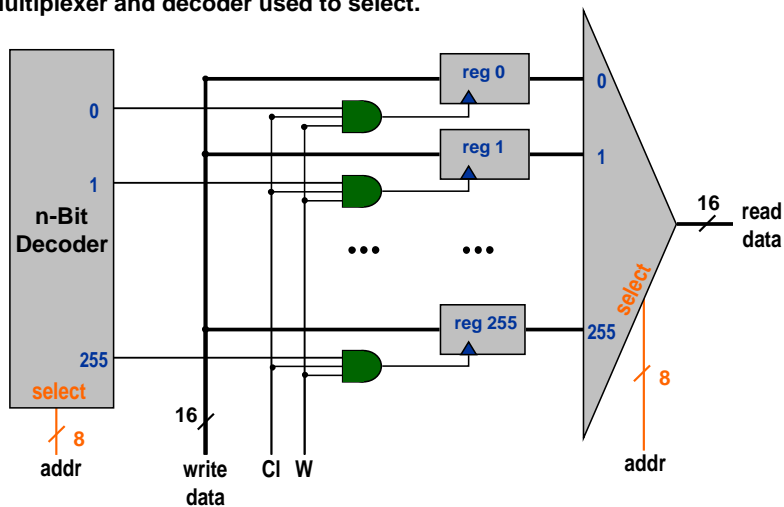
### Implementation.

- Use n k-bit registers.
- Multiplexer and decoder used to select.



15