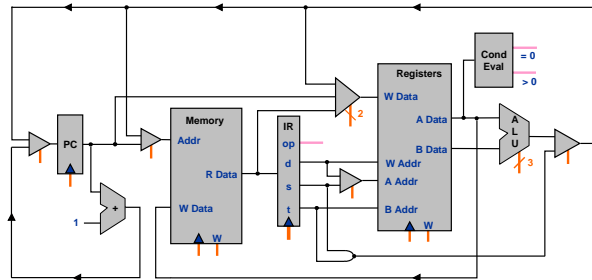


Lecture A6: Building an X-TOY



The X-TOY Machine ISA

X-TOY machine ISA.


- 256 16-bit words of memory.
- 16 16-bit registers.
- 1 8-bit program counter.
- 16 instructions types.

What we've done.

- Software implementation of fetch-execute cycle.
X-TOY simulator

Our goal today.

 - Hardware implementation of fetch-execute cycle.
X-TOY computer



2

Designing a Processor

How to build a microprocessor?

- **Develop instruction set architecture (ISA).**
 - 16-bit words, 16 TOY machine instructions
- Determine major components.
 - memory, registers, ALU, program counter
- Determine datapath requirements.
 - flow of bits
- Establish clocking methodology.
 - 2-cycle design: fetch, execute
- Analyze how to implement each instruction.
 - determine settings of control signals

3

Instruction Set Architecture

Instruction set architecture (ISA).

- Determine set of primitive instructions.
 - too narrow \Rightarrow cumbersome to program
 - too broad \Rightarrow cumbersome to build hardware
- X-TOY machine: 16 instructions.

Instructions	
0:	halt
1:	add
2:	subtract
3:	and
4:	xor
5:	shift left
6:	shift right
7:	load address

Instructions	
8:	load
9:	store
A:	load indirect
B:	store indirect
C:	branch zero
D:	branch positive
E:	jump register
F:	jump and link

4

Designing a Processor


How to build a microprocessor?

- Develop instruction set architecture (ISA).
 - 16-bit words, 16 TOY machine instructions
- Determine major components.
 - memory, registers, ALU, program counter
- Determine datapath requirements.
 - flow of bits
- Establish clocking methodology.
 - 2-cycle design: fetch, execute
- Analyze how to implement each instruction.
 - determine settings of control signals

5

Main Memory

 TOY main memory: 256 x 16-bit register file.




6

Registers

TOY registers: extend 16 x 16-bit register file.

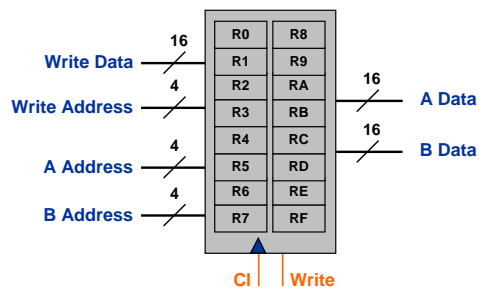- Want to be able to read two registers, and write to a third in the same instructions: $R1 \leftarrow R2 + R3$.
- 3 address inputs, 2 data outputs.
- Add extra bank of muxes to bit-slice memory.



7

Designing a Processor

How to build a microprocessor?

- Develop instruction set architecture (ISA).
 - 16-bit words, 16 TOY machine instructions
- Determine major components.
 - memory, registers, ALU, program counter
- Determine datapath requirements.
 - flow of bits
- Establish clocking methodology.
 - 2-cycle design: fetch, execute
- Analyze how to implement each instruction.
 - determine settings of control signals

8


Datapath and Control

Datapath.

- Wires that transfer contents of memory, registers, and PC.
- Must accommodate for all types of instructions.


Control.

 - Wires used to choreograph the flow of information on the datapath.
- Depending on instruction, different control wires are turned on.




9

The X-TOY Datapath

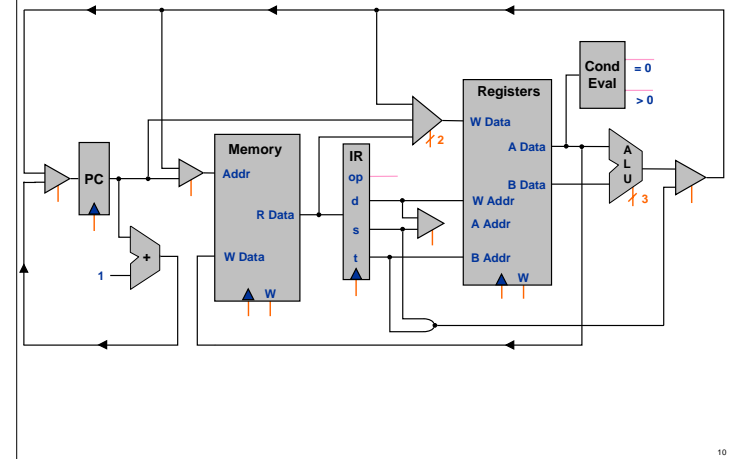

10

The X-TOY Datapath: Add

 


Before fetch:
pc = 20, mem[20] = 1234

After fetch:
pc = 21
IR = 1234

11

The X-TOY Datapath: Add

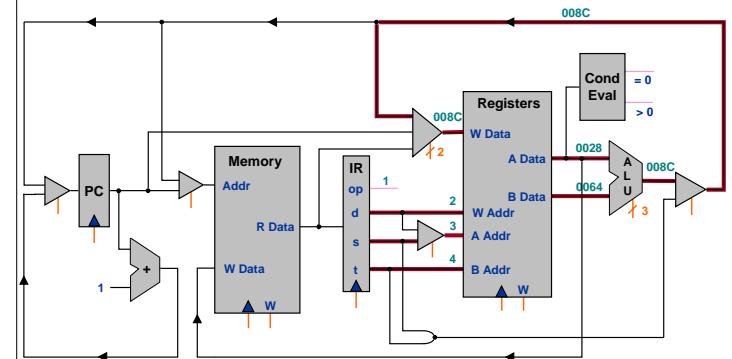


Before execute:
pc = 20, IR = 1234
R[3] = 0028, R[4] = 0064

After execute:
pc = 21
R[2] = 008C

12


The X-TOY Datapath: Jump and Link

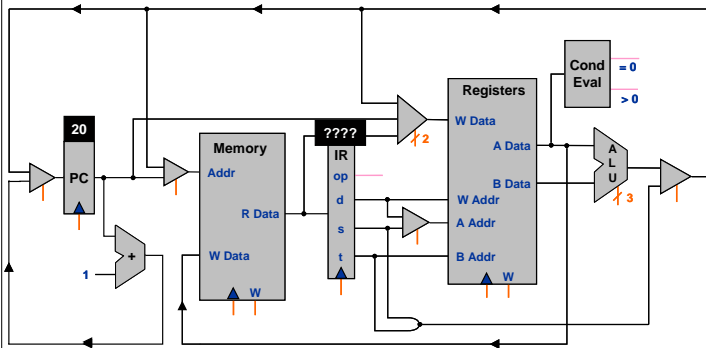

Before fetch:
 pc = 20
 mem[20] = FF30

13

The X-TOY Datapath: Jump and Link

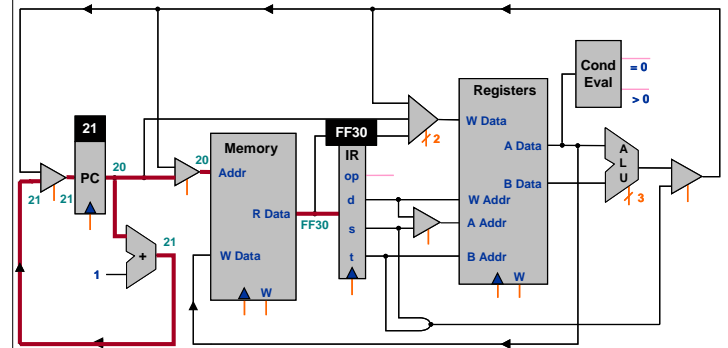


Before fetch:
 pc = 20
 mem[20] = FF30

After fetch:
 pc = 21
 IR = FF30

14


The X-TOY Datapath: Jump and Link

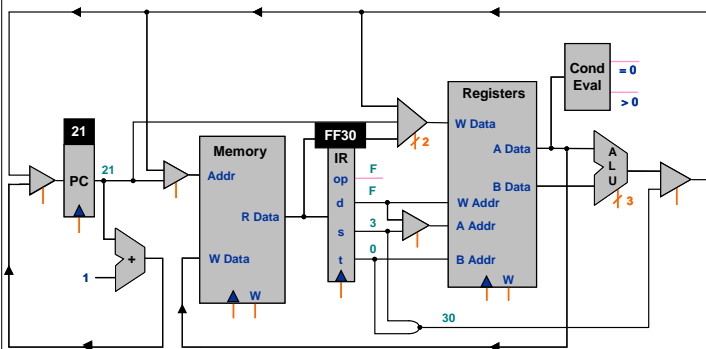

Before execute:
 pc = 21
 IR = FF30

15

The X-TOY Datapath: Jump and Link

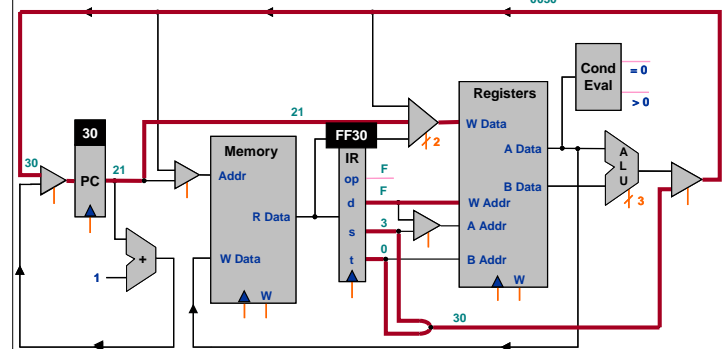

Before execute:
 pc = 21
 IR = FF30

After execute:
 pc = 30
 R[F] = 21

16

Designing a Processor

How to build a microprocessor?



- Develop instruction set architecture (ISA).
 - 16-bit words, 16 TOY machine instructions
- Determine major components.
 - memory, registers, ALU, program counter
- Determine datapath requirements.
 - flow of bits
- Establish clocking methodology.
 - 2-cycle design: fetch, execute
- Analyze how to implement each instruction.
 - determine settings of control signals

17

Clocking Methodology

Two cycle design (fetch and execute).

  - Use 1-bit counter to distinguish between 2 cycles.
- Why not just use 1 cycle?





18

Clocking Methodology

4 distinguishable events.

 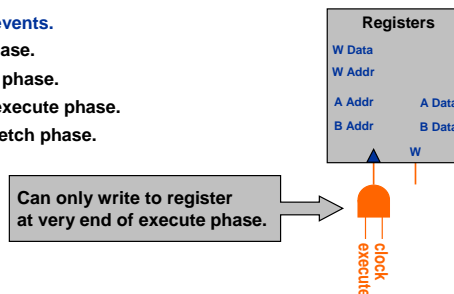- During fetch phase.
- During execute phase.
- At very end of execute phase.
- At very end of fetch phase.



19

Designing a Processor

How to build a microprocessor?


- Develop instruction set architecture (ISA).
 - 16-bit words, 16 TOY machine instructions
- Determine major components.
 - memory, registers, ALU, program counter
- Determine datapath requirements.
 - flow of bits
- Establish clocking methodology.
 - 2-cycle design: fetch, execute
- Analyze how to implement each instruction.
 - determine settings of control signals

20

Control


Control: controls components, enables connections.

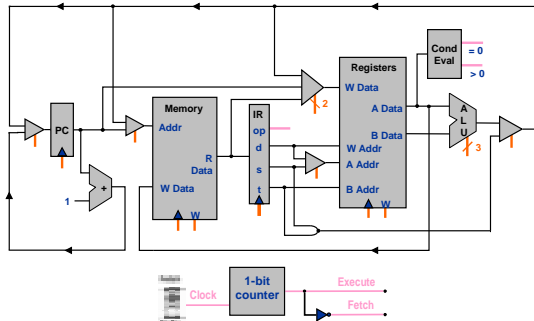- Turn on certain control wires, depending on:
 - opcode, clock, conditional evaluation
- Determine orange control wires from pink ones.




21

Control

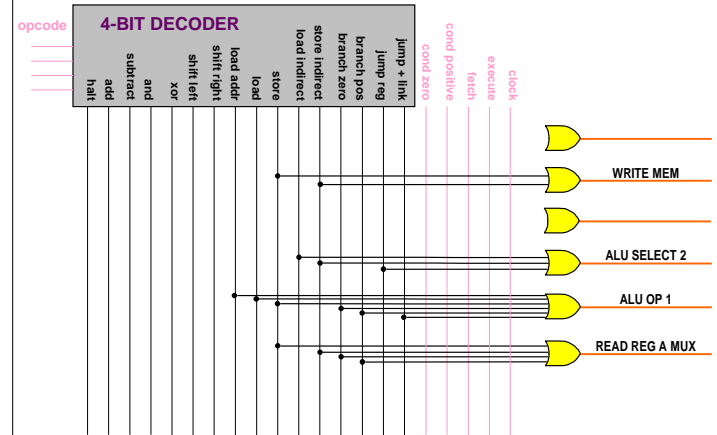


22

Stand-Alone Registers

 


Instruction Register

 

Program Counter


23

ALU Control

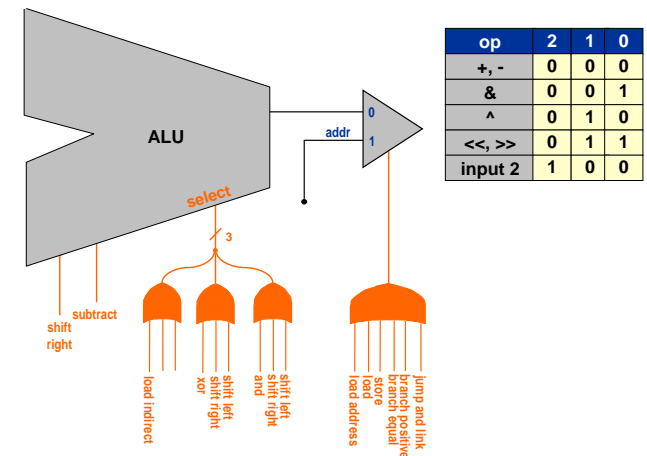


24

Memory Control

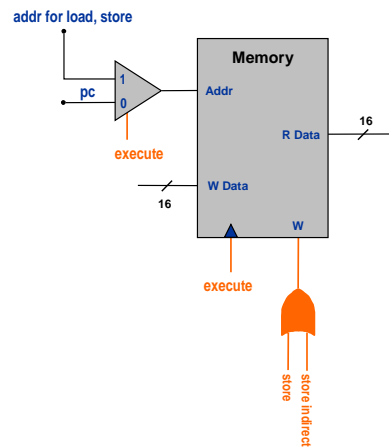

25

Register Control

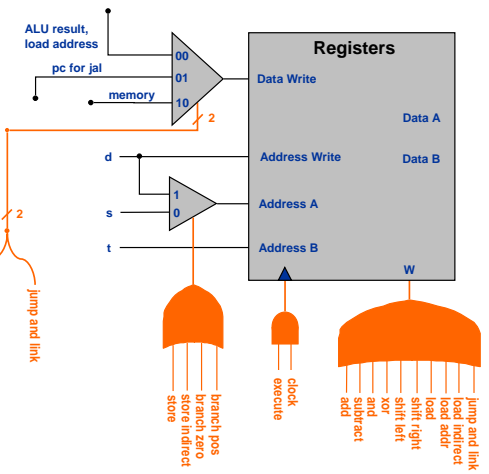

26

Pipelining

Pipelining.

- At any instant, processor is either fetching instructions or executing them (half of circuitry is idle).
- Why not fetch next instruction while current instruction is executing?

Issues.

- Jump and branch instructions change PC.
- Fetch and execute cycles may need to access same memory.

Result.

- Better utilization of hardware.
- Can double speed of processor.

27

Layers of Abstraction

Layers of abstraction.

- Raw materials.
 - abstract switch (transistor)
 - connector (wire)
 - clock
- Logic gates.
 - AND, OR, NOT
- Combinational circuits.
 - decoder, multiplexer, majority, odd parity, adder, ALU
- Sequential circuits.
 - flip-flops, register, memory, counter
- X-TOY computer.

28

History + Future

Computer constructed by layering abstractions.

- Better implementation at low levels improves EVERYTHING.
- Ongoing search for better abstract switch!

History.


- 1820s: mechanical switches (Babbage's difference engine).
- 1940s: relays, vacuum tubes.
- 1950s: transistor, core memory.
- 1960s: integrated circuit.
- 1970s: microprocessor.
- 1980s: VLSI.
- 1990s: integrated systems.
- 2000s: web computer.
- Future: DNA, quantum, optical soliton, . . .

29

Lecture A5: Extra Notes




The X-TOY Computer

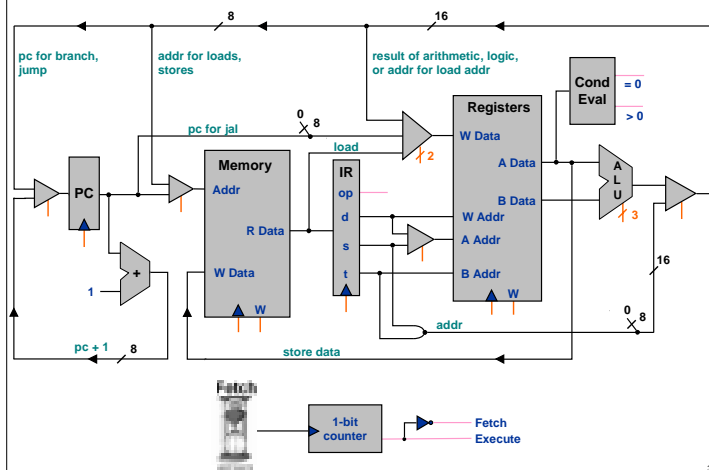

31

The Big Picture

 The five classic components of a computer in the von Neumann model.



32