
Lecture 7: Datapath

COS / ELE 375

Computer Architecture and Organization

Princeton University
Fall 2015

Prof. David August


Datapath

Datapath

“The component of the processor that performs arithmetic operations” – P&H

Datapath

 The collection of state elements, computation elements, and interconnections that together provide a conduit for the flow and transformation of data in the processor during execution. - DIA



Datapath - Part of the Microarchitecture

Architecture

- The ISA - the programmer's view of the machine
- Implementation independent, **an interface**



Microarchitecture

- The lower-level implementation of the ISA
- Design specific, **an implementation**



Example use of terminology


- Architectural state: **Register r5**
- Microarchitectural state: **Carry bit on the 5th 1-bit ALU**

Datapath Elements

- ALUs are just one datapath building block
- What about the other elements?


Computational Elements

 - Combination Circuits
- Outputs follow inputs
- Familiar Example: ALU




State Elements

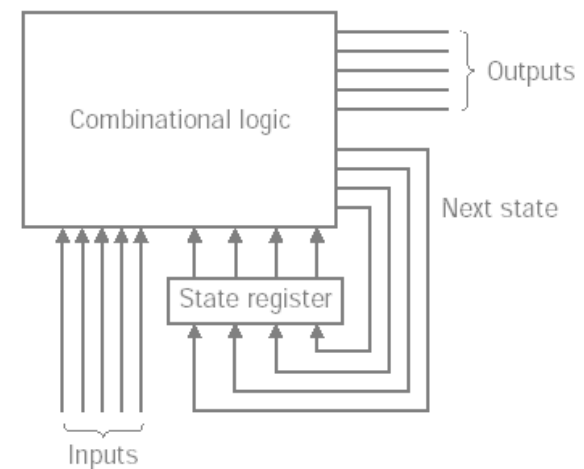- Sequential Circuits
- Outputs change on clock edge
- Familiar Example: A Register



Computation Element: ALU

 
- Combinational - you had better know how to design it by now!!!
- Refine for MIPS
 - Zero equality test on all results - why?
 - Set on less than for `slt` instruction



ALU Control	Function
000	AND
001	OR
010	add
110	subtract
111	set on less than

Computation Element: Sign Extender

 - 16 → 32 bit Sign extender
- Why is this necessary in MIPS?




- Hint:

	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits
R:	op	rs	rt	rd	shamt	funct
I:	op	rs	rt	address / immediate		
J:	op	target address				

Implementation?


Computation Element: Adder

 - Not an ALU, just add
- Why would we need this in MIPS to execute instructions?



Computational Element: The Magical Mux

 
- Mux is short for Multiplexer (Think: selector)
- n input lines (of any common width)
- m control wires to select
- $n = 2^m$



Implementation?

State Element: Register File

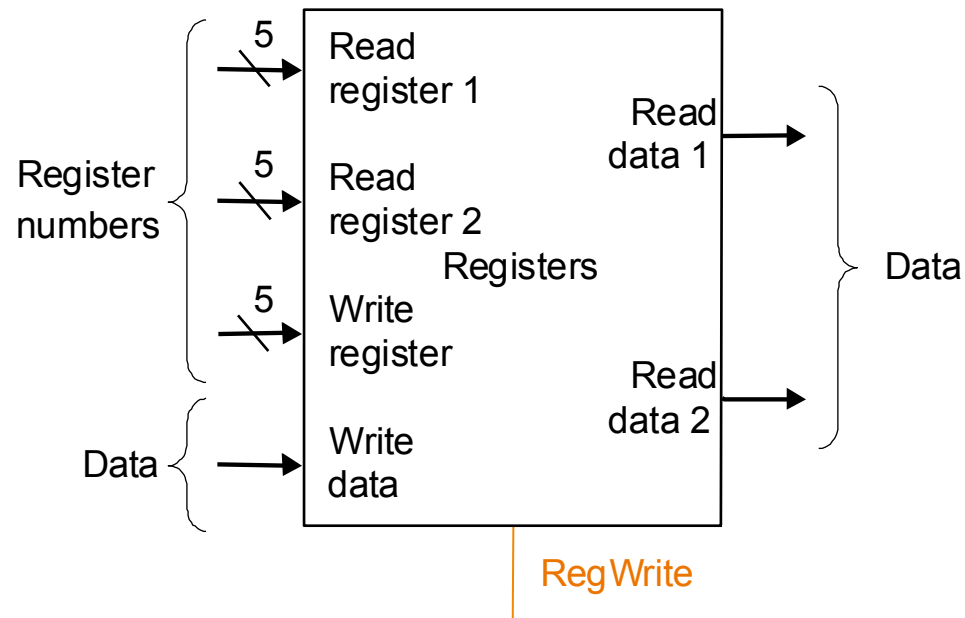
- Microarchitecture to implement architectural state
- Built using D flip-flops
- MIPS:
 - Need to be able to read two operands at once
 - 2 source operands per instruction




5-bits? 2 Reads? 1 Write?

State Element: Register File

Register Implementation

 



D latch

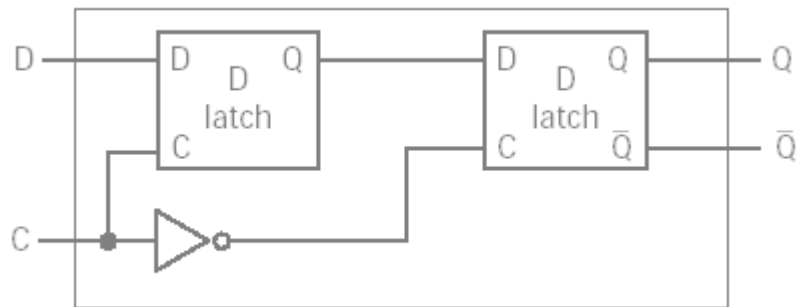

Falling edge triggered D flip-flop



State Element: Register File

Read Implementation

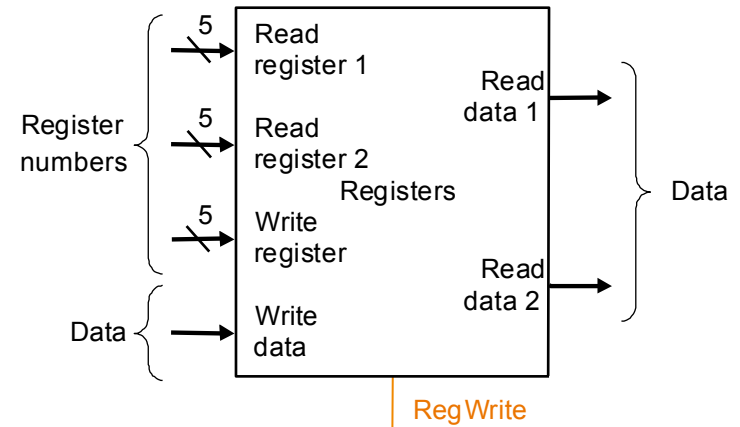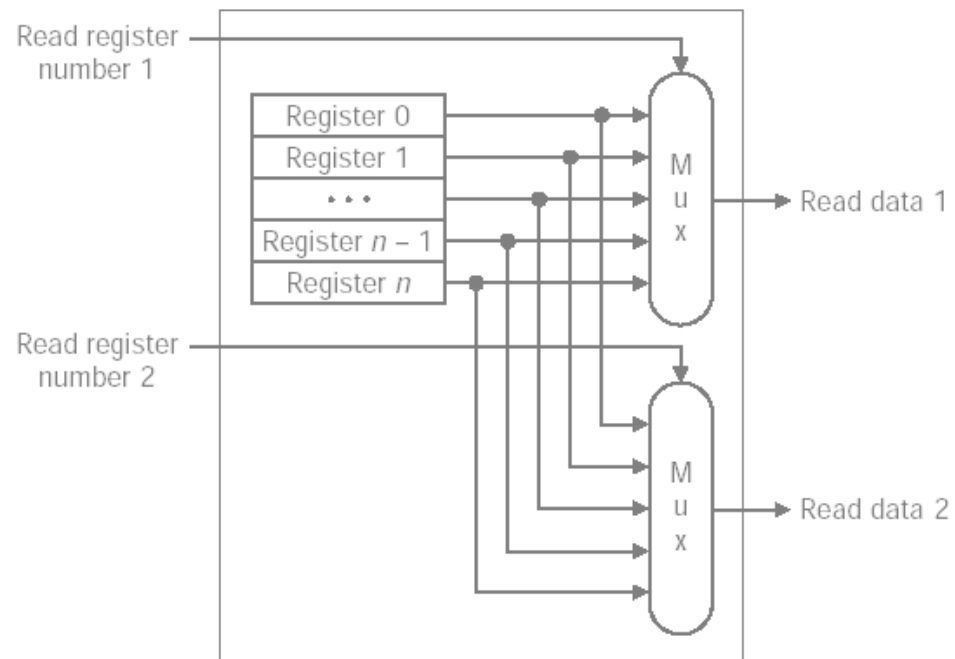

State Element: Register File


Write Implementation

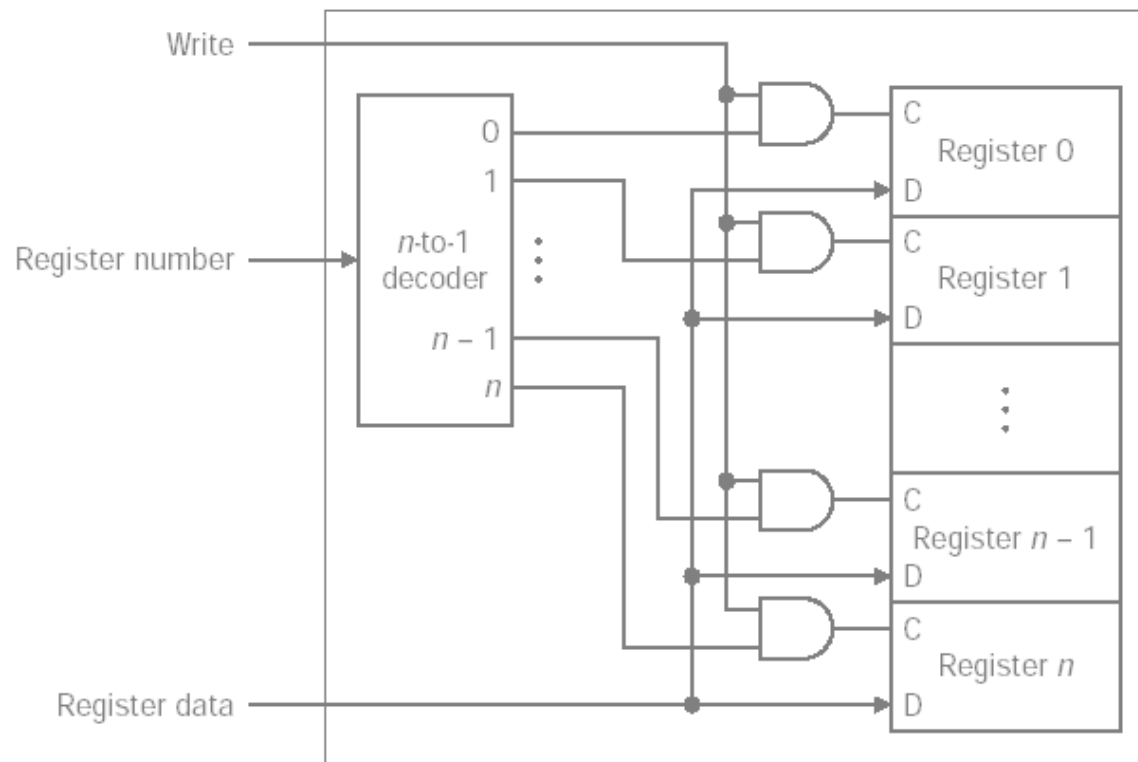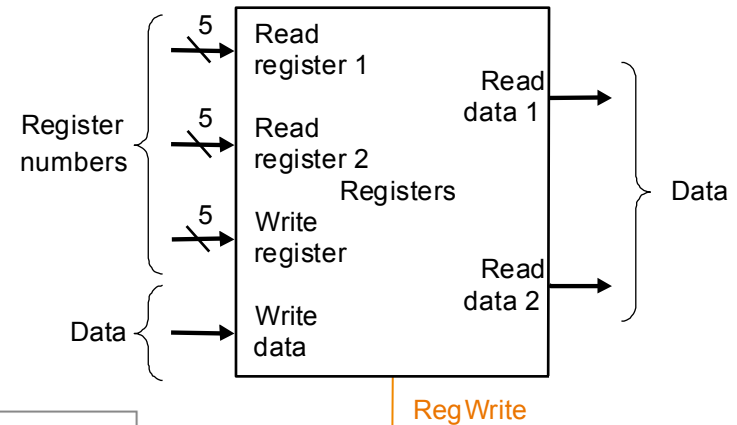

Know decoders


State Element: Data and Instruction Memory

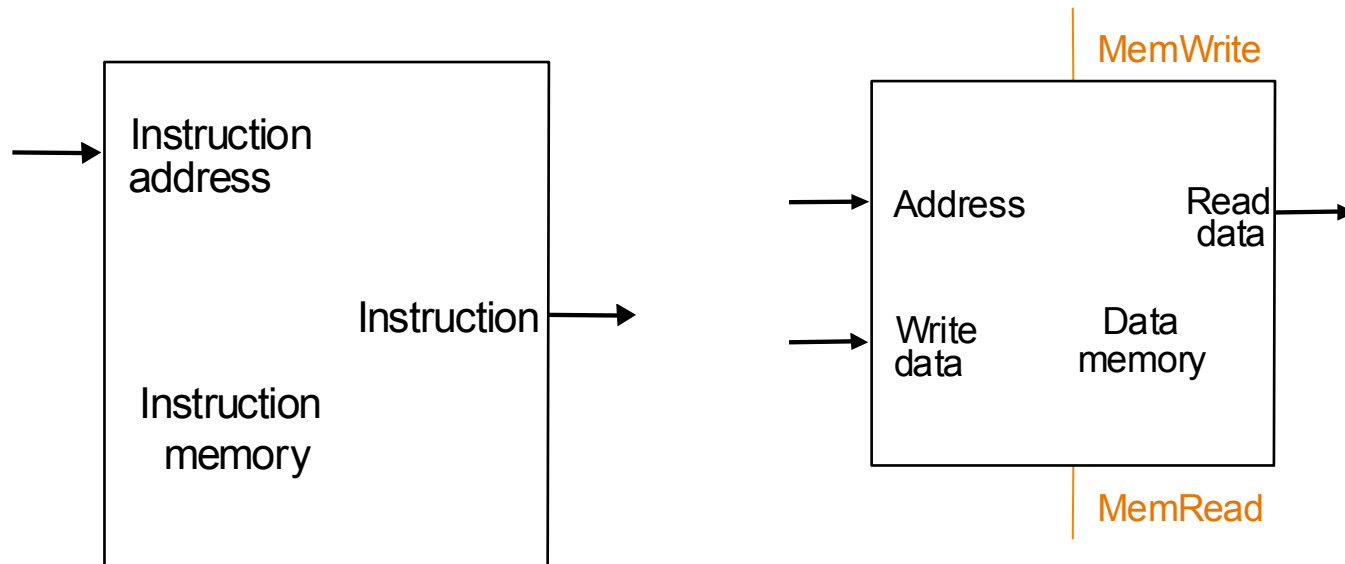- Microarchitectural element to hold the architectural memory state
- See Appendix B for implementation details




State Element: The Program Counter

 - To hold the architectural PC state
- Just like a single register




Our Complete Line of Products!

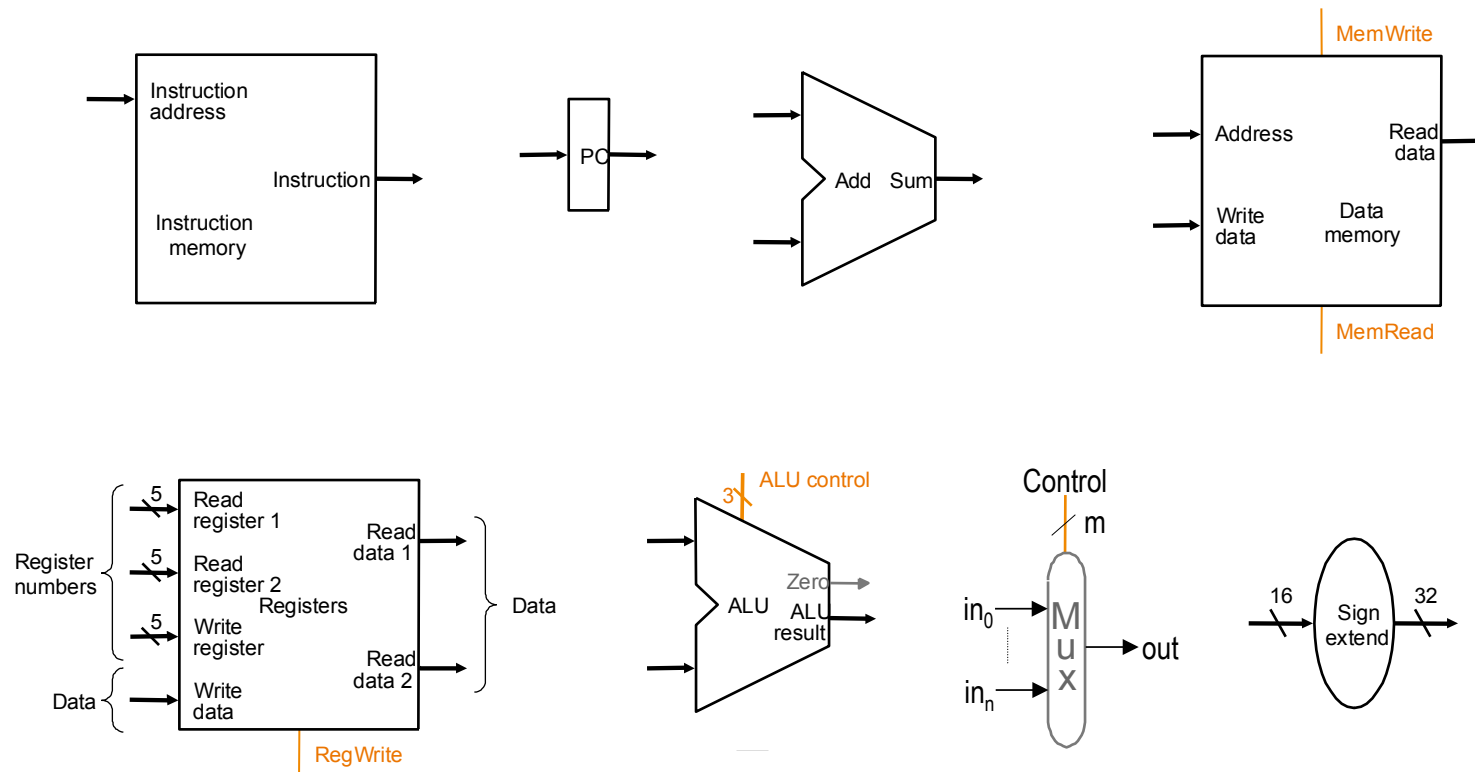There may be others, but this is good for MIPS




Fetching Instructions (no branching)

 


The ALU (R-Type) Instructions

	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits
R:	op	rs	rt	rd	shamt	funct

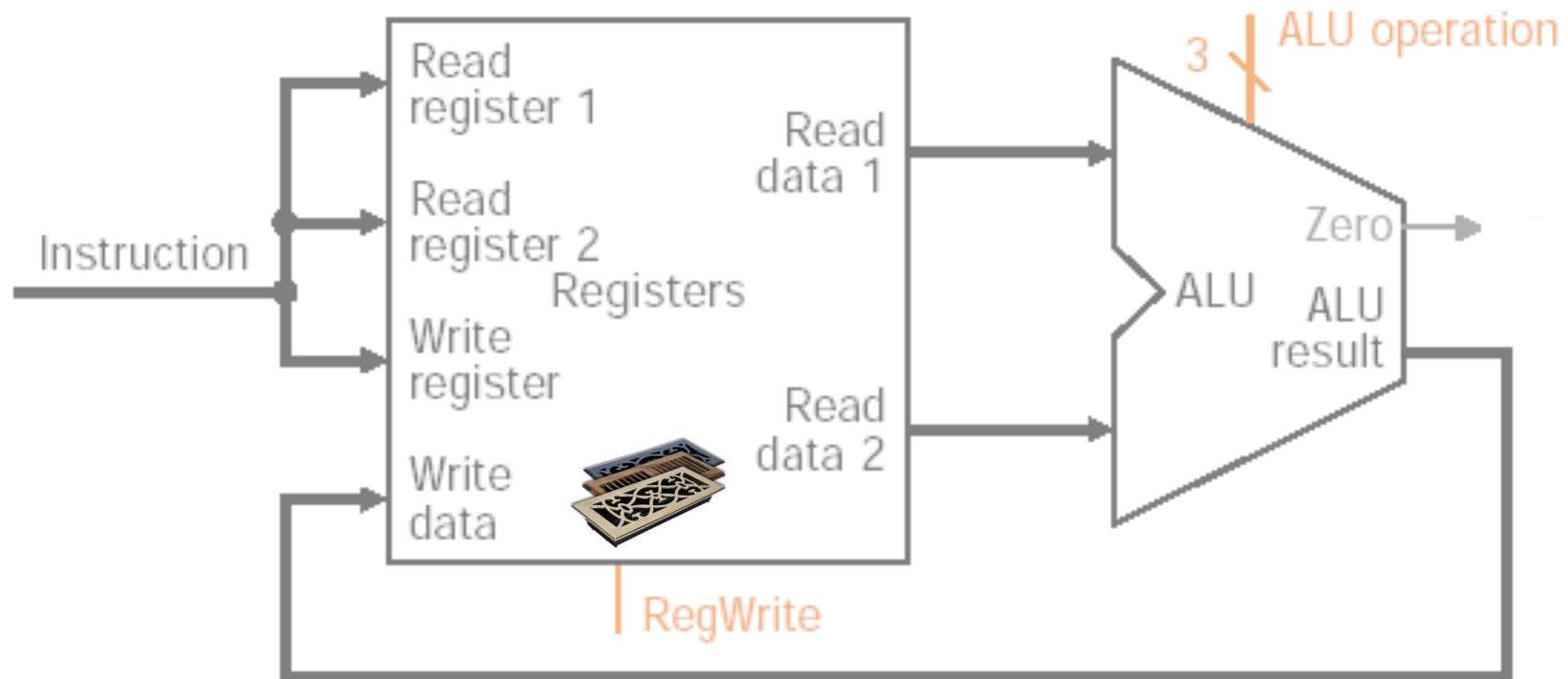

Consider: $r1 = r2 - r3$




Load and Store Instructions

 


Consider: $r1 = M[r2 - 3]$

Composition of Memory and R-Type Datapath


The Magic of the Mux

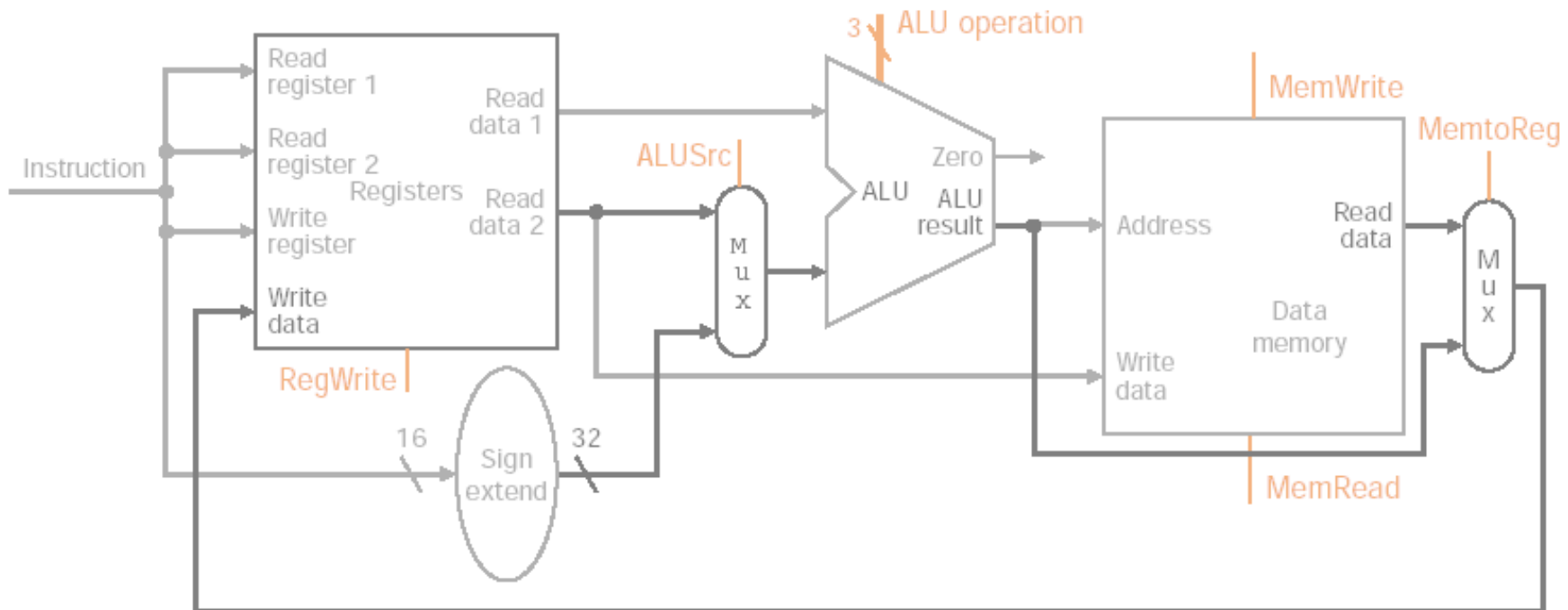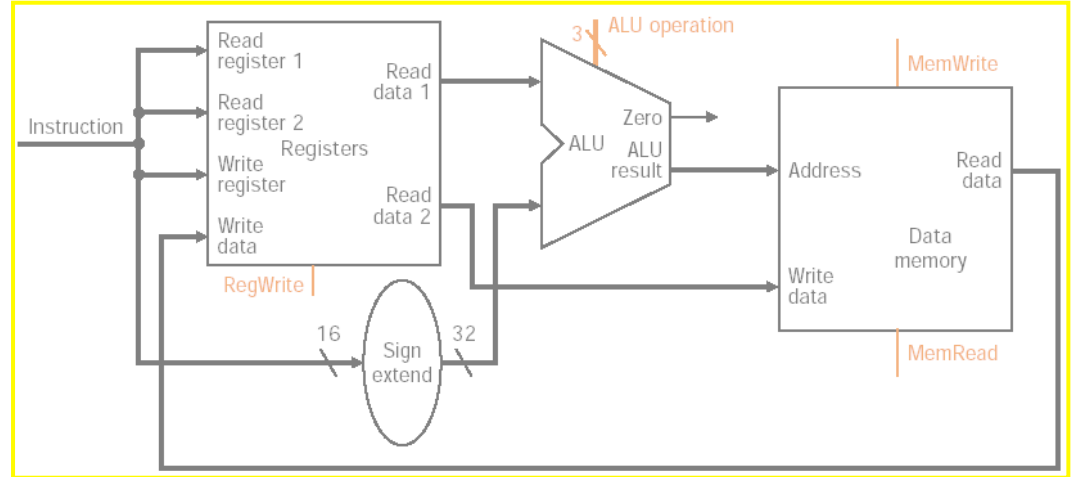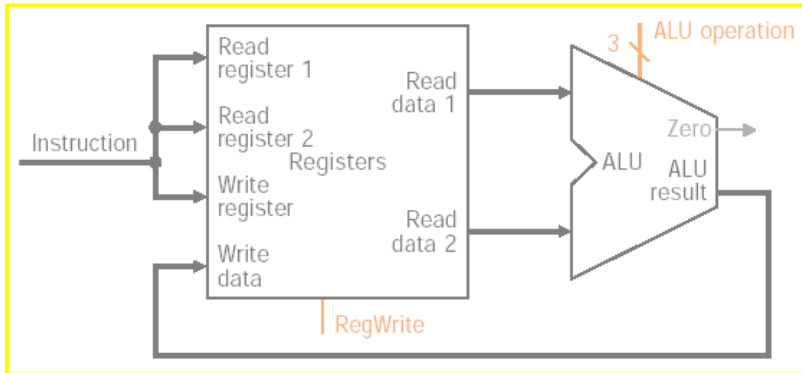


Recall Fetch

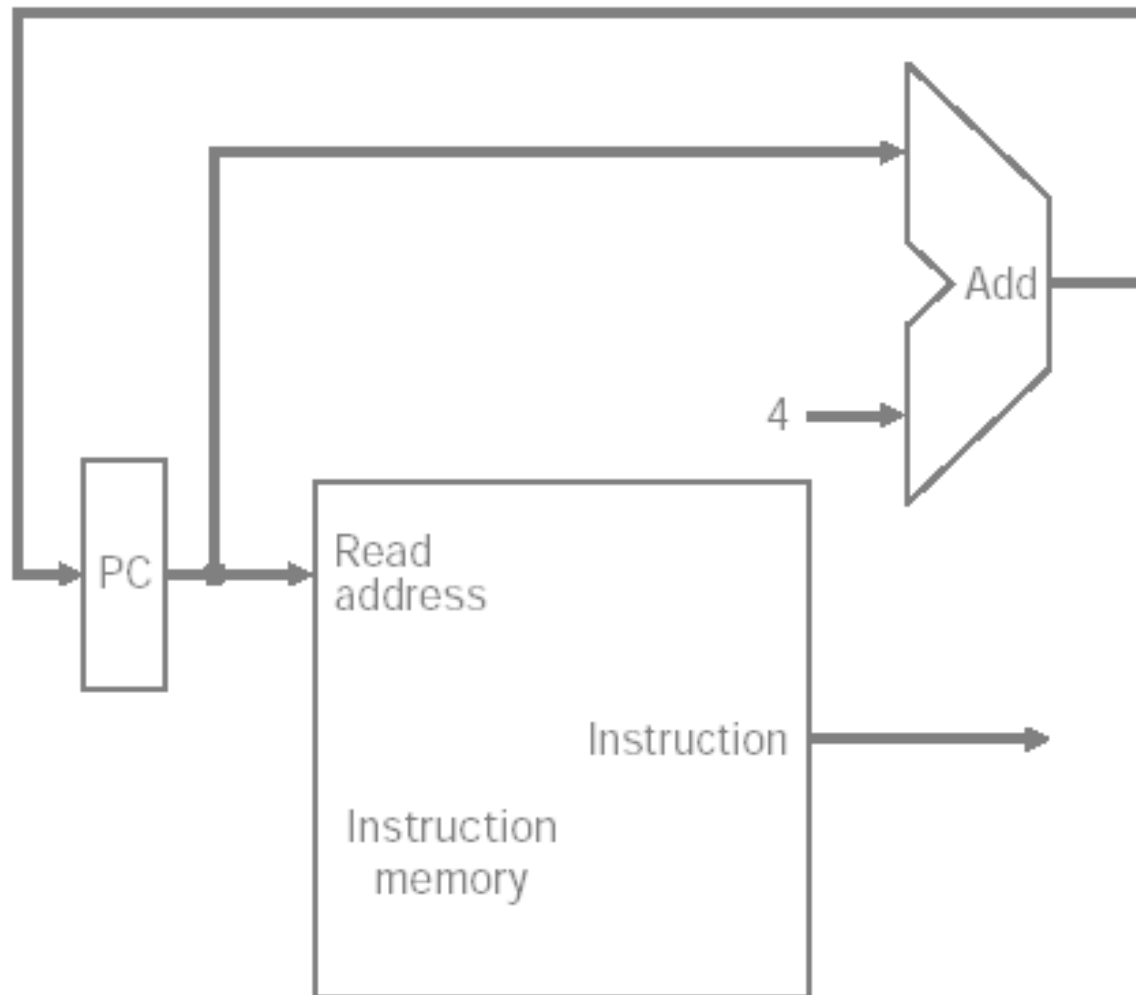

Now Add Instruction Fetch

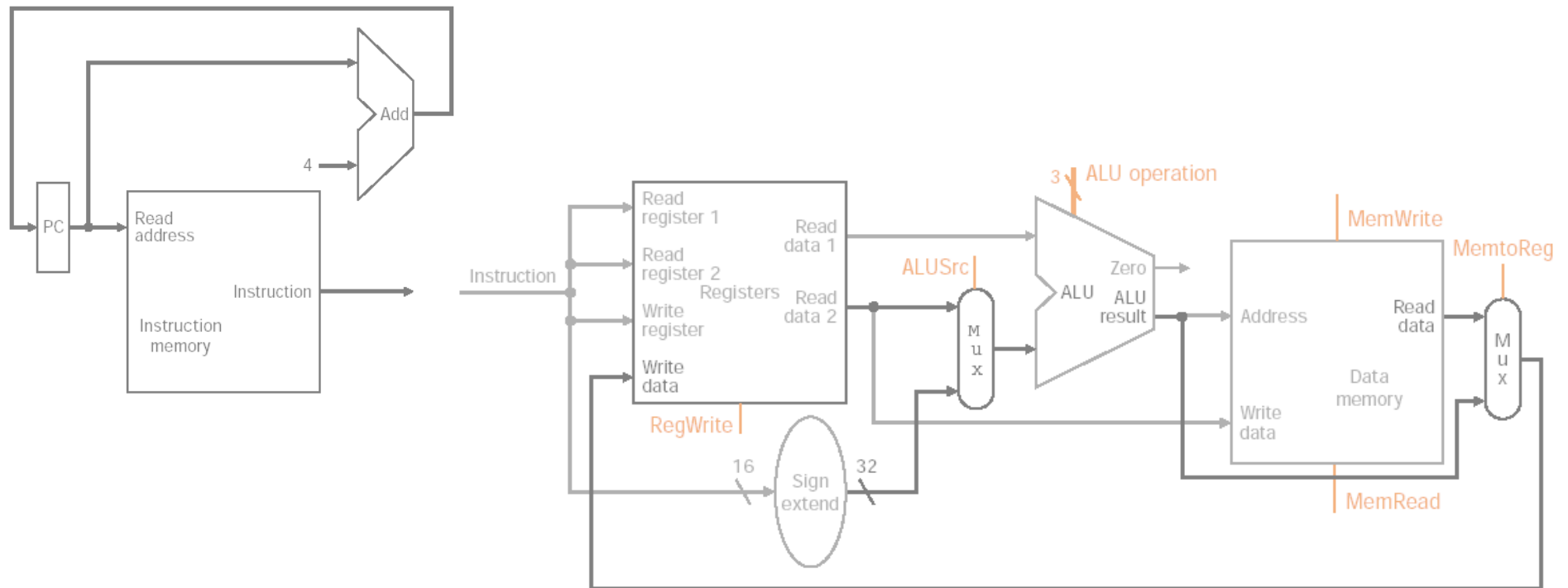


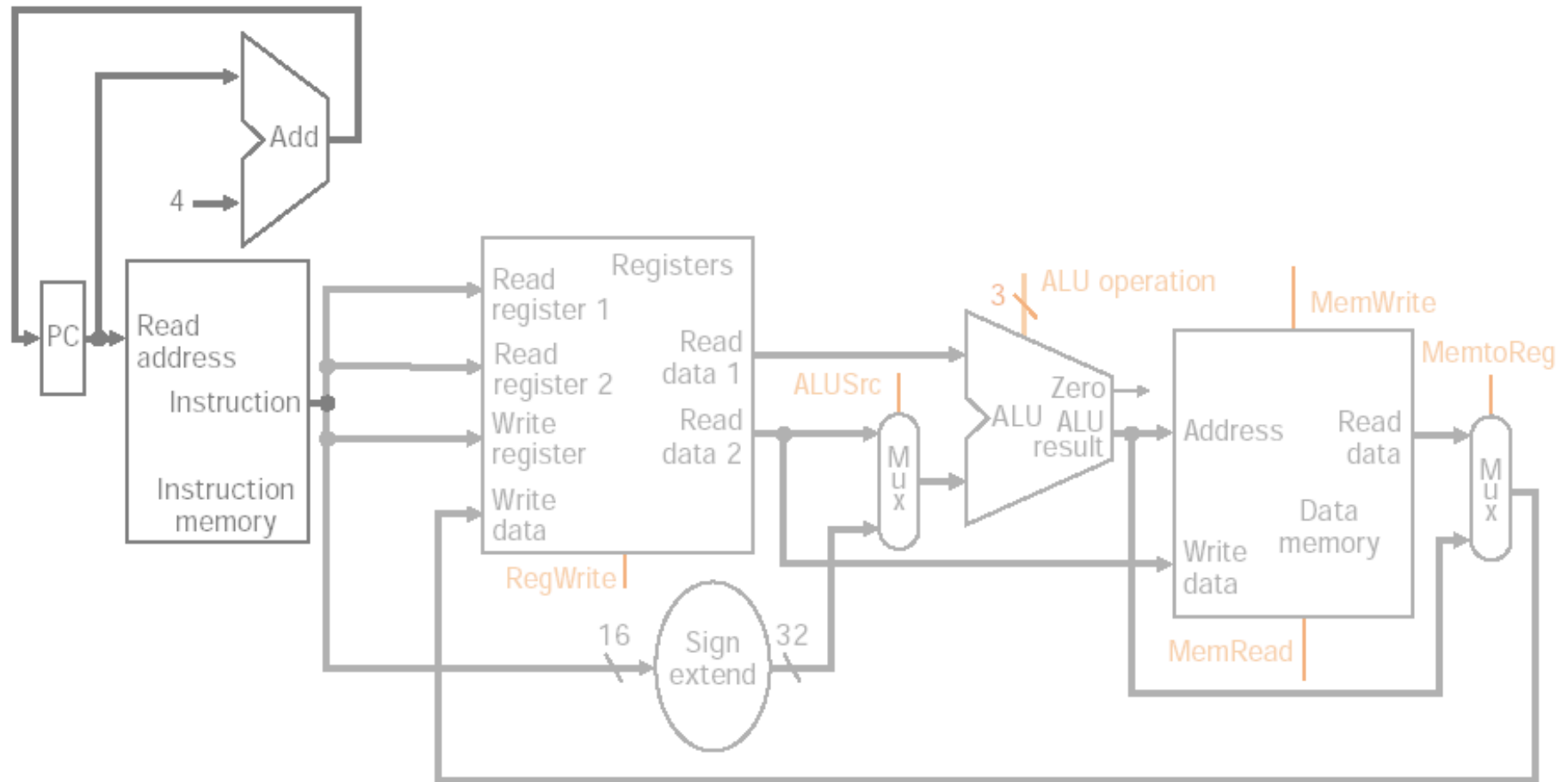Now Add Instruction Fetch (ALU + MEM + Fetch)




Data and Instruction memory?

Branch Instructions

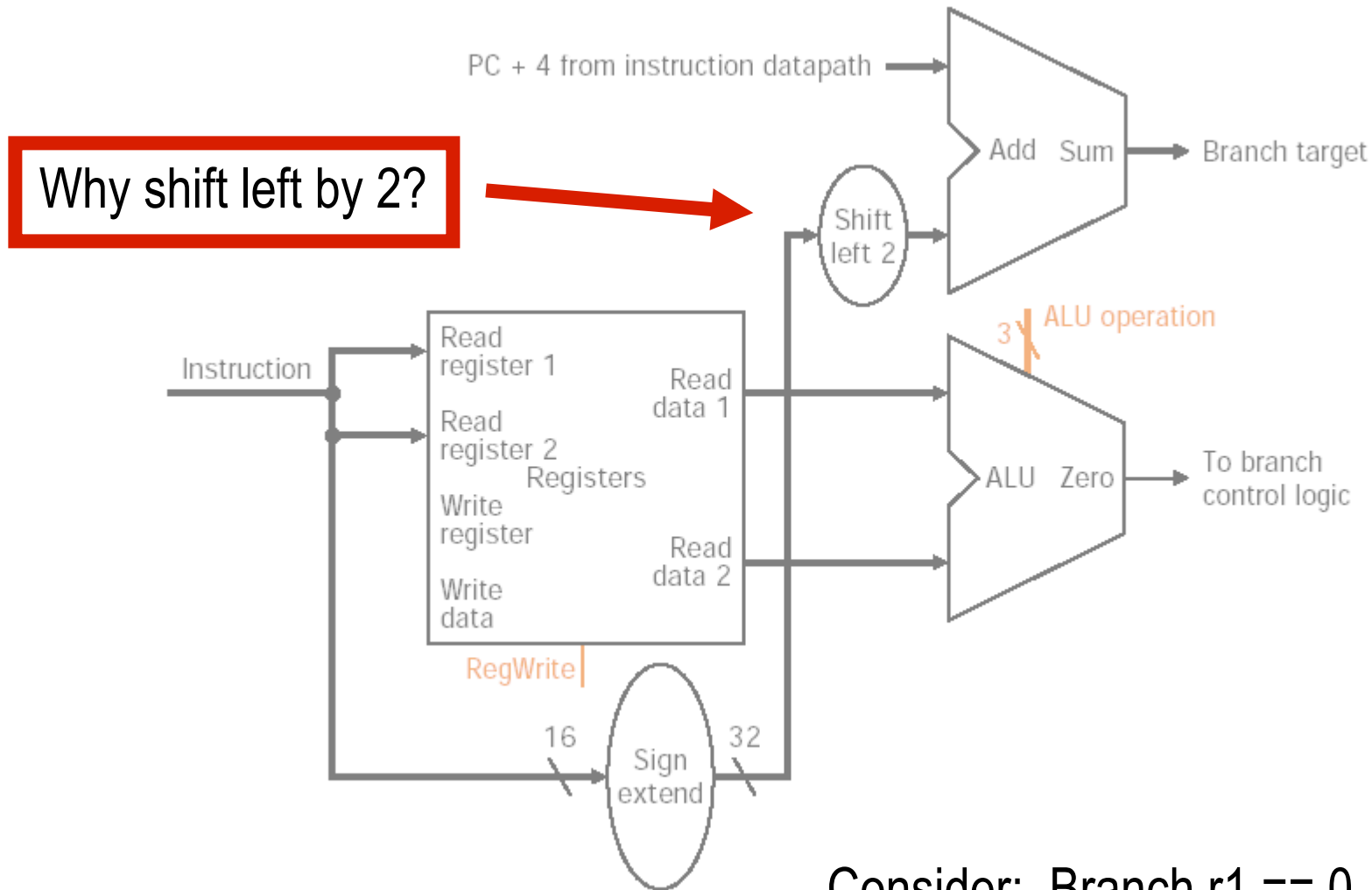

Consider: Branch r1 == 0, TARGET

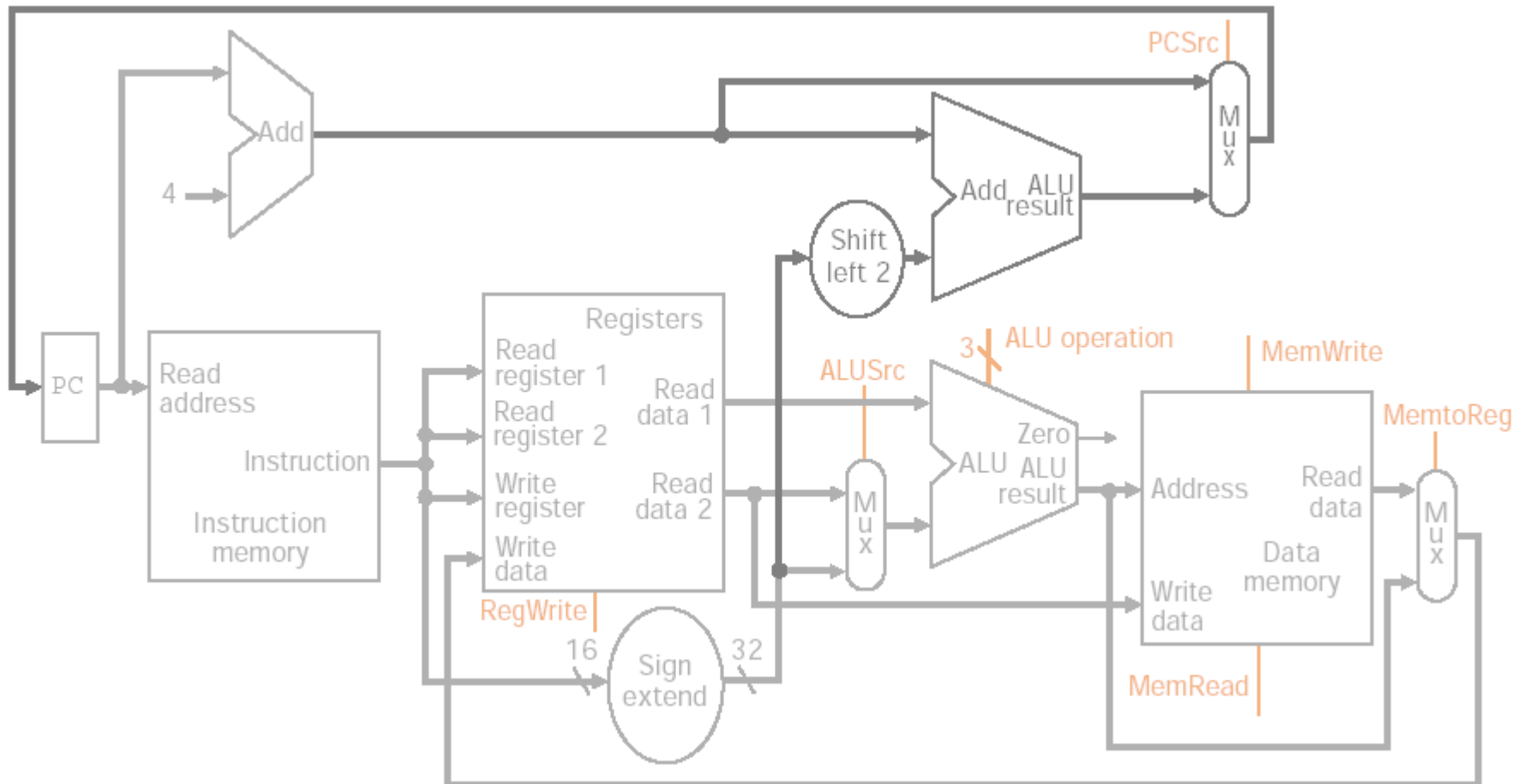Add Branch to Datapath (ALU + MEM + Fetch + Branch)



What will zero be connected to?

MIPS Instruction Quirk


- The Destination Register may be in different locations
 - 11-15: Loads use rt
 - 16-20: All R-Types use rd

	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits
R:	op	rs	rt	rd	shamt	funct


	6 bits	5 bits	5 bits	26 bits
I:	op	rs	rt	address / immediate





Again, The Magic of the Mux!

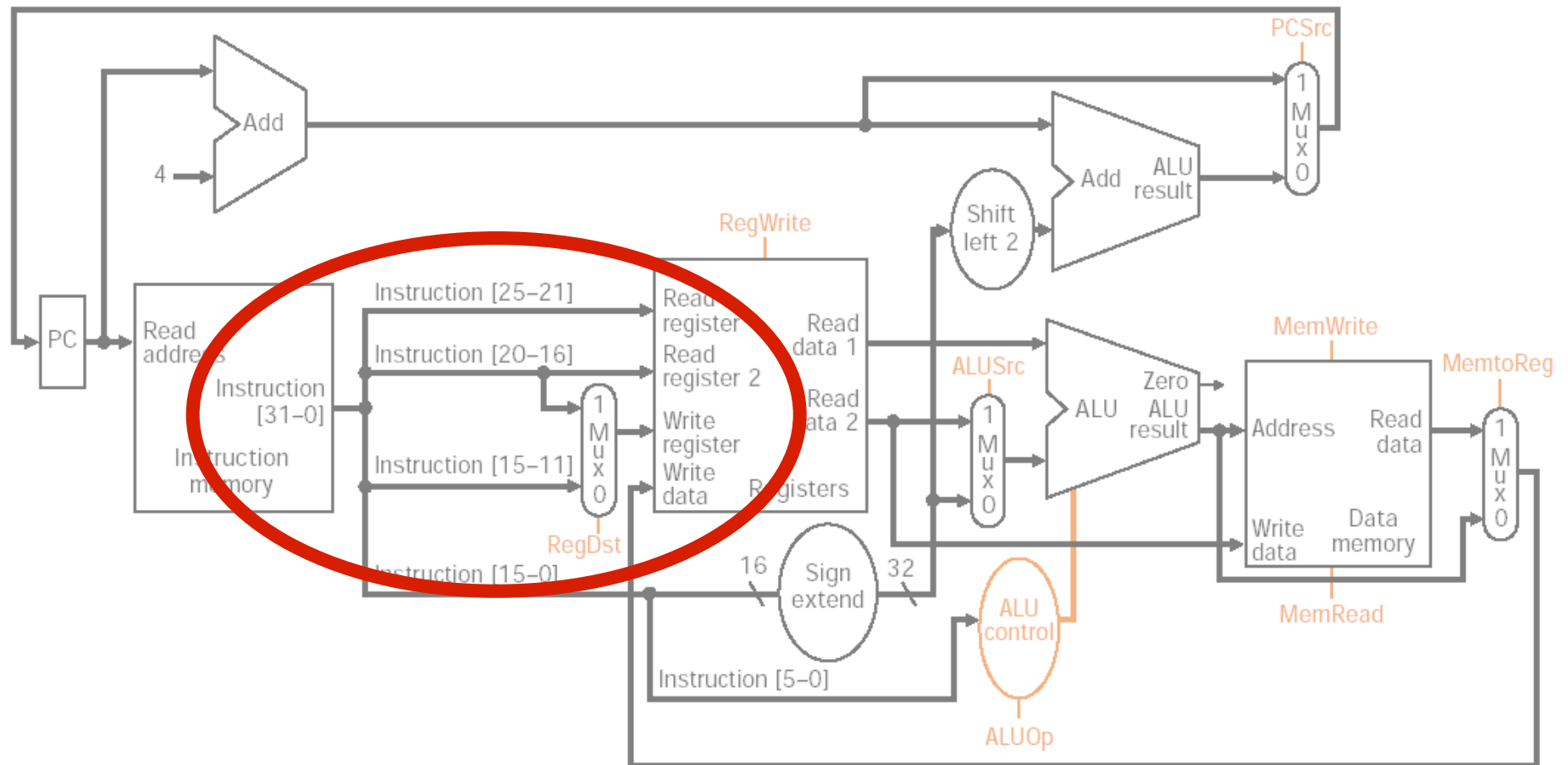

Ugh, what is going on here!?!

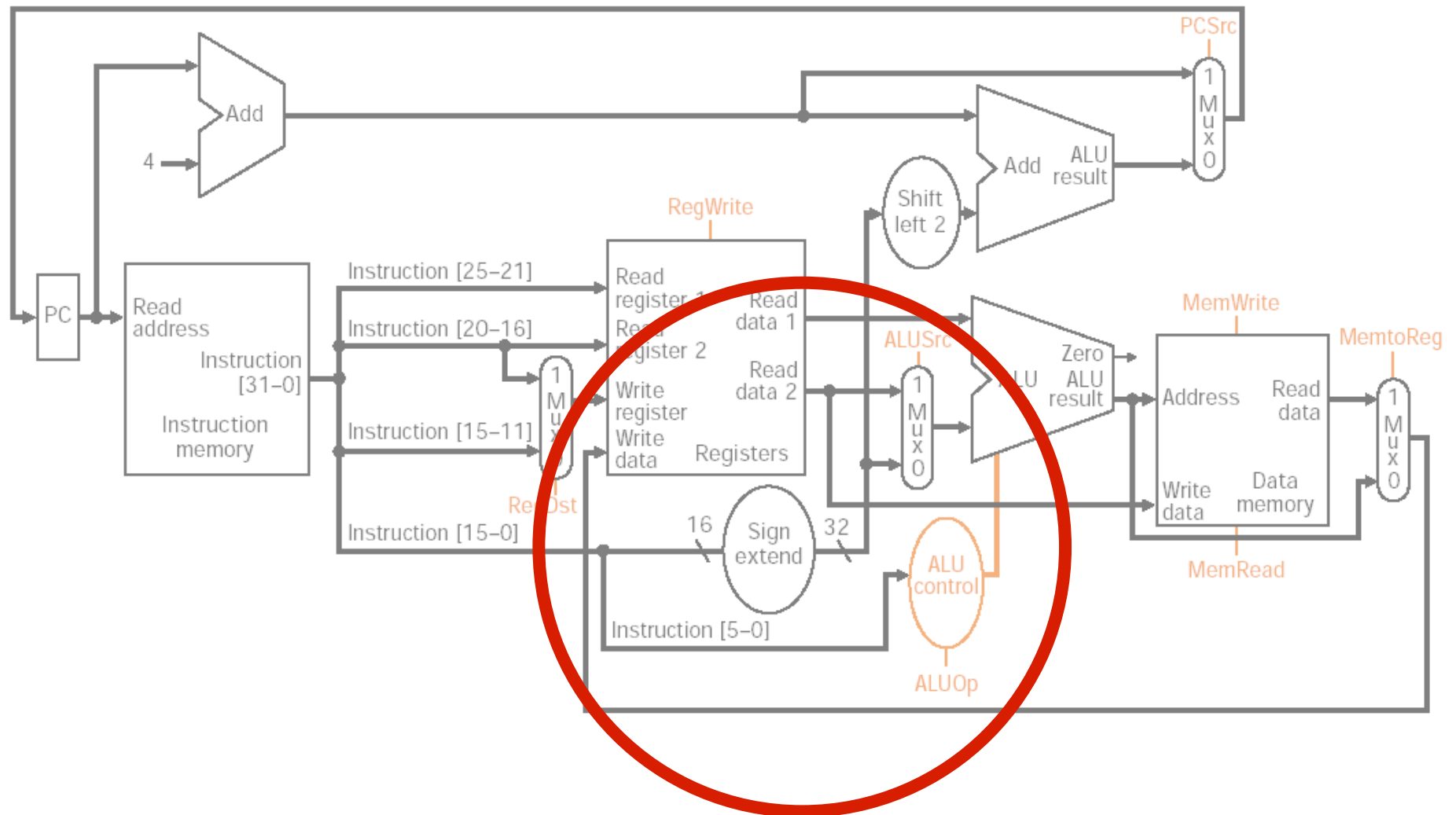

Control vs. Datapath (Blurring the Line)

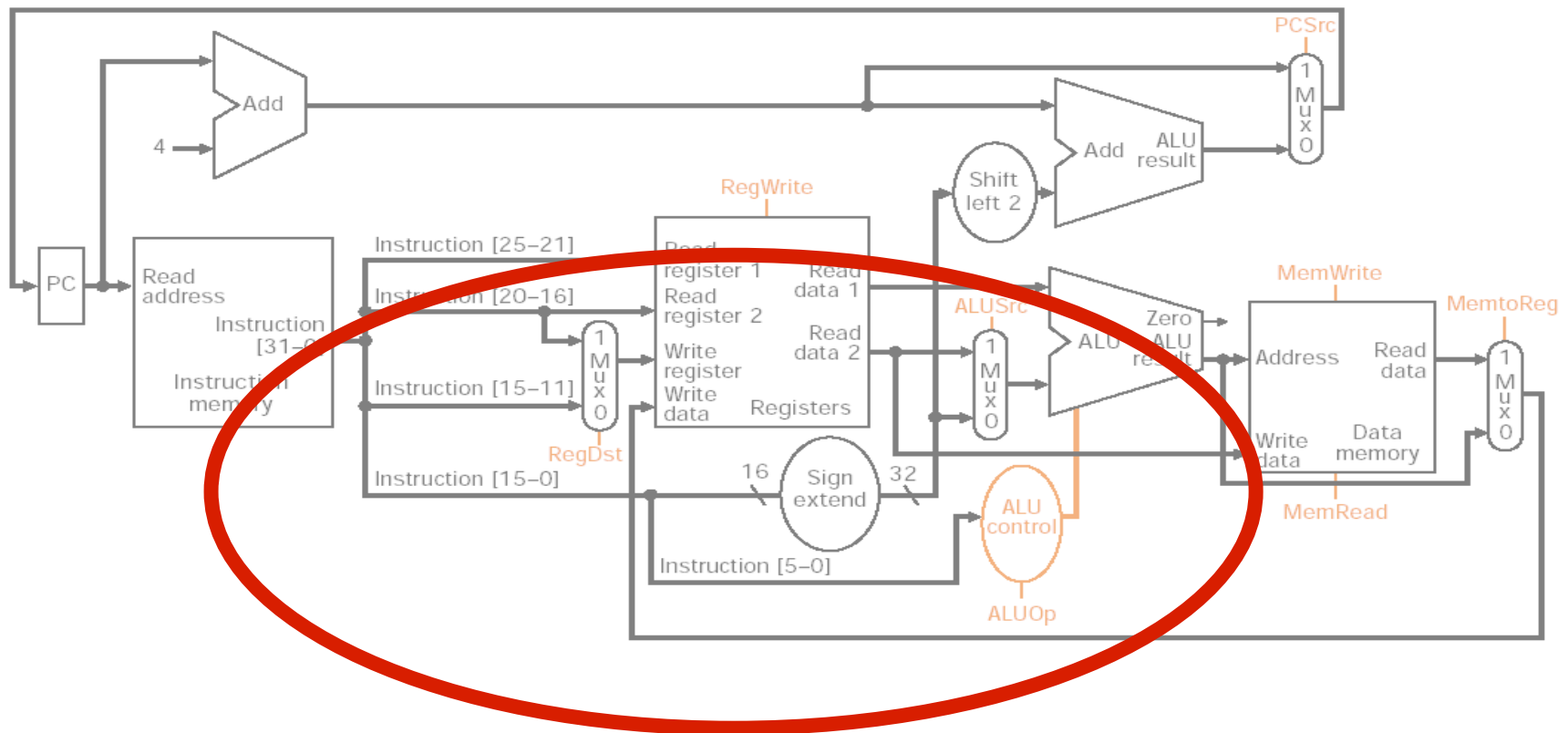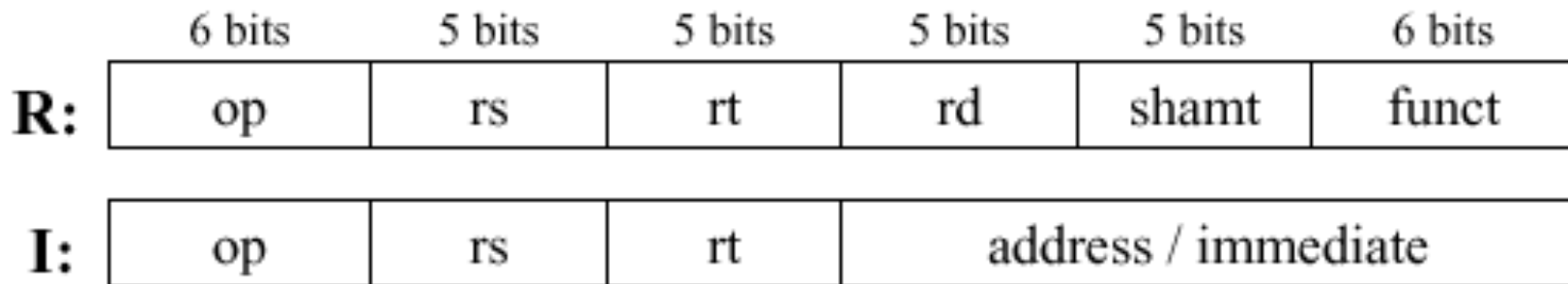

What is Control?


Control


“The component of the processor that commands the datapath, memory, and I/O devices according to the instructions of the program.” – P&H

Control

The component of the processor that commands the datapath, memory, and I/O devices according to the instructions of the program. - DIA

Full Datapath with Control

 

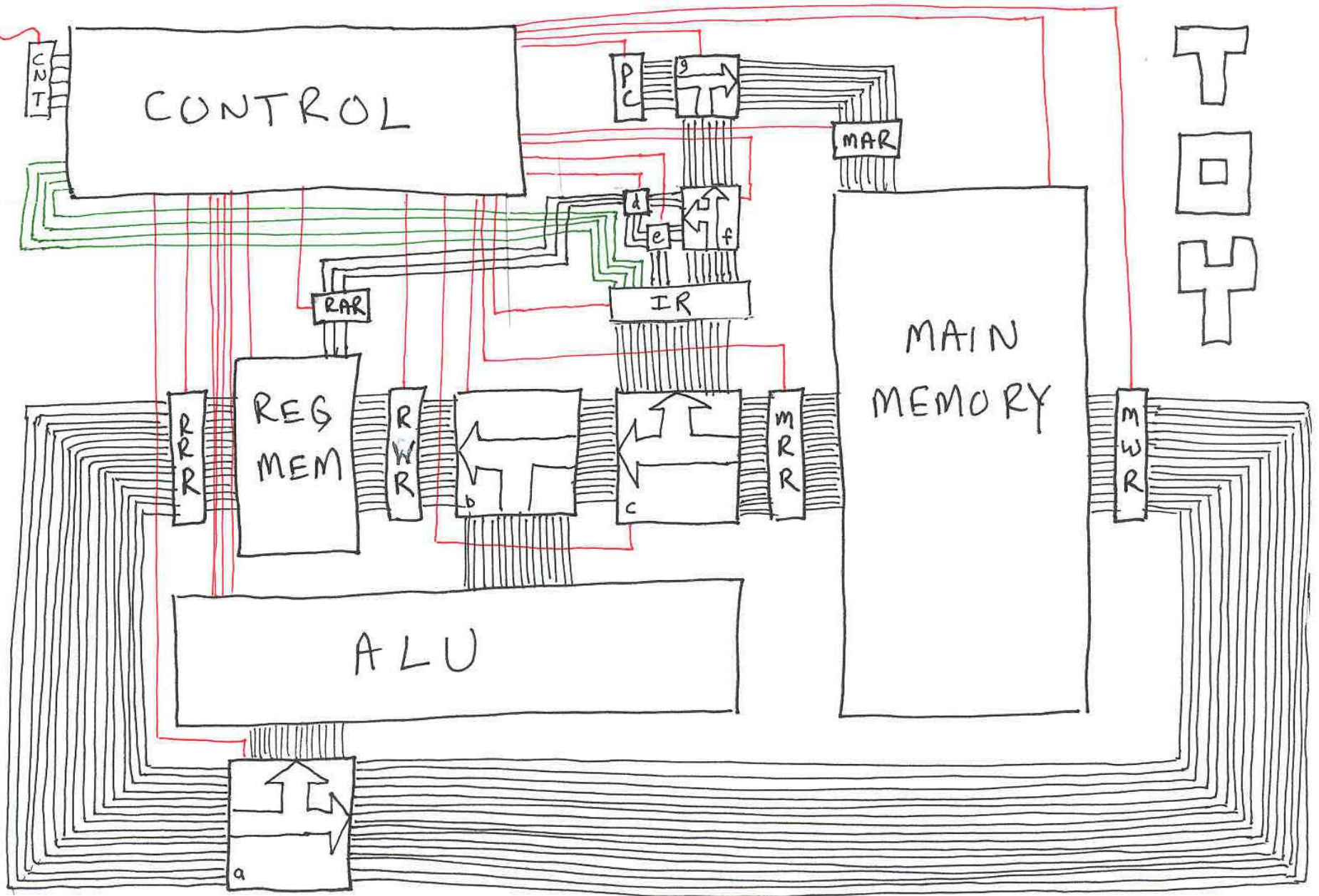

Summary and Next Steps

- The book doesn't define datapath well
- Computation and State elements compose datapath
- Look for reuse across instruction types
- Build minimal HW datapath with the magic of the mux

Next Steps

- Need to define control
- Understand Timing
 - Single cycle
 - Multi-cycle
- Understand how to implement control

For Next Time

- Review finite state machines:

