
Lecture 8: Control

COS / ELE 375

Computer Architecture and Organization

Princeton University
Fall 2015

Prof. David August

1

Datapath and Control

Datapath


The collection of state elements, computation elements, and interconnections that together provide a conduit for the flow and transformation of data in the processor during execution. - DIA

Control

The component of the processor that commands the datapath, memory, and I/O devices according to the instructions of the program. - P&H


2

A Real MIPS Datapath

 

3


Datapath with Control

 

4

Datapath with Control

 - Memory reference: lw, sw
- Arithmetic/logical: add, sub, and, or, slt
- Control flow: beq, j (see book)




5

The Control Unit

- Generates Control Signals

 
RegDst, Branch, MemRead, MemtoReg, ALUOp, MemWrite, ALUSrc, RegWrite



6

The Control Unit

 - Generates Control Signals
- Uses Op Field [31-26]




R:	6 bits op	5 bits rs	5 bits rt	5 bits rd	5 bits shamt	6 bits funct
I:	op	rs	rt	address / immediate		
J:	target address					

7

Control Signals

PCSrc

 - True: $PC = \text{SignExt}(\text{Imm}_{16}) \ll 2 + PC + 4$
 - False: $PC = PC + 4$
 - PCSrc = Branch & Zero
- (Branch from Control, Zero from ALU)





8

Control Signals

RegDst

  - True: WriteReg = Inst[15-11]
- False: WriteReg = Inst[20-16]





9

Control Signals

ALUSrc

  - True: SignExt(Imm₁₆)
- False: RegisterData2




10


Control Signals

ALUControl

 - Values: And, Or, Add, Sub
- Uses Funct Field



ALUControl	Function
000	AND
001	OR
010	add
110	subtract
111	set on less than

 

11


ALUControl

ALUOp		Funct field						Operation	
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0		
0	0	X	X	X	X	X	X	010	lw/sw
X	1	X	X	X	X	X	X	110	beq
1	X	X	X	0	0	0	0	010	} R-Type
1	X	X	X	0	0	1	0	110	
1	X	X	X	0	1	0	0	000	
1	X	X	X	0	1	0	1	001	
1	X	X	X	1	0	1	0	111	

ALUControl	Function
000	AND
001	OR
010	add
110	subtract
111	set on less than

12

ALU Control Combinational Implementation

 


13

Control Signals

MemtoReg


 
- True: RegisterWriteData = MemReadData
- False: RegisterWriteData = ALUResult



14

Control Signals


- MemRead
- MemWrite
- RegWrite

  

15

The Control Unit

 - Generates Control Signals
- Uses Op Field [31-26]



	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits
R:	op	rs	rt	rd	shamt	funct
I:	op	rs	rt	address / immediate		
J:	op	target address				

16

Control Design: Inputs

Opcode	op5	op4	op3	op2	op1	op0	Value
R-Format	0	0	0	0	0	0	0 ₁₀
lw	1	0	0	0	1	1	35 ₁₀
sw	1	0	1	0	1	1	43 ₁₀
beq	0	0	0	1	0	0	4 ₁₀

Where were these values chosen?



17

Control Design: Outputs


Signal	R-Format	lw	sw	beq
RegDst				
ALUSrc				
MemtoReg				
RegWrite				
MemRead				
MemWrite				
Branch				
ALUOp1				
ALUOp2				



You fill it out with: 0, 1, X (don't care) - check with book


18

Datapath with Control

 

19


Combinational Implementation

 

20




Single Cycle Implementation

 


- All of the logic is combinational
- We wait for everything to settle down
 - ALU might not produce “right answer” right away
 - Use write signals along with clock to determine when to write
- Cycle time determined by length of the longest path

Single Cycle Implementation

 Calculate cycle time assuming negligible delays except:
 memory (2ns), ALU/adders (2ns), register file access (1ns)



Single Cycle Implementation

 

Load Word is longest running instruction
 (prove to yourself by computing time for sw, br, R-type)
 memory (2ns), ALU/adders (2ns), register file access (1ns)
 $2ns + 1ns + 2ns + 2ns + 1ns = 8ns$

Magic Moment!


At this point, you should be able to design a computer!

1. Analyze instruction set for datapath requirements
2. Select set of datapath components
3. Assemble datapath meeting the requirements
4. Analyze implementation of each instruction to determine setting of control signals
5. Assemble the control logic
6. Set clock rate

25

What's Wrong with Single Cycle?

 Calculate cycle time assuming negligible delays except:
 memory (2ns), ALU/adders (2ns), register file access (1ns)



What's Wrong with Single Cycle?

memory (2ns), ALU/adders (2ns), register file access (1ns)

Inst.	Inst. Mem	Reg. Read	ALU	Data Mem	Reg. Write	Total
ALU	2	1	2		1	6
lw	2	1	2	2	1	8
sw	2	1	2	2		7
br	2	1	2			5


27

What's Wrong with Single Cycle?

Arithmetic & Logical




Load

 

Critical Path

Store

 

Branch



- Long Cycle Time
- All instructions take as much time as the slowest
- Real memory is not so nice as our idealized memory (cannot always get the job done in fixed amount of time)

28

How Bad?

- Assume: 100 instructions executed
 - 25% of instructions are loads (8ns),
 - 10% of instructions are stores (7ns),
 - 45% of instructions are adds (6ns), and
 - 20% of instructions are branches (5ns).
- Single-cycle execution:

$$100 * 8ns = 800 ns$$
- Optimal execution:


$$25*8ns + 10*7ns + 45*6ns + 20*5ns = 640 ns$$

$$\text{Speedup} = 800/640 = 1.25$$

29

Other Problems

 
- Instruction and Data Memory are the same
- Some units hold value long after job is complete
 - Could reuse ALU for example
 - Underutilized resources (wasteful of area/power)



30

Other Problems

 - What about floating point or other VERY LONG instructions?




31



Multicycle Approach


- Break up the instructions into steps, one per cycle
 - balance the amount of work to be done
 - restrict each cycle to use only one major functional unit
- At the end of a cycle
 - store values for use in later cycles (easiest thing to do)
 - introduce additional “internal” registers to hold values between cycles

Multicycle Approach

 

Architectural vs. Microarchitectural State?
Register File?


Multicycle Control More Mux Magic

 

Multicycle Control

- Reuse datapath components
 - ALU used to compute address and to increment PC
 - Memory used for instruction and data
- Control signals not determined solely by instruction
 - What should the ALU do for a “subtract” instruction?


Multicycle Control

 

37

Use Finite State Machine For Control

 - Set of states
- Next state function (determined by current state and the input)
- Output function (determined by current state and possibly input)



- We'll use a Moore machine (output based only on current state)
- To derive FSM, need steps of the instruction!



Step 4: (R-type or memory-access)

- Loads and stores access memory

```
MDR = Memory[ALUOut];
OR
Memory[ALUOut] = B;
```

- R-type instructions finish

```
Reg[IR[15-11]] = ALUOut;
```

Writes takes place at the end of the cycle on the edge

Step 5: Write-Back

```
Reg[IR[20-16]] = MDR;
```

What about all the other instructions?


Summary Of Steps

Step name	Action for R-type instructions	Action for memory-reference instructions	Action for branches	Action for jumps
Instruction fetch	IR = Memory[PC] PC = PC + 4			
Instruction decode/register fetch	A = Reg [IR[25-21]] B = Reg [IR[20-16]] ALUOut = PC + (sign-extend (IR[15-0]) << 2)			
Execution, address computation, branch/jump completion	ALUOut = A op B	ALUOut = A + sign-extend (IR[15-0])	if (A ==B) then PC = ALUOut	PC = PC [31-28] (IR[25-0]<<2)
Memory access or R-type completion	Reg [IR[15-11]] = ALUOut	Load: MDR = Memory[ALUOut] or Store: Memory [ALUOut] = B		
Memory read completion		Load: Reg[IR[20-16]] = MDR		


Implementing the Control

- Values of control signals are dependent upon:
 1. instruction is being executed
 2. step is being performed
- Using steps, specify a finite state machine
 - specify the finite state machine graphically, or
 - use “microprogramming” (more on this next time)
- Implementation can be derived from specification

Graphical Specification of FSM

 

Graphical Specification of FSM

 

Performance Evaluation

- What is the average CPI?
 - state diagram gives CPI for each instruction type
 - workload gives frequency of each type

Type	CPI _i for type	Frequency	CPI _i x freq _i
Arith/Logic	4	40%	1.6
Load	5	30%	1.5
Store	4	10%	0.4
branch	3	20%	0.6
			Average CPI: 4.1

52

Single/Multi-Cycle Summary

$$CPU\ time = \frac{Instructions}{Program} \times \frac{Cycles}{Instruction} \times \frac{Seconds}{Cycle}$$

Single Cycle Datapath:

- CPI = 1!!
- Long cycle time ☹️
(critical path based)

Multiple Cycle Datapath:

- Short cycle time!!
- CPI = 3-5 ☹️

Can we achieve a CPI of 1 (on average)
with a clock cycle time
similar to the multiple cycle datapath?

53