

Lecture 15:

Register Transfer Language and Verilog

COS / ELE 375

Computer Architecture and Organization

Princeton University
Fall 2015


Bochao Wang
(Based on slides by David Penry and Neil Vachharajani)
(Prof. David August)

1

RTL Tools

RTL, just like (most) programming languages:

 - Precise and unambiguous
- Programmer must debug
- Code can be checked automatically for certain properties
 - Type checking
 - Check RTL model against more abstract state machine
- Tools can process the code
 - RTL → simulator
 - RTL → processor
- RTL →



3

RTL (Register Transfer Language)

- Designing processors at the gate level is difficult
- Use a higher-level language

RTL: a language for describing the behavior of computers in terms of step-wise register contents

2

Hardware Description Languages

- Used to describe hardware for simulation and synthesis
- Why? Designs are too big to just draw schematics
- Major languages:
 - Verilog
 - Cadence, Inc.
 - Emphasis on practical use (I/O well-defined, ability to record)
 - Possibly most widely used
 - VHDL
 - Department of Defence
 - Emphasis on abstraction (derived from Ada)
 - Popular in academic circles, Europe; required of defence contractors
 - SystemC
 - Synopsys, Inc.
 - Emphasis is "higher-level" simulation – really just a C++ template library
 - Up-and-coming

4

Simulation vs. Synthesis



- HDLs are used for both simulation and synthesis
- Simulation: does the design work?
 - Can also be used for "does the design meet timing?"
- Synthesis: generate a circuit that is equivalent
 - Recognize state and combinational logic
 - Optimize the circuit

Not all valid HDL programs are synthesizable

5

  Example

Modules have initial, **continuous**, and always blocks




```
module example(a, b, c, f, e);
    input a, b, c;
    output f, e;
    wire d;
    and g1(d, a, b);
    not g2(e, c);
    or g3(f, d, e);
endmodule
```

Youpyo Hong, Dongguk University


7

Verilog Design Flow

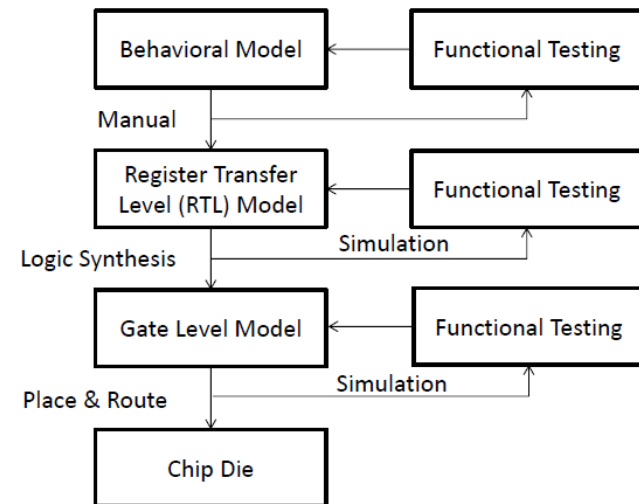

6

Modified Example

 

```
module example(a, b, c, f, e);
    input a, b, c;
    output f, e;
    assign d = a & b;
    assign e = ~c;
    assign f = d | e;
endmodule
```

Youpyo Hong, Dongguk University

- Use assign statement for combinational circuit
- Note the bit-wise operators (implies wire width...)

8

Elements of Verilog

9

Basic syntax

- `;` is the statement terminator (terminator, not separator)
- `/* */` for multi-line comments
- `//` can be used for single-line comments
- Constants can have bit-width and radix:
 `<bit-width>'<radix><val>`
 `32'h1234ab34` = 1234ab34₁₆
 `8'b0100_0110` = 01000110₂; note that underlines are legal

10

Datatypes

- 4-valued logic: 0, 1, x, z
 - 0, 1 – normal binary 0 and 1
 - z – high-impedance value: this is what tri-state buffers drive when they are off
 - x – simulator doesn't know; sometimes used as "don't care"
- Integers – don't use these outside of test benches
- At simulation start, all signals have x's in every bit
- Unconnected inputs to a module have value 'z'.

11

Module Overall Structure

```
module the_design ( input, output );  
    Declarations: ports, constants, variables(wire, reg)  
    Instantiations of other modules  
    Continuous assignment: assign y = ...  
    Behavioral statements (initial, always) {  
        procedural blocking assignment  
        procedural nonblocking assignment  
    }  
endmodule
```

12

Signals

- Signal: a “variable” that can have values assigned “ahead of time”
- Can be thought of as a wire or a group of wires
- Syntax:
 <kind> [<width specifier>] name, name, ...;
- Examples:
 reg [15:0] IR;
 wire [3:0] a; a[3] is MSB
 wire [1:8] b; b[1] is MSB //not recommend
 wire doit;
- Registers vs. wires:
 - Reg: inside “always” block, lhs, e.g. IR = ...
 - Wire: outside “always” block, lhs, e.g. assign a = ...

13

Register Transfer Language?

- Variables correspond to the hardware registers
- “always” blocks

```
Module D_FlipFlop(Q, D, CLK);  
    output Q;  
    reg Q;  
    input D, CLK;  
    always @(negedge CLK) // Sensitivity List  
    begin // Not needed for 1 statement  
        Q <= D; // Note: No assign  
    end  
endmodule
```

15

Wires

- Wires need not be declared unless it is multiple wires

```
module example(b, c);  
    input b;  
    output c;  
    wire a;           // not necessary  
    wire [3:0] d;      // necessary  
    ...  
    assign c = b | a;  
endmodule
```

14

Module Overall Structure

```
module the_design ( input, output );  
    Declarations: ports, constants, variables(wire, reg)  
    Instantiations of other modules  
    Continuous assignment: assign y = ...  
    Processes(initial, always) {  
        procedural blocking assignment  
        procedural nonblocking assignment  
    }  
endmodule
```

16

Modules

- Allow you to organize the design hierarchically
- Allow structural reuse of the design

- Defining a module:

- Example:

```
module flop (clk, D, Q); // name, list of ports
    input clk;           // define directions of ports
    input D;
    output Q;

    ... // code to do things

endmodule
```

- Instantiating a module:

```
flop U1 (.clk(someclk), .D(someD), .Q(someQ));
```

17

Kinds of assignments

- Continuous (`assign =`)
 - Only to "wire"
 - Always sensitive to things on the right-hand side
- Blocking (`=`)
 - Made inside a process
 - Only to "reg"
 - Value of lhs changes immediately
- Non-blocking (`<=`)
 - Made inside a process
 - Only to "reg"
 - Value of lhs changes only after all rhs have been evaluated
 - A time-spec after the statement says to wait before changing the value
 - Continue executing process even if there is a time-spec

19

Module Overall Structure

```
module the_design ( input, output );
    Declarations: ports, constants, variables(wire, reg)
    Instantiations of other modules
    Continuous assignment: assign y = ...
    Processes(initial, always) {
        procedural blocking assignment
        procedural nonblocking assignment
    }
endmodule
```


18

Assignment

<code>a = b</code>	Do Sequentially (blocking, sequentially)
<code>A <= b</code>	Do RHS first (nonblocking, grab at t=0)

Which 3 are Shift Registers?
 
```
Z<=Y; Y<=X;
Y<=X; Z<=Y;
Z=Y; Y=X;
Y=X; Z=Y;
```



20

Processes

- A group of sequential statements; three kinds:
 - Initial - runs only at simulation start
 - Always – runs over and over
 - Continuous – special syntax for a common kind of always block
- Can be suspended, waiting for something to happen
 - For a signal in a group of signals to change
 - For an amount of time to pass
 - For a signal to become true (I've never needed this)

21

Assignment examples

```
reg rst_l, Q;
wire cachehit;

initial begin
    rst_l = 0;      // blocking
    #300;
    rst_l = 1;      // blocking
end

always @(posedge clk)
    Q <= #1 D;  // non-blocking

assign cachehit = comparator_matches &
    valid; // continuous
```

23

Process examples

```
reg rst_l, Q;
wire cachehit;

initial begin
    rst_l = 0;
    #300;
    rst_l = 1;
end

always @(posedge clk)
    Q <= #1 D;

assign cachehit = comparator_matches & valid;
```

22

Blocking a process

- Wait for signals to change:
always @(signal1 or signal2)
- Wait for a signal edge:
always @(posedge clk or negedge rst_l)
- Wait for time:
300;
300 a = b; // can also put before a statement
- Wait for logical value:
wait(b); // I've never used this

24

Operators

- Most of the operators look like C:
 - Bitwise operators: `&`, `|`, `~`, `^`
 - Logical operators: `&&`, `||`, `!`
 - Comparisons: `==`, `!=`, `<`, `<=`, `>`, `>=`
 - If either operand is `x` or `z`, they return `FALSE`.
 - Arithmetic: `+`, `-`, `*`, `/`, `%`, `<<`, `>>`
 - Choice: `?:`
- Order of operations may differ from C; use parenthesis
- Special operators:
 - Comparison with `x` or `z` values: `===`, `!==`
 - Bitwise operators can be used as reduction operators:
`(|x)` = or all the bits of `x` together.

25

Case statements

- Rather different from C switch statements:

```
case (myvar)
1 : dothis = 1;
2 : dothat = 3;
3 : dosomemore = 4;
default: noneoftheabove = 1;
endcase
```
- Note that there are no fall-throughs
- Multiple statements inside one case require `begin/end` around them

27

Statements

- Control structures
 - C-like: `if`, `while`, `for`
 - `forever` – do following statement forever
 - `repeat (<#>)` – do following statement a number of times
 - `case` (see next slide)
- Parallel control structures
 - `fork/join` – do statements in between in parallel
- Signal overrides
 - `force` – override the value of a signal
 - `release` – stop overriding the value of a signal

26

Example: 4 to 1 Mux

```
module mux4_to_1 (out, i0, i1, i2, i3, s1, s0);
    output out;
    input i0, i1, i2, i3;
    input s1, s0;
    reg out;
    always @(s1 or s0 or i0 or i1 or i2 or i3)
    begin
        case ({s1, s0})
            2'b00: out = i0;
            2'b01: out = i1;
            2'b10: out = i2;
            2'b11: out = i3;
            default: out = 1'bx; // x is don't care
        endcase
    end
endmodule
```

28

Parameters

- Increases ability to reuse modules
- Defining a parameter (with a default value):
`parameter me = 3;`
- Overriding the default value
`defparam myunit.me = 4;`
 - Can also use a #(value) syntax when instantiating for modules with small numbers of parameters:
e.g. `module my_module #(parameter BIT_WIDTH = 32, ...)`
(input clk, input [BIT_WIDTH-1:0] addr, output a...)

29

Preprocessor directives

- Always begin with a back-tick
- ``define name value`
 - defined values are referenced as ``name`

31

Using the mux module

- It's a 4-input mux for busses with a 'width' parameter for the size of the bus

```
wire [7:0] A,B,C,D, result;
wire [1:0] sel;

mux4 mymux (.out(result), .in0(A), .in1(B),
            .in2(C), .in3(D), .sel(sel));
defparam mymux.width = 8;
```

OR

```
mux4 #(8) mymux (.out(result), .in0(A), .in1(B),
                .in2(C), .in3(D), .sel(sel));
```

30

A Sample Finite State Machine

```
reg [1:0] state;
`define IDLE 2'b00
`define READ 2'b01
`define WRITE 2'b10
`define DONE 2'b11

always @(posedge clk or negedge rst_1)
  if (~rst_1) state <= `IDLE;
  else
    case (state)
      `IDLE:
        if (req)
          if (wr) state <= `WRITE;
          else state <= `READ;
        else state <= `IDLE; // not strictly necessary
      `READ:
        state <= `DONE;
      `WRITE:
        state <= `DONE;
      `DONE:
        state <= `IDLE;
      default:
        state <= `IDLE;
    endcase
```

32

Dealing with Synthesis

- Things you can't synthesize reliably:
 - Some for loops (hard to guess)
 - @() in the middle of a process
 - **Time specifiers**
 - force/release
- Watch out for hidden latches!

```
always @(a)
  c = a | b;
```

 - Actually creates a latch
 - All things on the rhs must go on the sensitivity list unless you are trying to create a state element
- Using don't cares:
 - If you really don't care about a value, assign x to it, and the synthesis tool will choose a value which simplifies the logic

33

My Rules

- Make all flops (edge-sensitive always blocks) use a non-blocking assignment with #1 delay
 - Easier to see what's going on in waveforms
- Make all other always blocks use blocking assignment and use complete sensitivity lists
 - always @(*) for next state logic combinational
 - always @(posedge clk) for sequential
- Do combinational logic in continuous assignments except for next state logic

34

Another Sample Finite State Machine

```
module fsm
(
    input      clk,
    input      rst,
    input      in,
    output     redOut,
    output     yellowOut,
    output     greenOut
);

localparam RED = 0;
localparam YELLOW = 1;
localparam GREEN = 2;

reg [1:0] state_f;
reg [1:0] state_next;

// Combinational Logic
always @ *
begin
    state_next = state_f;
    case (state_f)
        RED:
            if (in)
                state_next = GREEN;
        YELLOW:
            if (in)
                state_next = RED;
        GREEN:
            if (in)
                state_next = YELLOW;
        default: state_next = RED;
    endcase
end

// Sequential Logic
always @ (posedge clk)
begin
    if (rst)
        state_f <= RED;
    else
        state_f <= state_next;
    end
end
```

35

Thank you

36

Using the regfile2 module

- You should use this module for your register file.
 - It synthesizes properly
 - It has a nice task for displaying the register file contents
- Interesting characteristics:
 - One read ports, one read/write port
 - Port A writes if the enable bits are set (bytes are controlled individually); it will always read as well
 - Port B can only read
 - Clocked on the positive edge of the clock (you can't do the write in first half, read in second half trick from P & H)
- If you name your datapath DATA (the instance name, not the module name), and make IR_Enable a signal indicating when the IR is to be loaded with a new instruction, you can uncomment code in monitors.v to get automatic register dumps before each instruction.

37

Functions and tasks

- Functions are like C functions, but cannot have side effects
- Tasks do not have return values, but can have side effects

- Examples:

```
function [31:0] add1;
    input [31:0] x;
    begin
        add1 = x + 1;
    end
endfunction
```

```
task addtask;
    input [31:0] x;
    output [31:0] y;
    begin
        y = x + 1;
        mycrazysignal = 3;
    end
endtask
```

38

I/O

- Displaying data:
`$display(<format string>, ...);`
 - Like printf, but
 - %b gives binary; %h gives hex
 - %t formats a time value
 - automatically puts on a newline
- Recording signals:
 - `$dumpfile(<file name>);` – set the dumpfile name
 - `$dumpvars(<# levels>, <hierarchy>);`
 - Adds signals below a particular point in the hierarchy to the list of signals to dump; only decends the hierarchy for the number of levels specified; 0 means no limit
 - `$dumpon;` - turns on dumping
 - `$dumpoff;` - turns off dumping

39

Simulation control

- `$finish;` – end simulation and exit the simulator
- `$stop;` – stop simulating; go to the command-line interface

40