 


Lecture A3: Boolean Circuits



George Boole
(1815 – 1864)




Claude Shannon
(1916 – present)

Architecture

Lecture A1 – A2.

- TOY machine.

 

Lecture A3 – A4.

- Digital circuits.

Lecture A5.

- Putting it all together.



Digital Circuits

What is a digital system?



Why digital systems?



Basic abstraction.

- On, off.
- Switch that can turn something on or off.

Digital circuits and you.

- Computer microprocessors.
- Antilock brakes.
- VCR.
- Cell phone.

Switches

Abstract switch.

- Electrical (transistor).
- Electro-mechanical (relay).
- Hydraulic (water valve).













Hydraulic OR Gate

Logical Gates

Logical gates.

- Fundamental building blocks.

          

NOT

AND


OR

5

Multiway AND Gates

$\text{AND}(x_0, x_1, x_2, x_3, x_4, x_5, x_6, x_7)$.

- 1 if all inputs are 1.
- 0 otherwise.

 


6

Multiway OR Gates

$\text{OR}(x_0, x_1, x_2, x_3, x_4, x_5, x_6, x_7)$.

 - 1 if at least one input is 1.
- 0 otherwise.



7

Boolean Algebra

History.

- Developed by Boole to solve mathematical logic problems (1847).
- Shannon first applied to digital circuits (1939).

Basics.

- Boolean variable: value is 0 or 1.
- Boolean function: function whose inputs and outputs are 0, 1.

Relationship to circuits.

- Boolean variables: signals.
- Boolean functions: circuits.


8

Truth Table

Truth table.

- Systematic method to describe Boolean function.
- One row for each possible input combination.
- N inputs $\Rightarrow 2^N$ rows.

AND Truth Table		
x	y	AND
0	0	0
0	1	0
1	0	0
1	1	1

 

9

Truth Table

Truth table.

- 16 Boolean functions of 2 variables.
 - every 4-bit value represents one

Truth Table for All Boolean Functions of 2 Variables									
x	y	ZERO	AND	???	X	???	Y	XOR	OR
0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1

Truth Table for All Boolean Functions of 2 Variables									
x	y	NOR	EQ	Y'	???	X'	???	NAND	ONE
0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1

10

Truth Table

Truth table.

- 16 Boolean functions of 2 variables.
 - every 4-bit value represents one
- 256 Boolean functions of 3 variables.
 - every 8-bit value represents one
- 2^{2^N} Boolean functions of N variables!

Some Functions of 3 Variables							
x	y	z	AND	OR	MAJ	ODD	MUX
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	1	0	1	0
0	1	1	0	1	1	0	1
1	0	0	0	1	0	1	1
1	0	1	0	1	1	0	0
1	1	0	0	1	1	0	1
1	1	1	1	1	1	1	1

11

Universality of AND, OR, NOT

Any Boolean function can be expressed using AND, OR, NOT.

- "Universal."
- $XOR(x,y) = xy' + x'y$

Expressing XOR Using AND, OR, NOT							
x	y	x'	y'	x'y	xy'	x'y + xy'	XOR
0	0	1	1	0	0	0	0
0	1	1	0	1	0	1	1
1	0	0	1	0	1	1	1
1	1	0	0	0	0	0	0

Exercise: {AND, NOT}, {OR, NOT}, {NAND} are universal.

12

Sum-of-Products

Any Boolean function can be expressed using AND, OR, NOT.

- Sum-of-products is systematic procedure.
 - form AND term for each 1 in Boolean function
 - OR terms together


Expressing MAJ Using Sum-of-Products								
x	y	z	MAJ	$x'yz$	$xy'z$	xyz'	xyz	$x'yz + xy'z + xyz' + xyz$
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0
0	1	1	1	1	0	0	0	1
1	0	0	0	0	0	0	0	0
1	0	1	1	0	1	0	0	1
1	1	0	1	0	0	1	0	1
1	1	1	1	0	0	0	1	1

13

Translate Boolean Formula to Boolean Circuit

Use sum-of-products form.

- $XOR(x, y) = xy' + x'y$.

 


14

Translate Boolean Formula to Boolean Circuit

Use sum-of-products form.

 - $MAJ(x, y, z) = x'yz + xy'z + xyz' + xyz$.




15

Simplification Using Boolean Algebra


Many possible circuits for each Boolean function.

- Sum-of-products not optimal.

 - $MAJ(x, y, z) = x'yz + xy'z + xyz' + xyz = xy + yz + xz$.



size = 8, depth = 4

 

size = 4, depth = 3

16

Recipe for Making Combinational Circuit

Ingredients.

- AND
- OR
- NOT
- wire



White Chocolate Mousse
Cake, Balducci's

Instructions.

- Step 1: represent input and output signals with Boolean variables.
- Step 2: construct truth table to carry out computation.
- Step 3: derive (simplified) Boolean expression using sum-of-products.
- Step 4: transform Boolean expression into circuit.

17

ODD Parity Circuit

ODD(x, y, z).

- 1 if odd number of inputs are 1.
- 0 otherwise.


Expressing ODD Using Sum-of-Products								
x	y	z	ODD	$x'y'z$	$x'yz'$	$xy'z'$	xyz	$x'y'z + x'yz' + xy'z' + xyz$
0	0	0	0	0	0	0	0	0
0	0	1	1	1	0	0	0	1
0	1	0	1	0	1	0	0	1
0	1	1	0	0	0	0	0	0
1	0	0	1	0	0	1	0	1
1	0	1	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0
1	1	1	1	0	0	0	1	1

18

ODD Parity Circuit

ODD(x, y, z).

 - 1 if odd number of inputs are 1.
- 0 otherwise.



19

Let's Make an Adder Circuit

Goal: $x + y = z$.

- We build 4-bit adder: 8 inputs, 4 outputs.
(Same idea scales to 64-bit adder.)

Step 1.

- Represent input and output in binary.

	1	1	1	
	2	4	8	7
+	3	5	7	9
	6	1	6	6

	1	1	0	
	0	0	1	0
+	0	1	1	1
	1	0	0	1

	c_3	c_2	c_1	
	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
	z_3	z_2	z_1	z_0

20

Let's Make an Adder Circuit

Goal: $x + y = z$.

Step 2.

- Build truth table.

	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
	z_3	z_2	z_1	z_0

Adder Truth Table												
x_0	x_1	x_2	x_3	y_0	y_1	y_2	y_3	z_0	z_1	z_2	z_3	
0	0	0	0	0	0	0	0	0	0	0	0	
0	0	0	0	0	0	0	0	1	0	0	1	
0	0	0	0	0	0	0	1	0	0	1	0	
0	0	0	0	0	0	1	1	0	0	1	1	
0	0	0	0	0	1	0	0	0	1	0	0	
0	0	0	0	0	1	0	1	0	1	0	1	
.	
1	1	1	1	1	1	1	1	1	1	1	0	

$2^8 = 256$ rows!

21

Let's Make an Adder Circuit

Goal: $x + y = z$.

Step 2.

- Build truth table for carry bit.
- Build truth table for summand bit.

	c_3	c_2	c_1	$c_0 = 0$
	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
	z_3	z_2	z_1	z_0

Carry Bit			
x_i	y_i	c_i	c_{i+1}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Summand Bit			
x_i	y_i	c_i	z_i
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

22

Let's Make an Adder Circuit

Goal: $x + y = z$.

Step 3.

- Derive (simplified) Boolean expression.

	c_3	c_2	c_1	$c_0 = 0$
	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
	z_3	z_2	z_1	z_0

Carry Bit				
x_i	y_i	c_i	c_{i+1}	MAJ
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Summand Bit				
x_i	y_i	c_i	z_i	ODD
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


23

Let's Make an Adder Circuit

Goal: $x + y = z$.

Step 4.

 - Transform Boolean expression into circuit.




Let's Make an Adder Circuit


Goal: $x + y = z$.

Step 4.

 - Transform Boolean expression into circuit.



Lecture A1: Extra Slides

 

Two Important Combinational Circuits

Multiplexer.

- Selects an addressed input line.

Decoder.

- Converts from binary to unary.

Translates directly to circuit without sum-of-products.

Useful to implement key computer components.

Multiplexer

N-bit multiplexer.

- N address inputs, 2^N data inputs.
- 1 output.
- Copies one data input to output.
- Which one?

Ex.

- 2-bit multiplexer.
- Address inputs: s_0, s_1 .
- Data inputs: x_0, x_1, x_2, x_3 .
- Output: Q.

s_1	s_0	x_3	x_2	x_1	x_0
1	1	1	0	0	1



$$11_2 = 3_{10}$$

Q
1

2-Bit Multiplexer Circuit

MUX($x_0, x_1, x_2, x_3, s_0, s_1$).

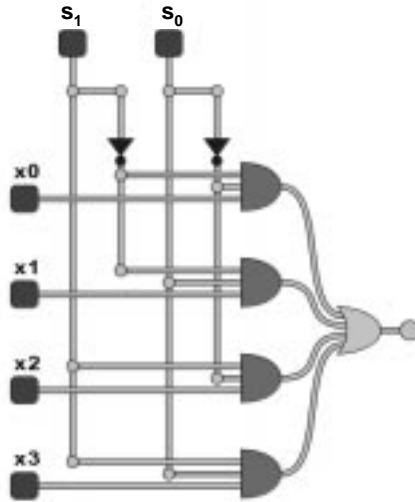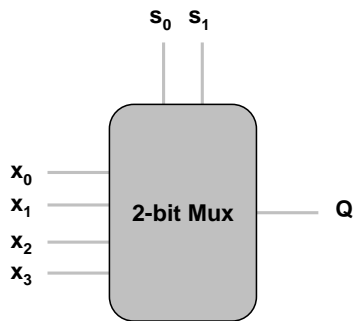- x_0 if $s_1 = 0, s_0 = 0$.
- x_1 if $s_1 = 0, s_0 = 1$.
- x_2 if $s_1 = 1, s_0 = 0$.
- x_3 if $s_1 = 1, s_0 = 1$.



30

Decoder

N-bit decoder.

- N inputs.
- 2^N outputs.
- Exactly one of outputs is 1; rest are 0.
- Which one?

Ex.

- 3-bit decoder.
- Inputs: x_0, x_1, x_2 .
- Outputs: $Q_0, Q_1, Q_2, \dots, Q_7$.



x_2	x_1	x_0	
0	1	1	$011_2 = 3_{10}$

Q_7	Q_6	Q_5	Q_4	Q_3	Q_2	Q_1	Q_0
0	0	0	0	1	0	0	0

31







3-Bit Decoder

DECODE(x, y, z).

  

32

Cheat Sheet

      

33