

# CS 126 Lecture A5: Computer Architecture

## Outline


- Introduction
- Some basics
- Single-cycle TOY design
- Multicycle TOY design
- Conclusions

CS126

13-1

Randy Wang

## What We Have

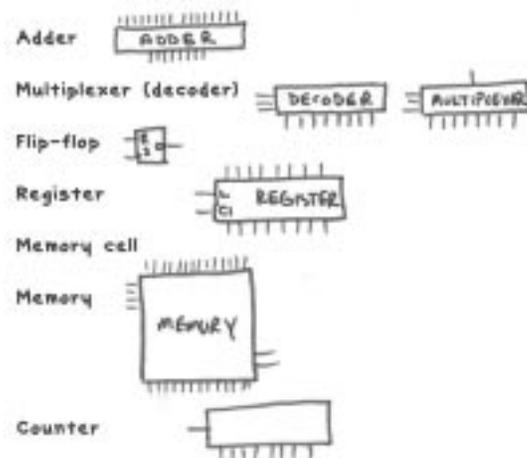

CS126

13-2

Randy Wang

## What We Want to Do

```
repeat
  fetch instruction;
  update PC;
  decode instruction;
  execute instruction;
until halt signal
```

- Remember the TOY simulator written in C?
- Now it's time to use the components we have to implement this loop in hardware!

CS126

13-3

Randy Wang

## Outline

- Introduction
- **Some basics**
- Single-cycle TOY design
- Multicycle TOY design
- Conclusions


CS126

13-4

Randy Wang
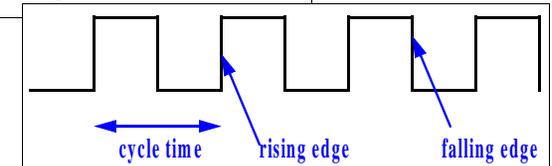
## Single Cycle vs. Multicycle Design

```
repeat
  fetch instruction;
  update PC;
  decode instruction;
  execute instruction;
until halt signal
```




- Single cycle design: each iteration is completed within one clock cycle, long cycles, simple
- Multi-cycle design: each iteration is broken down into multiple clock cycles: short cycles, more complex
- More tradeoffs later

CS126

13-5

Randy Wang
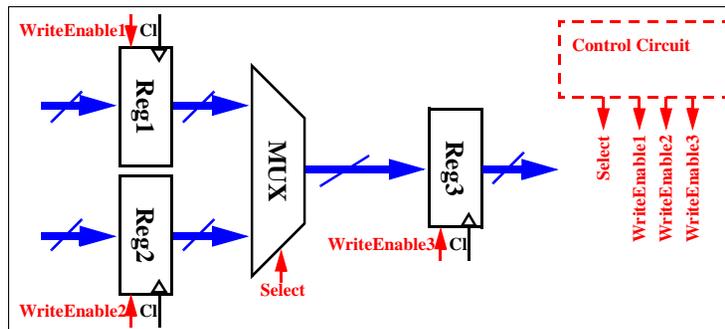
## Datapath and Control: Definition by Example




- Blue: datapath, Red: control signals
- Control circuit decides how to set **Select** and whether to enable **WriteEnable3**
- When clock ticks
  - One of Reg1 or Reg2 gets copied to Reg3 if **WriteEnable3** is on
  - Nothing gets copied to Reg3 if **WriteEnable3** is off

CS126

13-6

Randy Wang

## The Big Picture

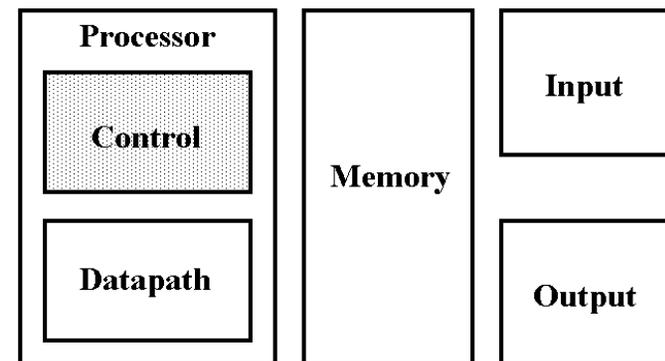

- The five classic components of a computer

CS126

13-7

Randy Wang

## Steps Towards Designing a Processor


- Analyze instruction set architecture (ISA) and understand datapath requirements
- Select set of datapath components and establish clocking methodology
- Assemble datapath to meet ISA requirements
- Analyze how to implement each instruction to determine the setting of various control signals
- Assemble the control logic

CS126

13-8

Randy Wang
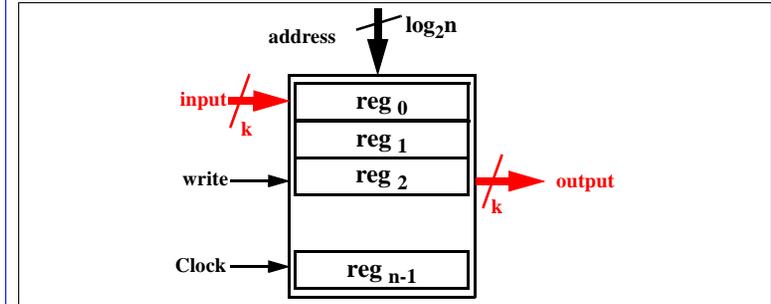
## Review: Register File (From Last Lecture)




- Register file of  $k$ -bit words
- One address port, so can't read and write in the same clock cycle

CS126

13-9

Randy Wang
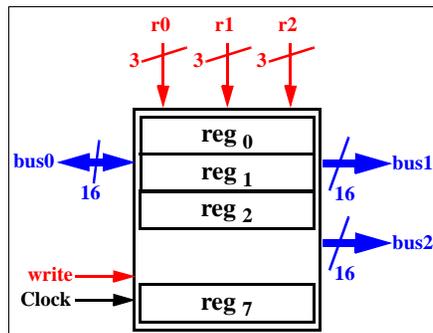
## What We Have (cont.): TOY Register File




- 8 general purpose registers
- 2 16-bit output busses, 1 16-bit input bus
- $r1, r2$  (3-bit numbers) specifies which registers go on bus1, 2
- $r0$  (3-bit) specifies which registers to receive input data when write enabled at clock pulse; when not write-enabled, the named register's value appears on bus 0

CS126

13-10

Randy Wang

## What We Have (cont.): TOY ALU

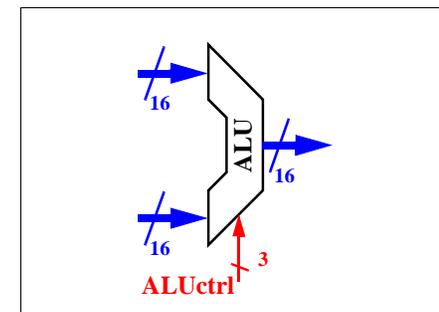

- We have learned about an adder. Generalize it to an ALU.
- Two 16-bit inputs, one 16-bit output
- A 3-bit control specifies which arithmetic or logic operation to perform (+ - \* ^ & >> <<)

CS126

13-11

Randy Wang

## Outline

- Introduction
- Some basics
- Single-cycle TOY design
  - Datapath design
  - Control design
- Multicycle TOY design
- Conclusions

CS126

13-12

Randy Wang

## TOY Datapath Components

repeat

```

fetch instruction;
perform arithmetic operation;
access memory if necessary;
write back to register if necessary;

```

until halt signal


- Refine the simulator code to be more specific
- Each of these four lines will be handled by a piece of hardware
  - Instruction fetch
  - Arithmetic (execution)
  - Memory
  - Write back
- We will assemble them one at a time, and assemble all four together at the end
- Caveat: I'm leaving out a few instructions as exercises

CS126

13-13

Randy Wang

## TOY Arithmetic (Execution) Data Path

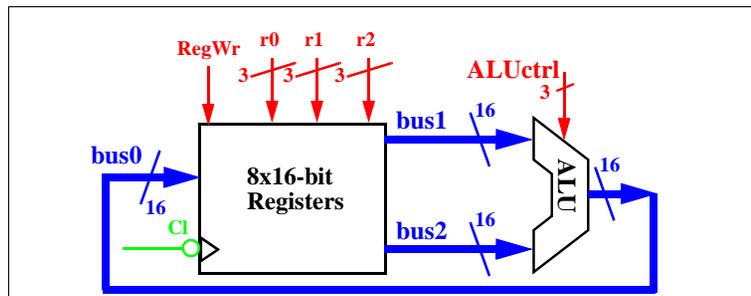


- Blue: datapath, Red: control signals
- (Part of) Implementation of TOY instruction:  
 $r0 = r1 + r2$
- r0, r1, r2 control signals come straight from instruction, more on control later
- Clock controls when write back occurs
- Reads behave as combinational logic: result valid after delay

CS126

13-14

Randy Wang

## TOY Instruction Fetch Unit

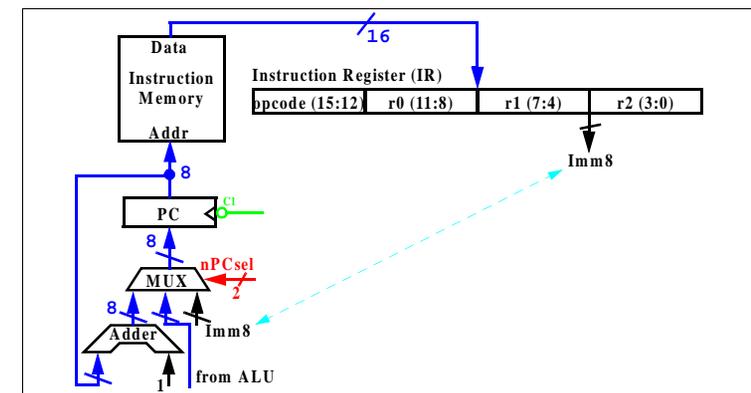


- Key question: which instruction to fetch
  - If jump, then fetch the jump target (which is in instruction itself)
  - Otherwise, fetch the next instruction

CS126

13-15

Randy Wang

## Timing Demo: Putting Instruction Fetch and Add Together

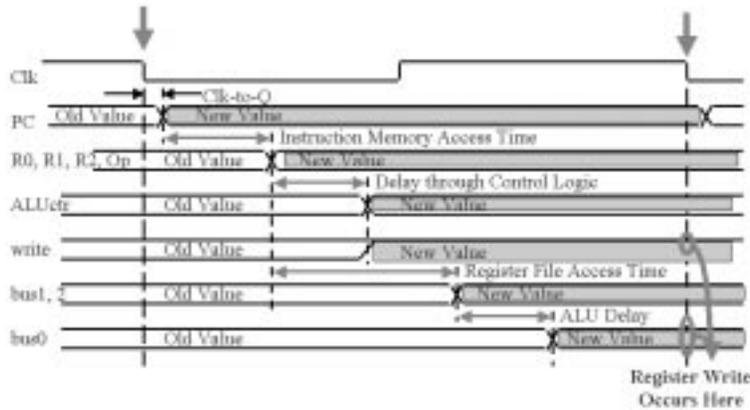


CS126

13-16

Randy Wang

## TOY Memory Datapath

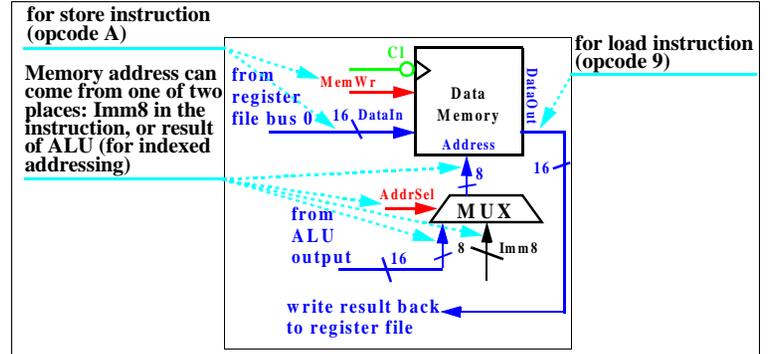


- For instructions that load from or write to memory
- Key question: where does address come from?
  - From instruction itself (example:  $r0 = \text{mem}[3D]$ )
  - From ALU (example:  $r0 = \text{mem}[r1+r2]$ )

CS126

13-17

Randy Wang

## TOY Write Back Datapath

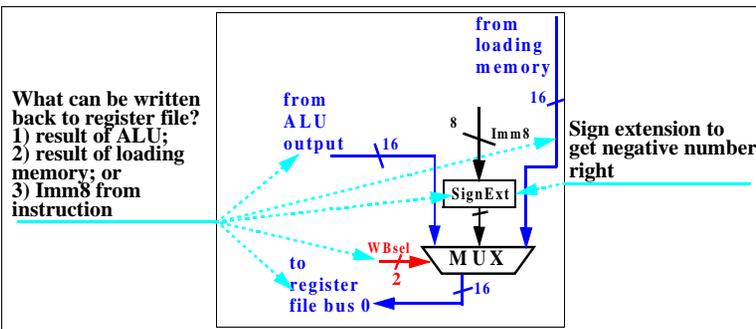


- Key question: what to write back to register file? One of three possibilities, examples:
  - $r0 = r1 + r2$
  - $r0 = \text{mem}[3D]$
  - $r0 = 3A$

CS126

13-18

Randy Wang
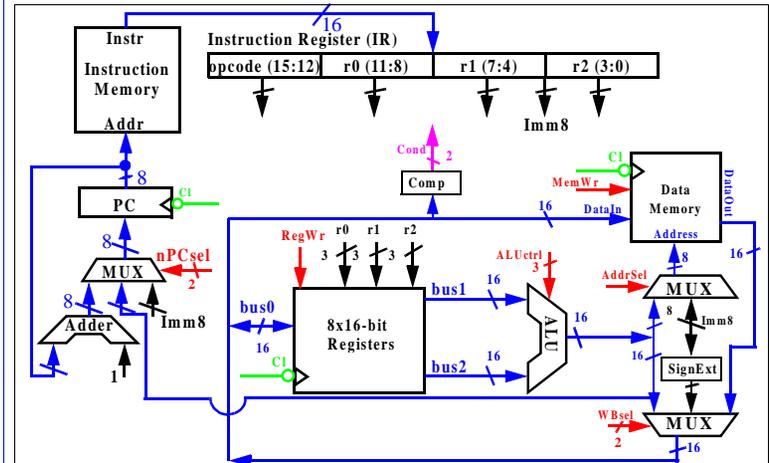
## Putting It All Together (Complete Single Cycle TOY Datapath)




- Example TOY instruction 1A:9A45 ( $r2 = \text{mem}[r4+r5]$ )
- Caveat: I'm leaving out a couple instructions as exercises

CS126

13-19

Randy Wang
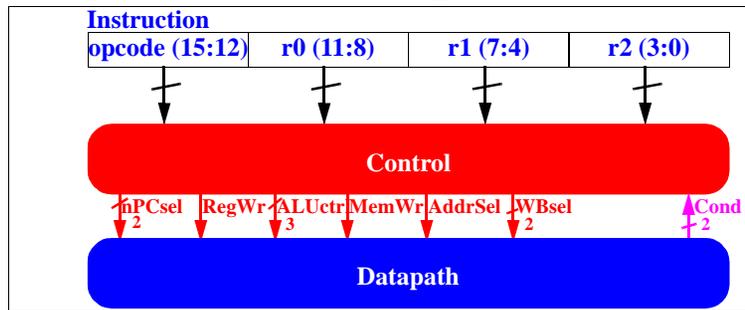
## Abstract View of Relationship Between Single Cycle TOY Datapath and Control




- The flow of data in the datapath commanded by control signals
- Control signals issued by the control unit
- Control unit gets its input from the current instruction and condition codes from the datapath
- Control unit is nothing but a big combinational circuit

CS126

13-20

Randy Wang

## Implementing Single Cycle TOY Control

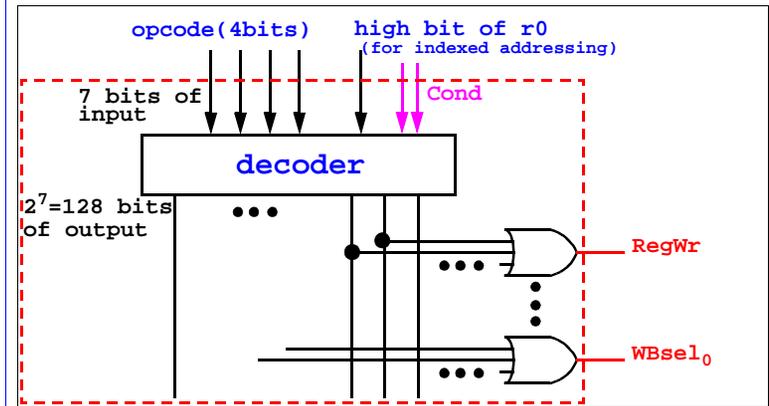

- Meaning of a decoder output that is 1: one particular instruction is executing and certain conditions are met
- Meaning of each OR-gate: turn on this control signal if any one of “these things” happen

CS126

13-21

Randy Wang

## Outline

- Introduction
- Some basics
- Single-cycle TOY datapath design
- Single-cycle TOY control design
- Multicycle TOY design
- Conclusions

CS126

13-22

Randy Wang

## Problems with Single-Cycle Implementation

- Long cycle time
  - Not all instructions are equal, some longer, some shorter
  - Memory accesses can be a lot longer
  - The slowest instruction determines cycle time
  - The processor sits idle for faster instructions
- Waste of chip area, for example:
  - Need an adder to compute  $PC += 4$  in addition to the ALU
  - Could in theory eliminate the adder and borrow ALU when it's not needed
  - But in a single cycle, we can't tell when ALU is done

CS126

13-23

Randy Wang

## Multicycle Design

```
repeat
  fetch instruction;
  decode instruction;
  execute instruction;
  access memory if necessary;
  write back to register if necessary;
until halt signal
```


- Multicycle design
  - Look at our TOY simulator again
  - Carefully break down each instruction into these roughly equal **stages**
  - Use one (short) clock cycle to execute each stage
- Advantages
  - Shorter instructions can just skip unnecessary cycles, more efficient in time
  - Can borrow ALU to increment PC earlier: more efficient in chip area

CS126

13-24

Randy Wang

## Multicycle TOY Datapath

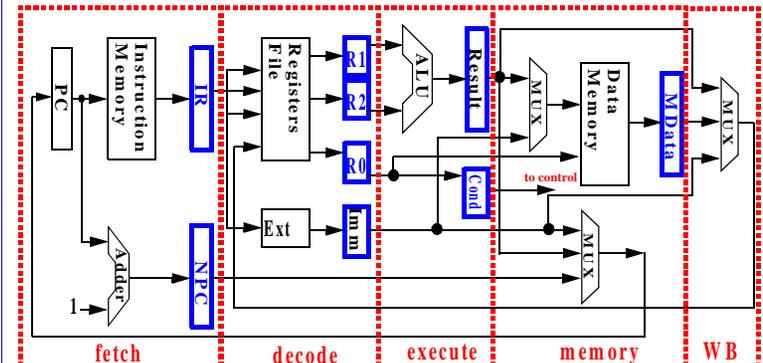


- Divide datapath up into 5 pieces (red boxes), analogous to the simulator code on previous slide: fetch, decode, execute, memory, write-back)
- Introduce temporary registers (blue boxes) to hold intermediate answers
- During each clock cycle, previous intermediate values are “clocked” into next stage, where the next intermediate value is calculated

CS126

13-25

Randy Wang
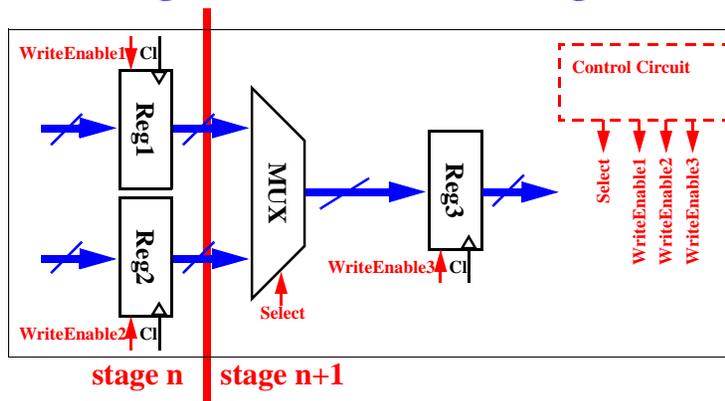
## “Clocking” Values from One Stage to Next




- (We have seen this slide before)
- The trick is to figure out how and when to set the control signals!

CS126

13-26

Randy Wang

## How to Modify Control

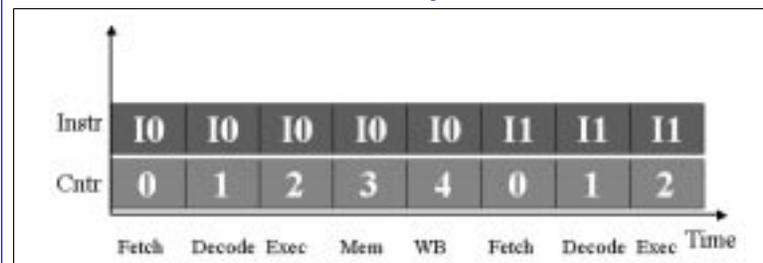


- Control depends on both instruction and time
- Use a counter to keep track of time (which stage the instruction is in)
- Will use counter to help determine control

CS126

13-27

Randy Wang

## What's New In This Picture?

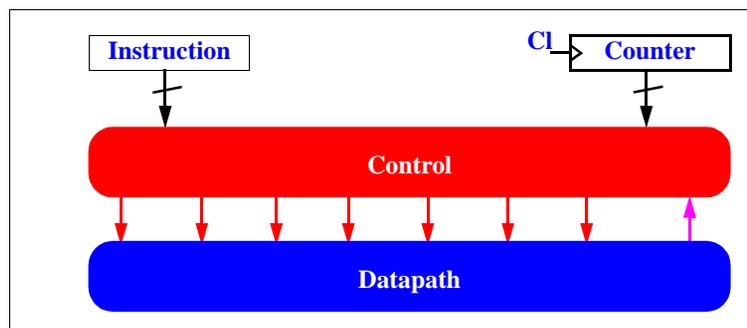

- Counter output becomes part of control input

CS126

13-28

Randy Wang

## Outline

- Introduction
- Some basics
- Single-cycle TOY datapath design
- Single-cycle TOY control design
- Multicycle TOY design
- Conclusions

CS126

13-29

Randy Wang

## Steps Towards Designing a Processor

- Analyze instruction set architecture (ISA) and understand datapath requirements
- Select set of datapath components and establish clocking methodology
- Assemble datapath to meet ISA requirements
- Analyze how to implement each instruction to determine the setting of various control signals
- Assemble the control logic

CS126

13-30

Randy Wang

## Where's the Science? Understanding Tradeoffs

- We saw a deceptively trivial tradeoff today: clocking methodology
  - Single cycle architecture vs. multicycle architecture
  - Multicycle sounds obviously superior, right?
  - Extra temporary registers and extra control logic of latter
    - + Introduce time overhead
    - + Introduce chip area overhead
    - + Introduce extra complexity, cost, time-to-market, .....
  - The question to a computer architect is whether this tradeoff is worth it
- More complex tradeoffs at each step of the prev. slide
- Nice to hide all this under the hood of an ISA

CS126

13-31

Randy Wang

## What We Have Learned Today


- Concepts:
  - Datapath vs. control
  - Single-cycle vs. multicycle designs
- More components: TOY register file and ALU
- Single-cycle design
  - How signals propagate in different parts of the datapath in general
  - How to implement control signals in general. Where do inputs come from?
- Multicycle design
  - Main general modifications made to datapath and control
- **I Don't expect people to memorize all the details**

CS126

13-32

Randy Wang

## Computer Architecture

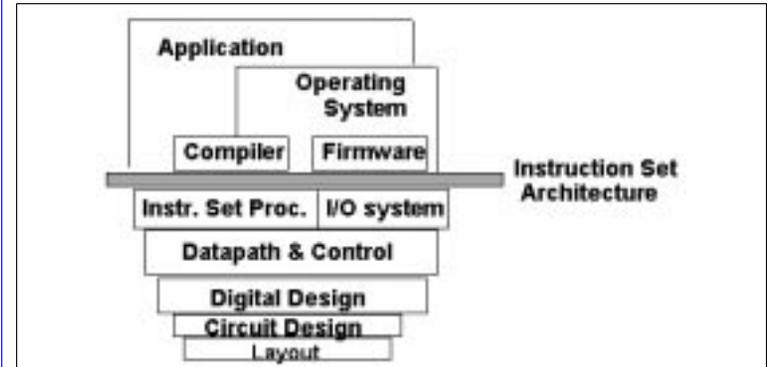


- Coordination of many levels of abstraction
- Under a rapidly changing set of forces
- Design, measurement, and evaluation

CS126

13-33

Randy Wang

## Forces Influencing Computer Architecture

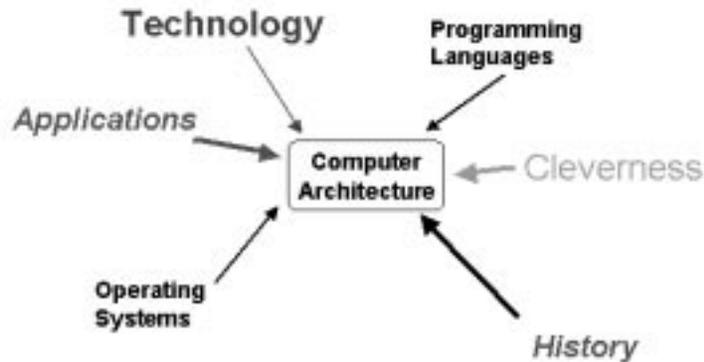

CS126

13-34

Randy Wang

## Dramatic Technology Change

- Technology
  - **Processor** logic capacity: +30% / yr; clock rate: +20% / yr; overall performance: ~+60% / yr!
  - **Memory and disk** capacity: ~+60% / yr
- Numbers, though impressive, are boring. What's really exciting is revolutionary leaps in applications!
- Quantitative improvement and revolutionary leaps interleave as technology advances
  - ~1985: **Single-chip** (32-bit) **processors** and **single-board computers** emerged, led to revolutions in all aspects of computer science!
  - Conjecture: ~2002: Emergence of powerful **single-chip systems**, what will be its implication?!

CS126

13-35

Randy Wang