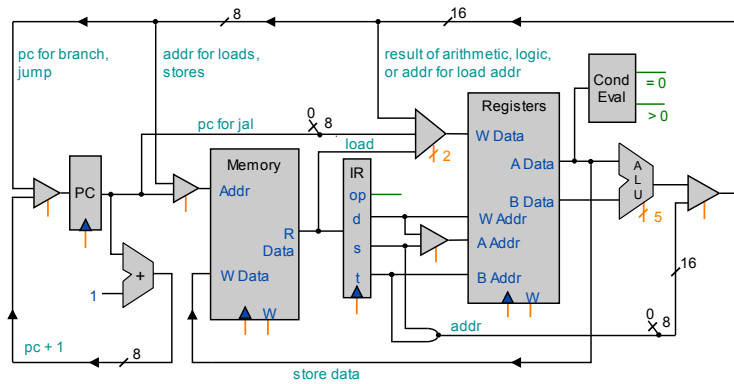


Lecture 12: TOY Machine Architecture



COS126: General Computer Science · <http://www.cs.Princeton.EDU/~cos126>


The TOY Machine

TOY machine.

- 256 16-bit words of memory.
- 16 16-bit registers.
- 1 8-bit program counter.
- 16 instructions types.

What we've done.

 - Written programs for the TOY machine.
- Software implementation of fetch-execute cycle.
 - TOY simulator.



Our goal today.

- Hardware implementation of fetch-execute cycle.
 - TOY computer.

Designing a Processor

How to build a microprocessor?

- ➔ ▪ Develop instruction set architecture (ISA).
 - 16-bit words, 16 TOY machine instructions
- Determine major components.
 - ALU, memory, registers, program counter
- Determine datapath requirements.
 - "flow" of bits
- Establish clocking methodology.
 - 2-cycle design: fetch, execute
- Analyze how to implement each instruction.
 - determine settings of control signals

Instruction Set Architecture

Instruction set architecture (ISA).

- 16-bit words, 256 words of memory, 16 registers.
- Determine set of primitive instructions.
 - too narrow ⇒ cumbersome to program
 - too broad ⇒ cumbersome to build hardware
- TOY machine: 16 instructions.

Instructions	
0:	halt
1:	add
2:	subtract
3:	and
4:	xor
5:	shift left
6:	shift right
7:	load address

Instructions	
8:	load
9:	store
A:	load indirect
B:	store indirect
C:	branch zero
D:	branch positive
E:	jump register
F:	jump and link

Designing a Processor

How to build a microprocessor?

- Develop instruction set architecture (ISA).
 - 16-bit words, 16 TOY machine instructions
- Determine major components.
 - ALU, memory, registers, program counter
- Determine datapath requirements.
 - "flow" of bits
- Establish clocking methodology.
 - 2-cycle design: fetch, execute
- Analyze how to implement each instruction.
 - determine settings of control signals


5

Arithmetic Logic Unit

TOY ALU.


- Big combinational circuit.
- 16-bit bus.
- Add, subtract, and, xor, shift left, shift right, copy input 2.

op	2	1	0
+, -	0	0	0
&	0	0	1
^	0	1	0
<<, >>	0	1	1
input 2	1	0	0

 

6

Arithmetic Logic Unit: Implementation

 


op	2	1	0
+, -	0	0	0
&	0	0	1
^	0	1	0
<<, >>	0	1	1
input 2	1	0	0

7

Main Memory

 TOY main memory: 256 x 16-bit register file.




8

Registers

TOY registers: fancy 16 x 16-bit register file.

 - Want to be able to read two registers, and write to a third in the same instructions: $R1 \leftarrow R2 + R3$.
- 3 address inputs, 1 data input, 2 data outputs.
- Add decoders and muxes for additional ports.



9

Designing a Processor

How to build a microprocessor?

- Develop instruction set architecture (ISA).
 - 16-bit words, 16 TOY machine instructions
- Determine major components.
 - ALU, memory, registers, program counter
- Determine datapath requirements.
 - "flow" of bits
- Establish clocking methodology.
 - 2-cycle design: fetch, execute
- Analyze how to implement each instruction.
 - determine settings of control signals

10


Datapath and Control

Datapath.

- Layout and interconnection of components.
- Must accommodate all instruction types.

Control.

 - Choreographs the "flow" of information on the datapath.
- Depending on instruction, different control wires are turned on.



11


Datapath and Control

Datapath.

- Layout and interconnection of components.
- Must accommodate all instruction types.


Control.

 - Choreographs the "flow" of information on the datapath.
- Depending on instruction, different control wires are turned on.




12

The TOY Datapath

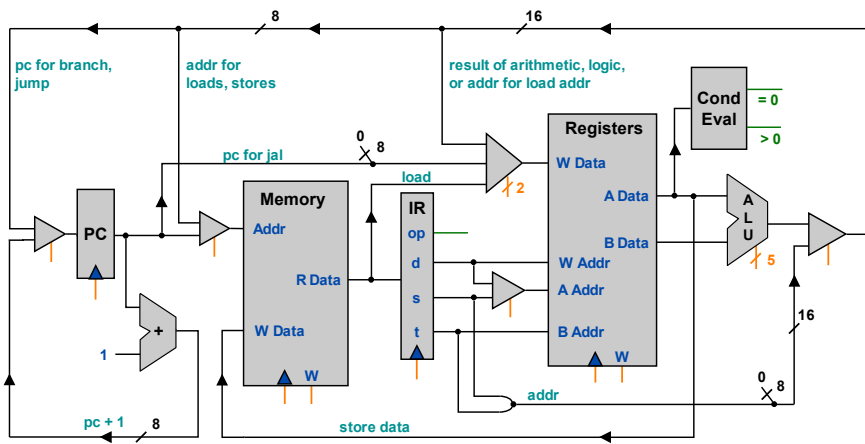

15

The TOY Datapath: Add

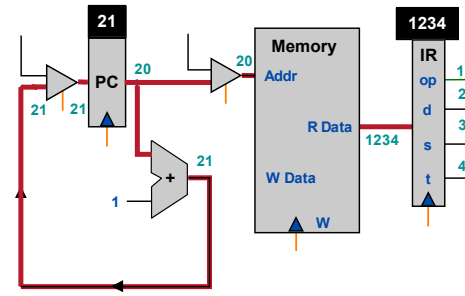


Before fetch:
pc = 20, mem[20] = 1234

After fetch:
pc = 21
IR = 1234: R[2] ← R[3] + R[4]

16

The TOY Datapath: Add

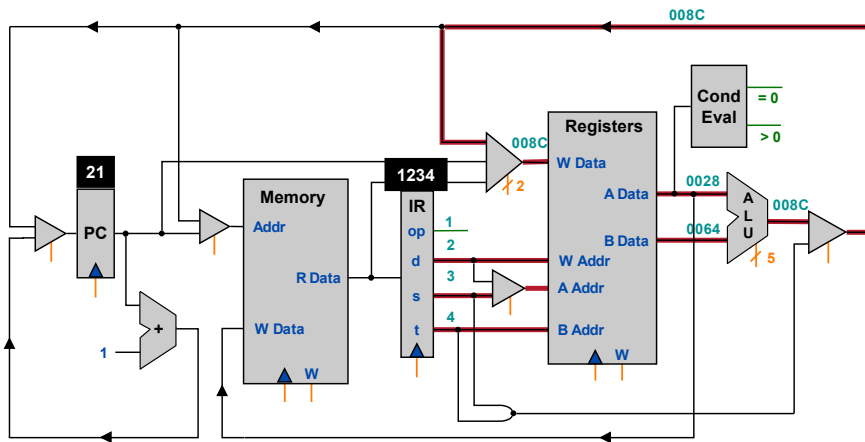


Before execute:
pc = 21
IR = 1234: R[2] ← R[3] + R[4]
R[3] = 0028, R[4] = 0064

After execute:
pc = 21
R[2] = 008C

17


The TOY Datapath: Jump and Link

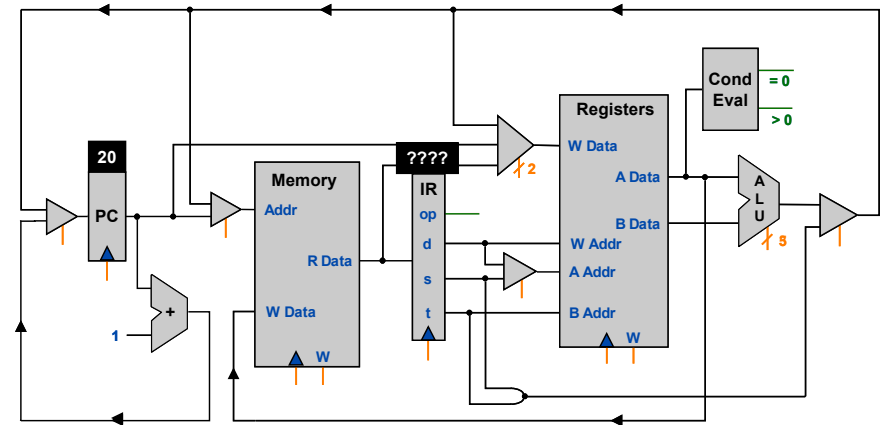

Before fetch:
pc = 20
mem[20] = FF30

18

The TOY Datapath: Jump and Link

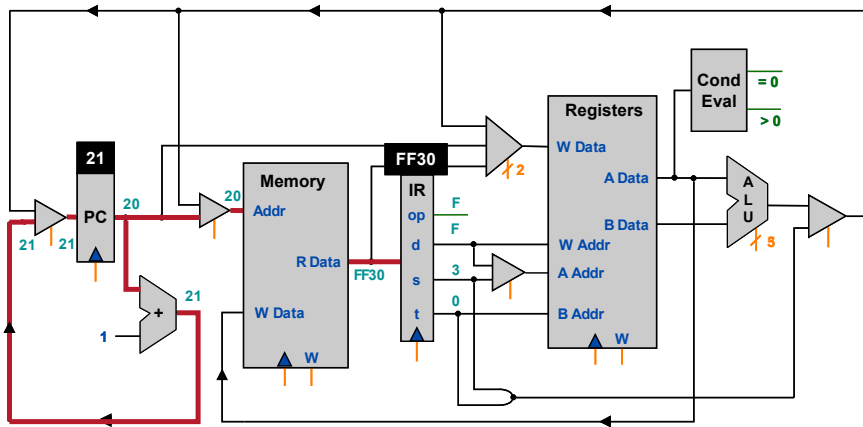

Before fetch:


pc = 20
mem[20] = FF30

After fetch:

pc = 21
IR = FF30: R[F] ← 21; pc ← 30

19

The TOY Datapath: Jump and Link

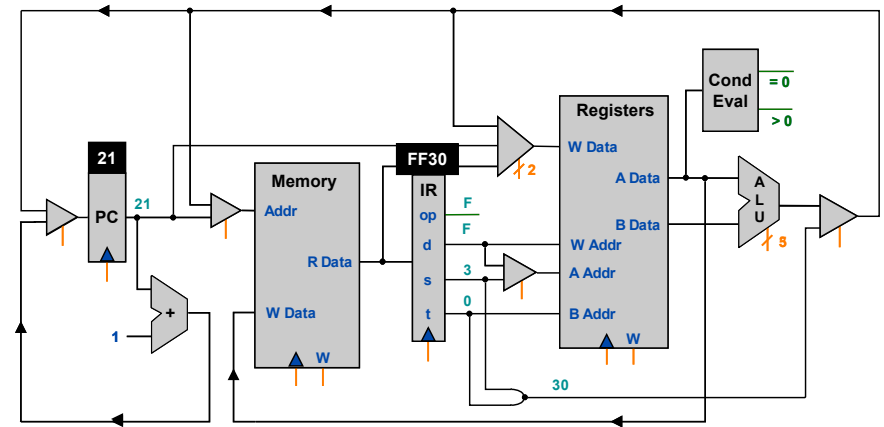


Before execute:

pc = 21
IR = FF30: R[F] ← 21; pc ← 30

20

The TOY Datapath: Jump and Link

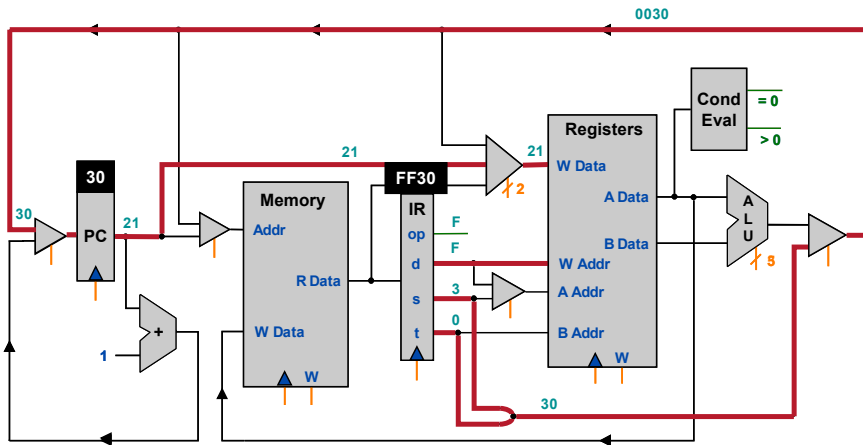

Before execute:


pc = 21
IR = FF30: R[F] ← 21; pc ← 30

After execute:

pc = 30
R[F] = 21

21

Do Try This At Home

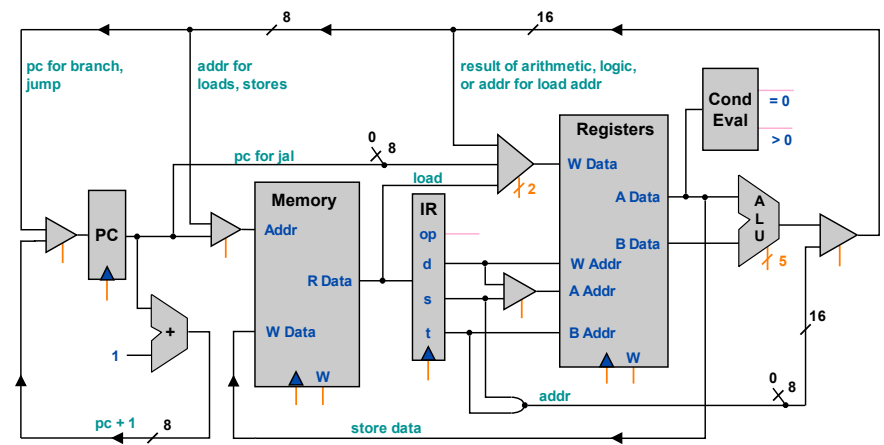

Trace the flow of some other instructions through the datapath picture.

22

Designing a Processor

How to build a microprocessor?



- Develop instruction set architecture (ISA).
 - 16-bit words, 16 TOY machine instructions
- Determine major components.
 - ALU, memory, registers, program counter
- Determine datapath requirements.
 - "flow" of bits
- ➔ ▪ Establish clocking methodology.
 - 2-cycle design: fetch, execute
- Analyze how to implement each instruction.
 - determine settings of control signals

25

Clocking Methodology

Two cycle design (fetch and execute).

  - Use 1-bit counter to distinguish between 2 cycles.
- Use two cycles since fetch and execute phases each access memory and alter program counter.



26


Clocking Methodology

4 distinguishable events.

- During fetch phase.
- At very end of execute phase.
- During execute phase.
- At very end of fetch phase.

Ex: can only write at very end of execute phase.

- $R1 \leftarrow R1 + R1$

 

27

Designing a Processor

How to build a microprocessor?


- Develop instruction set architecture (ISA).
 - 16-bit words, 16 TOY machine instructions
- Determine major components.
 - ALU, memory, registers, program counter
- Determine datapath requirements.
 - "flow" of bits
- Establish clocking methodology.
 - 2-cycle design: fetch, execute
- ➔ ▪ Analyze how to implement each instruction.
 - determine settings of control signals

28

Control

Control: controls components, enables connections.

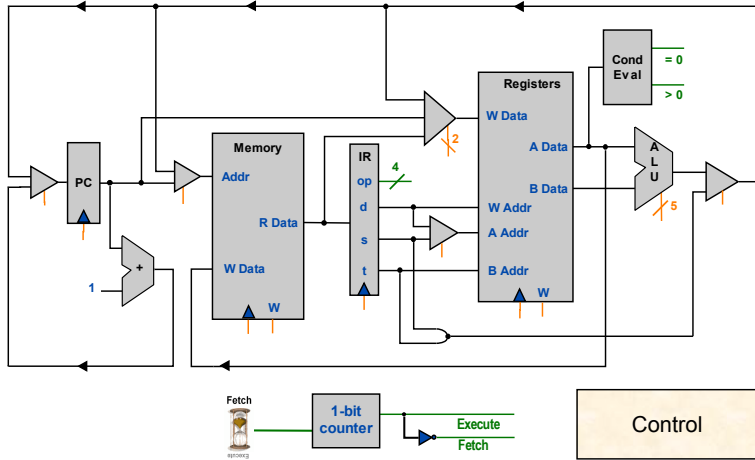- Input: opcode, clock, conditional evaluation. (green)
- Output: control wires. (orange)




29

Control


Control: controls components, enables connections.

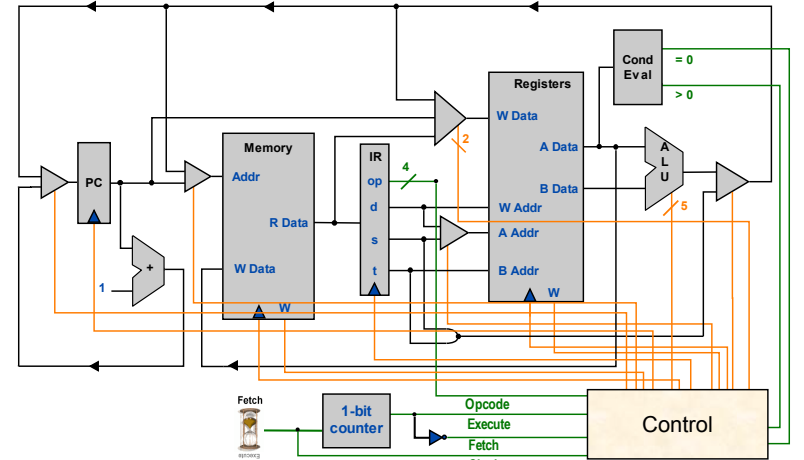- Input: opcode, clock, conditional evaluation. (green)
- Output: control wires. (orange)




30

Implementation of Control

 


31

Implementation of Control: Store


 


32

Control: Execute Phase of Store

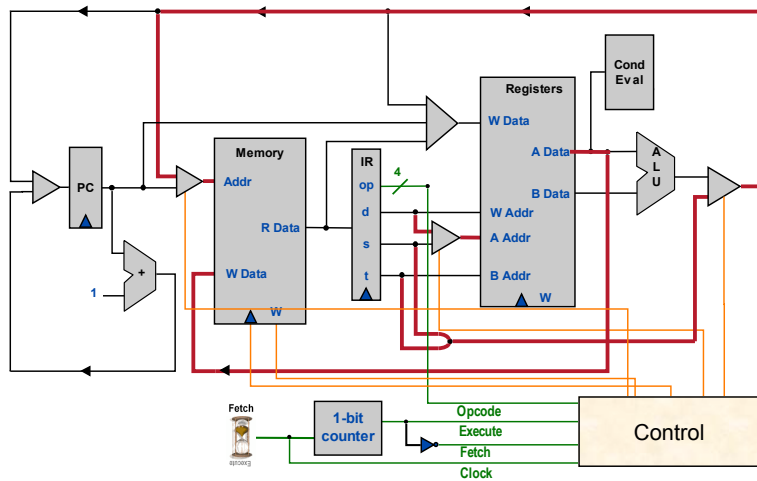

Stand-Alone Registers

  

Layers of Abstraction

Abstraction	Built From	Examples
Abstract Switch	raw materials	transistor
Connector	raw materials	wire
Clock	raw materials	crystal oscillator
Logic Gates	abstract switches, connectors	AND, OR, NOT
Combinational Circuit	logic gates, connectors	decoder, multiplexer, adder, ALU
Sequential Circuit	logic gates, clock, connector	flip-flop
Components	decoder, multiplexer, adder, flip-flop	registers, ALU, counter, control
Computer	components	TOY

Pipelining

Pipelining.

- At any instant, processor is either fetching instructions or executing them (and so half of circuitry is idle).
- Why not fetch next instruction while current instruction is executing?
 - Analogy: washer / dryer.

Issues.

- Jump and branch instructions change PC.
 - "Prefetch" next instruction.
- Fetch and execute cycles may need to access same memory.
 - Solution: use two memory caches.

Result.

- Better utilization of hardware.
- Can double speed of processor.

History + Future

Computer constructed by layering abstractions.


- Better implementation at low levels improves EVERYTHING.
- Ongoing search for better abstract switch!

History.

- 1820s: mechanical switches (Babbage's difference engine).
- 1940s: relays, vacuum tubes.
- 1950s: transistor, core memory.
- 1960s: integrated circuit.
- 1970s: microprocessor.
- 1980s: VLSI.
- 1990s: integrated systems.
- 2000s: web computer.
- Future: DNA, quantum, optical soliton, ...

37

Goodbye, TOY

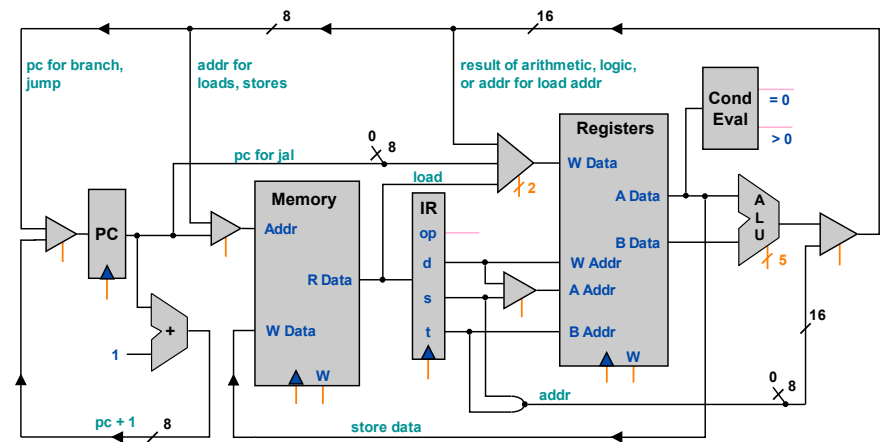

38