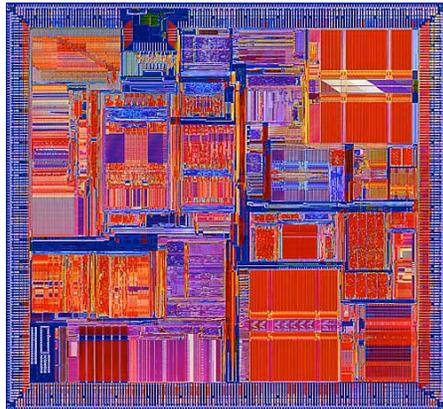


Let's build a computer!


Designing a CPU



Introduction to Computer Science · Robert Sedgewick and Kevin Wayne · Copyright © 2008 · <http://www.cs.Princeton.EDU/IntroCS>

CPU: "central processing unit"

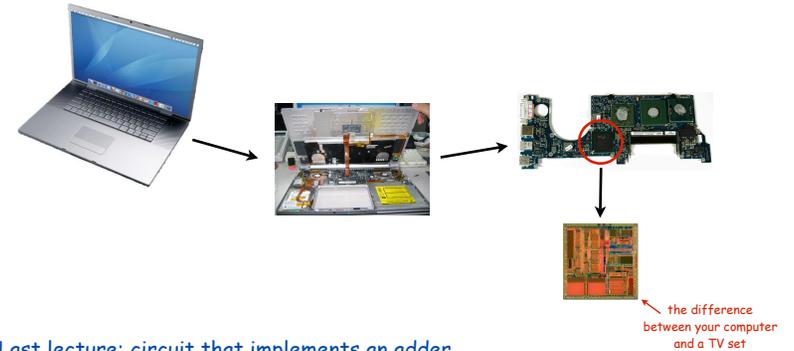computer: CPU + display + optical disk + metal case + power supply + ...



Last lecture: circuit that implements an adder


This lecture: circuit that implements a CPU

2

TOY Lite


TOY machine.

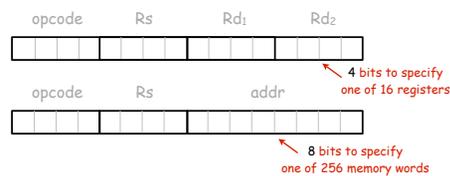- 256 16-bit words of memory.
- 16 16-bit registers.
- 1 8-bit program counter.
- 2 instruction types
- 16 instructions.



TOY-Lite machine.

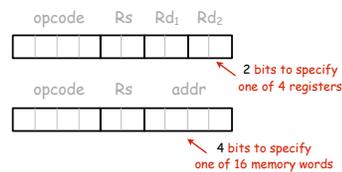- 16 10-bit words of memory.
- 4 10-bit registers.
- 1 4-bit program counter.
- 2 instruction types
- 16 instructions.



Goal: CPU circuit for TOY-Lite (same design extends to TOY, your computer)

3

Primary Components of Toy-Lite CPU

Arithmetic and Logic Unit (ALU)

Memory

Toy-Lite Registers

Processor Registers: Program Counter and Instruction Register


"Control"

4



Review of Combinational Circuits

Controlled switch.

Gates.

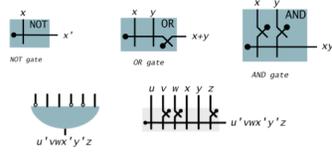

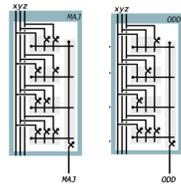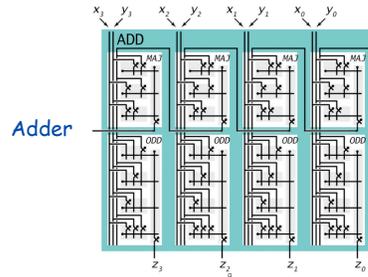
Sum-of products implementation of Boolean functions




5

Useful Combinational Circuits


Adder

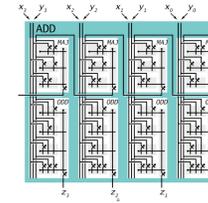

Incrementer (easy, add 0001)

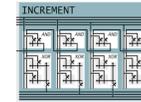


Bitwise AND, XOR (easy)

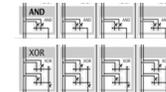

Decoder

Shifter (clever, but we'll skip details)

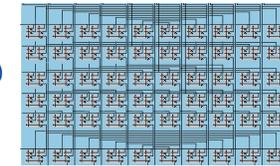


Multiplexer

Decoder

Decoder. [n-bit]

- n address inputs, 2^n data outputs.
- Addressed output bit is 1; others are 0.
- Implements n Boolean functions

x_0	x_1	x_2	z_0	z_1	z_2	z_3	z_4	z_5	z_6	z_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

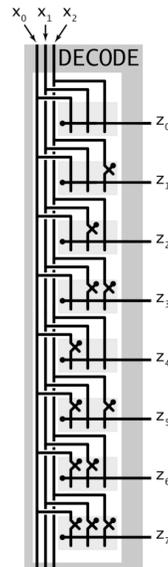

3-bit Decoder

7


Decoder application: ALU!

TOY arithmetic

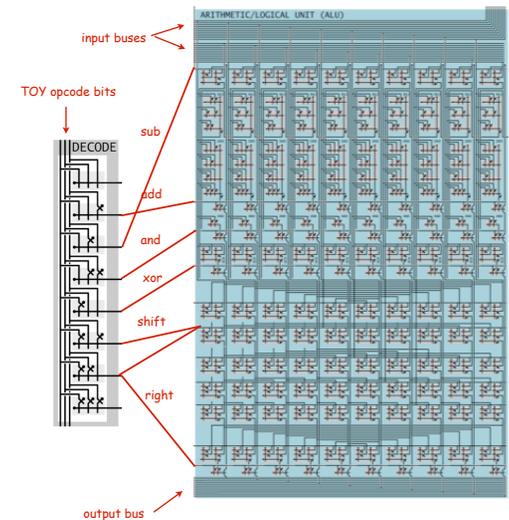- 1: add
- 2: subtract
- 3: and
- 4: xor
- 5: shift left
- 6: shift right

Details:

- All circuits compute their result.
- Decoder lines AND all results.
- "one-hot" OR collects answer.



8

Primary Components of Toy-Lite CPU

✓ Arithmetic and Logic Unit (ALU)

Memory

Toy-Lite Registers

Processor Registers: Program Counter and Instruction Register

"Control"


Nuts and Bolts: Buses and Multiplexers

Bus. Parallel wires connecting major component.

- Ex. Carry register bits to ALU.
- Ex. Carry register bits to memory

Multiplexer. Combinational circuit that selects among input buses.

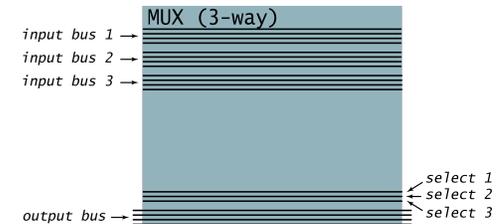- Exactly one select line i is activated.
- Copies bits from input bus i to output bus.



CPU is a **circuit**: everything is "connected" but wires that can be "on" can be selected by other wires.

9

10


Nuts and Bolts: Buses and Multiplexers

Bus. Parallel wires connecting major component.

- Ex. Carry register bits to ALU.
- Ex. Carry register bits to memory

Multiplexer (MUX). Combinational circuit that selects among input buses.

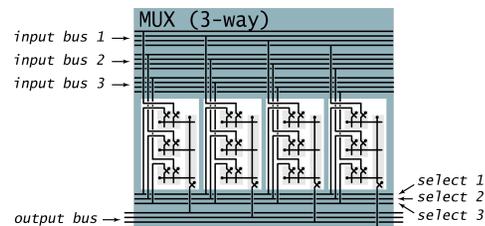- Exactly one select line i is activated.
- Copies bits from input bus i to output bus.




CPU is a **circuit**: everything is "connected" but wires that can be "on" can be selected by other wires.

11

A New Ingredient: Circuits With Memory

Combinational circuits.

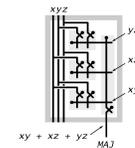- Output determined solely by inputs.
- Ex: majority, adder, decoder, MUX, ALU.




Sequential circuits.

- Output determined by inputs and current "state".
- Ex: memory, program counter, CPU.

Ex. Simplest feedback loop.

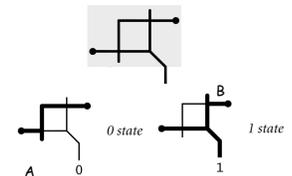- Two controlled switches A and B, both connected to power, each blocked by the other.
- State determined by whichever switches first.
- Stable.



Aside. Feedback with an odd number of switches is a **buzzer** (not stable).

Doorbell: buzzer made with relays.




12

SR Flip-Flop

SR Flip-flop.

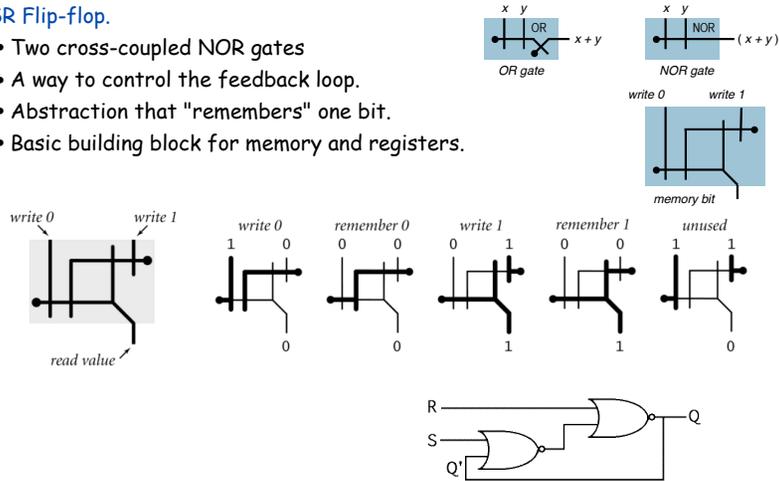- Two cross-coupled NOR gates
- A way to control the feedback loop.
- Abstraction that "remembers" one bit.
- Basic building block for memory and registers.



Caveat. Timing, switching delay.

13

Memory Overview

Computers and TOY have several memory components.

- Program counter and other processor registers.
- TOY registers (4 10-bit words in Toy-Lite).
- Main memory (16 10-bit words in Toy-Lite).


Implementation.

- Use one flip-flop for each bit of memory.
- Use buses and multiplexers to group bits into words.

Access mechanism: when are contents available?

- Processor registers: enable write.
- Main memory: select and enable write.
- TOY register: dual select and enable write

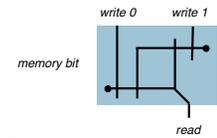
need to be able to read two registers at once



14

Processor register Bit

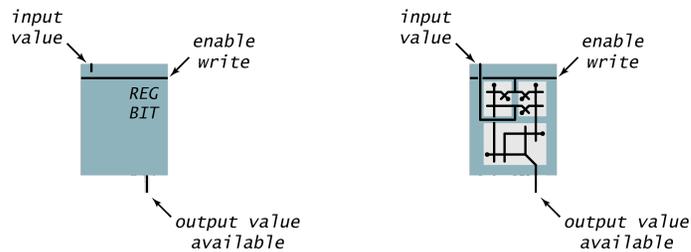
Processor register bit. Extend a flip-flop to allow easy access to values.



15

Memory Bit Interface

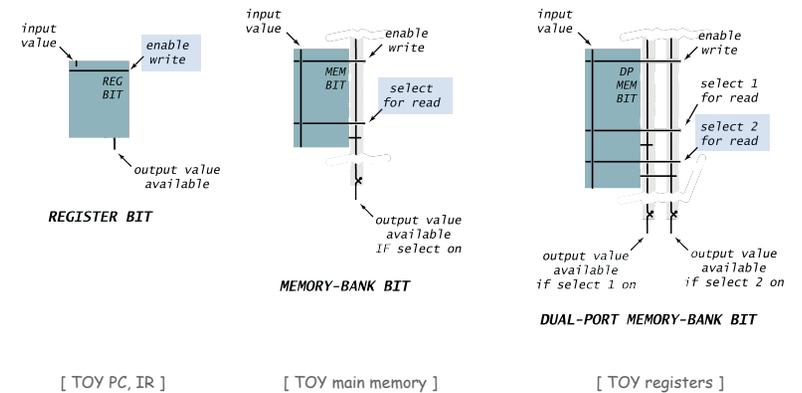
Memory and TOY register bits: Add selection mechanism.



16

Memory Bit: Switch Level Implementation

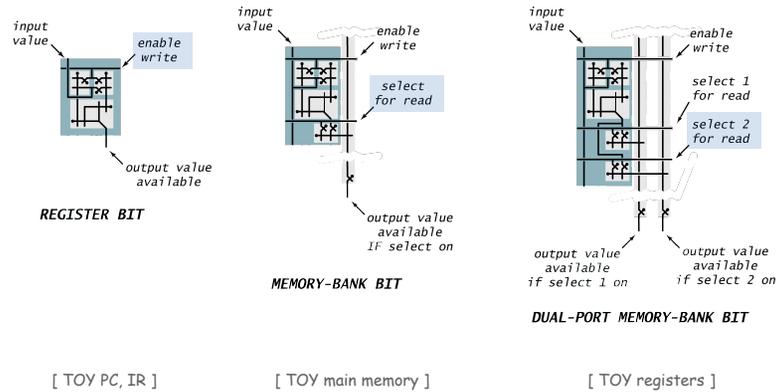Memory and TOY register bits: Add selection mechanism.



17

Processor Register

Processor register. ← don't confuse with TOY register

- Stores k bits.
- Register contents always available on output bus.
- If enable write is asserted, k input bits get copied into register.

Ex 1. TOY-Lite program counter (PC) holds 4-bit address.

Ex 2. TOY-Lite instruction register (IR) holds 10-bit current instruction.



18


Processor Register

Processor register. — don't confuse with TOY register

- Stores k bits.
- Register contents always available on output bus.
- If enable write is asserted, k input bits get copied into register.

Ex 1. TOY program counter (PC) holds 8-bit address.

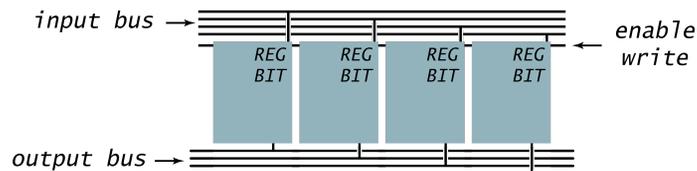Ex 2. TOY instruction register (IR) holds 16-bit current instruction.



19


Processor Register

Processor register. — don't confuse with TOY register

- Stores k bits.
- Register contents always available on output bus.
- If enable write is asserted, k input bits get copied into register.

Ex 1. TOY program counter (PC) holds 8-bit address.

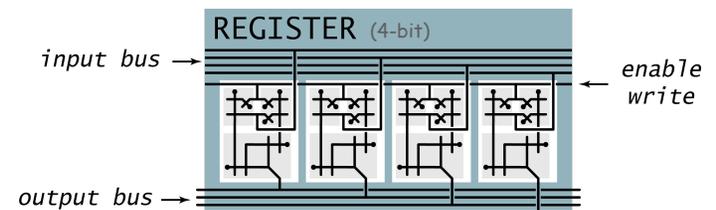Ex 2. TOY instruction register (IR) holds 16-bit current instruction.




20

Memory Bank

Memory bank.

- Bank of n registers; each stores k bits.
- Read and write information to one of n registers.
- Address inputs specify which one. — $\log_2 n$ address bits needed
- Addressed bits always appear on output.
- If write enabled, k input bits are copied into addressed register.

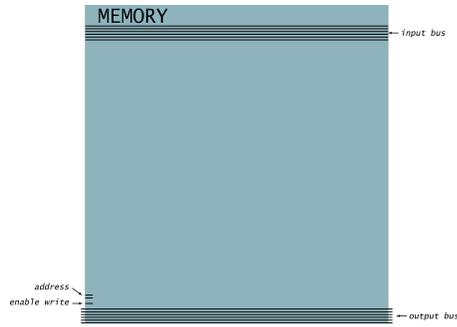Ex 0 (for lecture). 4-by-6
(four 6-bit words)



21


Ex 1. Main memory bank.

- TOY: 256-by-16
- TOY-Lite: 16-by-10

Ex 2. Registers.

- TOY: 16-by-16
- TOY Lite: 4-by-10
- Two output buses.


Memory: Interface

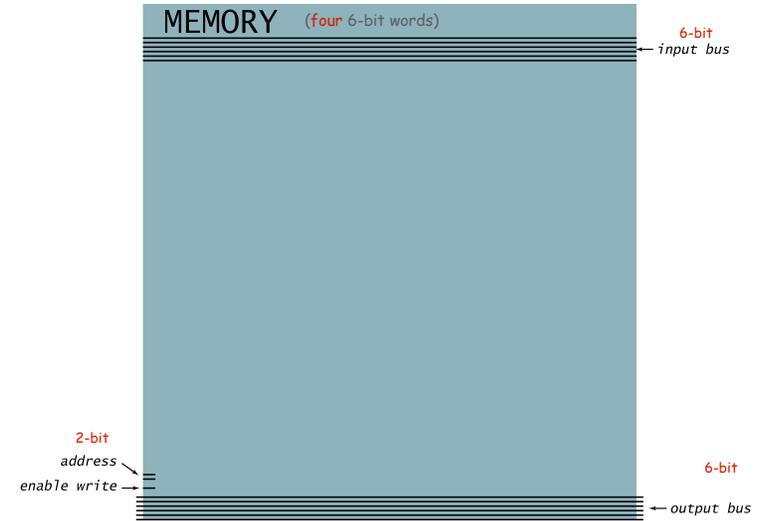

22


Memory: Component Level Implementation

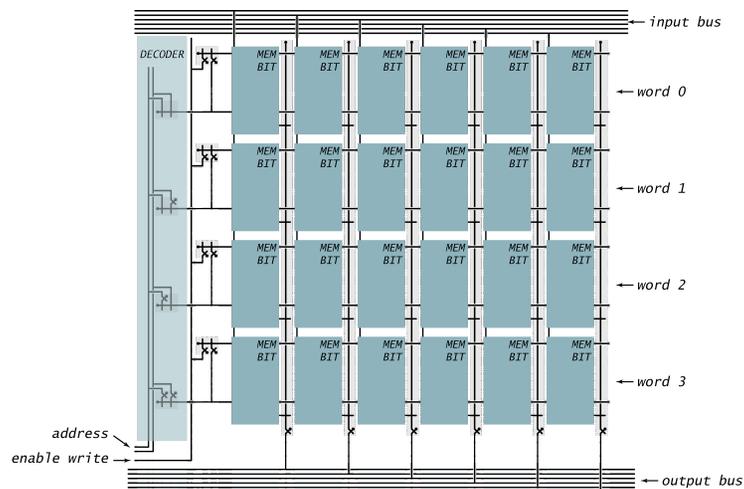Decoder plus memory selection: connect only to addressed word.



23

Memory: Switch Level Implementation

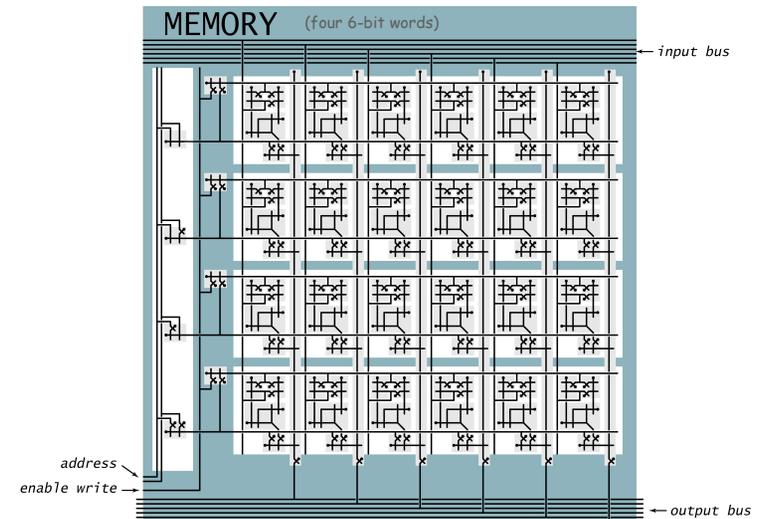


24

TOY-Lite Memory

16 10-bit words

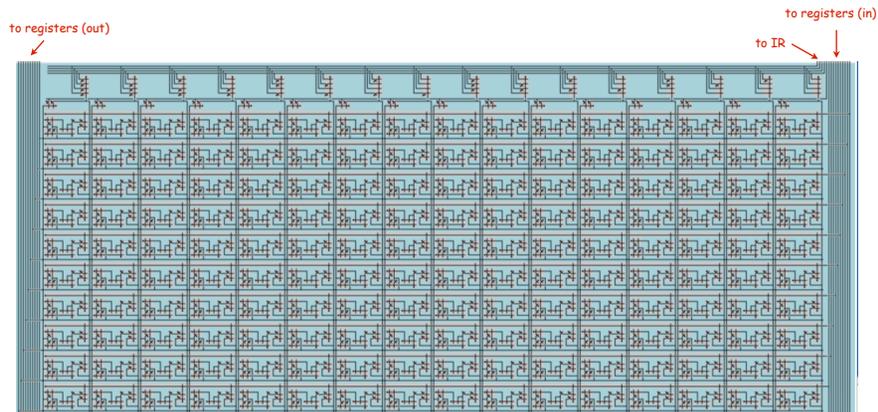- input connected to registers for "store"
- output connected to registers for "load"
- addr connect to processor Instruction Register (IR)




25

Toy-Lite Registers

4 10-bit words

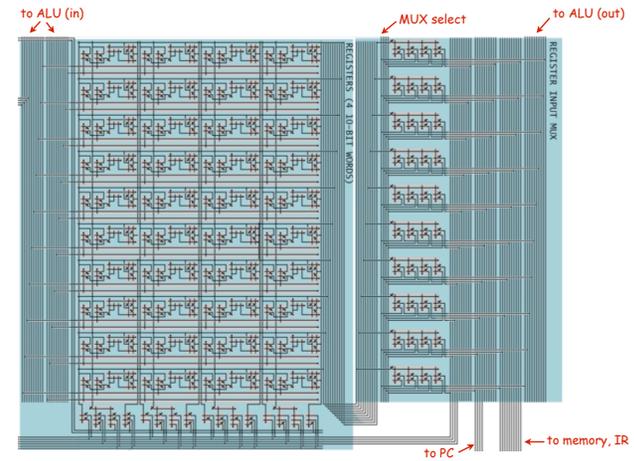- Dual-ported to support connecting two different registers to ALU
- Input MUX to support input connection to ALU, memory, IR, PC



26

Primary Components of Toy-Lite CPU

- ✓ ALU
- ✓ Memory
- ✓ Registers
- ✓ Processor Registers: Program Counter and Instruction Register

← Not quite done.
Need to be able to increment.

"Control"

27

How To Design a Digital Device

How to design a digital device.

- Design **interface**: input buses, output buses, control wires.
- Determine **components**.
- Determine **datapath** requirements: "flow" of bits.
- Establish **control sequence**.

Warmup. Design a program counter (3 devices, 3 control wires).

Goal. Design TOY-Lite computer (10 devices, 27 control wires).


28

Program Counter: Interface

Counter. Holds value that represents a binary number.

- **Load:** set value from input bus.
- **Increment:** add one to value.
- **Enable Write:** make value available on output bus.

Ex. TOY-Lite program counter (4-bit).

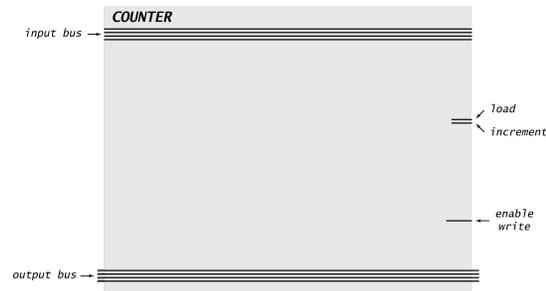

29

Program Counter: Components

Components.

- Register.
- Incrementer.
- Multiplexer (to provide connections for both load and increment).


30

Program Counter: Datapath and Control

Datapath.

- Layout and interconnection of components.
- Connect input and output buses.

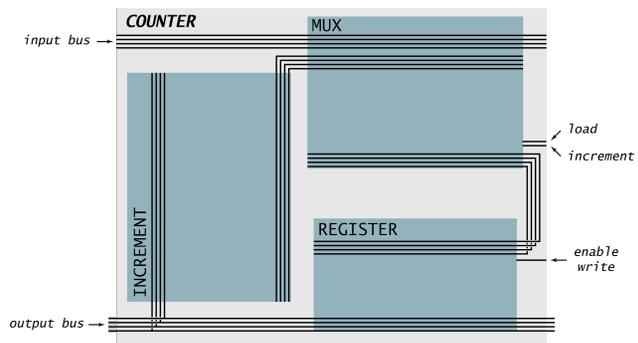Control. Choreographs the "flow" of information on the datapath.



31

Program Counter: Datapath and Control

Datapath.

- Layout and interconnection of components.
- Connect input and output buses.

Control. Choreographs the "flow" of information on the datapath.


32

Program Counter: Datapath and Control

Datapath.


- Layout and interconnection of components.
- Connect input and output buses.

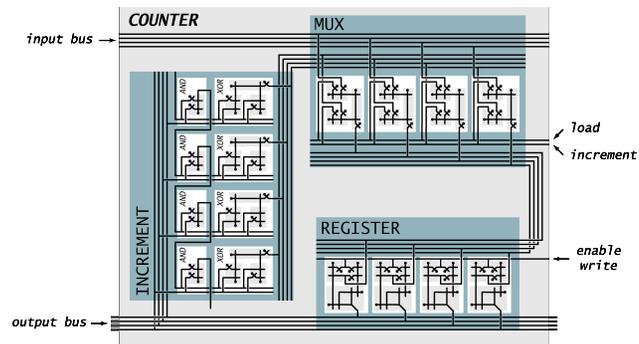Control. Choreographs the "flow" of information on the datapath.



33

Program Counter: Datapath and Control

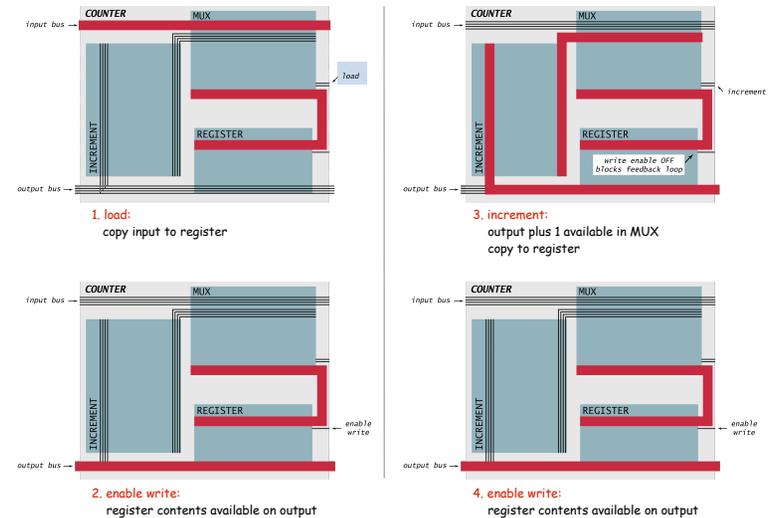

34

Primary Components of Toy-Lite CPU

- ✓ ALU
- ✓ Memory
- ✓ Toy-Lite Registers
- ✓ Processor Registers: Program Counter and Instruction Register

"Control"

35

How To Design a Digital Device

How to design a digital device.

- Design **interface**: input buses, output buses, control wires.
- Determine **components**.
- Determine **datapath** requirements: "flow" of bits.
- Establish **control sequence**.

Warmup. Design a program counter (3 devices, 3 control wires).

Next. Design TOY-Lite computer (10 devices, 27 control wires).

36

TOY-Lite: Interface

CPU is a circuit.


Interface: switches and lights.

- set memory contents
- set PC value
- press RUN
- [details of connection to circuit omitted]




37

TOY-Lite: Components

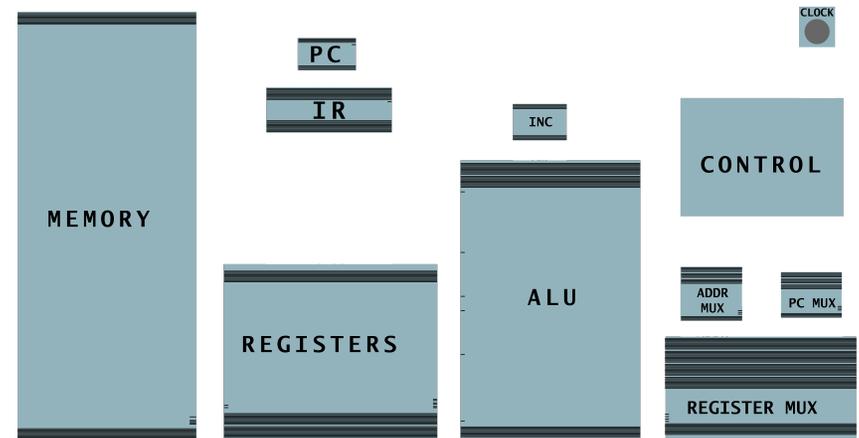

38

TOY-Lite: Layout

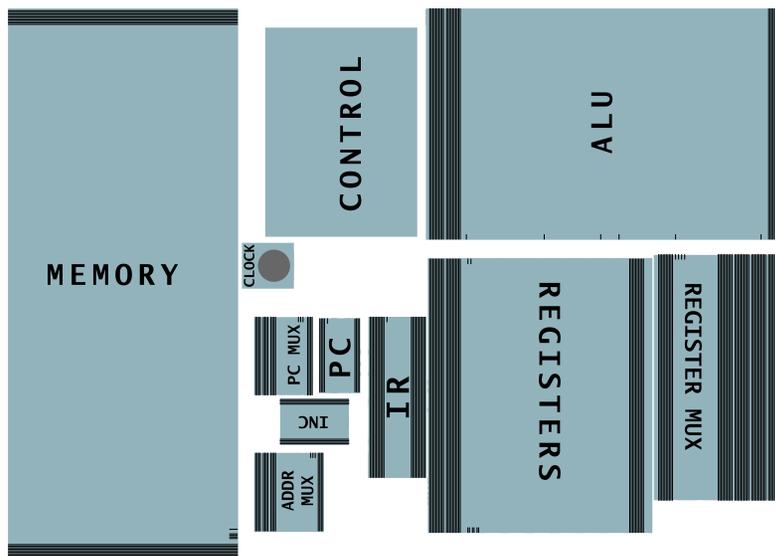

39

TOY-Lite Datapath Requirements: Fetch

Basic machine operation is a cycle.

- Fetch
- Execute

Fetch.

- Memory[PC] to IR
- Increment PC

Execute.

- Datapath depends on instruction



40


TOY-Lite Datapath Requirements: Execute

Instructions determine datapaths and control sequences for execute

		...
0	halt	...
1	add	IR opcode to control control to ALU two registers to ALU ALU to register MUX
2	subtract	
3	and	
4	xor	
5	shift left	
6	shift right	
7	load address	...
8	load	...
9	store	...
A	load indirect	...
B	store indirect	...
C	branch zero	...
D	branch positive	...
E	jump register	...
F	jump and link	...


41

TOY-Lite: Datapaths and Control

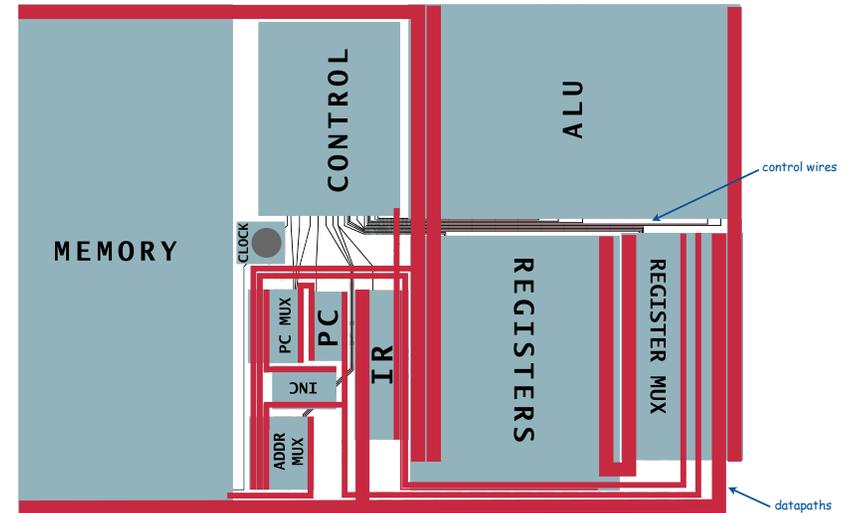


42

Datapath: Add

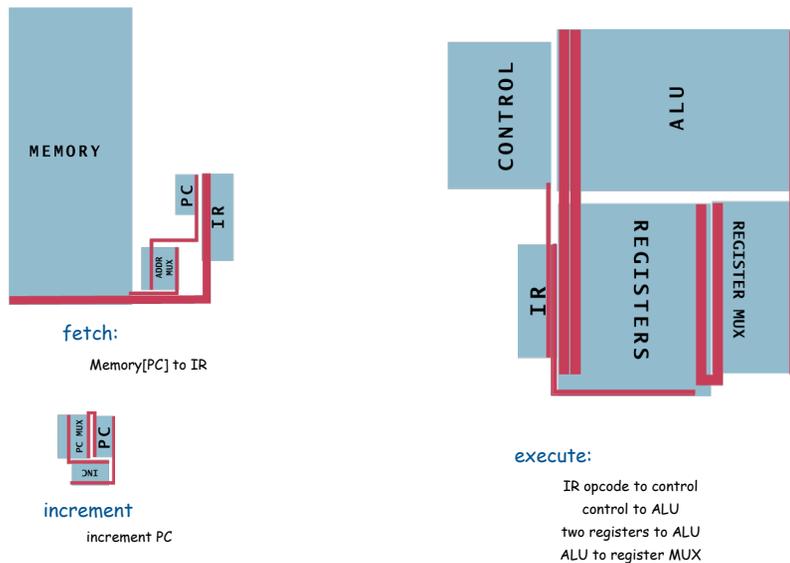

43

Datapath: Load

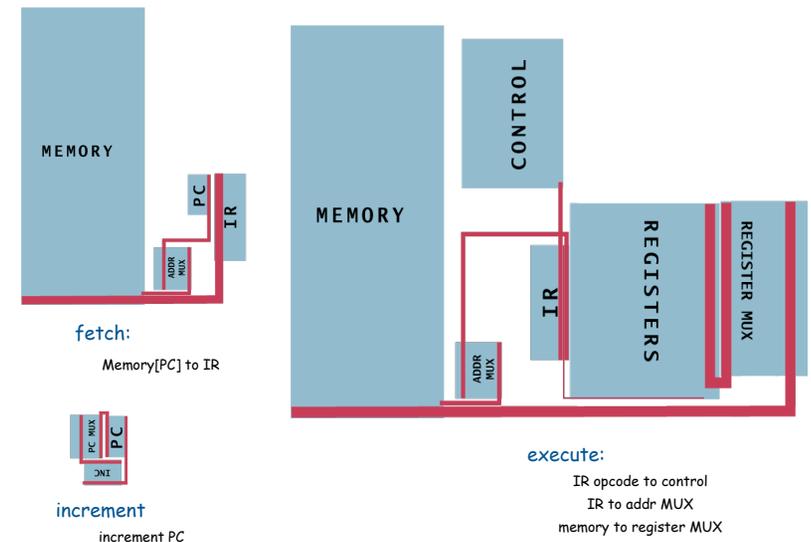

44


Last step

Control. Each instruction corresponds to a **sequence** of control signals.


Q. How do we create the sequence?

A. Need a "physical" clock.

Solution 1: Use some other technology

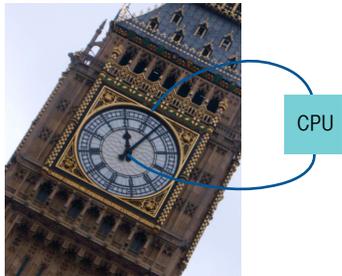

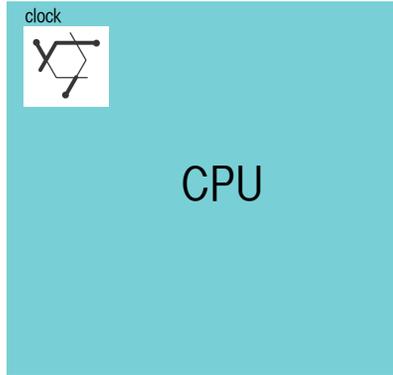Solution 2: Use a buzzer [need sufficiently long cycle to cover CPU switching]



45

Clock

Clock.


- Fundamental abstraction: regular on-off pulse.
 - on: fetch phase
 - off: execute phase
- "external" device.
- Synchronizes operations of different circuit elements.
- Requirement: clock cycle longer than max switching time.

Solution 3?

Fetch



Execute

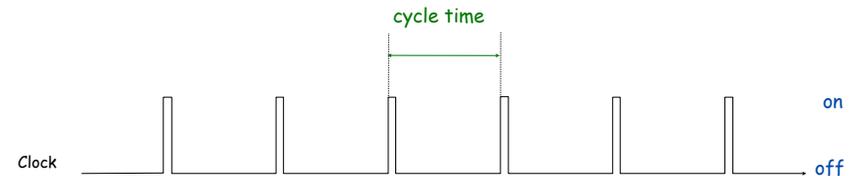

46

How much does it Hertz?

Frequency is inverse of cycle time.

- Expressed in hertz.
- Frequency of 1 Hz means that there is 1 cycle per second.
 - 1 kilohertz (kHz) means 1000 cycles/sec.
 - 1 megahertz (MHz) means 1 million cycles/sec.
 - 1 gigahertz (GHz) means 1 billion cycles/sec.
 - 1 terahertz (THz) means 1 trillion cycles/sec.




Heinrich Rudolf Hertz
(1857-1894)

47

Clocking Methodology

Two-cycle design.

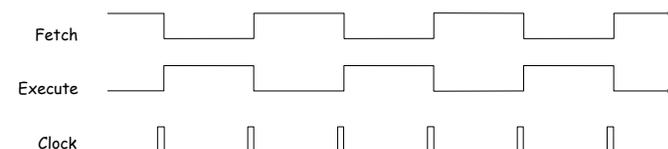
- Each control signal is in one of four epochs.
 - fetch [set memory address from pc]
 - fetch and clock [write instruction to IR]
 - execute [set ALU inputs from registers]
 - execute and clock [write result of ALU to registers]



48

Control

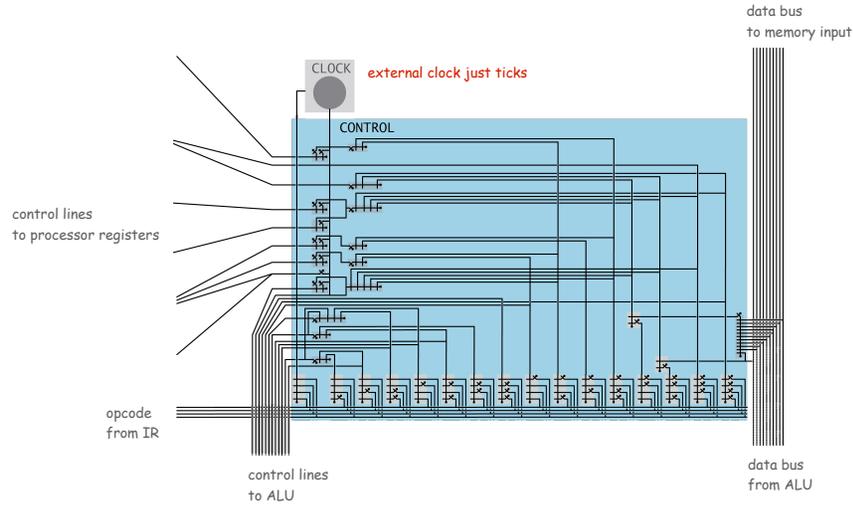Control. Circuit that determines control line sequencing.



49

Tick-Tock

CPU is a circuit, driven by a clock.

Switches initialize memory, PC contents

Clock ticks

- **fetch** instruction from memory[PC] to IR
- increment PC
- **execute** instruction

[details of instruction execution differ]

- **fetch** next instruction
- ...

That's all there is to it!



Fetch




Execute



50

TOY "Classic", Back Of Envelope Design

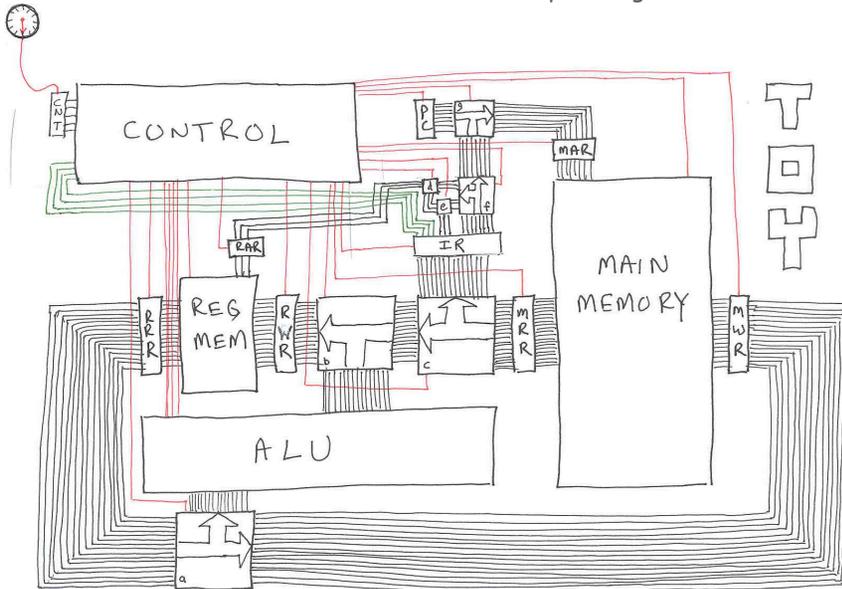


51

TOY-Lite CPU



52

Real Microprocessor (MIPS R10000)

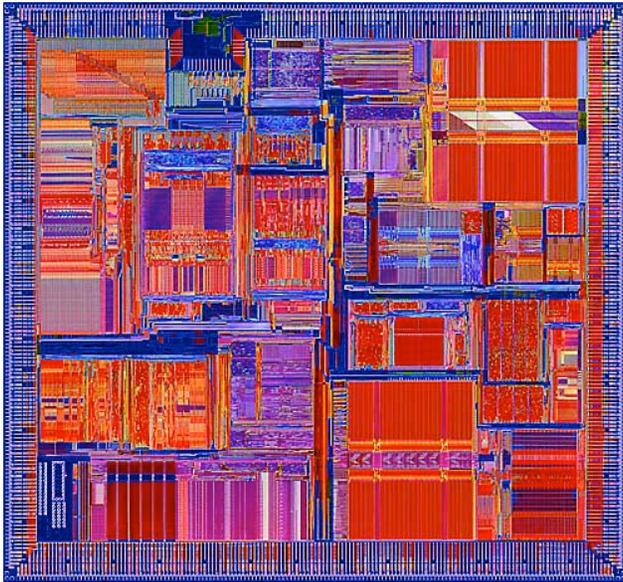

53

Layers of Abstraction

Abstraction	Built From	Examples
Abstract Switch	raw materials	transistor, relay
Connector	raw materials	wire
Clock	raw materials	crystal oscillator
Logic Gates	abstract switches, connectors	AND, OR, NOT
Combinational Circuit	logic gates, connectors	decoder, multiplexer, adder, ALU
Sequential Circuit	logic gates, clock, connector	flip-flop
Components	decoder, multiplexer, adder, flip-flop	registers, ALU, counter, control
Computer	components	TOY

54


History + Future

Computer constructed by layering abstractions.

- Better implementation at low levels improves **everything**.
- Ongoing search for better abstract switch!

History.

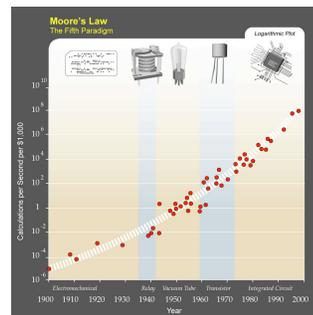- 1820s: mechanical switches.
- 1940s: relays, vacuum tubes.
- 1950s: transistor, core memory.
- 1960s: integrated circuit.
- 1970s: microprocessor.
- 1980s: VLSI.
- 1990s: integrated systems.
- 2000s: web computer.
- Future: quantum, optical soliton, ...



Ray Kurzweil
<http://en.wikipedia.org/wiki/Image:PFPMooresLaw1.jpg>

55

Overview

What is COS 126?

- Broad, but technical, intro to CS.
- No prerequisites, intended for novices.

Goals.

- Demystify computer systems.
- Empower you to exploit available technology.
- Build awareness of substantial intellectual underpinnings.

Topics.

- **Programming** in Java.
- Machine architecture.
- Theory of computation.
- **Applications** to science, engineering, and commercial computing.

56