

20. Central Processing Unit

<http://introc.cs.princeton.edu>

20. CPU

- Overview
- Bits, registers, and memory
- Program counter
- Components and connections

CS.20.A.CPU.Overview

Let's build a computer!

CPU = Central Processing Unit

Computer

- Display
- Touchpad
- Battery
- Keyboard
- ...
- CPU (difference between a TV set and a computer)

Previous lecture

- Combinational circuits
- ALU (calculator)

This lecture

- Sequential circuits with *memory*
- CPU (computer)



3

A smaller computing machine: TOY-8



TOY instruction-set architecture.

- 256 16-bit words of memory.
- 16 16-bit registers.
- 1 8-bit program counter.
- 2 instruction types.
- 16 instructions.



TOY-8 instruction-set architecture.

  - 16 8-bit words of memory.
- 1 8-bit register.
- 1 4-bit program counter.
- 1 instruction type.
- 8 instructions.



Purpose of TOY-8. Illustrate CPU circuit design for a "typical" computer.

4

TOY-8 reference card


opcode	addr
0	0

opcode	operation	pseudo-code
0	halt	halt
2	add	$R = R + M[\text{addr}]$
4	bitwise and	$R = R \& M[\text{addr}]$
6	bitwise xor	$R = R \wedge M[\text{addr}]$
8	load addr	$R = \text{addr}$
A	load	$R = M[\text{addr}]$
C	store	$M[\text{addr}] = R$
E	branch zero	if $(R == 0)$ $PC = \text{addr}$

ZERO $M[0]$ is always 0.

STANDARD INPUT Load from $M[F]$.

STANDARD OUTPUT Store to $M[F]$.

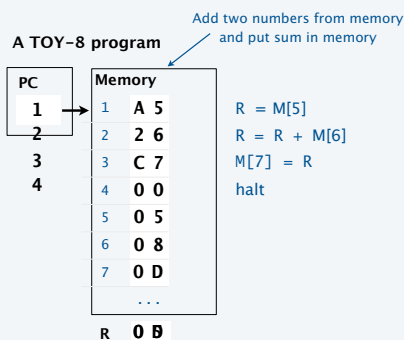

Challenge for the bored:


Write Fibonacci seq, add numbers on stdin, ...

5

CPU circuit components for TOY-8

TOY-8 CPU

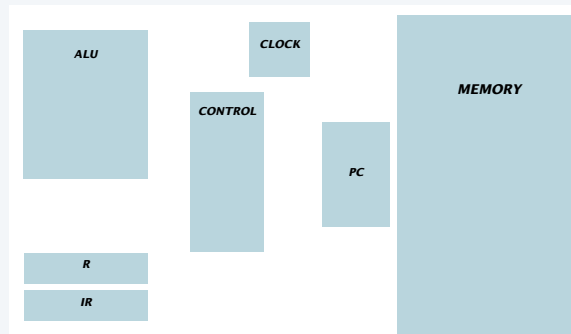- ALU (adder, AND, XOR)
- Memory
- Register (R)
- PC
- IR
- Control
- Clock



Goal. Complete CPU circuit for TOY-8 (same design extends to TOY and to your computer).

6

Review: Components, busses, and control lines

Basic design of our circuits

- Organized as *components* (functional units of TOY: ALU, memory, register, PC, and IR).
- Connected by *busses* (groups of wires that propagate information between components).
- Controlled by *control lines* (single wires that control circuit behavior).

Conventions

- Bus inputs are at the top, input connections are at the left.
- Bus outputs are at the bottom, output connections are at the right.
- Control lines are blue.




These conventions *make circuits easy to understand.*
 (Like style conventions in coding.)

7

Perspective

Q. Why TOY-8?

 A. TOY circuit width would be about 5 times TOY-8 circuit width.



Sobering fact. The circuit for your computer is *hundreds to thousands* of times wider.

Reassuring fact. Design of all three is based on the same fundamental ideas.

8

20. CPU

- Overview
- **Bits, registers, and memory**
- Program counter
- Connections

CS.20.A.CPU.Overview

CS.20.B.CPU.Memory

Sequential circuits

Q. What is a sequential circuit?

A. A digital circuit (all signals are 0 or 1) *with feedback* (loops).

Q. Why sequential circuits?

A. *Memory* (difference between a DFA and a Turing machine).

Basic abstractions

- On and off.
- Wire: Propagates an on/off value.
- Switch: Controls propagation of on/off values through wires.
- Flip-flop: *Remembers a value* (next).


Simple circuits with feedback

Loops in circuits lead to time-varying behavior

- *Sequence* of switch operation matters.
- Need tight control (see next slide).


Example 1. Two switches, each blocked by the other.

- State determined by whichever switches first.
- Stable (once set, state never changes).
- *Basic building block for memory circuits.*

 

 Example 2. Three switches, blocked in a cycle.


- State determined by whichever switches first.
- *Not stable* (cycles through states).




A new ingredient: Circuits with memory

An SR flip-flop controls feedback.

 - Add control lines to switches in simple feedback loop.
- R (reset) sets state to 0.
- S (set) sets state to 1.
- Q (state) is always available.



examples

 


Caveat. Timing of switch vs. propagation delay.

13

Flip-flop application: Memory bit

Add logic to an SR flip-flop for more precise control

 - Provide data value on an *input* wire instead of using S and R controls.
- Use *WRITE* control wire to enable change in flip-flop value.
- Flip-flop value always available as *output*.



14


Memory bit application I: fetch/execute clock

Assumptions

- Physical clock provides regular on/off pulses.
- Duration is *just enough* to trigger a flip-flop.
- Space between pulses is long enough to allow the longest chain of flip-flops in the circuit to stabilize.

Fetch/execute clock. Attach clock to a memory bit.

 - *RUN* control wire starts clock when on.
- *HALT* control wire stops clock when on.
- Memory bit flips on each clock tick (flip value and feed back to input).
- Result: on/off sequence for *FETCH* and *EXECUTE* control wires that control the CPU (stay tuned).



15

Fetch/execute clock with write pulses

Generates on/off signals for 4 control wires


- *FETCH*.
- *FETCH WRITE* pulse.
- *EXECUTE*.
- *EXECUTE WRITE* pulse.

Implementation

- Add AND gates to fetch/execute clock.
- *FETCH WRITE* = *FETCH AND CLOCK*.
- *EXECUTE WRITE* = *EXECUTE AND CLOCK*.

Application

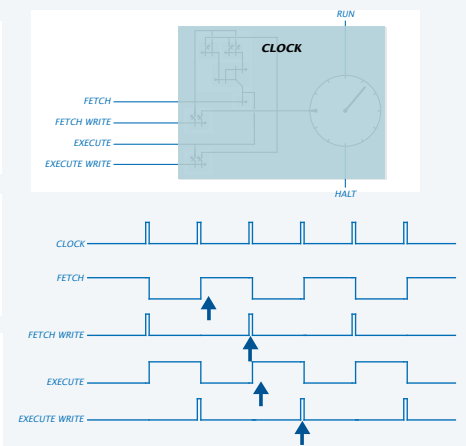- Implements CPU fetch/execute cycles.
- Signals turn on control wires that change the state of PC, R, IR, and memory.



Interesting events occur at four distinct times in the cycle

16

Memory bit application II: Register

Register


- w memory bits.
- w -bit input bus.
- values available on output bus.
- input loaded on *WRITE* pulse.

Implementation

- Connect memory bits to busses.
- Use *WRITE* pulse for all of them.

Applications for TOY-8

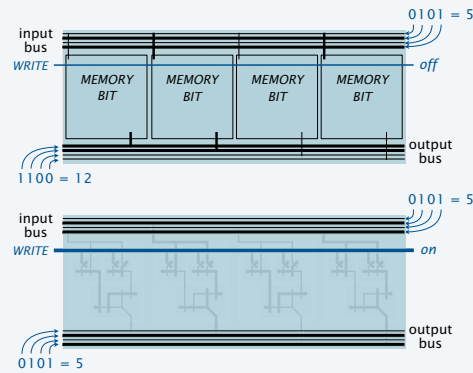- PC holds 4-bit address.
- IR holds 8-bit instruction.
- R holds 8-bit data value.



17

Memory bit application III: Memory bank

Memory bank

- 2^n words, each w bits.
- n -bit address input.
- w -bit input bus.
- value of *selected word* available on output bus.
- input loaded *to selected word* on *WRITE* pulse.



18

Memory bit application III: Memory bank

Memory bank


- 2^n words, each w bits.
- n -bit address input.
- w -bit input bus.
- value of *selected word* available on output bus.
- input loaded *to selected word* on *WRITE* pulse.

Implementation

- Decoder/demux selects word.
- One-hot muxes take selected word to output bus.

Application for TOY-8

- Main memory.

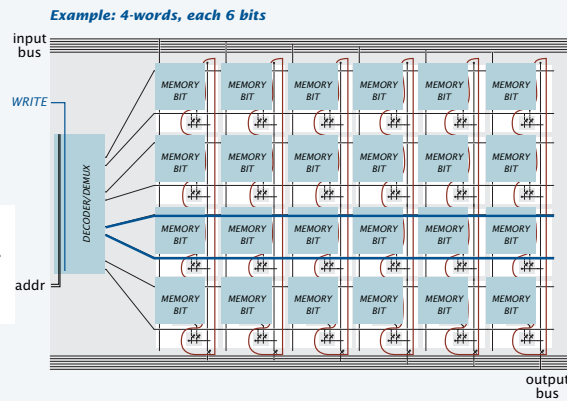

19

TOY-8 main memory bank


Interface

- Input bus (for store)
- Output bus (for load)
- Address to select a word
- Write control signal

Connections

- Input bus from registers
- Output bus to IR and R
- Address bits from PC and IR

	words	bits/word	addr bits
TOY-8	16	8	4
TOY	256	16	8
your computer	1 billion	64	32

 

20

20. CPU

- Overview
- Bits, registers, and memory
- **Program counter**
- Components and connections

CS.20.B.CPU.Memory

CS.20.C.CPU.PC

Designing a digital circuit: overview

Steps to design a digital (sequential) circuit

- Design interface: input busses, output busses, control signals.
- Determine components.
- Determine connections.
- Establish control sequence.



Warmup. Design TOY-8 program counter (PC).

First challenge. Need an *incrementer* circuit.

Second challenge. Multiple bus connections.

23

Pop quiz on combinational circuit design

Q. Design a circuit to compute $x + 1$.

24

Pop quiz on combinational circuit design

Q. Design a circuit to compute $x + 1$.

A. Start with a bitwise adder

- Delete y inputs, set carry in to 1.
- Compute carry with AND and sum with XOR.

C_4	C_3	C_2	C_1	1
+	X_3	X_2	X_1	X_0
	Z_3	Z_2	Z_1	Z_0


carry bit

X_i	C_i	C_{i+1}	AND
0	0	0	0
0	1	0	0
1	0	0	0
1	1	1	1

sum bit

X_i	C_i	Z_i	XOR
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

4-bit incrementer

 


25

Multiple bus connections


If component *outputs go to multiple other components*

 - No problem, just use T connections.
- Values on both busses are the same.
- Example: Register connects to ALU and memory.



If component *inputs come from multiple other components*

 - **Problem.**
- Values on the busses are *different*.
- Example: ALU, memory, and IR connect to register.
- Solution: Need a *selector switch* (bus mux).





26

A (virtual) bus selector switch

One-hot m -way bus mux

- m input busses.
- m control lines (selection).
- One output bus.
- At most one selection line is 1.
- Output bus lines have same value as selected input bus lines.

Example: 4-bit 3-way bus mux

  


Important to note. No direct connection from input to output.

27

One-hot bus mux

One-hot m -way bus mux

 - m input busses.
- m control lines (selection).
- One output bus.
- At most one selection line is 1.
- Output bus lines have same value as selected input bus lines.



Implementation

- Bitwise one-hot muxes for output.

Application (next): Select among inputs to a component.

28

Program counter (PC)

The *PC* holds an address and supports 3 control wires:

- **INCREMENT**. Add 1 to value when *WRITE* becomes 1.
- **LOAD**. Set value from input bus when *WRITE* becomes 1.
- **WRITE**. Enable PC address to change as specified.


The current address is always available on the output bus.

Components

- PC register (4-bit).
- Incrementer (add 1).

Connections

 - Input bus to PC register.
 - Incrementer to PC register.
 - PC register to incrementer.
 - PC register to output bus.
- need 2-way bus mux*



output bus 29

Program counter (PC)

The *PC* holds an address and supports 3 control wires:

- **INCREMENT**. Add 1 to value when *WRITE* becomes 1.
- **LOAD**. Set value from input bus when *WRITE* becomes 1.
- **WRITE**. Enable PC address to change as specified.


The current address is always available on the output bus.

Components

- PC register (4-bit).
- Incrementer (add 1).
- 2-way bus mux.

Connections

 - Input bus to bus mux.
- Incrementer to bus mux.
- Bus mux to PC register.
- PC register to incrementer.
- PC register to output bus.




output bus 30

Summary of TOY-8 PC circuit

The *PC* supports two control-signal sequences:

- **Load, then write**. Set address from input bus (example: branch instruction).
- **Increment, then write**. Add one to value.

 Address is written to the PC register in both cases and always available on the output bus.



Next. CPU circuit.

Important note: write pulse must be very short because of the cycle in this circuit.

31

20. CPU

- Overview
- Bits, registers, and memory
- Program counter
- Components, connections, and control

TOY-8: Interface

CPU is a circuit inside the machine




Interface to outside world

- Switches and lights
- ON/OFF
- RUN

Connections to outside (omitted)

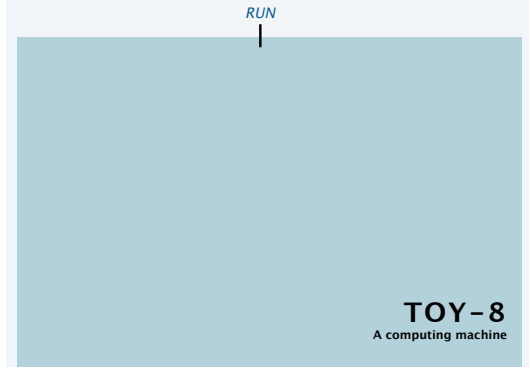
- ADDR to PC
- DATA to memory bank input bus
- Buttons to control lines that activate memory load/store



Review: CPU circuit components for TOY-8


TOY-8 CPU

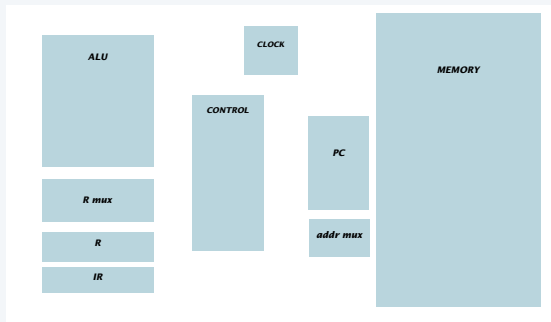- ALU (adder, AND, XOR)
- Memory
- Register (R)
- PC
- IR
- Control
- Clock




Also needed (see next slide): Bus muxes for R and memory addr.

Connections for TOY-8 CPU

 

instructions	bus connections
fetch (all)	PC (to memory addr)
	memory to IR
halt	none
	IR addr (to memory addr)
add, and, xor	memory to ALU I
	R to ALU O
load address	ALU (to R)
	IR addr (to R)
load	IR addr to memory addr
	memory (to R)
store	IR addr to memory addr
	R to memory
branch if zero	IR addr to PC

Control wires for TOY-8 CPU

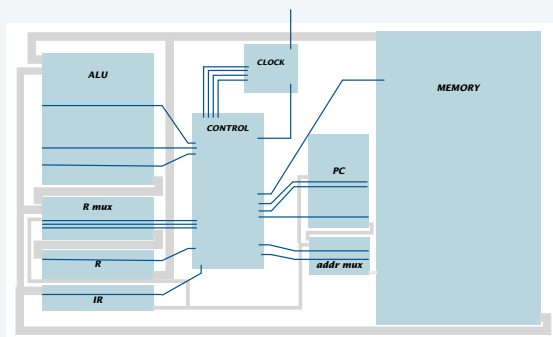

component	control wires
CLOCK	RUN
	HALT
CONTROL	FETCH
	FETCH WRITE
	EXECUTE
ALU	EXECUTE WRITE
	ADD
	XOR
R mux	AND
	R MUX ALU
	R MUX MEM
	R MUX IR
R	R WRITE
IR	IR WRITE
memory	MEMORY WRITE
	PC INCREMENT
PC	PC LOAD
	PC WRITE
	ADDR MUX PC
addr mux	ADDR MUX PC
	ADDR MUX IR

37

One final combinational circuit: Control


Control. Circuit for control wire sequencing.

Inputs

- Four control wires from clock.
- opcode from IR.
- contents of R.

Outputs

- 15 control wires for CPU components.

 

Key feature. A simple combinational circuit.


38

Control wire sequences

	FETCH	FETCH WRITE	EXECUTE WRITE
all instructions	ADDR MUX PC		
	PC INCREMENT*	IR WRITE	PC WRITE

* PC LOAD for branch if 0 if R is 0.


instruction	EXECUTE	EXECUTE WRITE
halt	HALT	
add	ALU ADD	R WRITE
	R MUX ALU	
xor	ALU ADD	R WRITE
	R MUX ALU	
and	ALU ADD	R WRITE
	R MUX ALU	
load address	R MUX IR	R WRITE
load	R MUX MEMORY	R WRITE
	R MUX IR	
store	ADDR MUX IR	MEMORY WRITE

 

39

Sample program

1 A5
2 26
3 C7
4 00
5 05
6 08

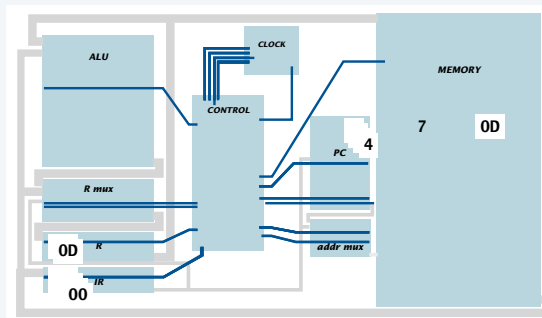


And THAT . . . is how your computer works!

	control signal	result
FETCH	ADDR MUX PC	
FETCH WRITE	IR WRITE	IR = A5
EXECUTE	PC INCREMENT	
	ADDR MUX IR	
EXECUTE WRITE	R MUX MEMORY	R = 05
	PC WRITE	PC = 2
FETCH	ADDR MUX PC	
FETCH WRITE	IR WRITE	IR = 26
EXECUTE	PC INCREMENT	
	ALU ADD	
EXECUTE WRITE	R MUX ALU	R = 0D
	PC WRITE	PC = 3
FETCH	ADDR MUX PC	
FETCH WRITE	IR WRITE	IR = C7
EXECUTE	PC INCREMENT	
	ADDR MUX IR	
EXECUTE WRITE	MEMORY WRITE	M[7] = 0D
	PC WRITE	PC = 4
FETCH	ADDR MUX PC	
FETCH WRITE	IR WRITE	IR = 00
EXECUTE	PC INCREMENT	
	HALT	


40

TOY-8 CPU

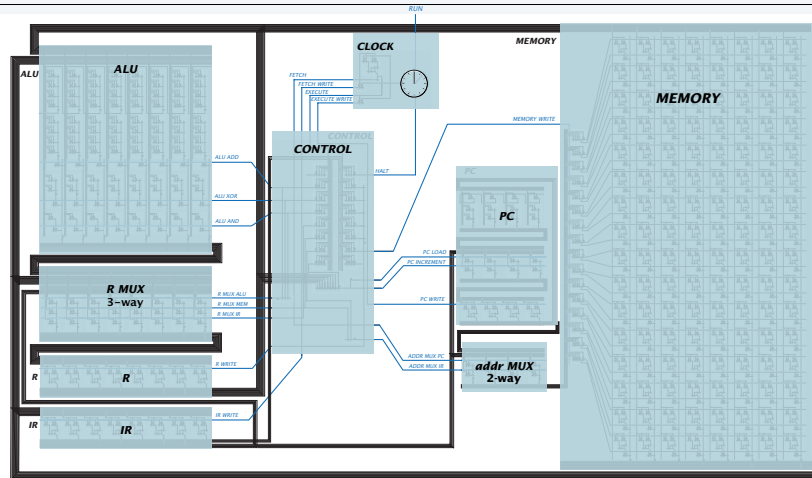


41

TOY-8 CPU

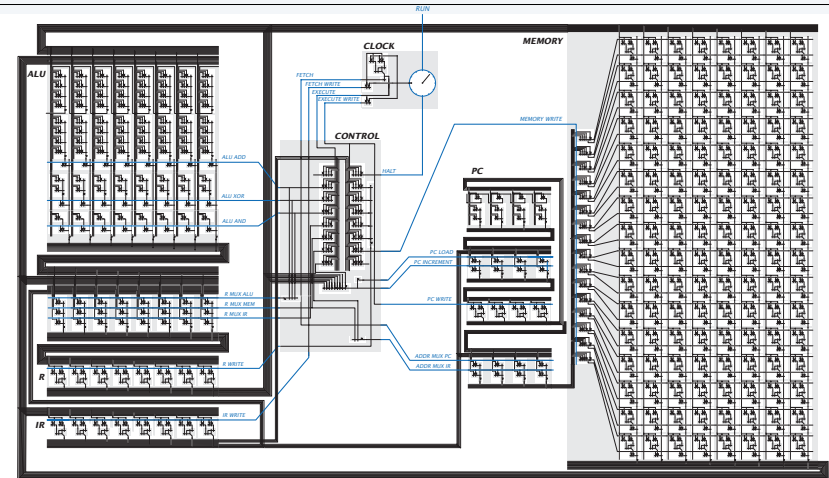

42

 Scanning electron microscope image of a real microprocessor





Memory bits per square cm	
modern microprocessor	25 billion
TOY-8	1

43

How does your computer work?

A not-so-short answer, in case someone asks...

- A circuit known as the *CPU* is built from *switches* connected by *wires*.
- The CPU performs operations on information encoded in binary, *including its own instructions*.
- Circuits with feedback implement *memories*.
- Instructions move information among memories, specify the next operation, or implement mathematical functions based on *Boolean logic*.
- Clock pulses activate sequences of *control signals*, which cause state changes that implement machine instructions.
- Virtually everything else is implemented as *layers of software*, each layer adding additional power and scope.

  

44

What is this course about?

A broad introduction to **computer science**.

Goals

- Empower you to exploit available technology. ✓
- Build awareness of intellectual underpinnings. ✓
- Demystify computer systems. ✓

45

What is this course about?

A broad introduction to **computer science**.

Goals

- Empower you to exploit available technology. ✓
- Build awareness of intellectual underpinnings. ✓
- Demystify computer systems. ✓

Next: Algorithms.



46

COMPUTER SCIENCE
SEDGWICK / WAYNE

Image sources

<http://download.intel.com/pressroom/images/corefamily/westmere4.jpg>

<http://www.sciencefoto.de/detail.php?rubrik=Nano&id=214956&lang=en&q=&qrubrik=>

20. Central Processing Unit



<http://introc.cs.princeton.edu>