

<https://introcs.cs.princeton.edu>

## 7. DIGITAL CIRCUITS

---

- ▶ *boolean algebra*
- ▶ *logic gates*
- ▶ *sum-of-products*
- ▶ *adder circuit*

# Context

---

Q. How are computers built?


A. Not nearly as complicated as you might think.

This lecture. Introduction to **digital circuits**.


- Digital = all signals are either 0 or 1.
- Analog = signals vary continuously.
- Advantages of digital: accurate, reliable, fast, cheap, scalable, ...



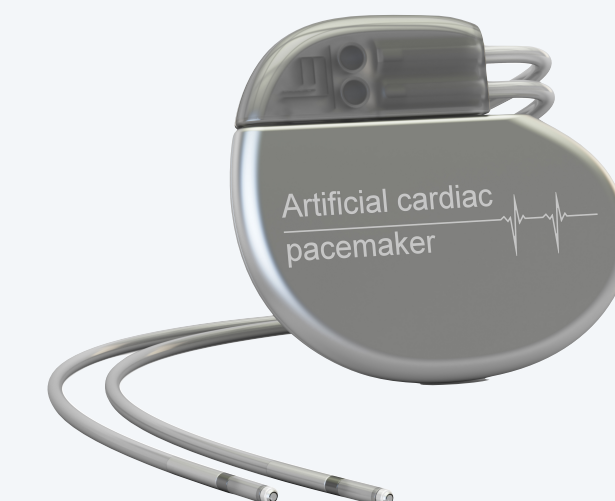Applications. Laptop, smartphone, gaming console, pacemaker, ...





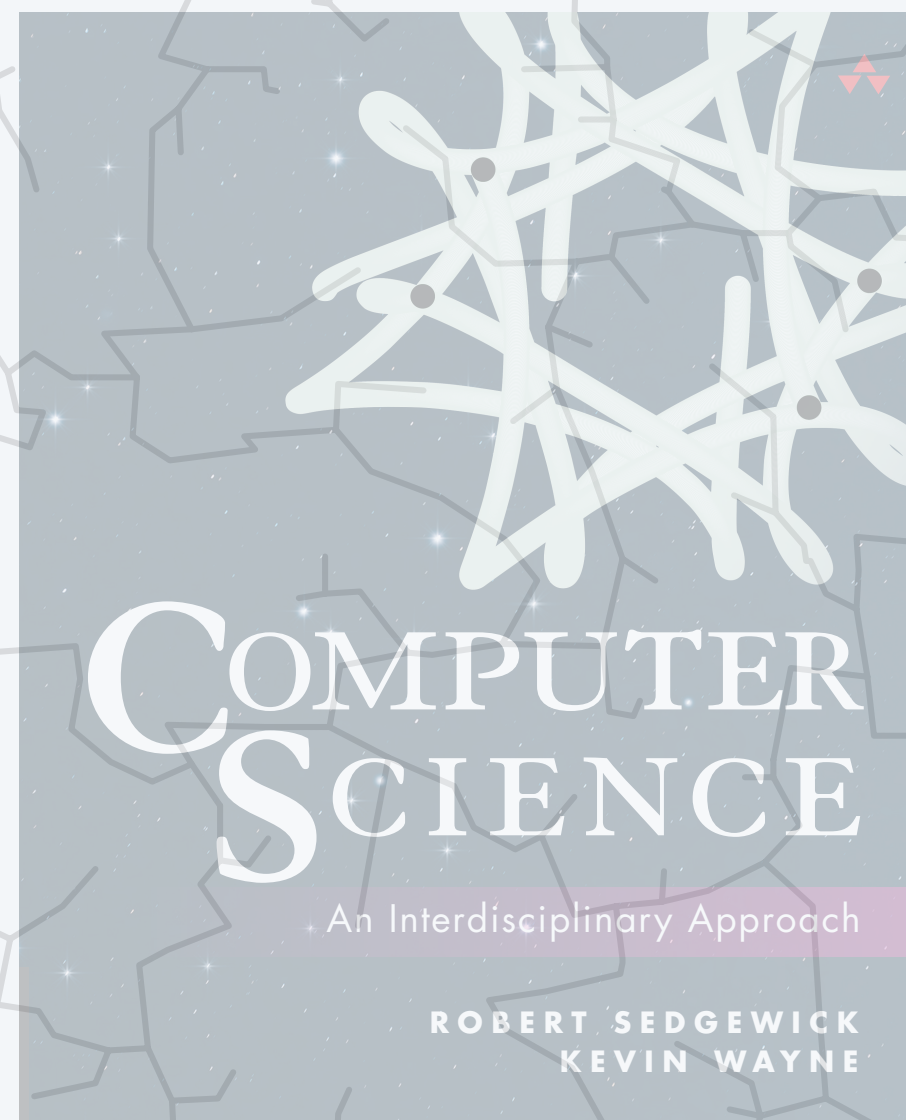

<https://introcs.cs.princeton.edu>

## 7. DIGITAL CIRCUITS


---

- ▶ *boolean algebra*
- ▶ *logic gates*
- ▶ *sum-of-products*
- ▶ *adder circuit*
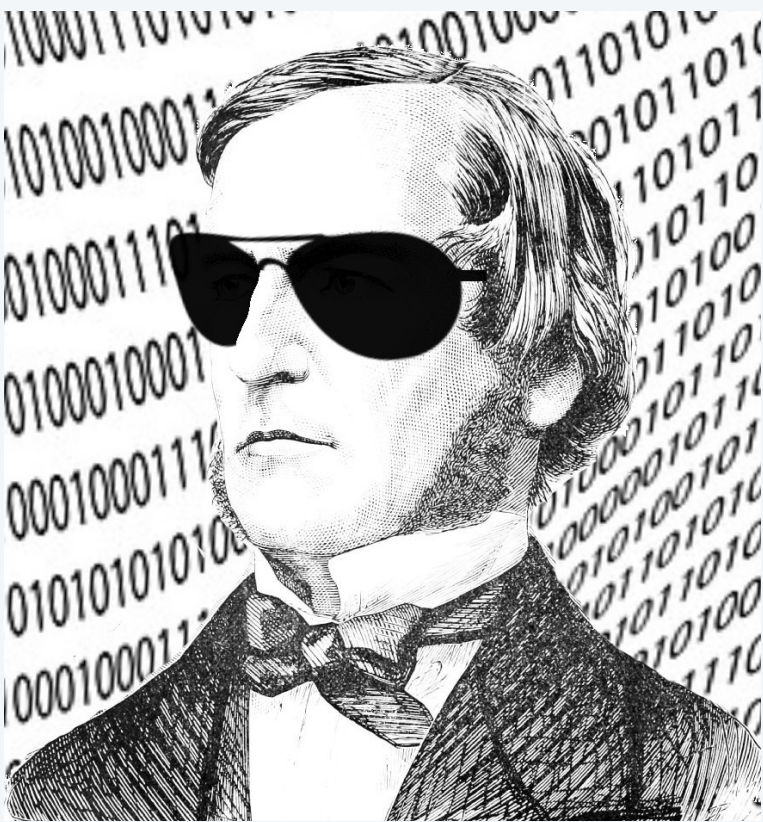
# Boolean algebra

**Boolean algebra.** Developed by George Boole in 1840s to study logic problems.

- Values of variables are *true* (1) or *false* (0).
- Primitive operations are *NOT*, *AND*, and *OR*.
- Widely used in mathematics, logic, computer science, ...



George Boole is Coole

operation	logic notation	Java syntax	circuit notation	precedence	
<i>NOT</i>	$\neg x$	<code>!x</code>	$x'$	highest	
<i>AND</i>	$x \wedge y$	<code>x &amp;&amp; y</code>	$x \cdot y$	middle	$\bar{x}$ (alternative)
<i>OR</i>	$x \vee y$	<code>x    y</code>	$x + y$	lowest	$xy$ (shorthand)

↑  
*this lecture*

**Relevance to circuits.** Provides the mathematical foundation.



# Truth tables

**Boolean function.** A function whose arguments and result assume the values 0 and 1.

**Truth table.** A systematic way to define a boolean function.

- One row for each possible assignment of arguments.
- Each row gives the function value for the specified arguments.
- The truth table of a boolean function of  $n$  variables has  $2^n$  rows.

$x$	$x'$
0	1
1	0

NOT

$x$	$y$	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

AND

$x$	$y$	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

OR

$x$	$y$	$z$	$f(x, y, z)$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



*count in binary from 0 to  $2^n - 1$*

# Boolean algebra properties

Boolean algebra shares many properties with elementary algebra. ← *justifies use of  $\cdot$  and  $+$  for AND and OR*

property	AND	OR	
<i>commutative</i>	$x \cdot y = y \cdot x$	$x + y = y + x$	
<i>associative</i>	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$	$x + (y + z) = (x + y) + z$	<span style="color: #808080;">←</span> <i>same as elementary algebra</i>
<i>identity</i>	$x \cdot 1 = x$	$x + 0 = x$	
<i>distributive</i>	$x \cdot (y + z) = (x \cdot y) + (x \cdot z)$	$x + (y \cdot z) = (x + y) \cdot (x + z)$	
<i>complementary</i>	$x \cdot x' = 0$	$x + x' = 1$	
<i>idempotent</i>	$x \cdot x = x$	$x + x = x$	<span style="color: #808080;">←</span> <i>different from elementary algebra</i>
<i>De Morgan</i>	$(x \cdot y)' = x' + y'$	$(x + y)' = x' \cdot y'$	
<i>duality</i>	<i>for any property, can interchange <math>+</math> and <math>\cdot</math>, along with 0 and 1</i>		
$\vdots$	$\vdots$		



# Proving a theorem in Boolean algebra

Q. How to prove a theorem, such as De Morgan’s law?

A1. Apply sequence of known theorems.

A2. For each possible assignment of truth values to variables, evaluate the purported theorem; confirm that it is *true*. ← “method of perfect induction”

Ex. De Morgan’s law:  $(x \cdot y)' = (x' + y')$ .

$x$	$y$	$x \cdot y$	$(x \cdot y)'$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

truth table for LHS

$x$	$y$	$x'$	$y'$	$x' + y'$
0	0	1	1	1
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0

truth table for RHS

# Boolean functions of two variables

---

**Boolean function.** A function whose arguments and result assume the values 0 and 1.

<i>x</i>	<i>y</i>	<i>AND</i>	<i>OR</i>	<i>XOR</i>	<i>NAND</i>	<i>NOR</i>	<i>XNOR</i>
0	0	0	0	0	1	1	1
0	1	0	1	1	1	0	0
1	0	0	1	1	1	0	0
1	1	1	1	0	0	0	1

commonly used boolean functions of 2 variables



# Boolean functions of three (and more) variables

**Boolean function.** A function whose arguments and result assume the values 0 and 1.

<i>x</i>	<i>y</i>	<i>z</i>	<i>AND</i>	<i>OR</i>	<i>MAJ</i>	<i>ODD</i>
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	0	1	0	1
0	1	1	0	1	1	0
1	0	0	0	1	0	1
1	0	1	0	1	1	0
1	1	0	0	1	1	0
1	1	1	1	1	1	1

commonly used boolean functions of 3 variables

function	shorthand	description
<i>logical AND</i>	<i>AND</i>	all inputs are 1
<i>logical OR</i>	<i>OR</i>	at least one input is 1
<i>majority</i>	<i>MAJ</i>	more inputs are 1 than 0
<i>odd parity</i>	<i>ODD</i>	odd number of inputs are 1

*these functions  
extends to n variables*



Which of the following does **not** represent majority function?

A.  $(x \cdot y) + (y \cdot z)$


B.  $(x \cdot y) + (y \cdot z) + (x \cdot z)$

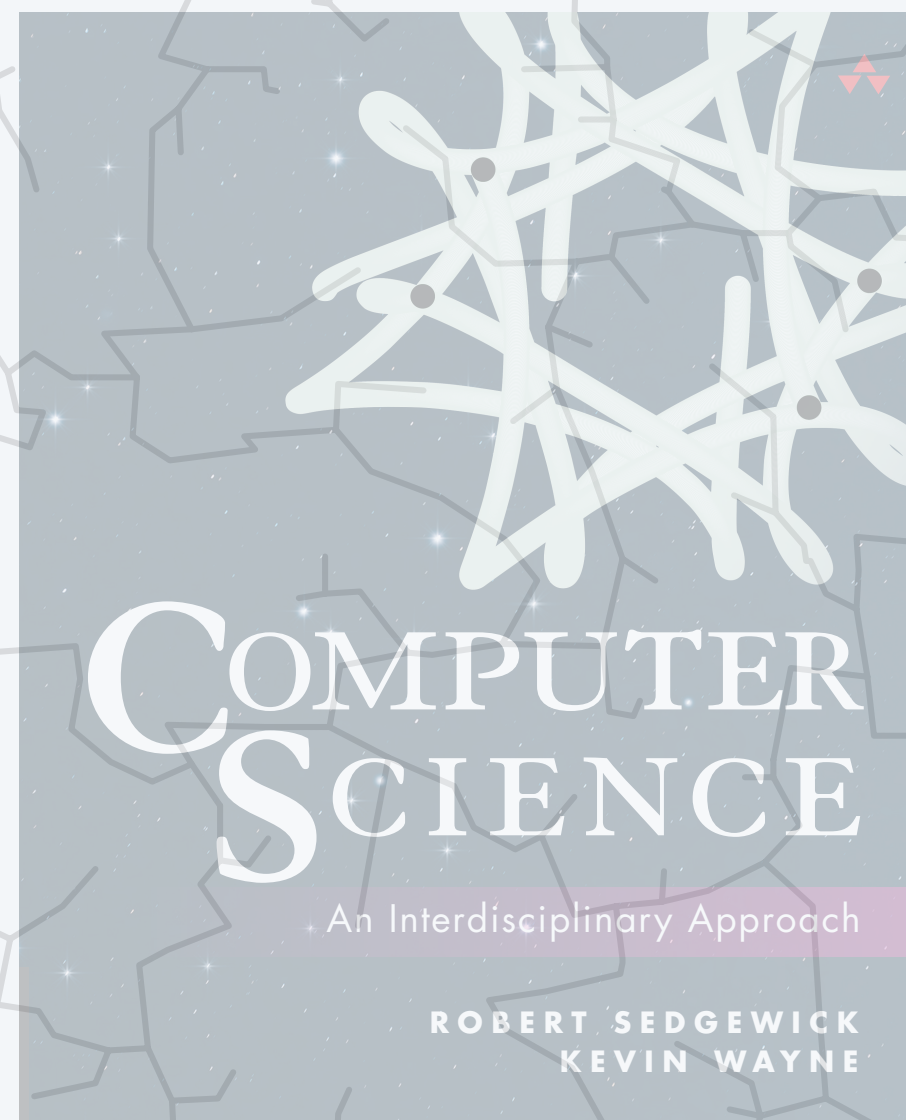C.  $z \cdot (x' \cdot y + x \cdot y') + x \cdot y$

D.

```
public static boolean majority(boolean x, boolean y, boolean z) {  
    int count = 0;  
    if (x) count++;  
    if (y) count++;  
    if (z) count++;  
    return count >= 2;  
}
```





<https://introcs.cs.princeton.edu>

## 7. DIGITAL CIRCUITS

---


- ▶ *boolean algebra*
- ▶ *logic gates*
- ▶ *sum-of-products*
- ▶ *adder circuit*

# A basis for digital devices

---

**Claude Shannon.** Identified the deep connection between **Boolean algebra** and **circuits**.

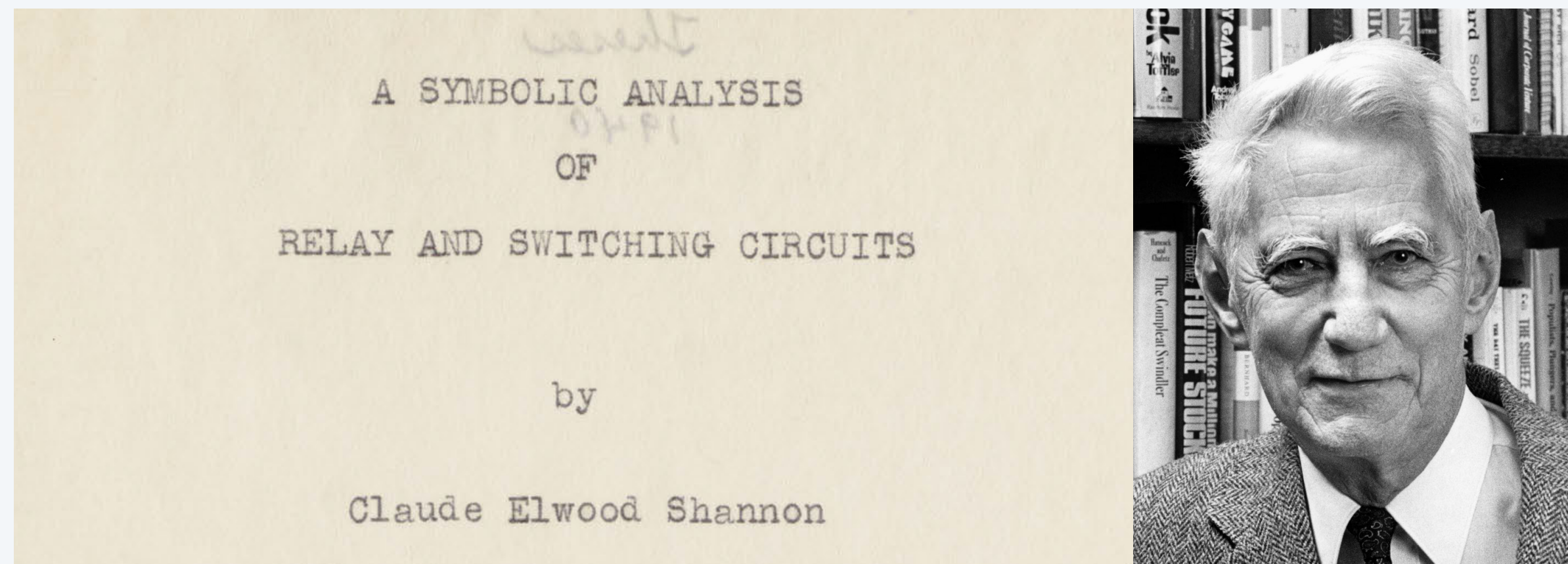- Demonstrated how circuits could be analyzed using Boolean algebra.
- Designed circuits to perform mathematical operations on binary numbers. ← *add, subtract, multiply, factor, ...*






Claude Shannon's master's thesis at MIT (1937)

**Impact.** Every electronic device we use today is based upon Shannon's foundational work.



# Primitive logic gates: AND, OR, and NOT


Logic gate. Physical device that implement a boolean function with one output.

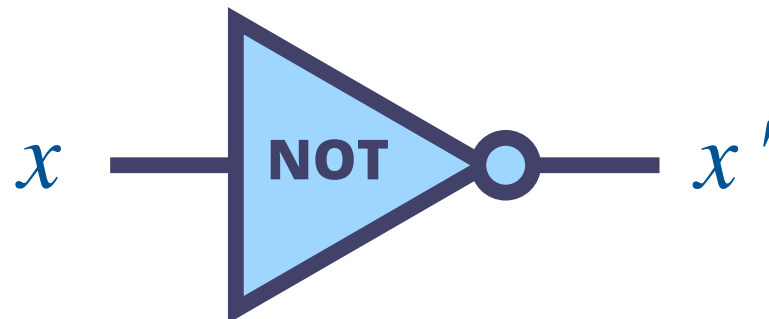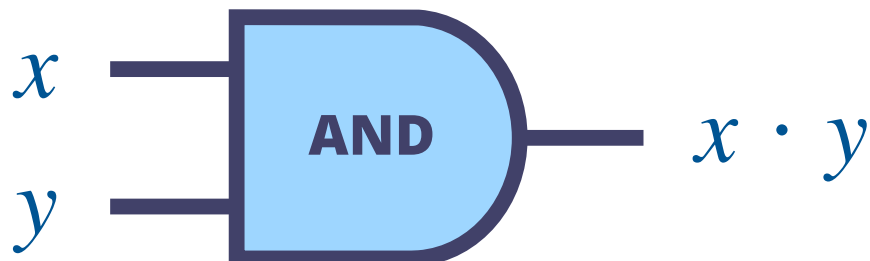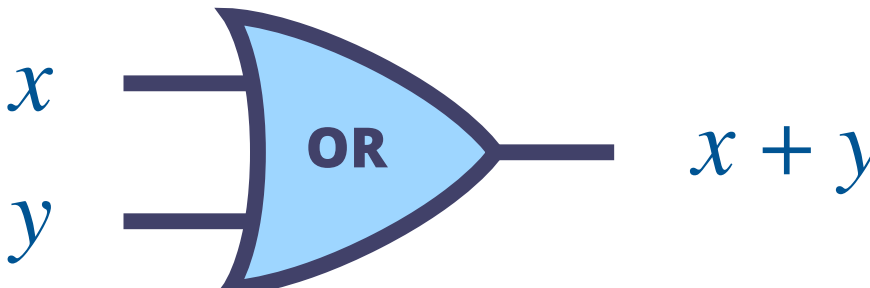gate	truth table	notation	symbol															
<i>NOT</i> ( <i>inverter</i> )	<table><tr><th><i>x</i></th><th><i>NOT</i></th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	<i>x</i>	<i>NOT</i>	0	1	1	0	$x'$										
<i>x</i>	<i>NOT</i>																	
0	1																	
1	0																	
<i>AND</i>	<table><tr><th><i>x</i></th><th><i>y</i></th><th><i>AND</i></th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	<i>x</i>	<i>y</i>	<i>AND</i>	0	0	0	0	1	0	1	0	0	1	1	1	$x \cdot y$	
<i>x</i>	<i>y</i>	<i>AND</i>																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
<i>OR</i>	<table><tr><th><i>x</i></th><th><i>y</i></th><th><i>OR</i></th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	<i>x</i>	<i>y</i>	<i>OR</i>	0	0	0	0	1	1	1	0	1	1	1	1	$x + y$	
<i>x</i>	<i>y</i>	<i>OR</i>																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
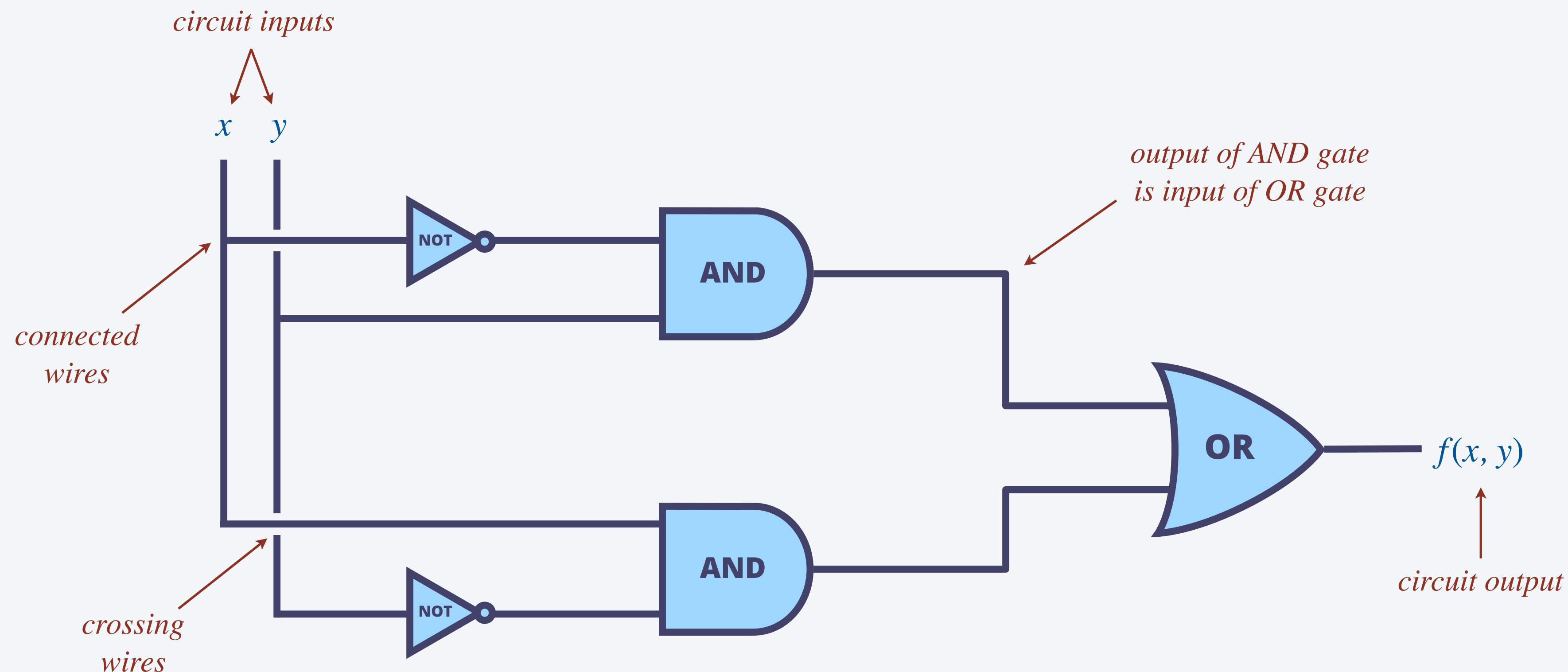
# Digital circuits

**Digital circuit.** A network of **logic gates** connected by **wires**.

- Every wire is either *on* (1) or *off* (0).
- Can connect output of one gate to input of another gate.
- Any wire connected to a wire that is *on* is also *on* (and same for *off*).




$x$	$y$	$XOR$
0	0	0
0	1	1
1	0	1
1	1	0



**Digital circuit.** A network of **logic gates** connected by **wires**.

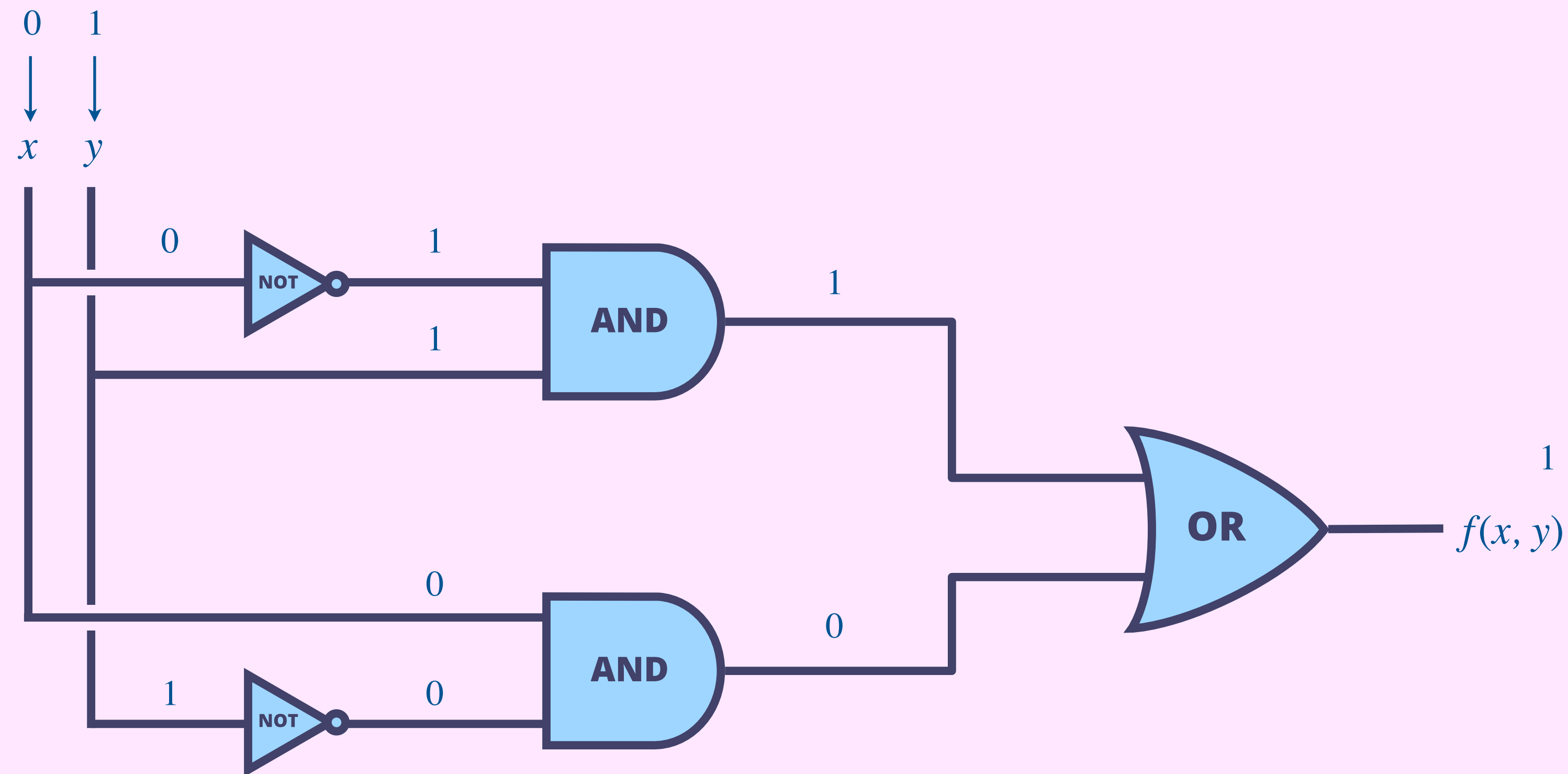- Every wire is either *on* (1) or *off* (0).
- Can connect output of one gate to input of another gate.
- Any wire connected to a wire that is *on* is also *on* (and same for *off*).




$x$	$y$	$XOR$
0	0	0
0	1	1
1	0	1
1	1	0





For which values of  $x$  and  $y$  does the following circuit output 1 ?

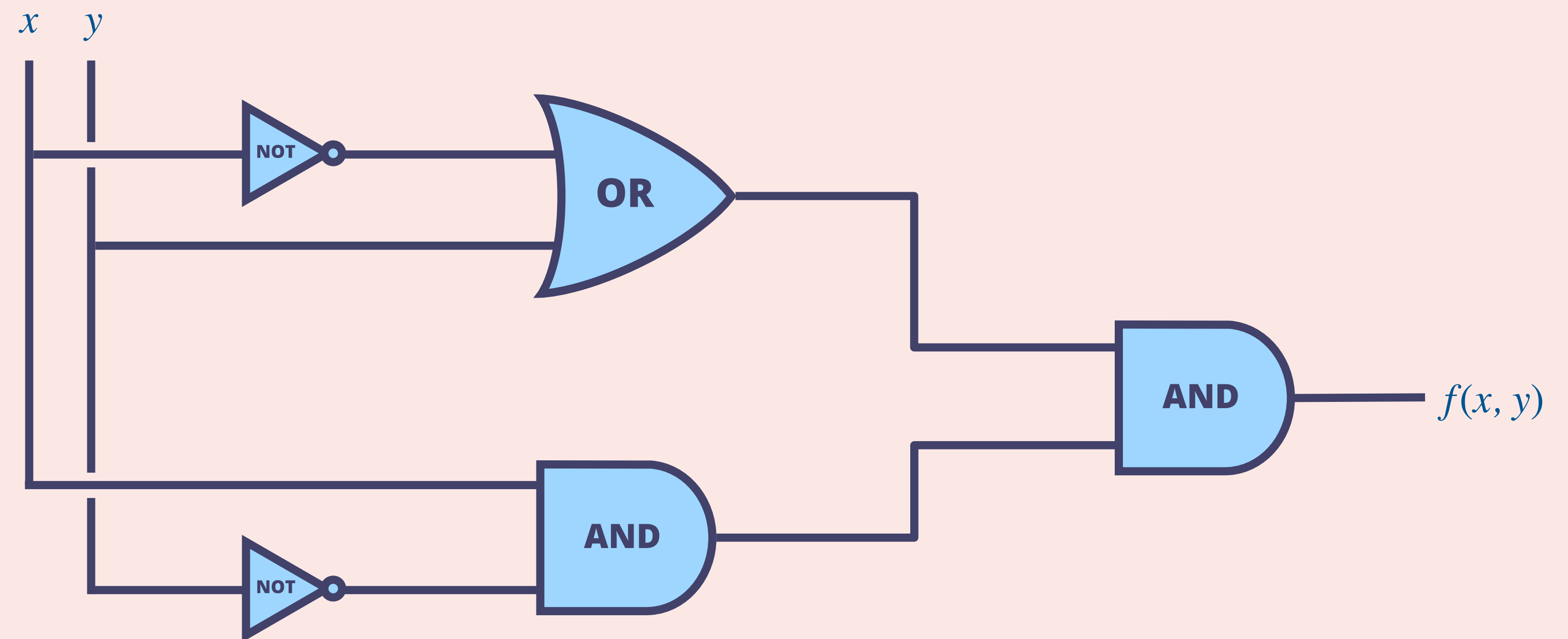
- A.  $x = 0, y = 0$
- B.  $x = 0, y = 1$
- C.  $x = 1, y = 0$
- D.  $x = 1, y = 1$
- E. None of the above.




# Multiway *AND* gates
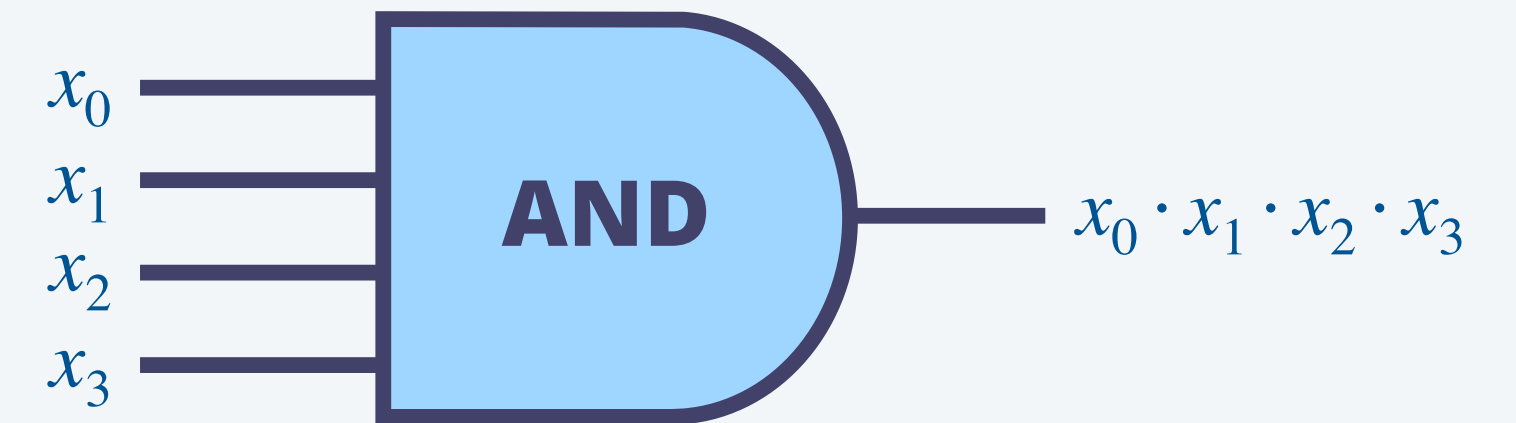
## Multiway *AND* gate.

- 1 if all inputs are 1.
- 0 if any input is 0.



4-way AND gate symbol

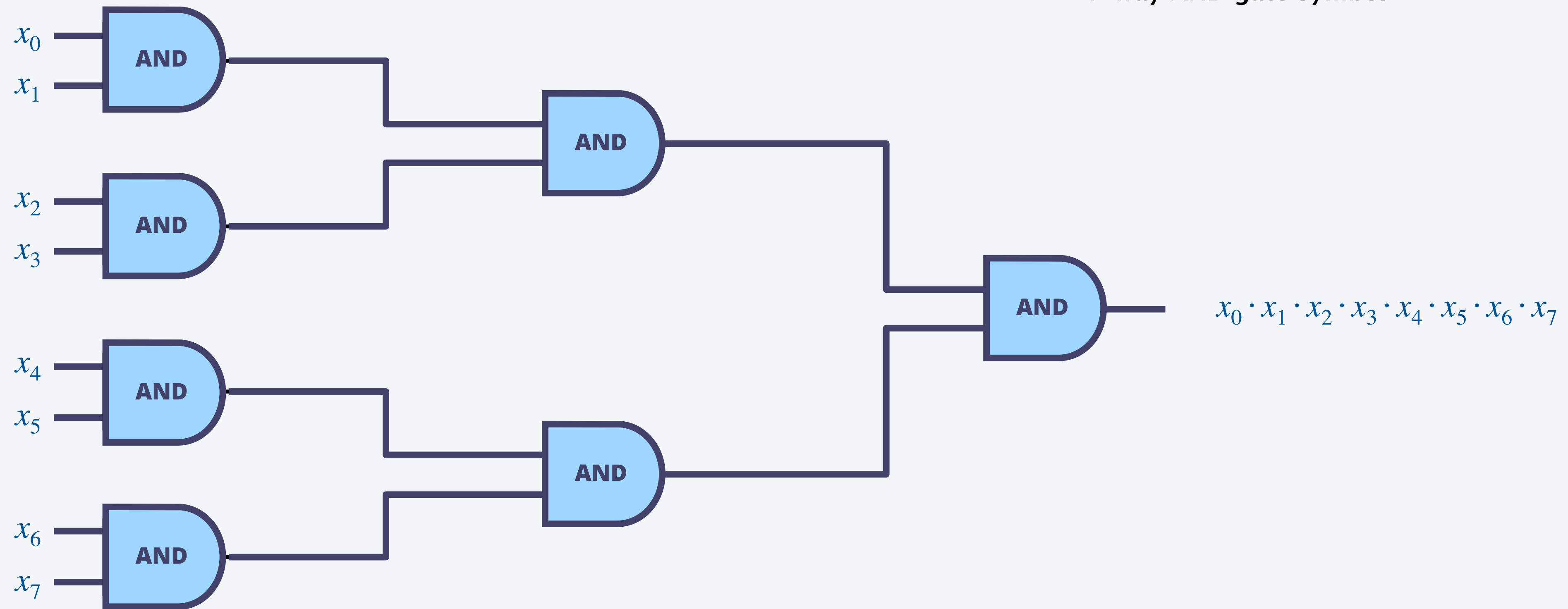


8-way AND gate implementation  
(tree of 2-way AND gates)


# Multiway OR gates
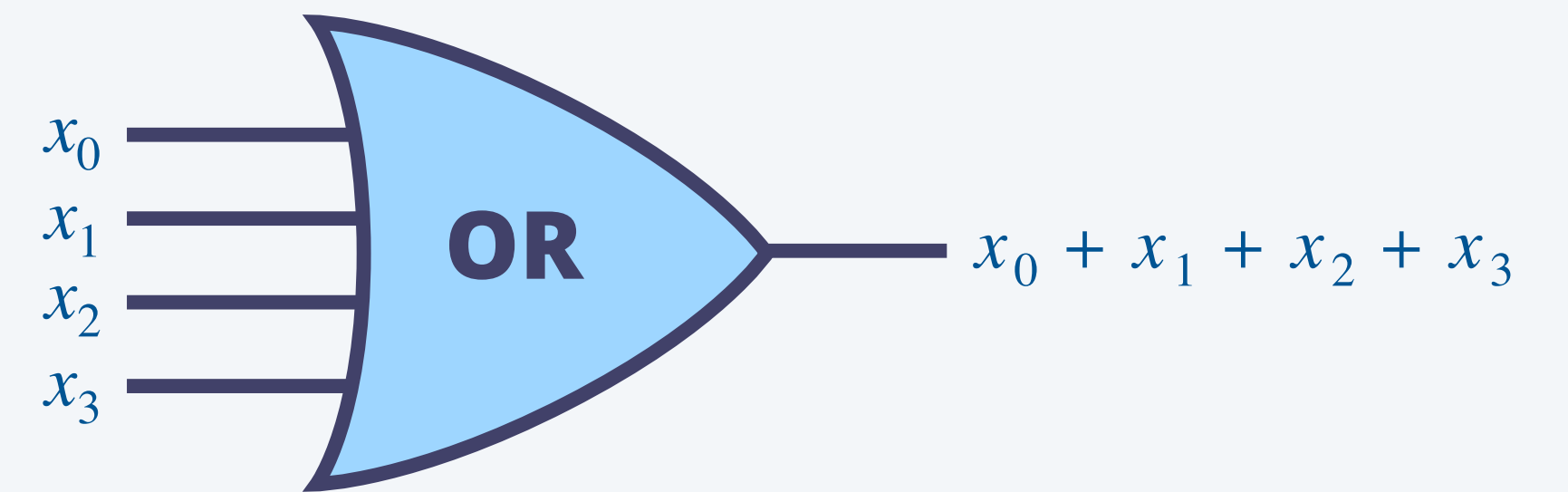
## Multiway OR gate.

- 1 if any input is 1.
- 0 if all inputs are 0.



4-way OR gate symbol

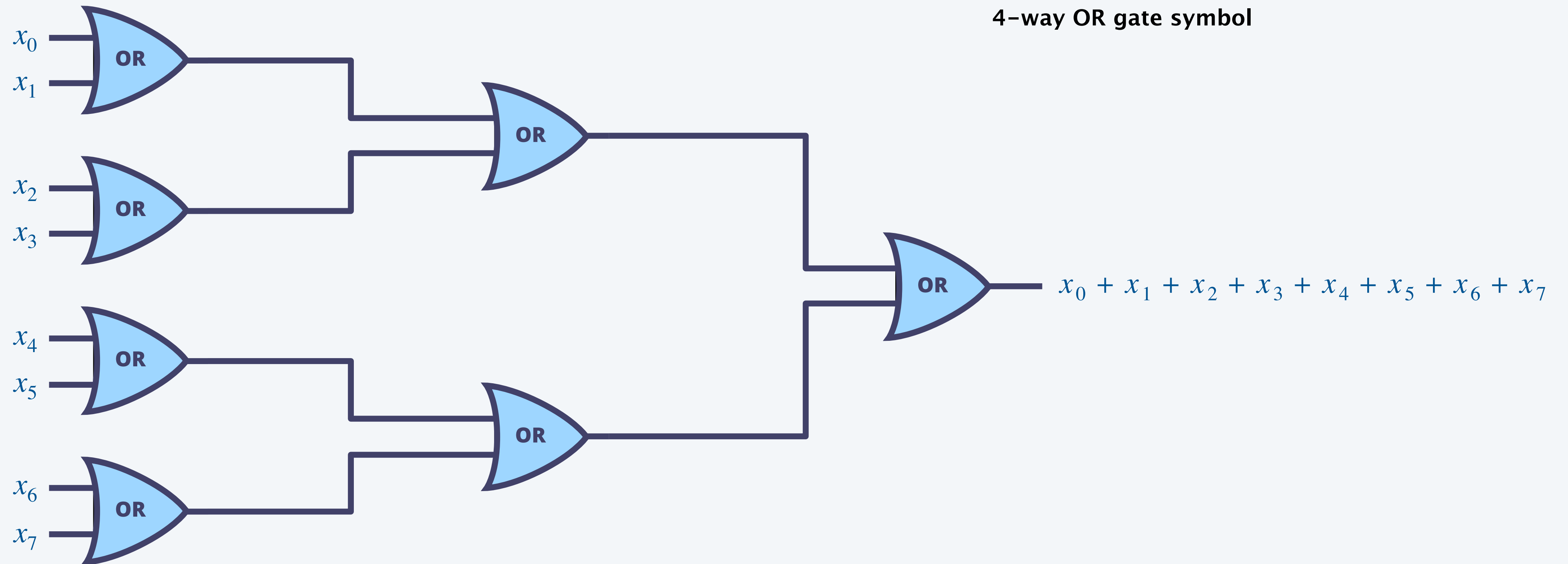


8-way OR gate implementation  
(tree of 2-way OR gates)


# Generalized *AND* gates
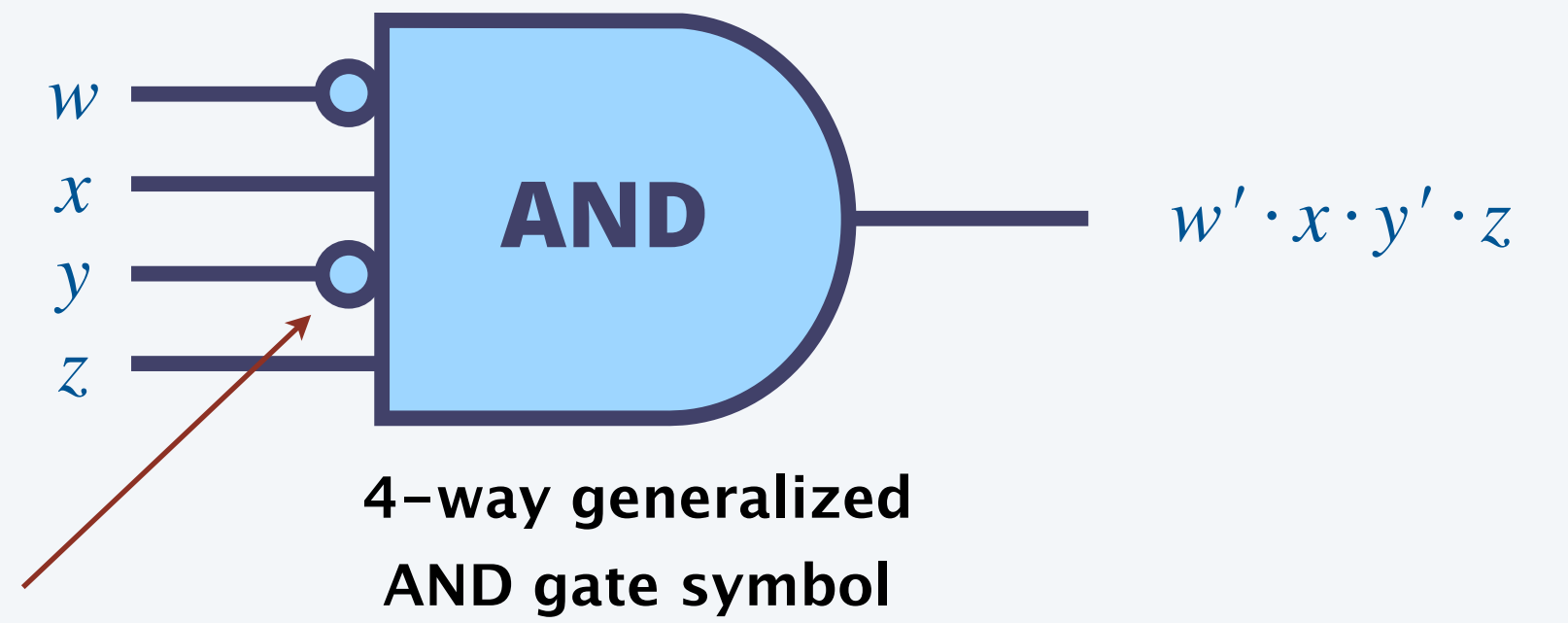
## Generalized *AND* gate.


- 1 for exactly one set of input values.
- 0 for all other sets of input values.



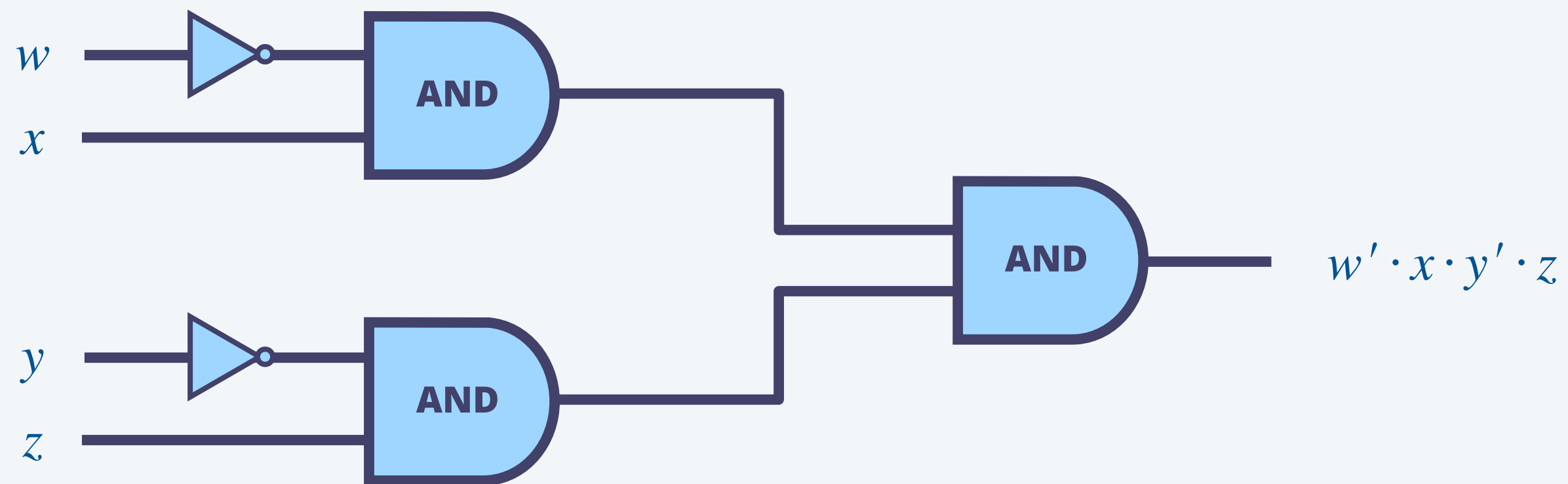*each "inversion bubble"  
denotes a NOT gate*



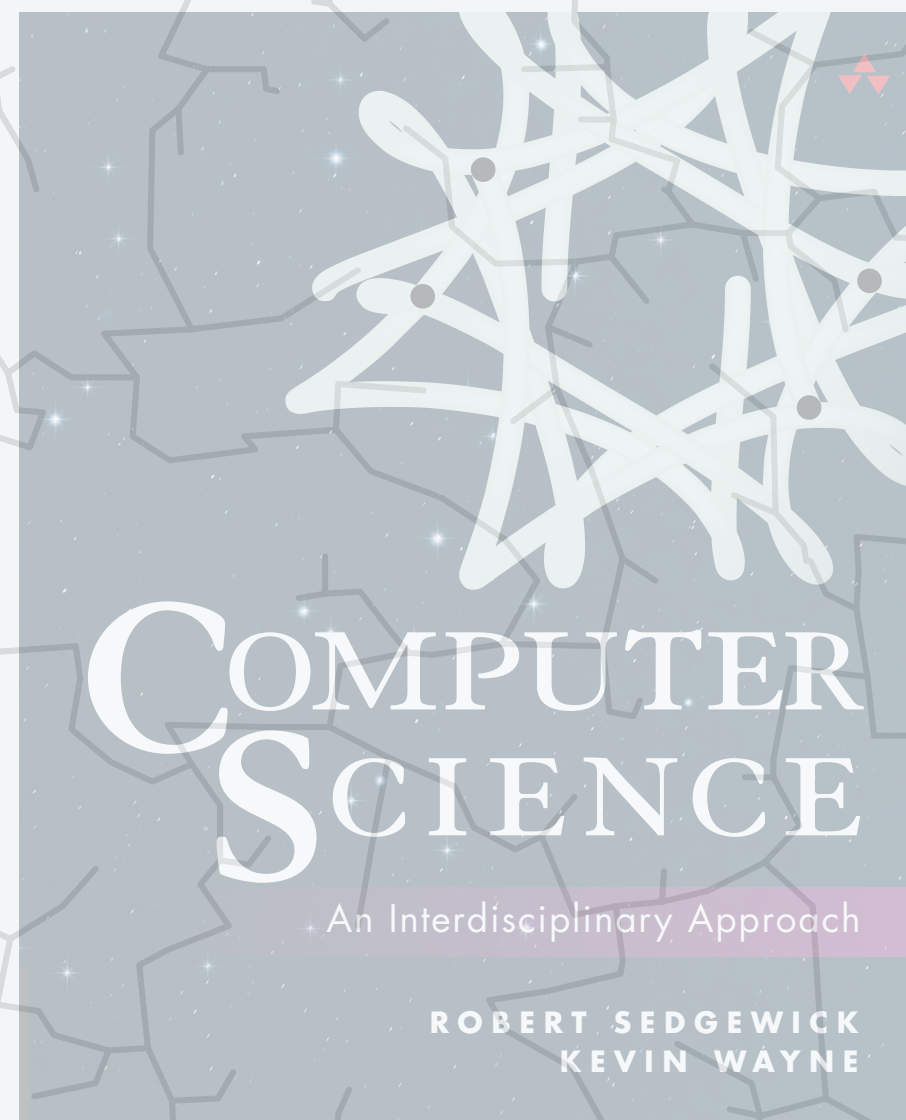4-way generalized AND gate implementation  
(tree of 2-way AND gates, plus NOT gates)



<https://introcs.cs.princeton.edu>

## 7. DIGITAL CIRCUITS

---

- ▶ *boolean algebra*
- ▶ *logic gates*
- ▶ *sum-of-products*
- ▶ *adder circuit*



# Sum-of-products

Sum-of-products. Every boolean function can be represented as a sum of products.

- Products: form an *AND* term for each 1 in truth table.
- Sum: combine the terms with the *OR* function.

also known as  
“disjunctive normal form”

$(x' y z) + (x y' z) + (x y z') + (x y z) = MAJ$

$x$	$y$	$z$	$MAJ$	$x' y z$	$x y' z$	$x y z'$	$x y z$
0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0
0	1	0	0	0	0	0	0
0	1	1	1	1	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	0	1	0	0
1	1	0	1	0	0	1	0
1	1	1	1	0	0	0	1

Expressing MAJ(x, y, z) as a sum of products

# Universality

---

**Def.** A set of operations is **universal** if every boolean function can be expressed using just those operations.

**Proposition.**  $\{AND, OR, NOT\}$  is a universal set of operations.


**Pf.** Sum-of-products construction on previous slide.

**Proposition.**  $\{NAND\}$  is a universal set of operations.

**Pf.**  $\{AND, OR, NOT\}$  can be constructed from  $NAND$ .  $\longleftarrow$  *see precept*

$x$	$y$	$NAND$
0	0	1
0	1	1
1	0	1
1	1	0

NAND

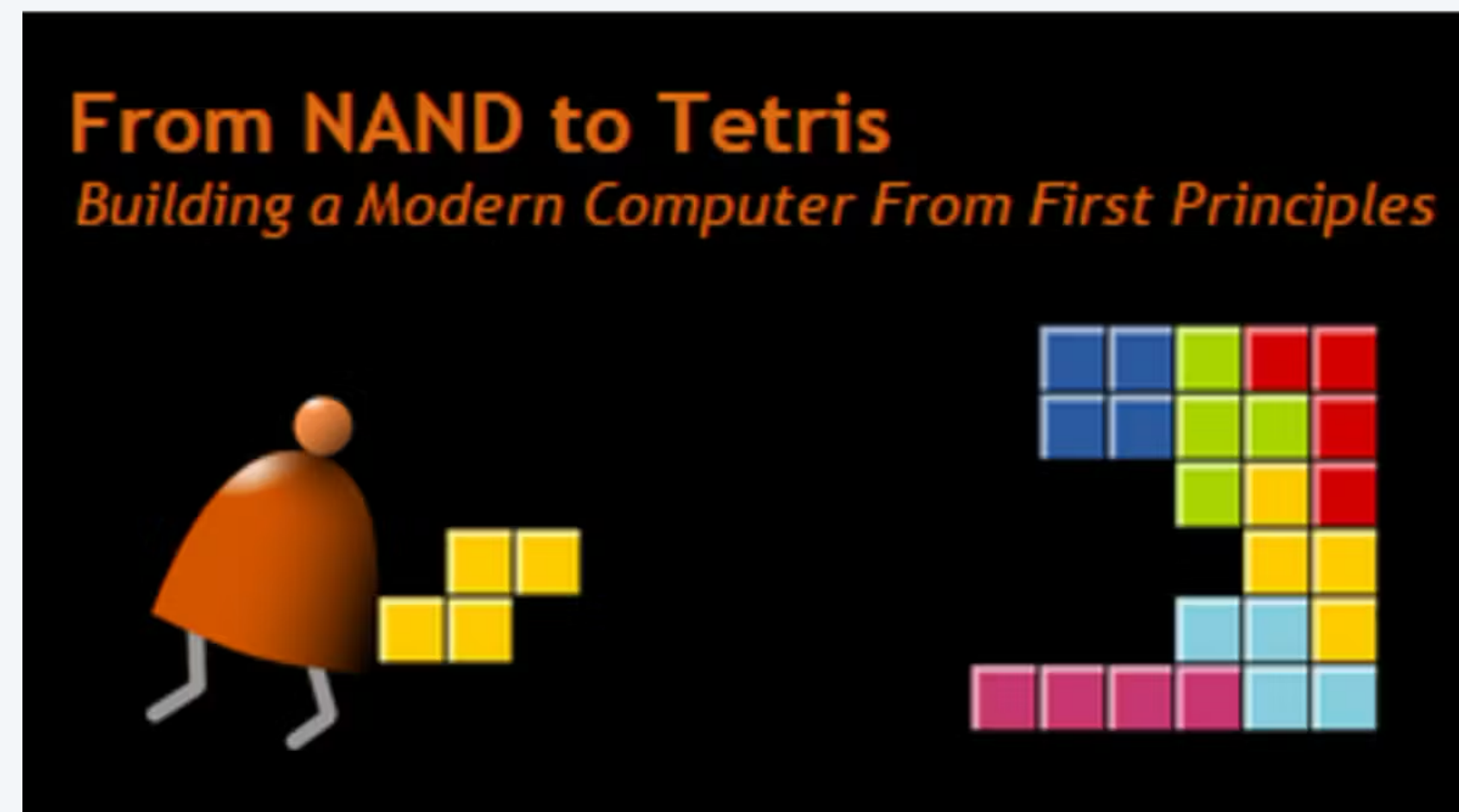

# Majority function


## Sum-of-products construction.

- Identify rows of truth table where the function is 1.
- Use a generalized *AND* gate for each term.
- Combine the terms using an *OR* gate.

### Ex 1. Majority function.

<i>x</i>	<i>y</i>	<i>z</i>	<i>MAJ</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1 ← $x'yz$
1	0	0	0
1	0	1	1 ← $xy'z$
1	1	0	1 ← $xyz'$
1	1	1	1 ← $xyz$
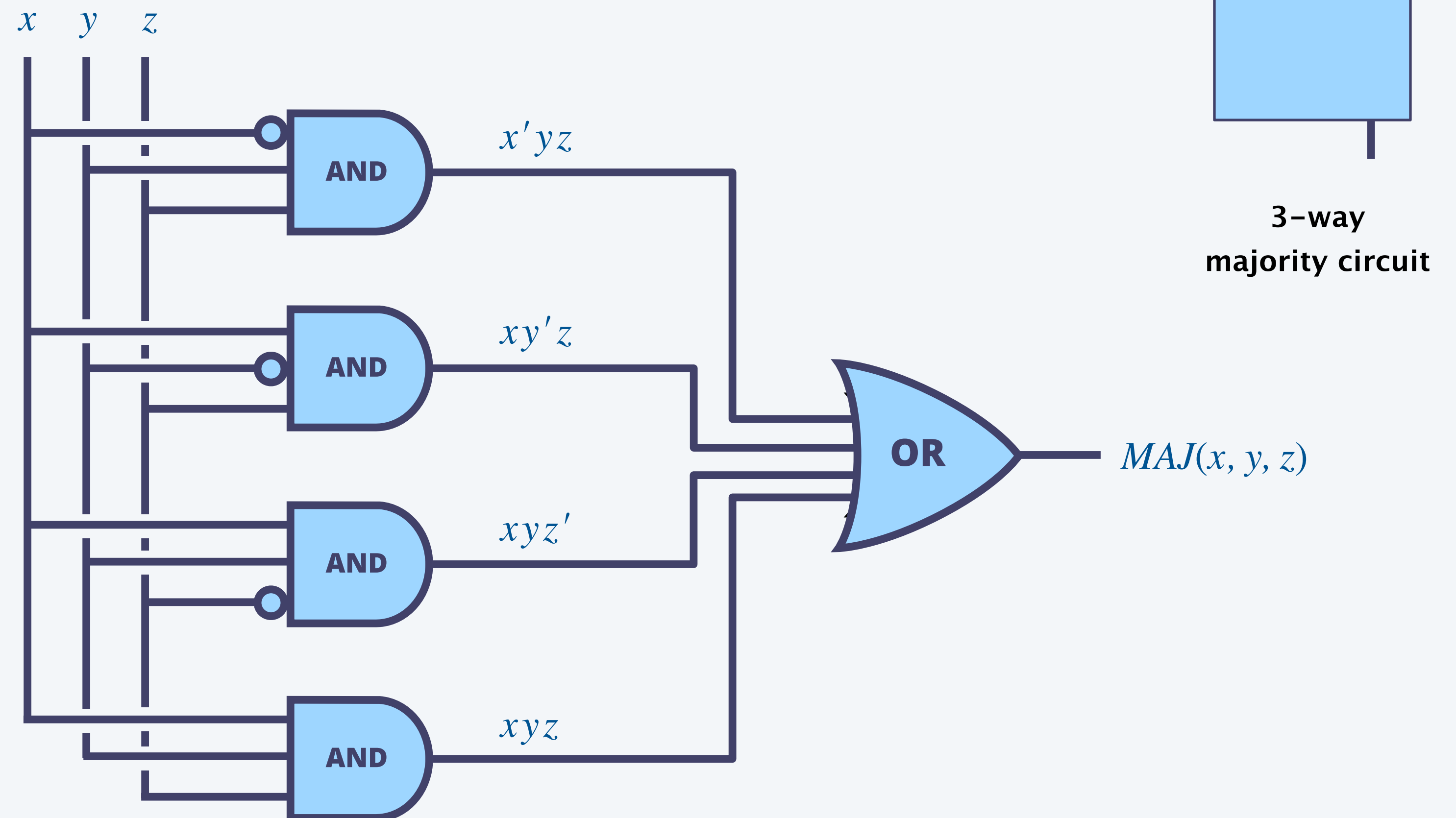
$$MAJ(x, y, z) = x'yz + xy'z + xyz' + xyz$$



# Odd-parity function


## Sum-of-products construction.

- Identify rows of truth table where the function is 1.
- Use a generalized *AND* gate for each term.
- Combine the terms using an *OR* gate.

### Ex 2. Odd-parity function.

<i>x</i>	<i>y</i>	<i>z</i>	<i>ODD</i>
0	0	0	0
0	0	1	1 ← $x'y'z$
0	1	0	1 ← $x'yz'$
0	1	1	0
1	0	0	1 ← $xy'z'$
1	0	1	0
1	1	0	0
1	1	1	1 ← $xyz$
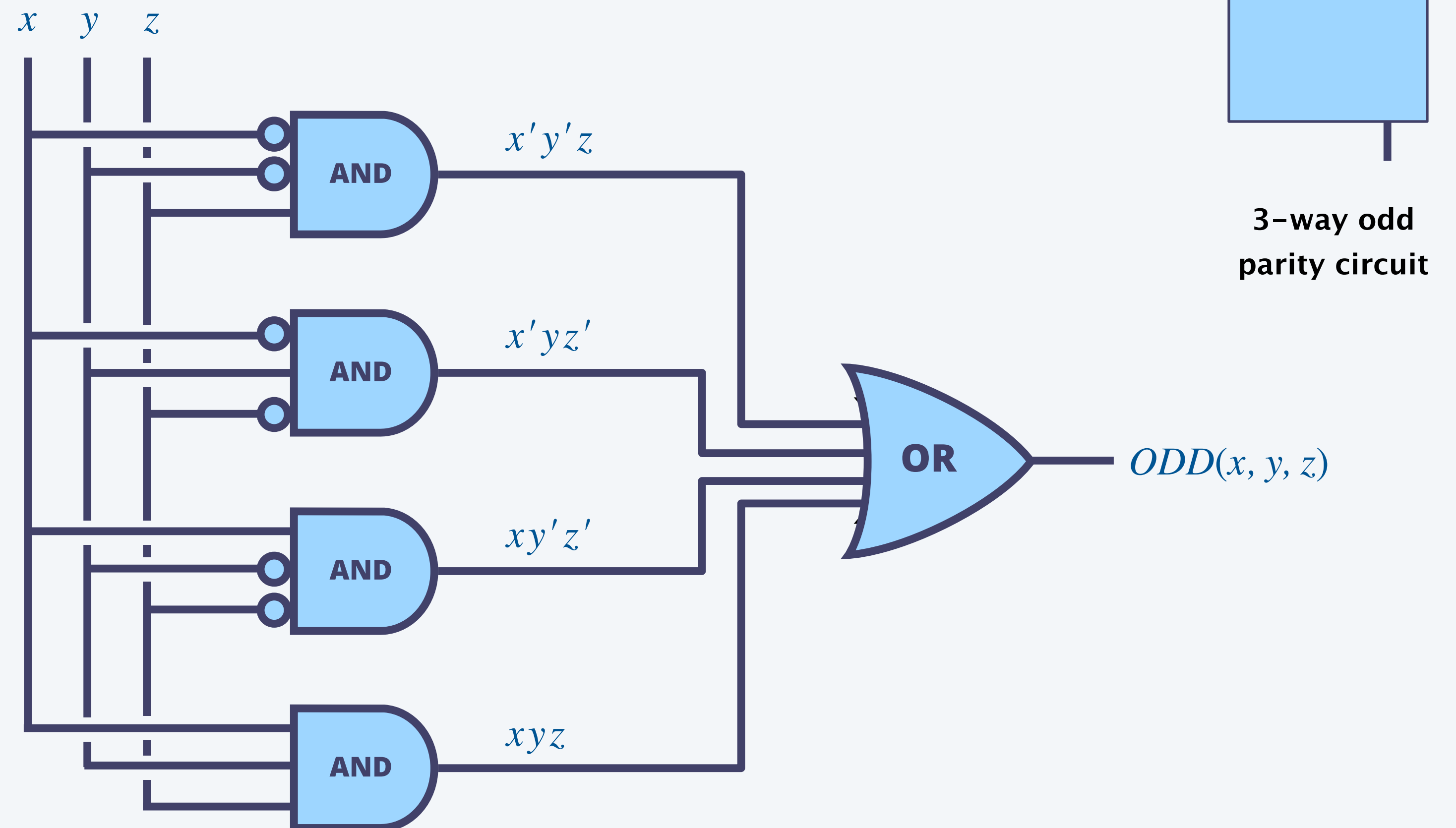
$$ODD(x, y, z) = x'y'z + x'yz' + xy'z' + xyz$$



# Sum-of-products construction (summary)

---

**Goal.** Design a digital circuit that computes a given boolean function.

**Recipe.**

- Step 1: Represent input and output with boolean variables.
- Step 2: Construct truth table to define the function.
- Step 3: Identify rows where the function is 1.
- Step 4: Use a generalized *AND* gate for each row, and *OR* the results.

**Profound consequence.** Can design a digital circuit for **ANY** boolean function.




# Optimized digital circuits

**Caveat.** Sum-of-products construction is **not optimal** in terms of:


- Space = number of gates.
- Time = depth of circuit.

← *this course: we'll ignore such low-level optimization*

**Ex.** Majority function (3-bit).

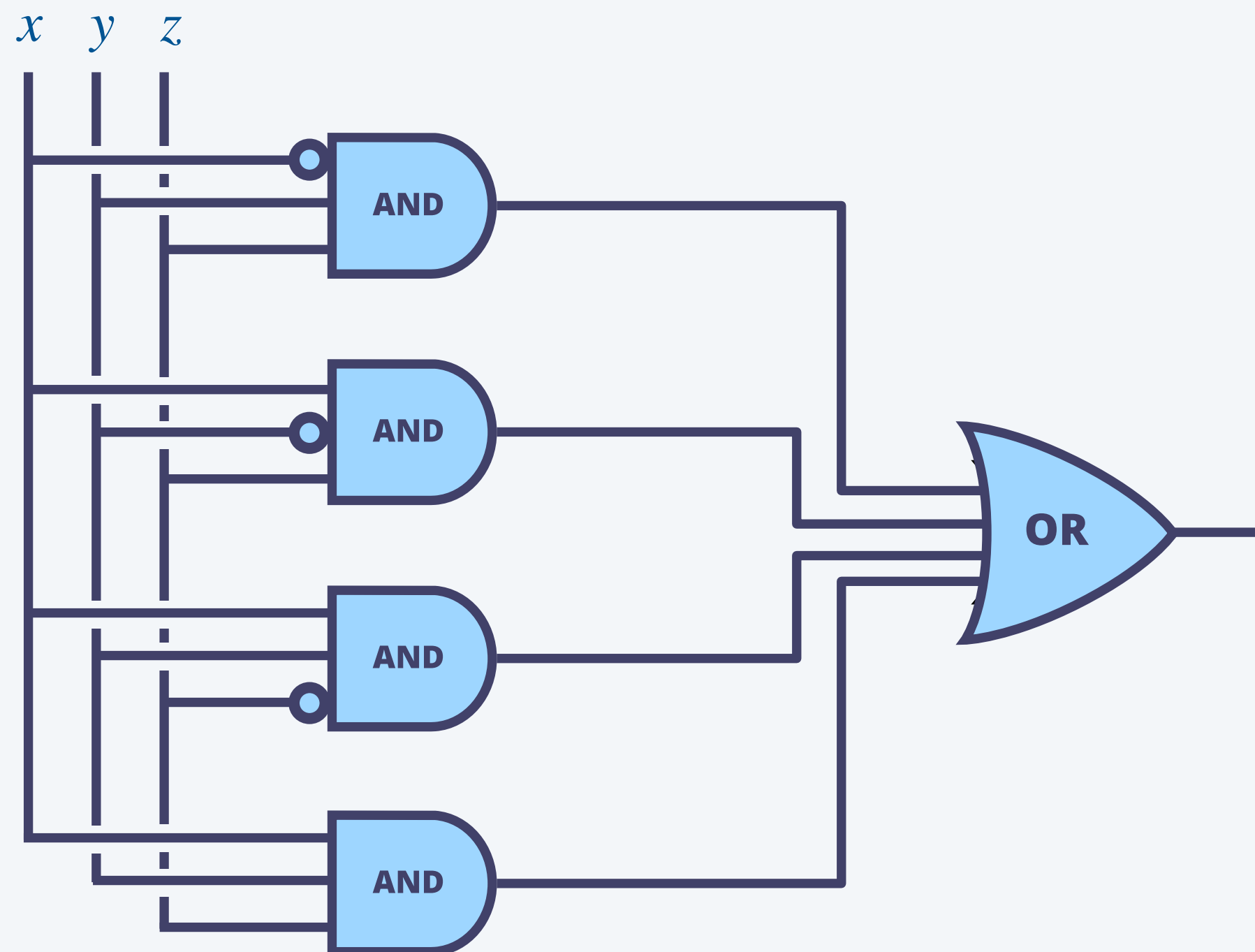

3-way majority circuit (sum-of-products)

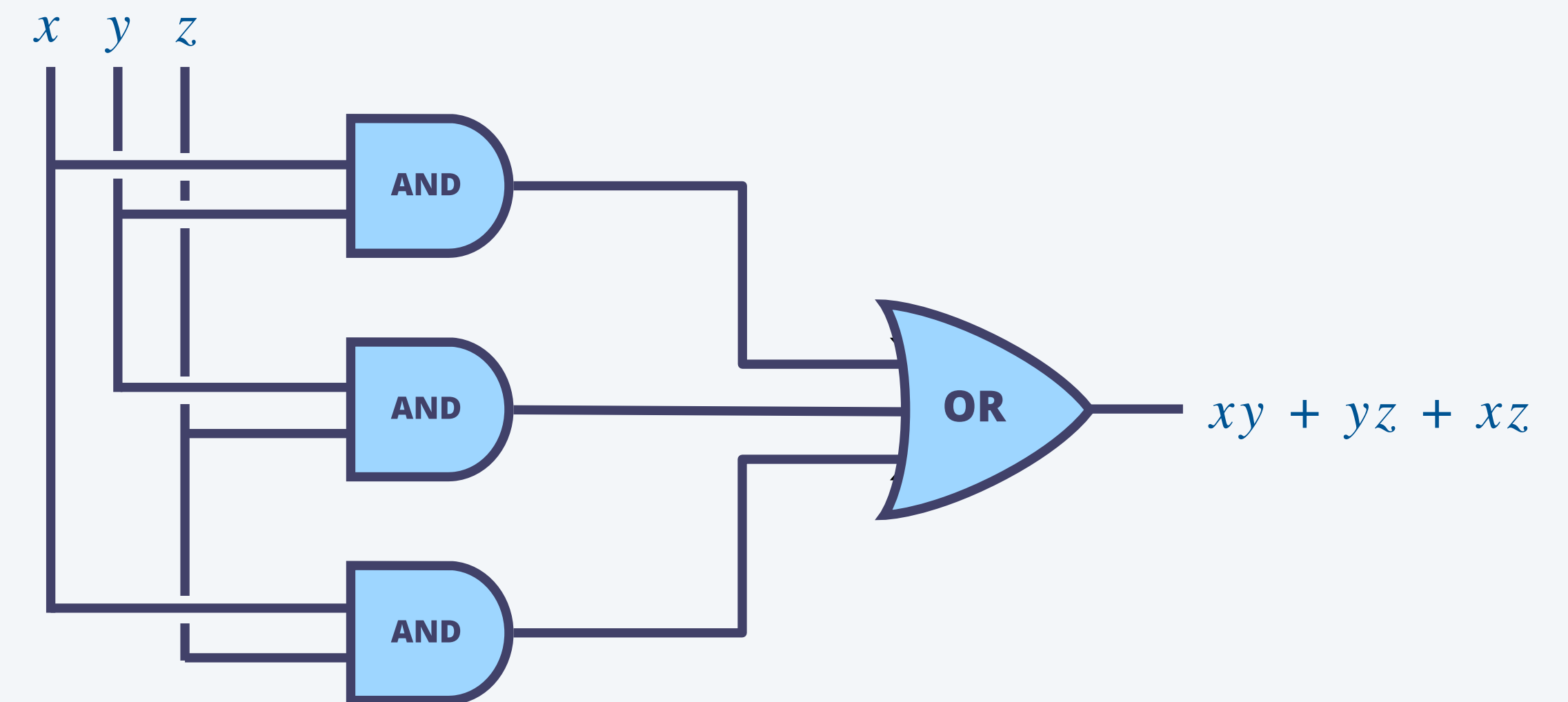

3-way majority circuit (optimized)



How many 3-way generalized AND gates are needed to build the sum-of-products circuit for the following truth table?


A. 1

B. 2

C. 3

D. 4

$x$	$y$	$z$	$EQ$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

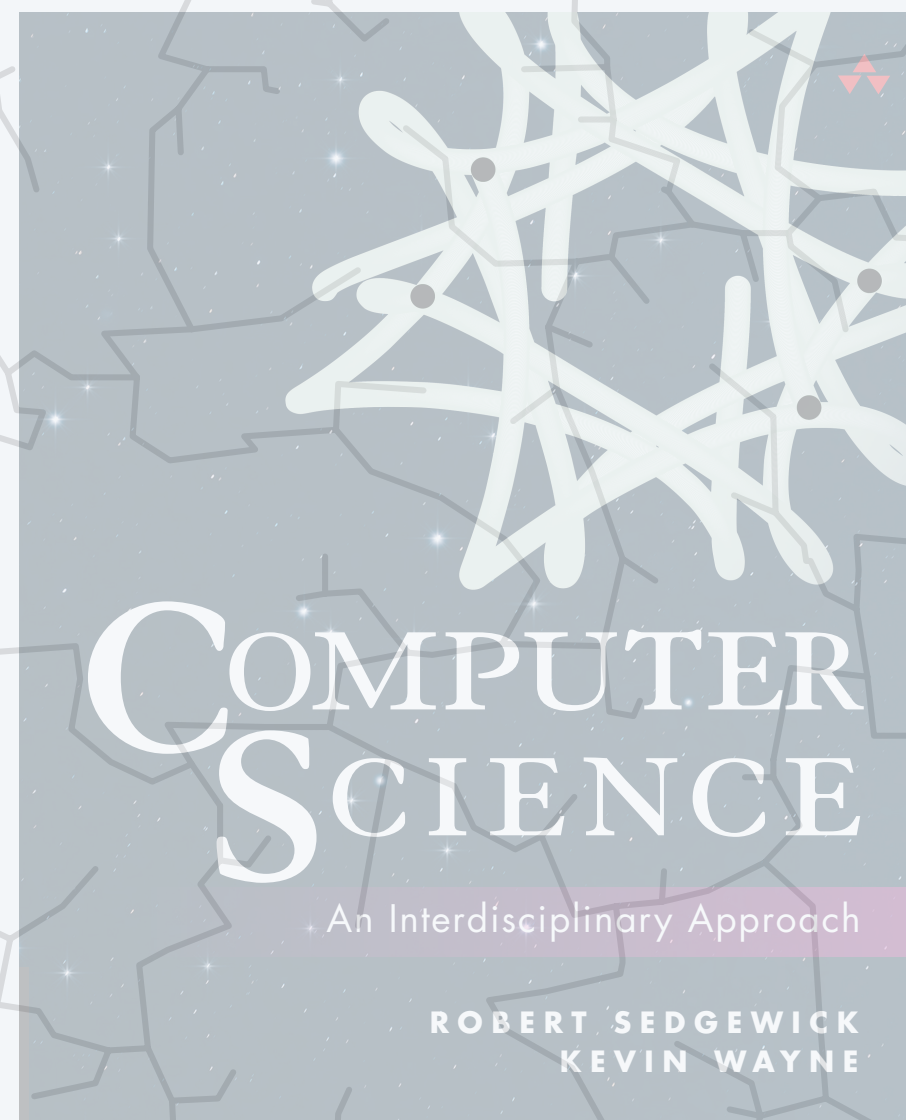

<https://introcs.cs.princeton.edu>

## 7. DIGITAL CIRCUITS

---


- ▶ *boolean algebra*
- ▶ *logic gates*
- ▶ *sum-of-products*
- ▶ *adder circuit*

# Let's make an adder circuit!

**Adder circuit.** Compute  $z = x + y$  for 4-bit binary integers. ← ignore integer overflow  
(as in TOY and Java)

**First step.** Represent inputs and outputs in binary.
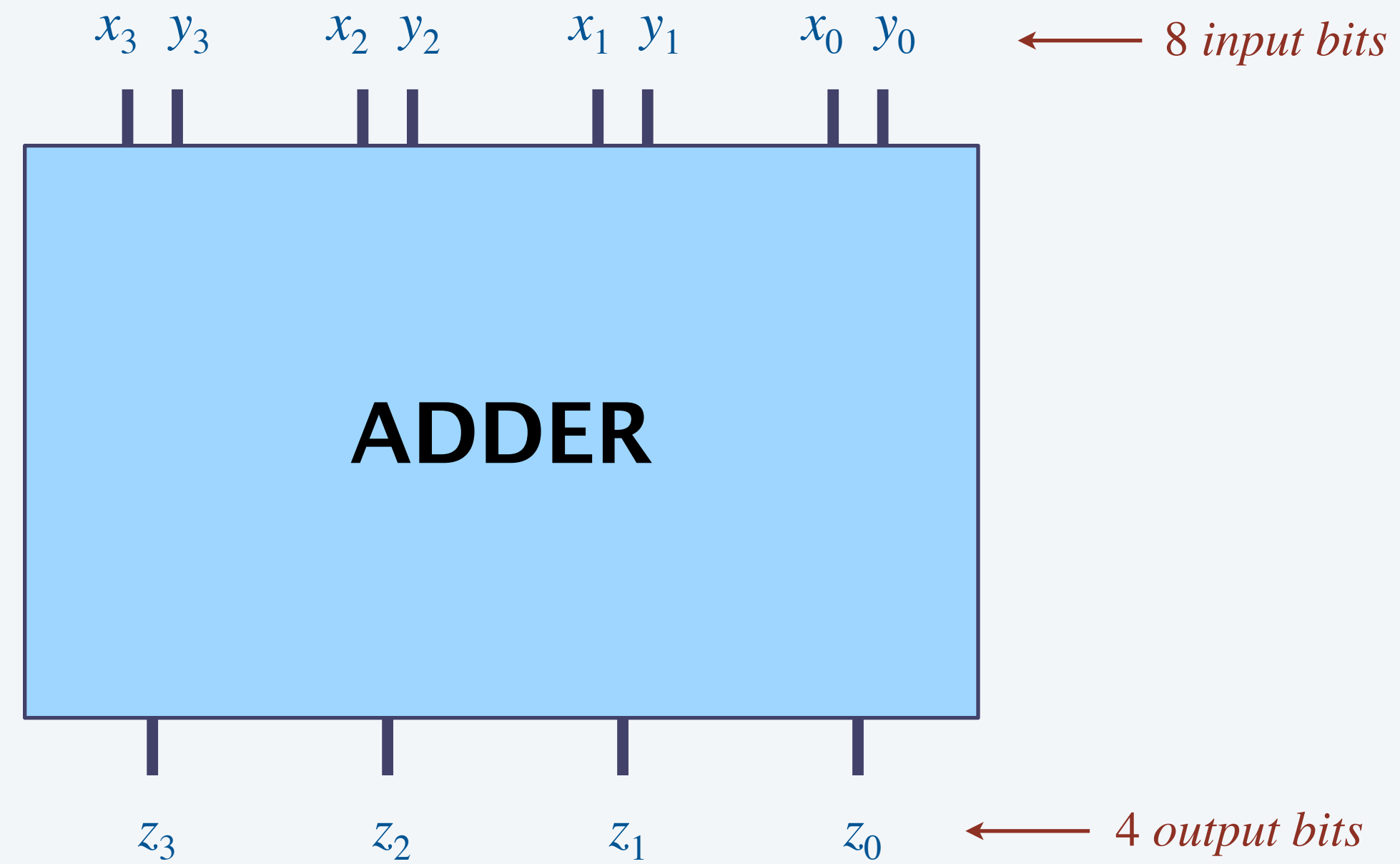
$$\begin{array}{r} x_3 \quad x_2 \quad x_1 \quad x_0 \\ + \quad y_3 \quad y_2 \quad y_1 \quad y_0 \\ \hline z_3 \quad z_2 \quad z_1 \quad z_0 \end{array}$$






# Let's make an adder circuit!

---

**Adder circuit.** Compute  $z = x + y$  for 4-bit binary integers. ← *ignore integer overflow*  
(as in TOY and Java)

**First step.** Represent inputs and outputs in binary.
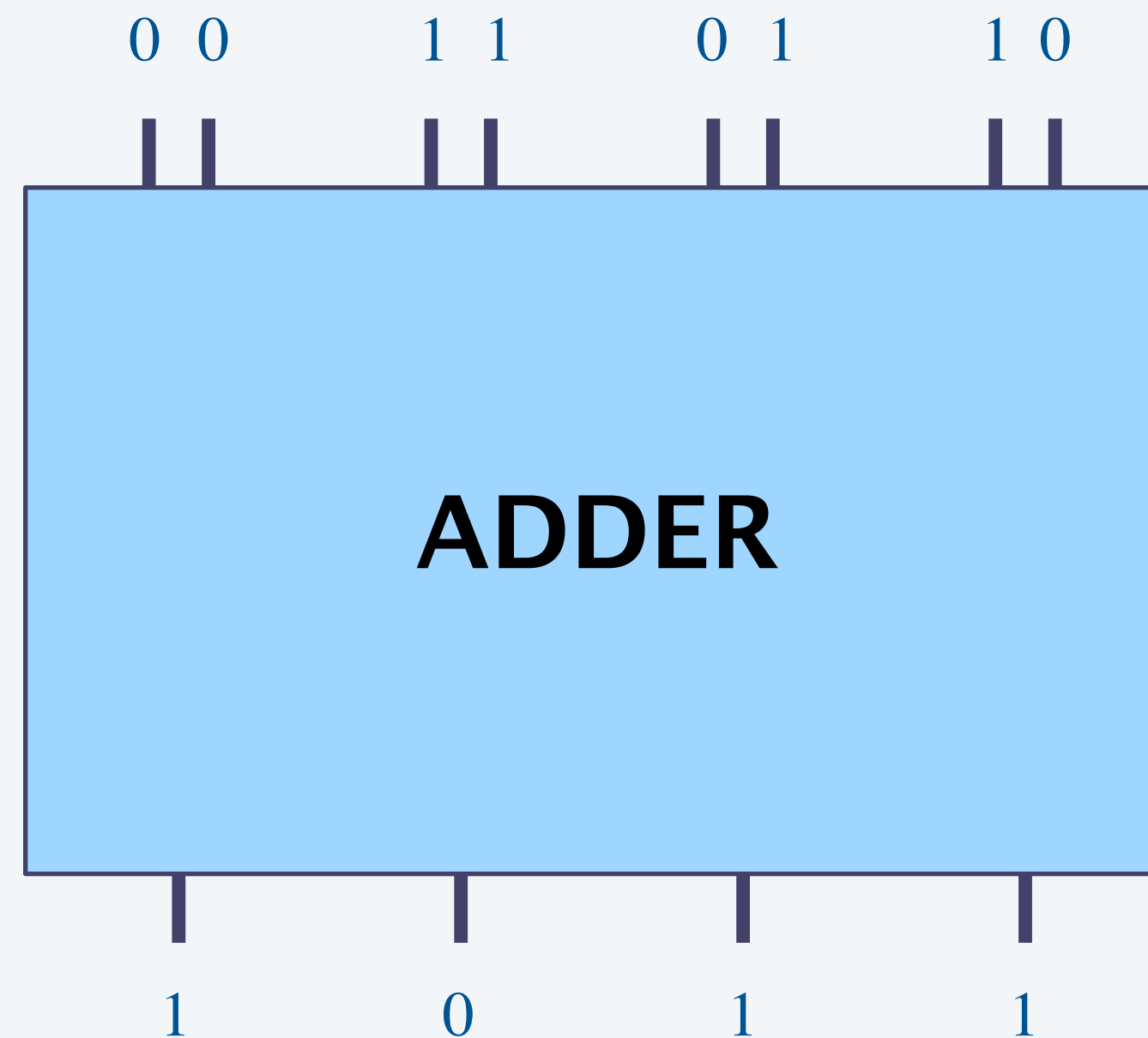
$$\begin{array}{r} 0101 \\ + 0110 \\ \hline 1011 \end{array}$$





# Let's make an adder circuit!

Adder circuit. Compute  $z = x + y$  for 4-bit binary integers.

$c_3$   
 $x_3$   
 $y_3$   
 $z_3$

$c_2$   
 $x_2$   
 $y_2$   
 $z_2$

$c_1$   
 $x_1$   
 $y_1$   
 $z_1$

$c_0$   
 $x_0$   
 $y_0$   
 $z_0$

$+$

$c_0 = 0$

Efficient solution. Do one bit at a time.

- Build truth table for each carry bit. ← 3-bit majority function (!)
- Build truth table for each sum bit.

$x_i$	$y_i$	$c_i$	$c_{i+1}$	$MAJ$
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

truth table for carry bit

$c_{i+1} = MAJ(x_i, y_i, c_i)$

# Let's make an adder circuit!

Adder circuit. Compute  $z = x + y$  for 4-bit binary integers.

$c_3$

$x_3$

$y_3$

$z_3$

$c_2$

$x_2$

$y_2$

$z_2$

$c_1$

$x_1$

$y_1$

$z_1$

$c_0$

$x_0$

$y_0$

$z_0$

$+$

$c_0 = 0$

$\swarrow$

Efficient solution. Do one bit at a time.

- Build truth table for each carry bit ← 3-bit majority function (!)
- Build truth table for each sum bit. ← 3-bit odd-parity function (!)

$x_i$	$y_i$	$c_i$	$z_i$	<i>ODD</i>
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

truth table for sum bit

$z_i = ODD(x_i, y_i, c_i)$

# Let's make an adder circuit!


**Adder circuit.** Compute  $z = x + y$  for 4-bit binary integers.

$$\begin{array}{cccc} & c_3 & c_2 & c_1 & c_0 \leftarrow c_0 = 0 \\ x_3 & x_2 & x_1 & x_0 \\ + & y_3 & y_2 & y_1 & y_0 \\ \hline z_3 & z_2 & z_1 & z_0 \end{array}$$

**Efficient solution.** Do one bit at a time.

- Carry bit is *MAJ*.
- Sum bit is *ODD*.
- Chain 1-bit adders to “ripple” carries.

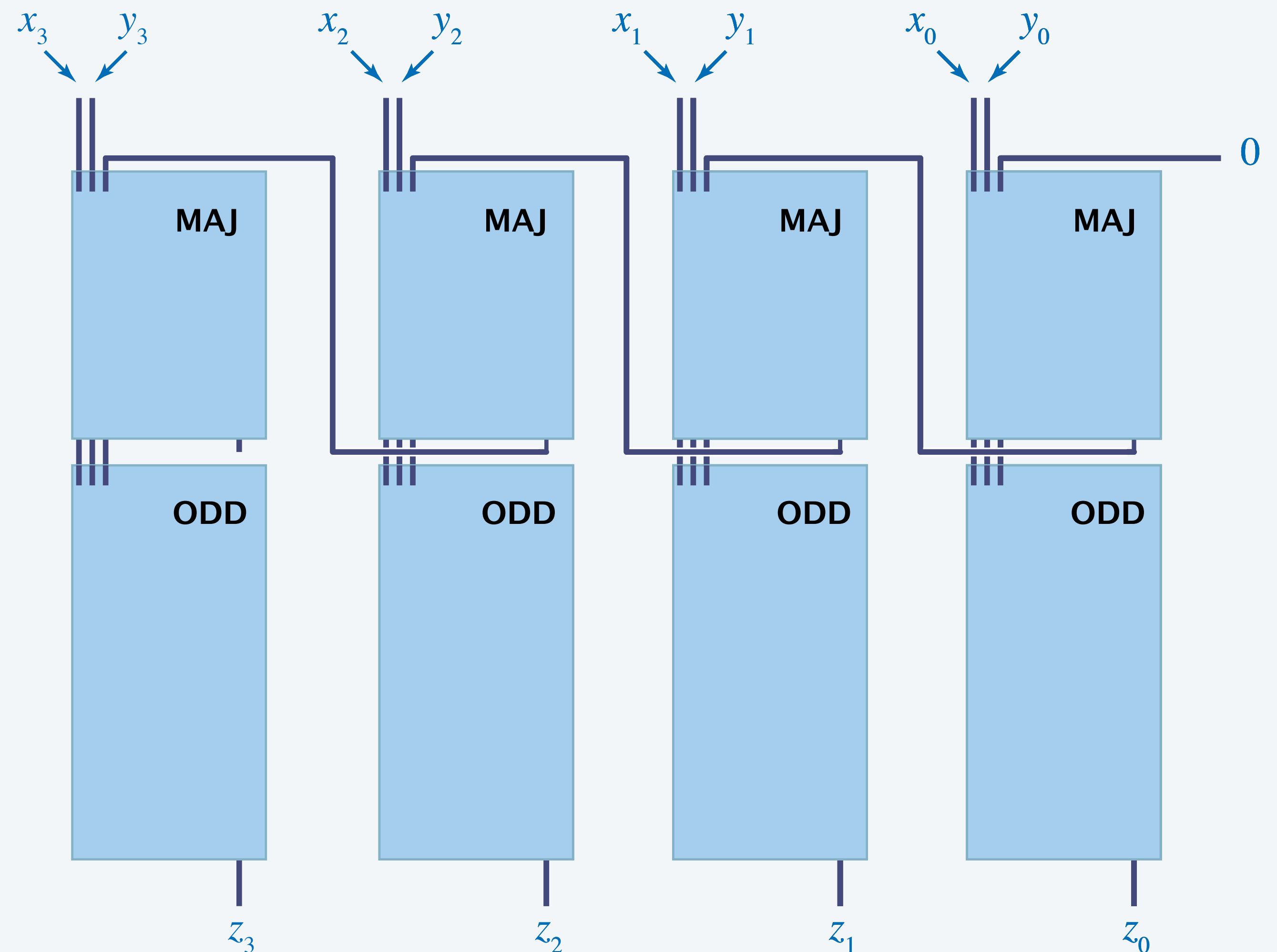**Size of circuit.**  $\Theta(n)$  gates for  $n$ -bit adder.






# Encapsulation

---

Encapsulation in circuit design mirrors familiar software design principle.

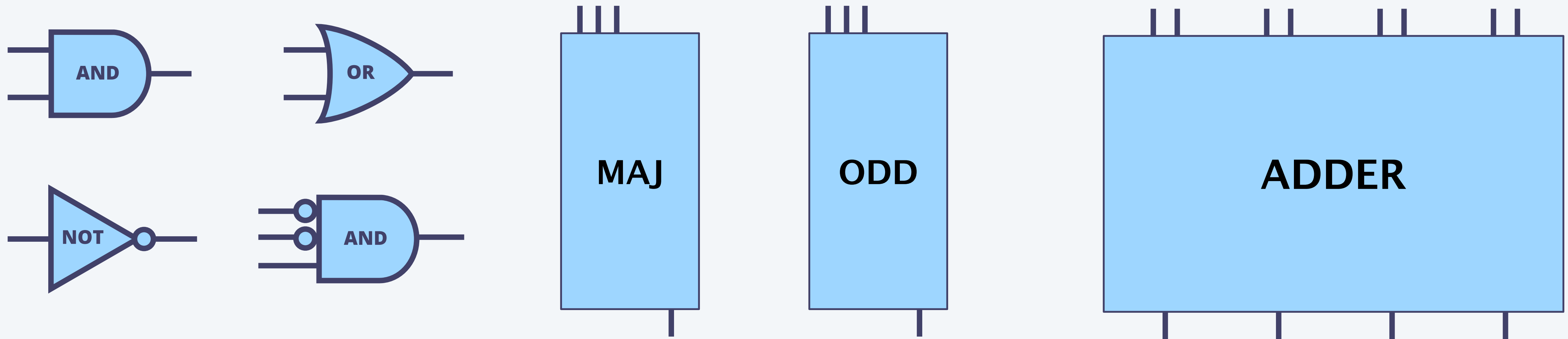- **API** describes behavior (input and outputs) of circuit.
- **Implementation** gives details of how to build it from wires and gates.
- **Client** uses circuit as a black box.




Bottom line. We manage complexity by **encapsulating** circuits.

# Layers of abstraction

Layers of abstraction apply with a vengeance.

- On/off.
- Switch.
- Primitive gates (*AND*, *OR*, *NOT*).
- Composite gates (multiway *AND/OR*, *MAJ*, *ODD*).
- Adder circuit.
- Memory.
- Arithmetic logic unit (ALU).
- Central processing unit (CPU).
- Input and output.
- Your computer.

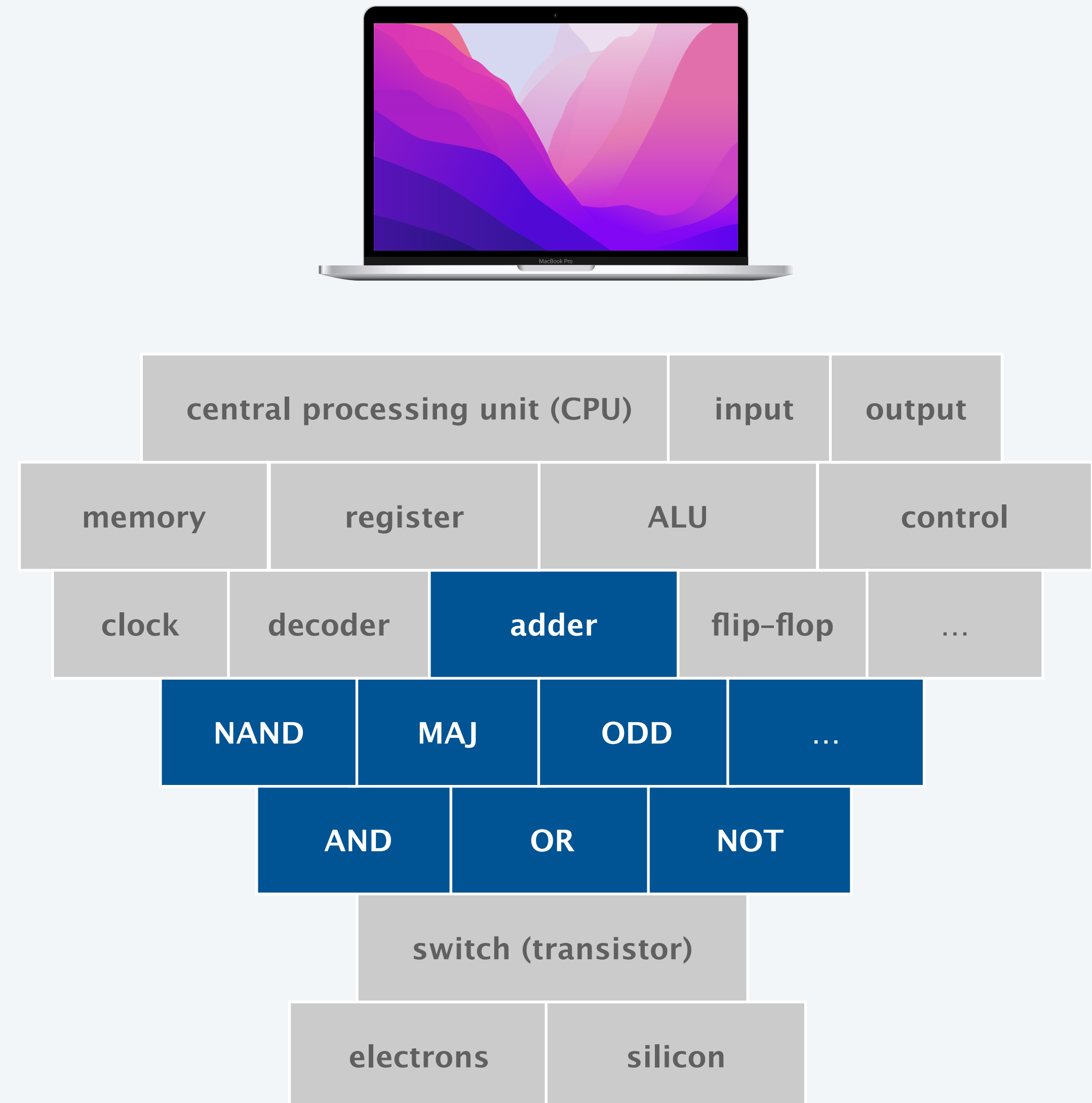Want to learn more? See ECE 206 and ECE 365.



# Credits

Co-instructors, course admin, and graduate student preceptors.

Undergrad graders, precept assistants, and lab TAs.

👉 Apply to be one next semester!

## Senior Staff



Kobi Kaplan



Donna Gabai



Alan Kaplan

## Assistant Instructors



Tanvi Namjoshi



Ruyu Yan



Owen Zhang



Nobline Yoo



Max Gonzalez-Saez



Kylie Zhang



Kathryn Wantlin



Jane Castleman



Beza Desta



Nicholas Alexander  
Sudarsky



Berlin Chen



Abhishek Joshi

## A final thought

---

# Credits

---

image	source	license
<i>Retro Telephone and Smartphone</i>	<u>Adobe Stock</u>	<u>education license</u>
<i>Macbook Pro</i>	<u>Apple</u>	
<i>Samsung Galaxy S23</i>	<u>Samsung</u>	
<i>Xbox One</i>	<u>Microsoft</u>	
<i>Cardiac Pacemaker</i>	<u>Adobe Stock</u>	<u>education license</u>
<i>Apple A16 Bionic Chip</i>	<u>Apple</u>	
<i>Boole is Coole</i>	<u>IrishPhilosophy</u>	<u>CC BY-NC-SA 2.0</u>
<i>Boole Orders Lunch</i>	<u>Sidney Harris</u>	
<i>Trick OR Treat</i>	<u>IFL Science</u>	
<i>From NAND to Tetris</i>	<u>nand2tetris.org</u>	



# Credits

---

image	source	license
<i>Claude Shannon</i>	<u>Lucent Technologies</u>	
<i>Bit Player Theatrical Poster</i>	<u>thebitplayer.com</u>	
<i>John Hutton as Claude Shannon</i>	<u>thebitplayer.com</u>	
<i>Logic Gate Symbols</i>	<u>Adobe Stock</u>	<u>education license</u>
<i>Apple MacBook Pro</i>	<u>Adobe Stock</u>	<u>education license</u>