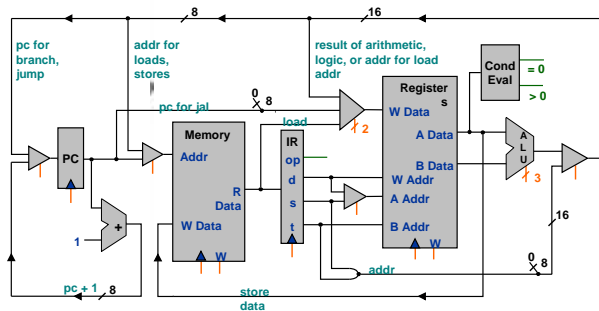


Lecture A5: Building a TOY



The TOY Machine

TOY machine.


- 256 16-bit words of memory.
- 16 16-bit registers.
- 1 8-bit program counter.
- 16 instructions types.

What we've done.

- Written programs for the TOY machine.
- Software implementation of fetch-execute cycle.
TOY simulator.

Our goal today.

 - Hardware implementation of fetch-execute cycle.
TOY computer.



Designing a Processor

How to build a microprocessor?

- ➔ • Develop instruction set architecture (ISA).
 - 16-bit words, 16 TOY machine instructions
- Determine major components.
 - ALU, memory, registers, program counter
- Determine datapath requirements.
 - "flow" of bits
- Establish clocking methodology.
 - 2-cycle design: fetch, execute
- Analyze how to implement each instruction.
 - determine settings of control signals

Instruction Set Architecture

Instruction set architecture (ISA).

- 16-bit words, 256 words of memory, 16 registers.
- Determine set of primitive instructions.
 - too narrow ⇒ cumbersome to program
 - too broad ⇒ cumbersome to build hardware
- TOY machine: 16 instructions.

Instructions	
0:	halt
1:	add
2:	subtract
3:	and
4:	xor
5:	shift left
6:	shift right
7:	load address


Instructions	
8:	load
9:	store
A:	load indirect
B:	store indirect
C:	branch zero
D:	branch positive
E:	jump register
F:	jump and link

Arithmetic Logic Unit

TOY ALU.

- Big combinational circuit. (lecture A2)
- 16-bit bus.
- Add, subtract, and, xor, shift left, shift right, copy input 2.


op	2	1	0
+, -	0	0	0
&	0	0	1
^	0	1	0
<<, >>	0	1	1
input 2	1	0	0

 

6

Main Memory

 TOY main memory: 256 x 16-bit register file.




7

Registers

TOY registers: fancy 16 x 16-bit register file.

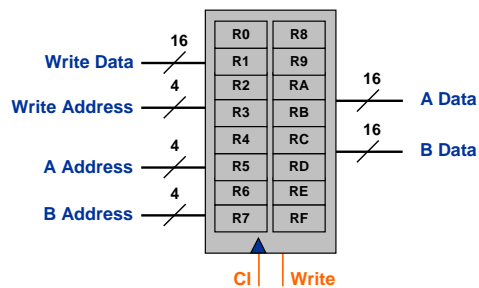- Want to be able to read two registers, and write to a third in the same instructions: $R1 \leftarrow R2 + R3$.
- 3 address inputs, 2 data outputs.
- Add extra bank of muxes for a second read port.



8


Datapath and Control

Datapath.

- Functional units like ALU, memory, plus wires that transfer contents of memory, registers, and PC.
- Must accommodate all instruction types.


Control.

 - Choreographs the "flow" of information on the datapath.
- Depending on instruction, different control wires are turned on.




10

TOY Classic, Back Of Envelope Design

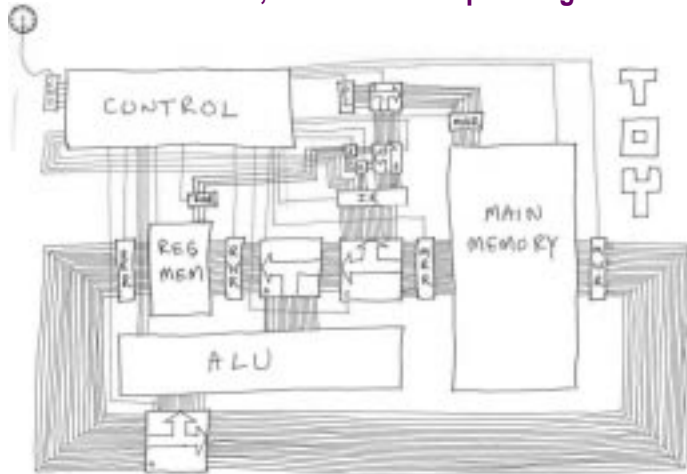


11

The TOY Datapath

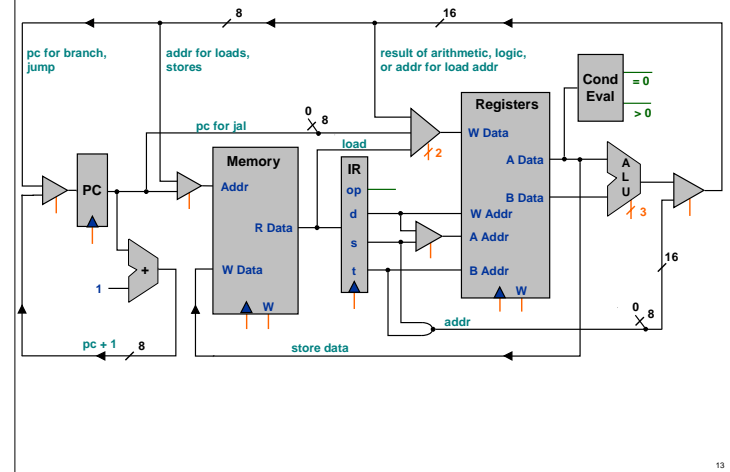

13

The TOY Datapath: Add

 


Before fetch:
pc = 20, mem[20] = 1234

After fetch:
pc = 21
IR = 1234: R[2] ← R[3] + R[4]

14

The TOY Datapath: Add

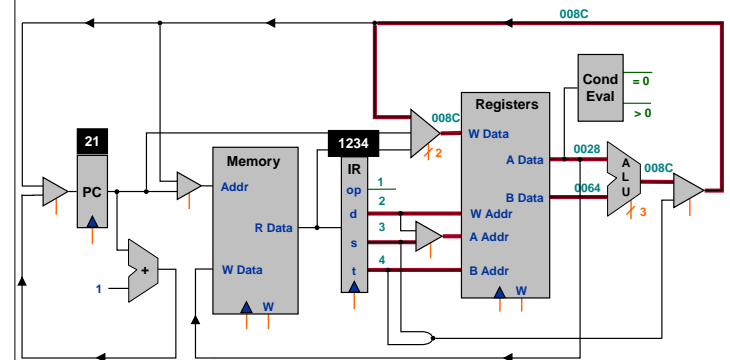


Before execute:
pc = 21
IR = 1234: R[2] ← R[3] + R[4]

After execute:
pc = 21
R[2] = 008C
R[3] = 0028, R[4] = 0064

15


The TOY Datapath: Jump and Link

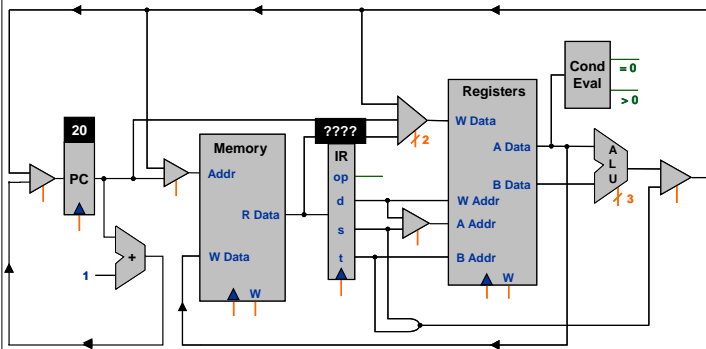

Before fetch:
 pc = 20
 mem[20] = FF30

16

The TOY Datapath: Jump and Link

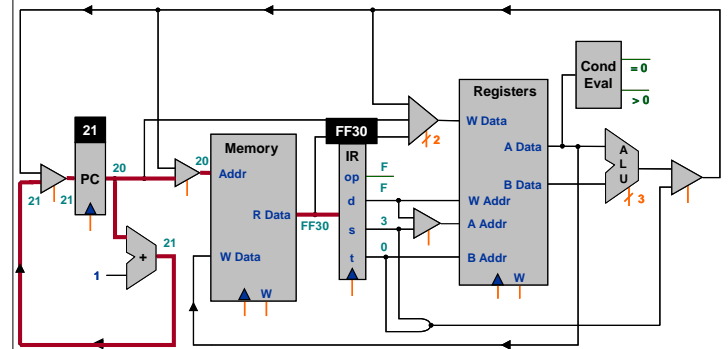


Before fetch:
 pc = 20
 mem[20] = FF30

After fetch:
 pc = 21
 IR = FF30: R[F] ← 21; pc ← 30

17


The TOY Datapath: Jump and Link

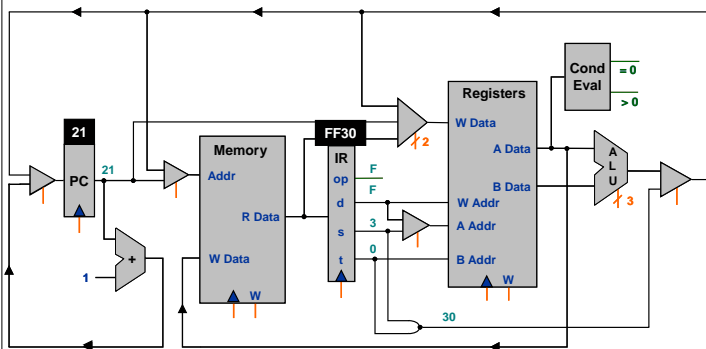

Before execute:
 pc = 21
 IR = FF30: R[F] ← 21; pc ← 30

18

The TOY Datapath: Jump and Link

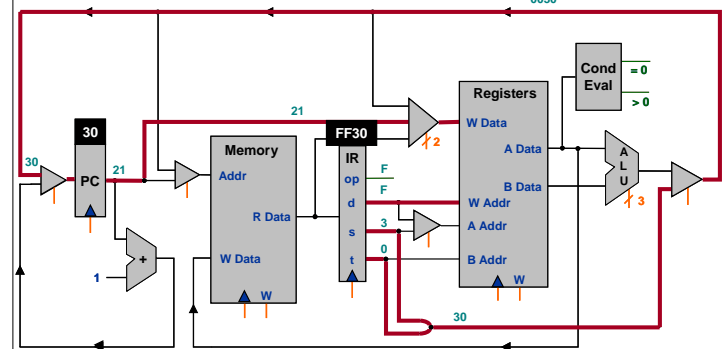

Before execute:
 pc = 21
 IR = FF30: R[F] ← 21; pc ← 30



After execute:
 pc = 30
 R[F] = 21

19

Clocking Methodology

Two cycle design (fetch and execute).

  - Use 1-bit counter to distinguish between 2 cycles.
- Why not just use 1 cycle?




21


Clocking Methodology

4 distinguishable events.

 - During fetch phase.
- During execute phase.
- At very end of execute phase.
- At very end of fetch phase.



 Can only write to register at very end of execute phase.




22

Control


Control: controls components, enables connections.

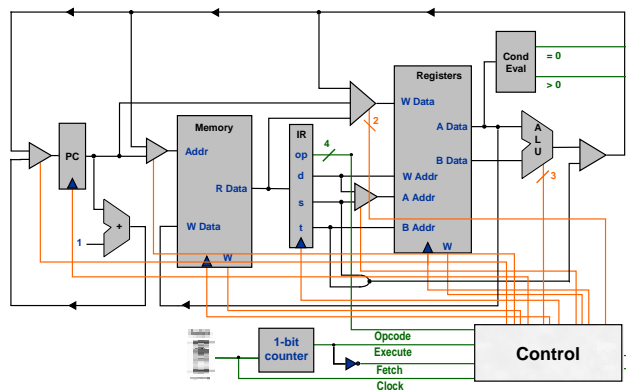- Input: opcode, clock, conditional evaluation. (green)
- Output: control wires. (orange)



25

Implementation of Control

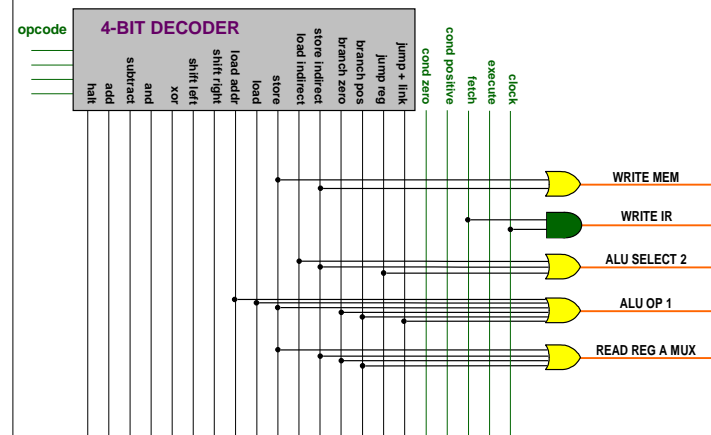


26

Lecture A5: Supplemental Notes



The Big Picture

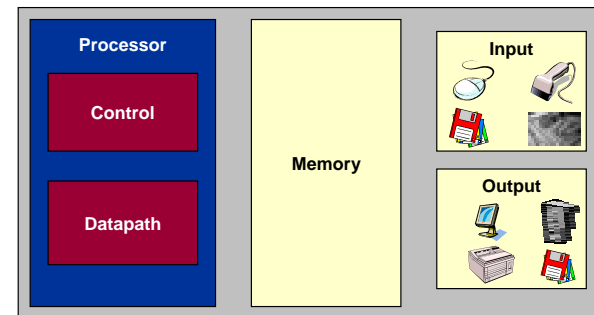The five classic components of a computer in the von Neumann model.



32

Pipelining

Pipelining.

- At any instant, processor is either fetching instructions or executing them (half of circuitry is idle).
- Why not fetch next instruction while current instruction is executing?
 - Analogy: washer / dryer.

Issues.


- Jump and branch instructions change PC.
 - "Prefetch" next instruction.
- Fetch and execute cycles may need to access same memory.
 - Solution: use two memory "caches".

Result.

- Better utilization of hardware.
- Can double speed of processor.

33

Memory Control

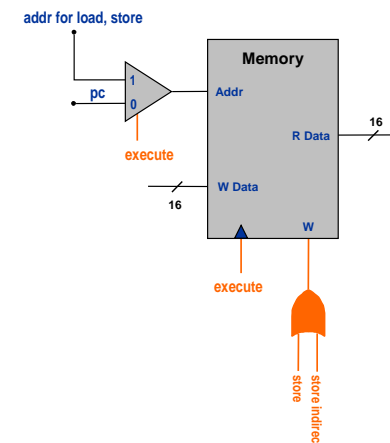

34

Register Control

