


# **How circuits acquire memory: Sequential & Clocked Circuits.**

COS 116, Spring 2011

Sanjeev Arora

# Midterm


Midterm exam scores

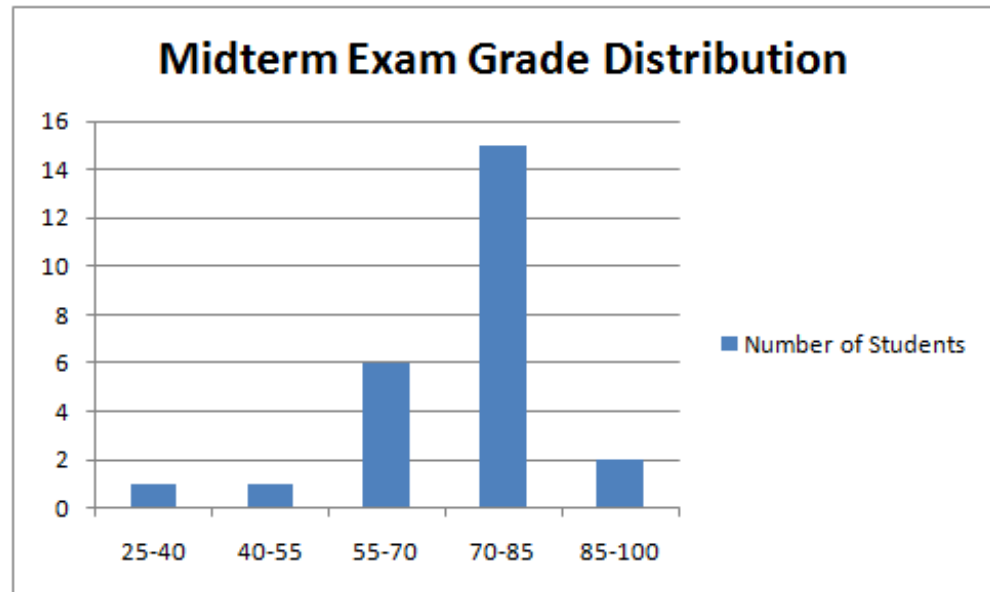


Formula for overall grade:

50% exam + 25% HW + labs, 25% participation


# Recap: Combinational Circuits

 

 Wires: transmit voltage  
(and hence value)




 
← Crossed wires that are not connected  
are sometimes drawn like this.



No loops allowed (direct or  
indirect)

# Timing Diagram

**NOT gate**

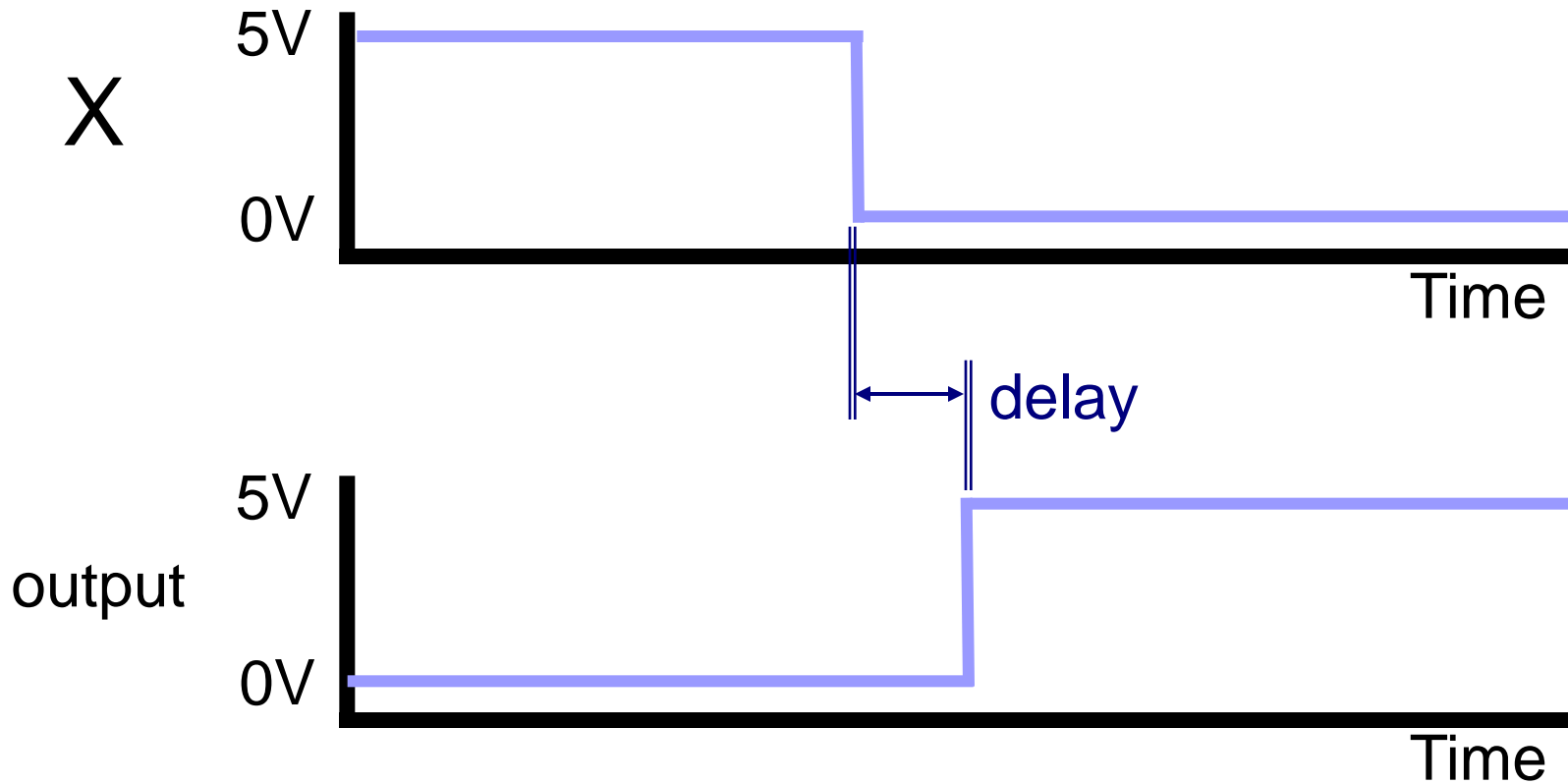 

# Recap: Combinational circuit for binary addition?

$$\begin{array}{r} 25 \qquad 11001 \\ +29 \qquad 11101 \\ \hline 54 \qquad 110110 \end{array}$$

- Want to design a circuit to add any two  $N$ -bit integers (say  $N = 64$ ).

Is the truth table method useful? Ideas?

# Modular design


Have small number  
of basic components.

Put them together to achieve  
desired functionality

Basic principle of modern industrial design;  
recurring theme in next few lectures.



# 1-bit adder

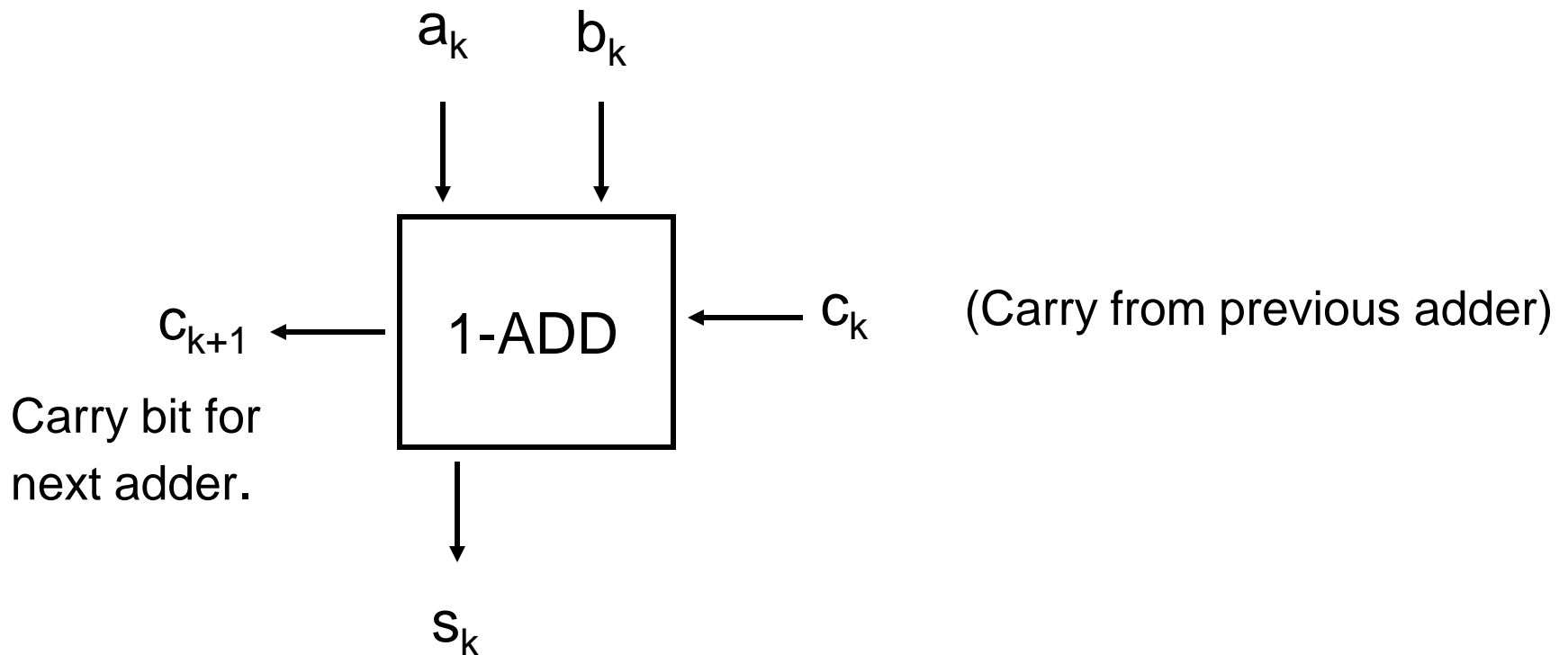

Hand in on Mar 22: Truth table, circuit for 1-bit adder.




# Modular Design for boolean circuits

An N-bit adder using N 1-bit adders  
(will do Mar 22)




# A Full Adder (from handout)

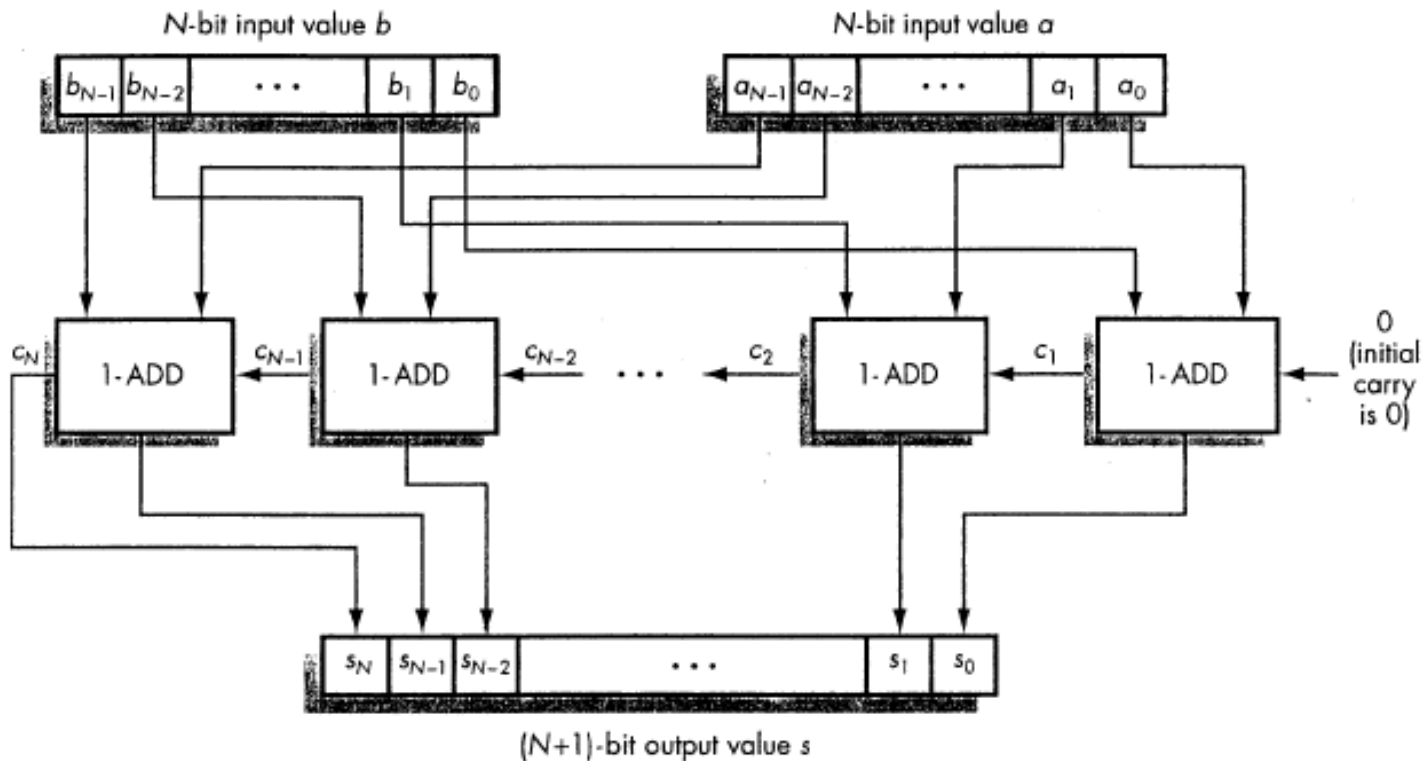


 
# Memory

Rest of this lecture:  
How boolean circuits can have “memory”.



# What do you understand by ‘memory’?”?




How can you tell that a 1-year old child has it?

Behaviorist' s answer:  
His/her actions depend upon past events.




# Why combinational circuits have no “memory”

- Boolean gates connected by wires

 

Wires: transmit voltage  
(and hence value)

- Important: no loops allowed

 


Output is determined by current inputs;  
no “memory” of past values of the inputs.

Today: Circuits with loops; aka “Sequential Circuits”
 
# Matt likes Sue but he doesn't like changing his mind

- Represent with a circuit:  
Matt will go to the party if Sue goes or if he already wanted to go





Is this well-defined?

# Sequential Circuits

- Circuits with AND, OR and NOT gates.
- Cycles **are** allowed (ie outputs can feed back into inputs)
- Can exhibit “memory”.
- Sometimes may have “undefined” values
- How to write the “truth table”? **Suggestions?**
  
# Enter Rita



- Matt will go to the party if Sue goes OR if the following holds: if Rita does not go *and* he already wanted to go.



R, S: “**control**”  
inputs

What combination of  
R, S changes M?


# R-S Latch

  

- M becomes 1 if Set is turned on
- M becomes 0 if Reset is turned on
- Otherwise (if both are 0), M just remembers its value



# A more convenient form of memory

 


No  
“undefined”  
outputs ever!

- If  $\text{Write} = 0$ ,  $M$  just keeps its value. (It ignores  $D$ .)
- If  $\text{Write} = 1$ , then  $M$  becomes set to  $D$

Fact: “Data Flip-Flop” or “D flip flop”;  
can be implemented using two R-S flip flops.

# “Register” with 4 bits of memory

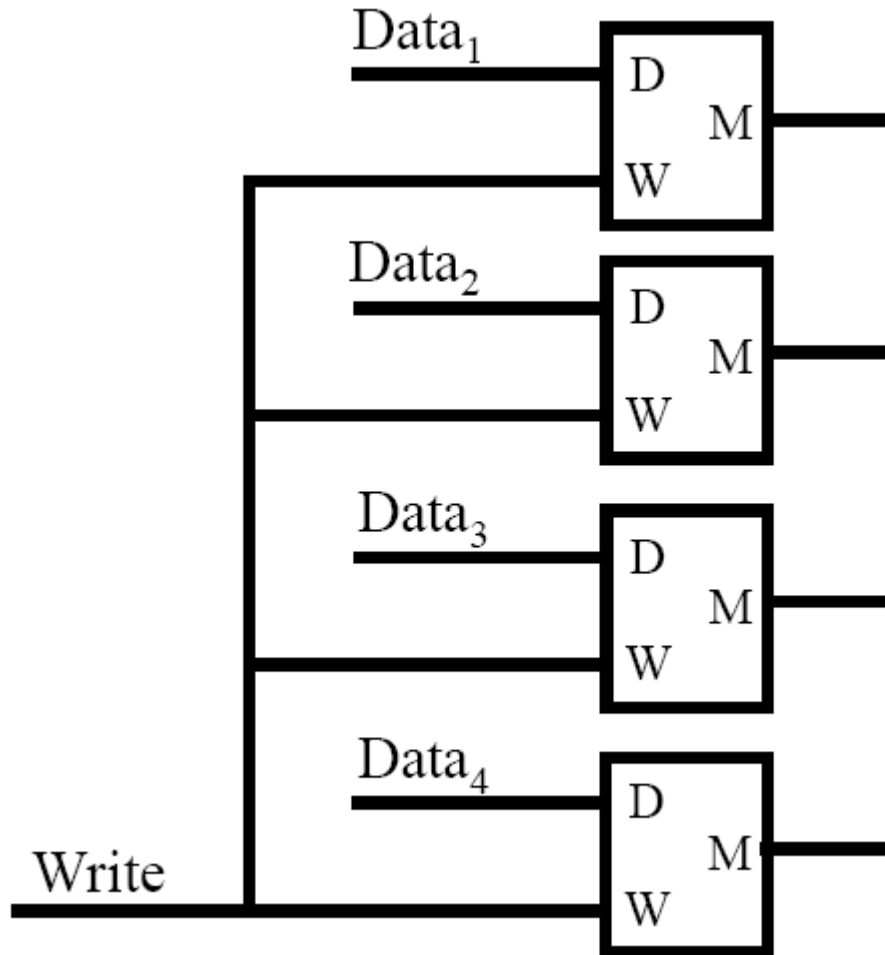

# What controls the “Write” signal?

- Often, the system clock!
- “clock” = device that sends out a fluctuating voltage signal that looks like this




“Computer speed” often refers to the clock frequency (e.g. 2.4GHz)

# The “symphony” inside a computer



Clock

 

Memory

Combinational  
circuit

Clocked  
Sequential  
Circuit  
(aka  
Synchronous  
Circuits)

# Timing diagram

(analog of truth table for sequential circuits)

R	S	M(t)	M(t+1)
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	




Fill in timing diagram for RS latch and hand in on a piece of paper.




# Clocked Sequential Circuits

# Synchronous Sequential Circuit

(aka Clocked Sequential Circuit)

 

# Shorthand

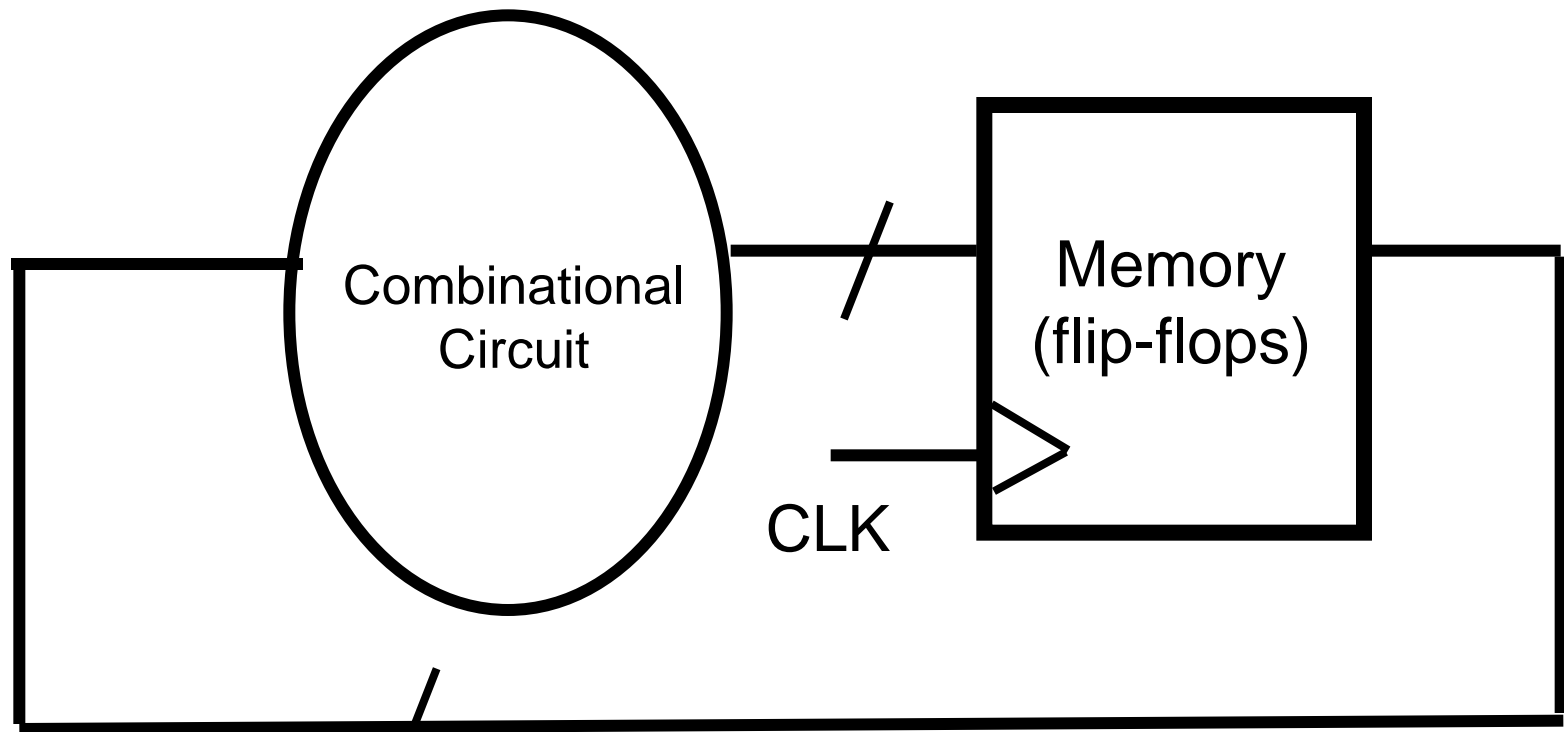

This stands for "lots of wires"  
(aka "bus")




# Clock Speeds



Heinrich Hertz  
1857-94

1974	Intel 8080	2 MHz (Mega = Million)
1981	Original IBM PC	4.77 MHz
1993	Intel Pentium	66 MHz
2005	Pentium 4	3.4 GHz (Giga = Billion)

# What limits clock speed?

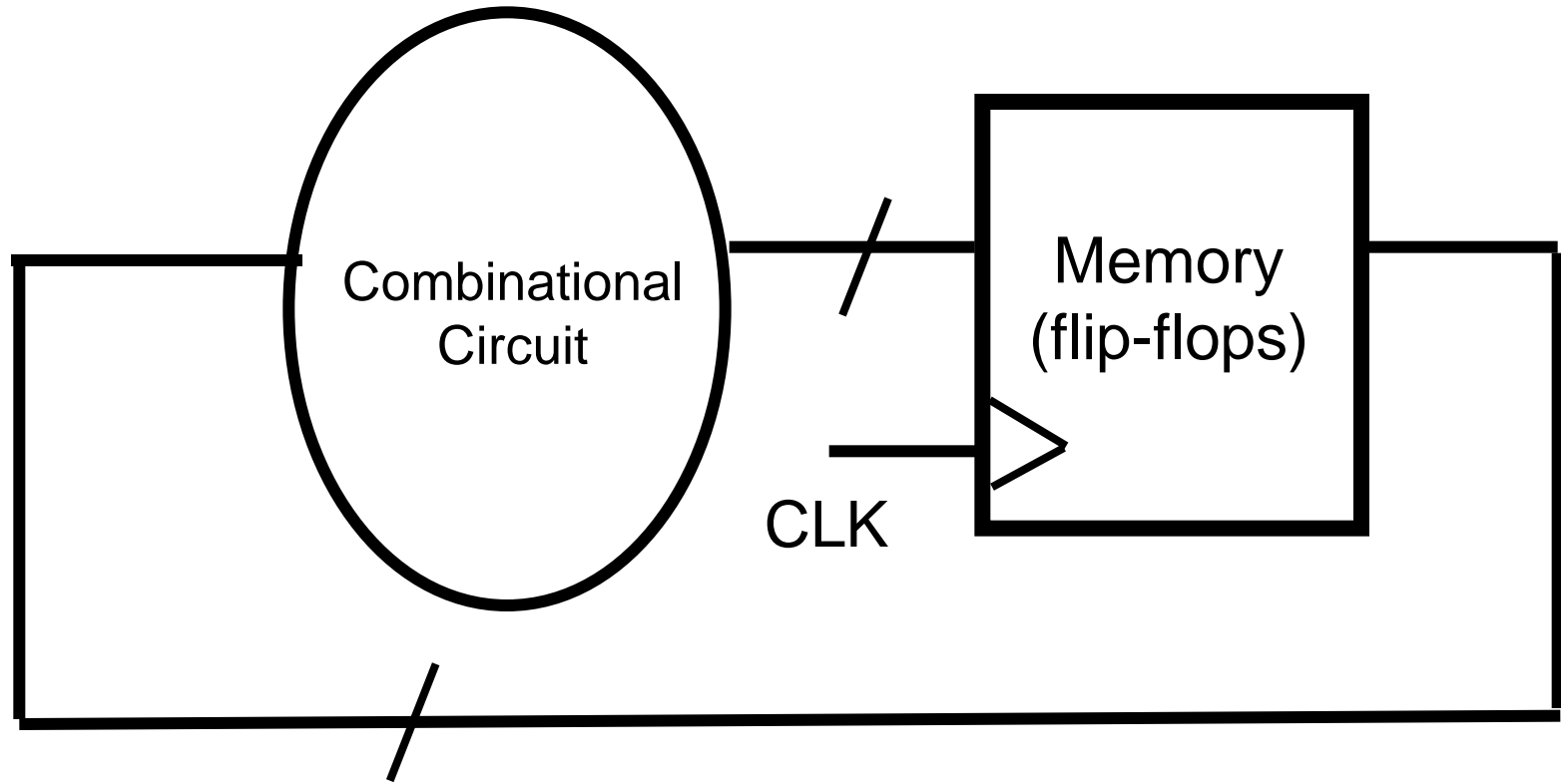

Delays in combinational logic (remember the adder).

Clock cycle = time needed for circuit value to settle.


During 1 clock cycle of Pentium 4, light travels: **4 inches**



# Finite State Machines

Read handout (Brian Hayes article) for next time.
 
# Example: State diagram for automatic door



*Finite # of "states";  
Transition rules  
between states*



# Next lectures...

- FSMs
- Computer organization: CPUs and RAM
- Lessons from computer architecture.