



Finite State Machines (FSMs) and RAMs and CPUs



**COS 116, Spring 2011
Sanjeev Arora**



Recap

- Combinational logic circuits: no cycles, hence no “memory”
- Sequential circuits: cycles allowed; can have memory as well as “undefined”/ambiguous behavior
- Clocked sequential circuits: Contain D flip flops whose “Write” input is controlled by a clock signal

Recap: R-S Latch

  


- M becomes 1 if Set is turned on
- M becomes 0 if Reset is turned on
- Otherwise (if both are 0), M just remembers its value

Forbidden to turn on both Set and Reset simultaneously (value is “ambiguous”)





Recap: D Flip Flop

Basic Memory Block – stores 1 bit.

 


If we “toggle” the write input (setting it 1 then setting it 0) then M acquires the value of D.

“Timing Diagram”

 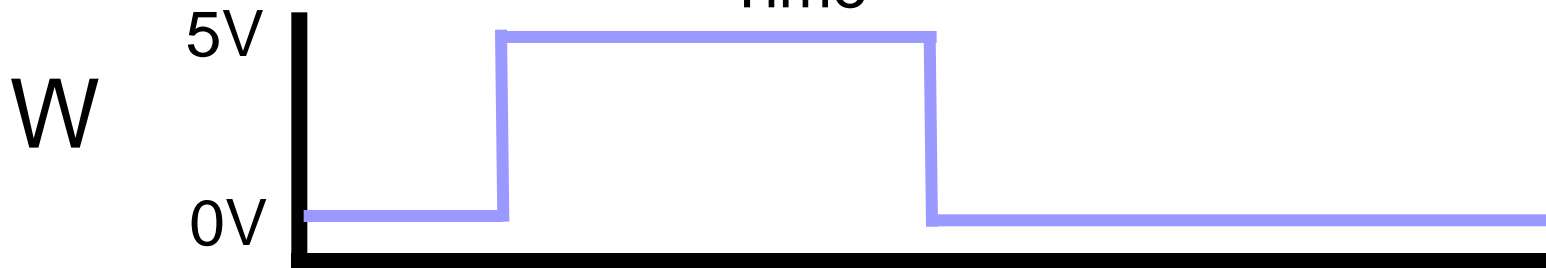  


Output appears when W becomes 0 again.

Finite State Machines (FSMs)

 

- Finite number of states
- Machine can produce outputs, these depend upon current state only (“Moore machine;” see Hayes article)
- Machine can accept one or more bits of input; reading these causes transitions among states.

 Implementing door FSM as synchronous circuit



INPUT


0 = No Person Detected
1 = Person Detected

STATE


0 = Door Closed
1 = Open

Input	Present State	Next State
0	0	0
1	0	1
0	1	0
1	1	1

Implementation of door FSM (contd)

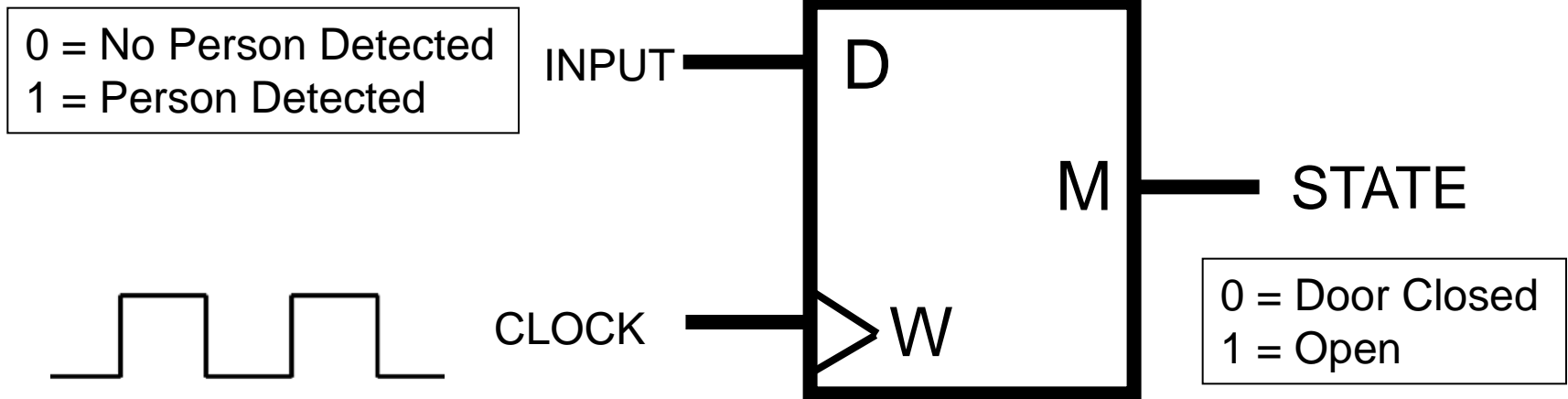

Implementation: General Schematic

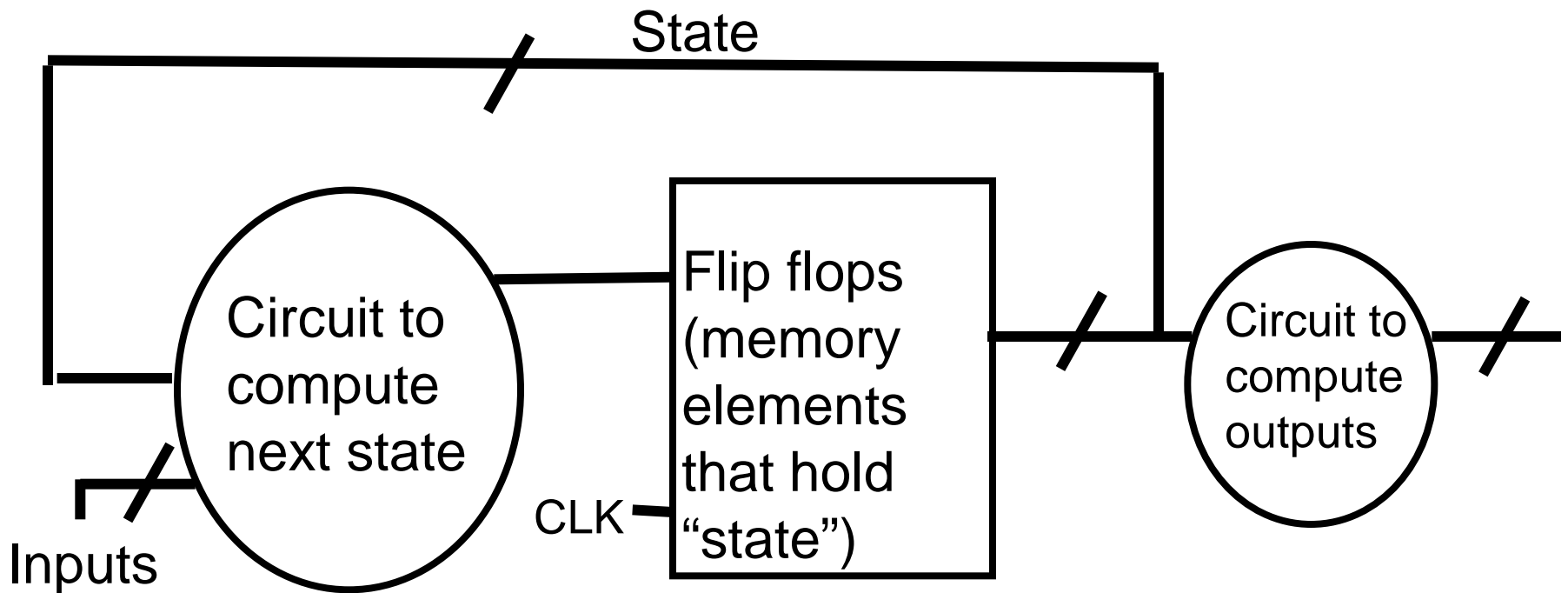

K Flip flops allow FSM to have 2^K states



Discussion Time

Example: 4-state machine; 1 bit of input; 1 bit of output

State variables: P, Q

Input variable: D

Next value of P = $(P + Q) \cdot D$

Next value of Q = P

Output = $P \cdot Q$

What is its state diagram? How can it be implemented as a clocked synchronous circuit?

Divide in groups of 3 and hand this in.


How to implement a FSM?

- If number of states = 2^k then represent “state” by k boolean variables.
- Identify number of input variables
- Write truth table expressing how “next state” is determined from “current state” and current values of the input. Convert to boolean circuit.
- Express as clocked synchronous circuit.

How an FSM does “reasoning”



 “If left infrared sensor detects an object, turn left”



Output goes to motor that turns the wheel


Next....

Random Access Memory (RAM)

Memory where each location has an address




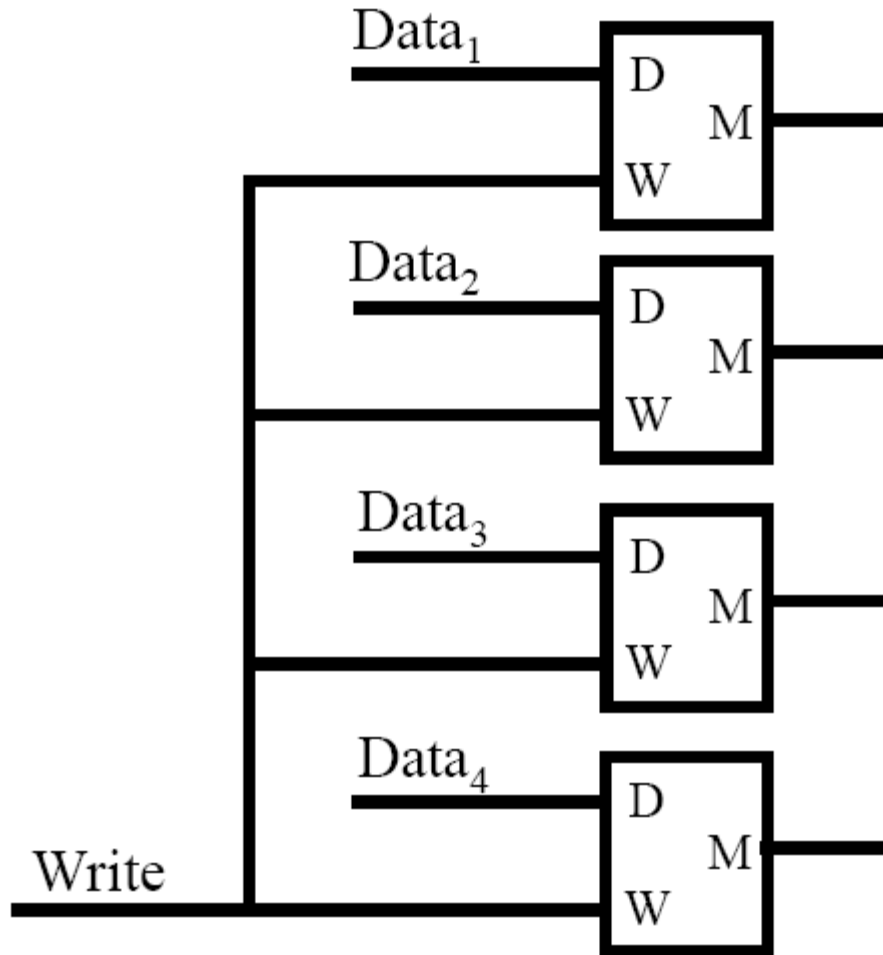Recall from last lecture: “Register” with 4 bits of memory




How can you set up an addressing system for large banks of memory?


RAM

 


2^K bits;
bank of
flipflops

 

If 4 locations, “address” has 2 bits

 


RAM: Implementing “Write”

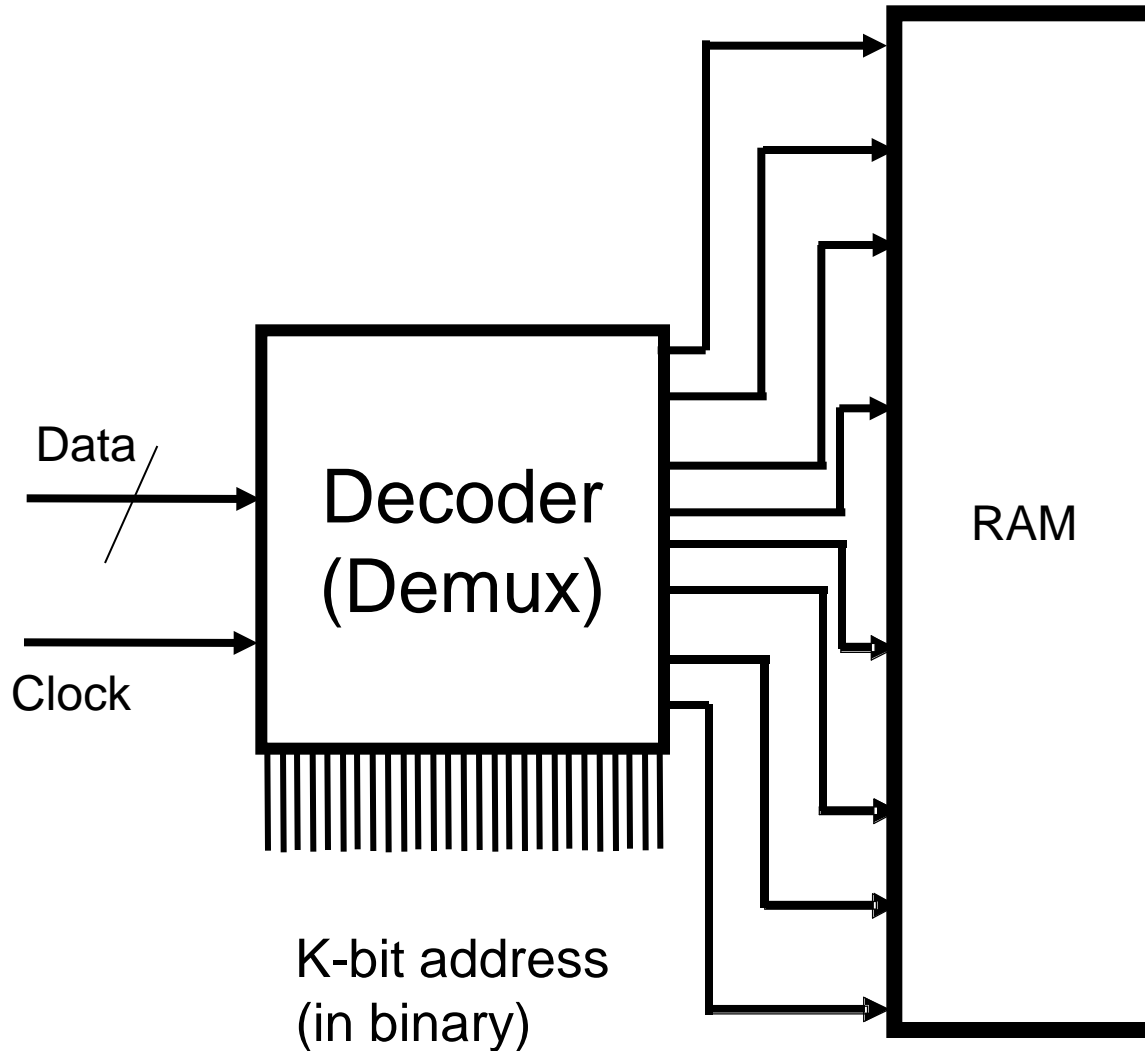

The decoder selects which cell in the RAM gets its “Write” input toggled

(simple combinational circuit; see logic handout)

Ram: implementing “Read”

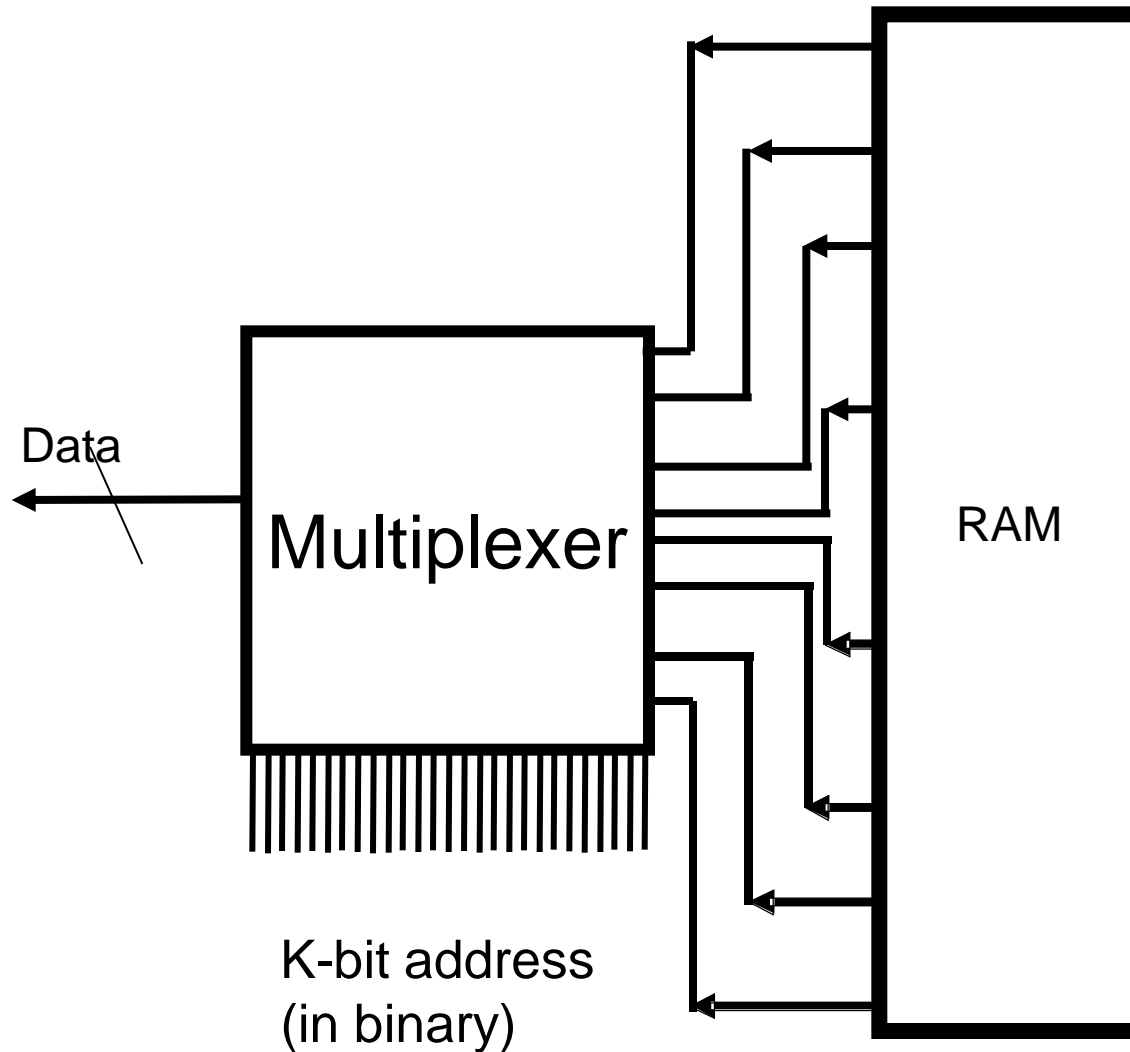

The multiplexer is connected to all cells in the RAM; selects the appropriate cell based upon the k-bit address (simple combinational circuit; see logic handout)



Next, the secret revealed...

How computers execute programs.

CPU = Central Processing Unit

Scribbler Control Panel Program

```
If <Obstacle on Either Side> Then
{
  Play Sound for 1s at Frequency 440Hz
}
Else
{
  LED: ON, ON, ON
}
END
```

F5



“Download to Robot”
(Compilation)

Machine Executable Code

Address	Hex	Hex	Hex	Hex	Hex	Hex	Hex	Hex
000000	47	49	46	38	39	61	14	0f
000009	00	b3	08	00	ff	60	00	cf
000012	00	cf	2f	00	cf	60	2f	ff
00001b	2f	90	2f	00	60	2f	00	ff
000024	2f	ff	ff	ff	00	00	00	00
00002d	00	00	00	00	00	00	00	00
000036	00	00	00	00	00	00	00	21
00003f	0b	4e	45	54	53	43	41	50
000048	32	2e	30	03	01	00	00	21
000051	f9	04	09	14	00	08	00	2c
00005a	00	00	00	14	00	0f	00	04
000063	55	10	c9	49	ab	9d	26	eb
00006c	af	19	44	28	8e	81	51	19

Point 1: Programs are “translated” into “machine language”; this is what’s get executed.


Similar to:

- T-P programs represented in binary
- .exe files in the Wintel world

Greatly simplified view of modern CPUs.



Program (in binary) stored in memory

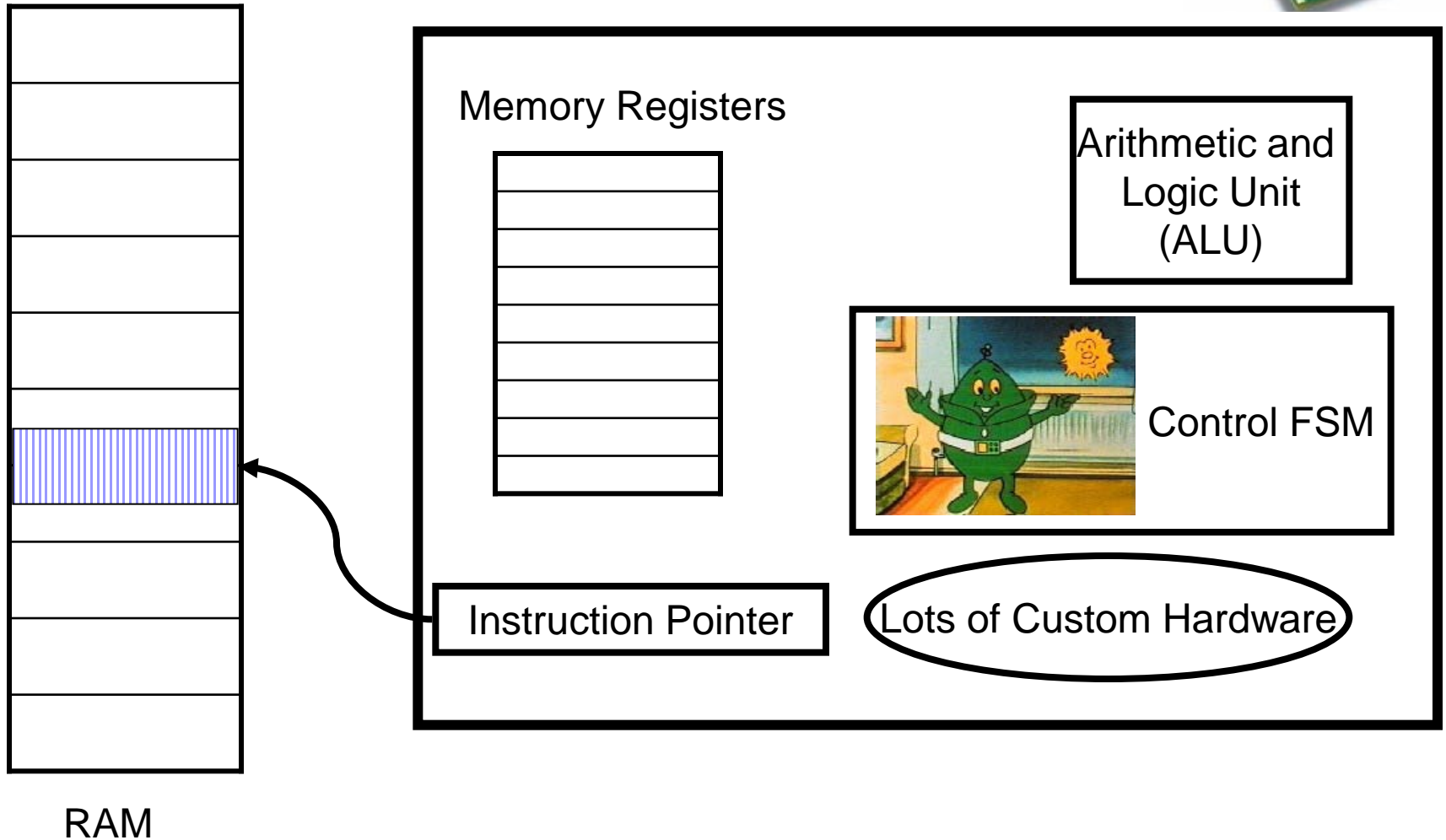

Examples of Machine Language Instructions

ADD	3	7	12	Add contents of Register 3 and Register 7 and store in Register 12
LOAD	3	67432		Read Location 67432 from memory and load into Register 3
JUMP	4	35876		If register 4 has a number > 0 set IP to 35876

Stored in binary (recall Davis' s binary encoding of T-P programs)

Different CPUs have different machine languages

- Intel Pentium, Core, Xeon, etc. (PC, recent Mac)
- Power PC (old Mac)
- ARM (cellphones, mobile devices, etc.)

“Backwards Compatibility” – Core 2’ s machine language extends Pentium’ s machine language

Machine languages now allow complicated calculations (eg for multimedia, graphics) in a single instruction




Main Insight

Computer = FSM controlling
a larger (or infinite) memory.


Meet the little green man..




The Fetch – Decode – Execute FSM

 

Fetch – Decode – Execute FSM


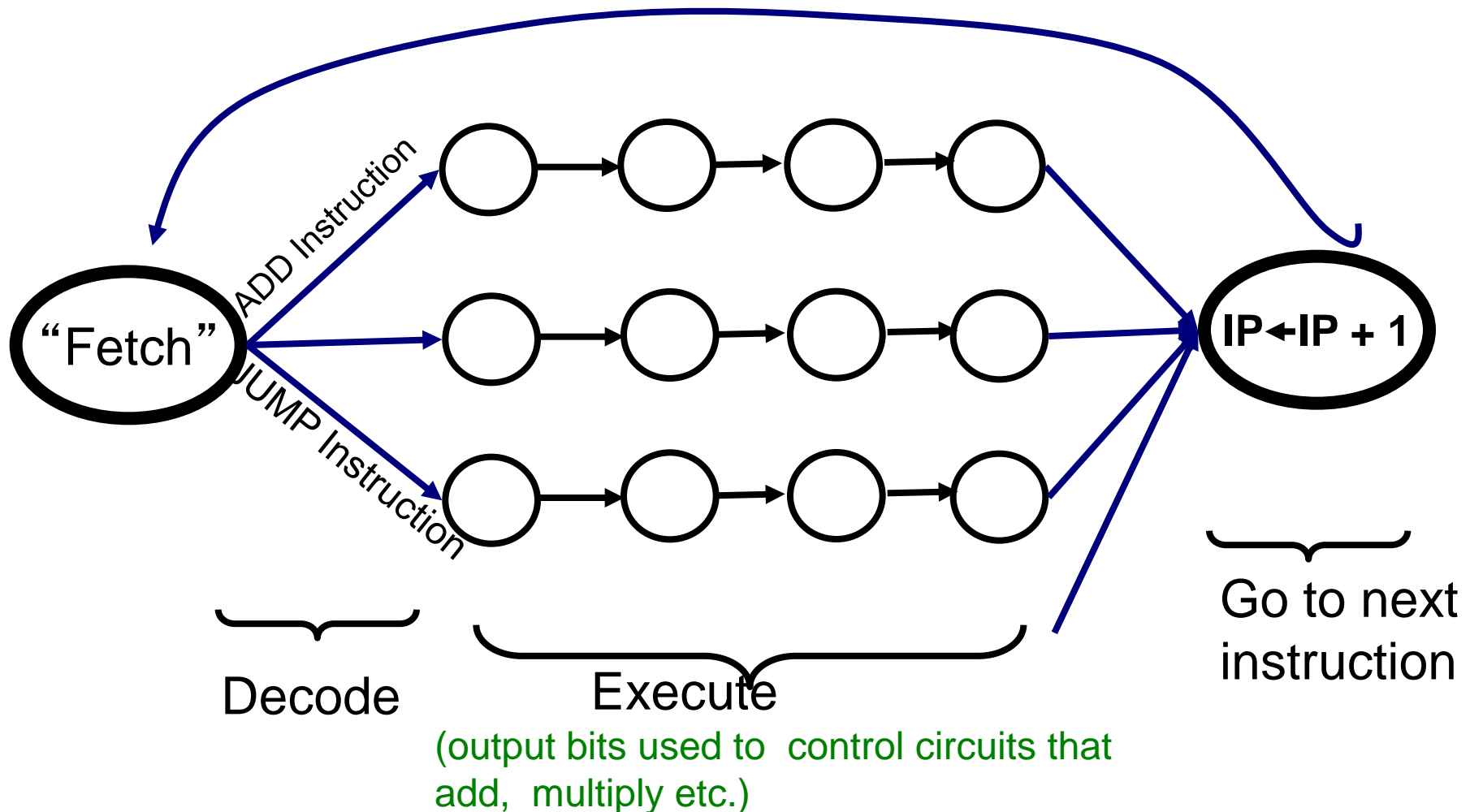


CPU as a conductor of a symphony

 

Bus: “Everybody hears everybody else”

Speculation: Brain as FSM?

  

- Network (“graph”) of 100 billion neurons; each connected to a few thousand others
- Neuron = tiny Computational Element; “switching time” 0.01 s
- Neuron generates a voltage spike depending upon how many neighbors are spiking.