

CS 126 Lecture A5: Computer Architecture

Outline


- Introduction
- Some basics
- Single-cycle TOY design
- Multicycle TOY design
- Conclusions

CS126

13-1

Randy Wang

What We Have

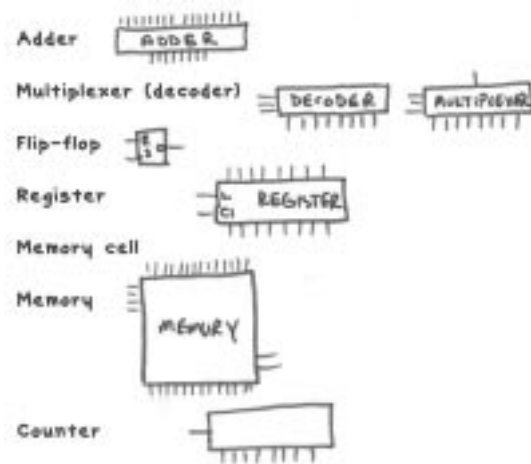

CS126

13-2

Randy Wang

What We Want to Do

```
repeat
  fetch instruction;
  update PC;
  decode instruction;
  execute instruction;
until halt signal
```

- Remember the TOY simulator written in C?
- Now it's time to use the components we have to implement this loop in hardware!

CS126

13-3

Randy Wang

Outline

- Introduction
- **Some basics**
- Single-cycle TOY design
- Multicycle TOY design
- Conclusions


CS126

13-4

Randy Wang

Single Cycle vs. Multicycle Design
 
```
repeat
  fetch instruction;
  update PC;
  decode instruction;
  execute instruction;
until halt signal
```




- Single cycle design: each iteration is completed within one clock cycle, long cycles, simple
- Multi-cycle design: each iteration is broken down into multiple clock cycles: short cycles, more complex
- More tradeoffs later

CS126

13-5

Randy Wang

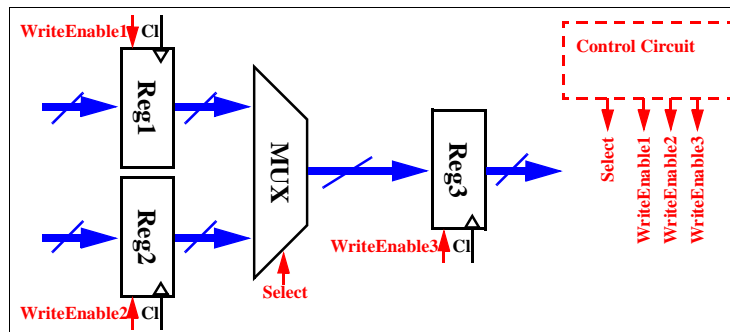Datapath and Control: Definition by Example




- Blue: datapath, Red: control signals
- Control circuit decides how to set **Select** and whether to enable **WriteEnable3**
- When clock ticks
 - One of Reg1 or Reg2 gets copied to Reg3 if **WriteEnable3** is on
 - Nothing gets copied to Reg3 if **WriteEnable3** is off

CS126

13-6

Randy Wang

The Big Picture

 

- The five classic components of a computer

CS126

13-7

Randy Wang

Steps Towards Designing a Processor


- Analyze instruction set architecture (ISA) and understand datapath requirements
- Select set of datapath components and establish clocking methodology
- Assemble datapath to meet ISA requirements
- Analyze how to implement each instruction to determine the setting of various control signals
- Assemble the control logic

CS126

13-8

Randy Wang

 Review: Register File (From Last Lecture)




- Register file of k -bit words
- One address port, so can't read and write in the same clock cycle

CS126

13-9

Randy Wang

What We Have (cont.): TOY Register File

 


- 8 general purpose registers
- 2 16-bit output busses, 1 16-bit input bus
- $r1, r2$ (3-bit numbers) specifies which registers go on bus1, 2
- $r0$ (3-bit) specifies which registers to receive input data when write enabled at clock pulse; when not write-enabled, the named register's value appears on bus 0

CS126

13-10

Randy Wang

What We Have (cont.): TOY ALU

 

- We have learned about an adder. Generalize it to an ALU.
- Two 16-bit inputs, one 16-bit output
- A 3-bit control specifies which arithmetic or logic operation to perform (+ - * ^ & >> <<)

CS126

13-11

Randy Wang

Outline

- Introduction
- Some basics
- Single-cycle TOY design
 - Datapath design
 - Control design
- Multicycle TOY design
- Conclusions

CS126

13-12

Randy Wang

TOY Datapath Components

repeat

```

fetch instruction;
perform arithmetic operation;
access memory if necessary;
write back to register if necessary;

```

until halt signal


- Refine the simulator code to be more specific
- Each of these four lines will be handled by a piece of hardware
 - Instruction fetch
 - Arithmetic (execution)
 - Memory
 - Write back
- We will assemble them one at a time, and assemble all four together at the end
- Caveat: I'm leaving out a few instructions as exercises

CS126

13-13

Randy Wang

TOY Arithmetic (Execution) Data Path

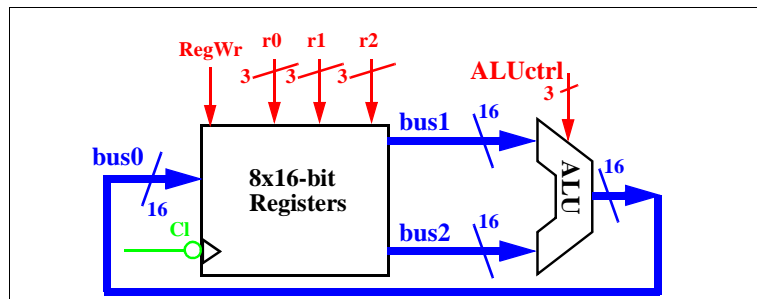


- Blue: datapath, Red: control signals
- (Part of) Implementation of TOY instruction:
 $r0 = r1 + r2$
- $r0, r1, r2$ control signals come straight from instruction, more on control later
- Clock controls when write back occurs
- Reads behave as combinational logic: result valid after delay

CS126

13-14

Randy Wang

TOY Instruction Fetch Unit

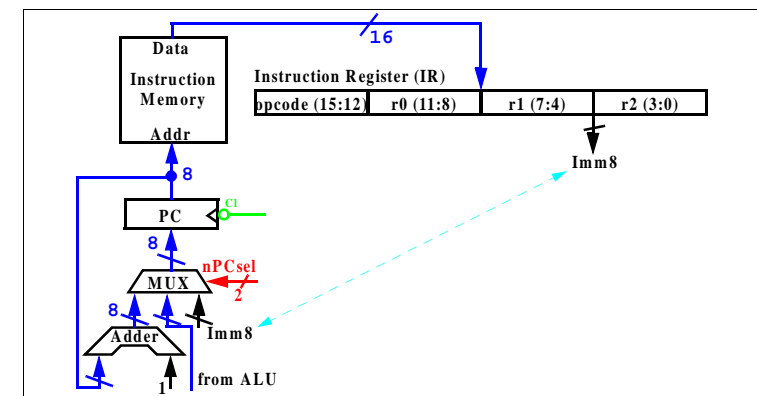


- Key question: which instruction to fetch
 - If jump, then fetch the jump target (which is in instruction itself)
 - Otherwise, fetch the next instruction

CS126

13-15

Randy Wang

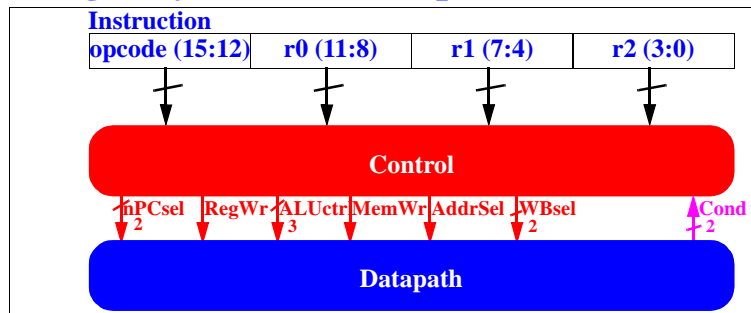Abstract View of Relationship Between Single Cycle TOY Datapath and Control




- The flow of data in the datapath commanded by control signals
- Control signals issued by the control unit
- Control unit gets its input from the current instruction and condition codes from the datapath
- Control unit is nothing but a big combinational circuit

CS126

13-20

Randy Wang

Implementing Single Cycle TOY Control

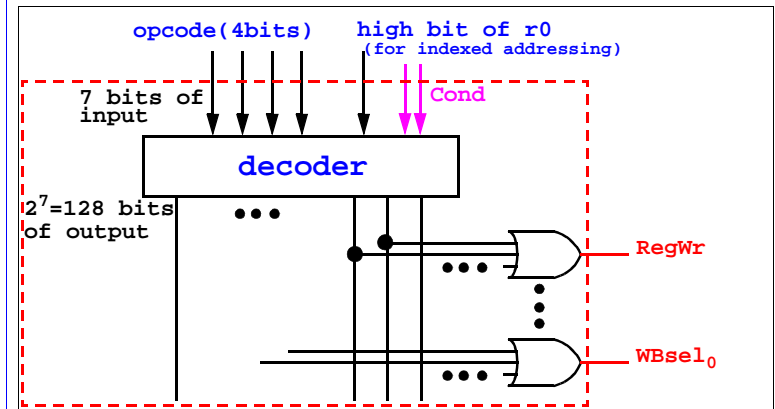

- Meaning of a decoder output that is 1: one particular instruction is executing and certain conditions are met
- Meaning of each OR-gate: turn on this control signal if any one of “these things” happen

CS126

13-21

Randy Wang

Outline

- Introduction
- Some basics
- Single-cycle TOY datapath design
- Single-cycle TOY control design
- Multicycle TOY design
- Conclusions

CS126

13-22

Randy Wang

Problems with Single-Cycle Implementation

- Long cycle time
 - Not all instructions are equal, some longer, some shorter
 - Memory accesses can be a lot longer
 - The slowest instruction determines cycle time
 - The processor sits idle for faster instructions
- Waste of chip area, for example:
 - Need an adder to compute $PC += 4$ in addition to the ALU
 - Could in theory eliminate the adder and borrow ALU when it's not needed
 - But in a single cycle, we can't tell when ALU is done

CS126

13-23

Randy Wang

Multicycle Design

```
repeat
  fetch instruction;
  decode instruction;
  execute instruction;
  access memory if necessary;
  write back to register if necessary;
until halt signal
```


- Multicycle design
 - Look at our TOY simulator again
 - Carefully break down each instruction into these roughly equal **stages**
 - Use one (short) clock cycle to execute each stage
- Advantages
 - Shorter instructions can just skip unnecessary cycles, more efficient in time
 - Can borrow ALU to increment PC earlier: more efficient in chip area

CS126

13-24

Randy Wang

Multicycle TOY Datapath

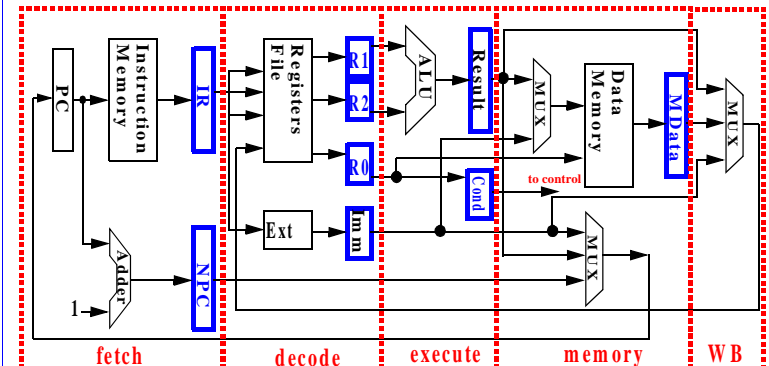


- Divide datapath up into 5 pieces (red boxes), analogous to the simulator code on previous slide: fetch, decode, execute, memory, write-back)
- Introduce temporary registers (blue boxes) to hold intermediate answers
- During each clock cycle, previous intermediate values are “clocked” into next stage, where the next intermediate value is calculated

CS126

13-25

Randy Wang

“Clocking” Values from One Stage to Next

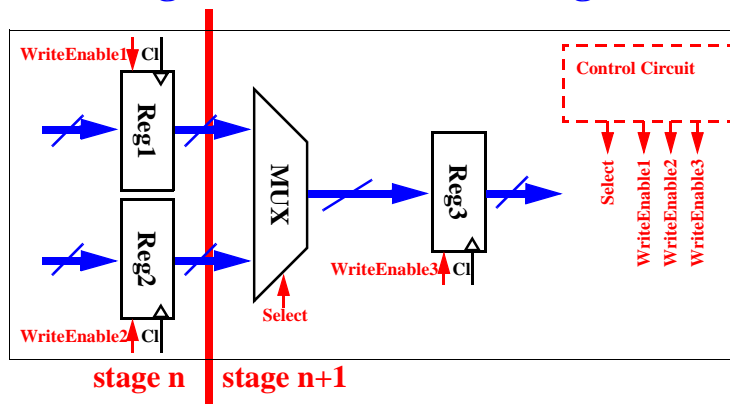


- (We have seen this slide before)
- The trick is to figure out how and when to set the control signals!

CS126

13-26

Randy Wang

How to Modify Control

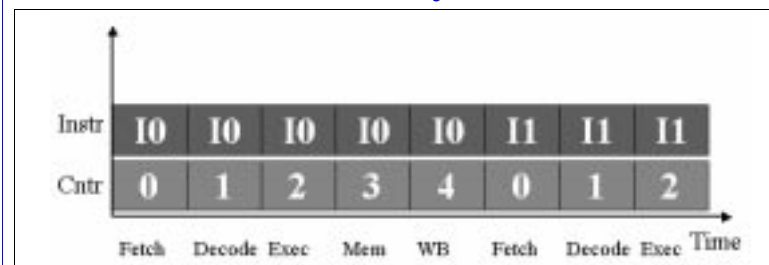


- Control depends on both instruction and time
- Use a counter to keep track of time (which stage the instruction is in)
- Will use counter to help determine control

CS126

13-27

Randy Wang

What's New In This Picture?

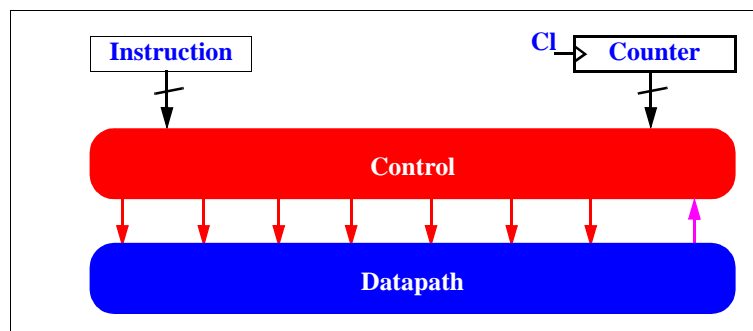

- Counter output becomes part of control input

CS126

13-28

Randy Wang

Outline

- Introduction
- Some basics
- Single-cycle TOY datapath design
- Single-cycle TOY control design
- Multicycle TOY design
- Conclusions

CS126

13-29

Randy Wang

Steps Towards Designing a Processor

- Analyze instruction set architecture (ISA) and understand datapath requirements
- Select set of datapath components and establish clocking methodology
- Assemble datapath to meet ISA requirements
- Analyze how to implement each instruction to determine the setting of various control signals
- Assemble the control logic

CS126

13-30

Randy Wang

Where's the Science? Understanding Tradeoffs

- We saw a deceptively trivial tradeoff today: clocking methodology
 - Single cycle architecture vs. multicycle architecture
 - Multicycle sounds obviously superior, right?
 - Extra temporary registers and extra control logic of latter
 - + Introduce time overhead
 - + Introduce chip area overhead
 - + Introduce extra complexity, cost, time-to-market,
 - The question to a computer architect is whether this tradeoff is worth it
- More complex tradeoffs at each step of the prev. slide
- Nice to hide all this under the hood of an ISA

CS126

13-31

Randy Wang

What We Have Learned Today


- Concepts:
 - Datapath vs. control
 - Single-cycle vs. multicycle designs
- More components: TOY register file and ALU
- Single-cycle design
 - How signals propagate in different parts of the datapath in general
 - How to implement control signals in general. Where do inputs come from?
- Multicycle design
 - Main general modifications made to datapath and control
- **I Don't expect people to memorize all the details**

CS126

13-32

Randy Wang

Computer Architecture

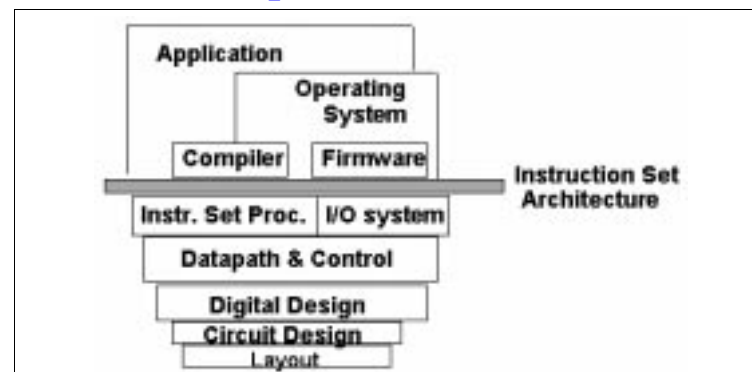


- Coordination of many levels of abstraction
- Under a rapidly changing set of forces
- Design, measurement, and evaluation

CS126

13-33

Randy Wang

Forces Influencing Computer Architecture

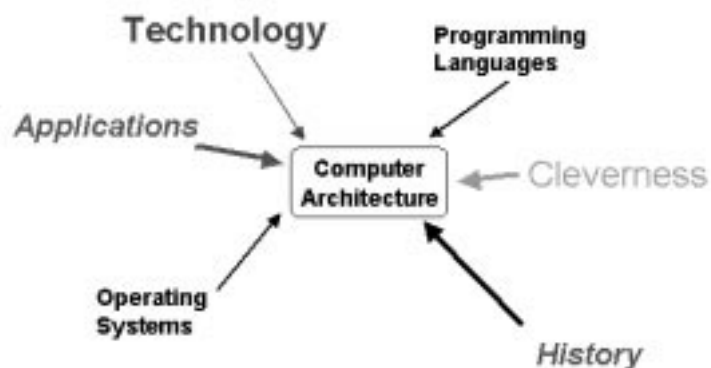

CS126

13-34

Randy Wang

Dramatic Technology Change

- Technology
 - **Processor** logic capacity: +30% / yr; clock rate: +20% / yr; overall performance: ~+60% / yr!
 - **Memory and disk** capacity: ~+60% / yr
- Numbers, though impressive, are boring. What's really exciting is revolutionary leaps in applications!
- Quantitative improvement and revolutionary leaps interleave as technology advances
 - ~1985: **Single-chip** (32-bit) **processors** and **single-board computers** emerged, led to revolutions in all aspects of computer science!
 - Conjecture: ~2002: Emergence of powerful **single-chip systems**, what will be its implication?!

CS126

13-35

Randy Wang